

Index

A

- ABSTOL, 28
- Abut, 98, 427, 429-430
- AC analysis in SPICE, 19-20, 285
- AC small-signal analysis, 280
- Accumulation, 132-134, 136, 159, 514
- Active area, 83-99
 - design rules, 99
- Active-PI loop filter, 573-574
- Active load, 657, 872
- Active pixel sensor, 504-505
- Adaptive biasing, 920-923
- ADC, see Analog-to-digital converter
- Adder, 367-369, 373, 395, 407-410, 412, 419-421
- Aliasing, see Analog-to-digital converter
- Amplifier,
 - adaptive biasing, 920-923
 - biasing, 291-292, 297-302, 613, 621, 624-625, 635-652, 699, 863-866
 - body effect 691-692, 709
 - cascode, 686-689, 696-697
 - class A, 672, 688, 691, 697, 701, 727
 - class AB, 672, 697-701, 709-710, 727-728, 800, 802-805, 810, 814, 817, 819-820, 865, 878
 - common-gate, 671, 689-690, 708-709, 732, 783
 - common-source, 657-658, 666-667, 671-673, 698-699, 717, 751, 756, 773-774, 793, 800, 814, 820-823
 - current source load, 657, 665, 671-674, 686, 689-691, 698-699, 704, 719, 731-733, 774, 876
 - distortion, 701, 704-706, 710, 737-740, 790, 807, 831
 - efficiency, 699-702
 - feedback, see Ch. 31
 - frequency response, 661-666, 674-685, 687, 696-697, 708, 721
 - gain, 279, 291, 657-673, 686-692, 719-720
 - input capacitance, 693, 1141
 - noise, 219-262, 669-670, 686, 688, 694
 - noise figure, 233-240
 - overshoot, 811, 895, 936
 - phase response, 662-665, 675-688
 - pole splitting, 676-685
 - push-pull, 698-703
 - slew rate, 672-673
 - source follower, 670, 690-698
 - Amplifier (continued),
 - transimpedance, 666-667
- Analog-to-digital converter (ADC), 931, 947-957, 985-1015
 - 0.5 LSB, 943
 - 1.5 bits/stage, 1068-1075
 - aliasing, 953-955, 1008
 - aperture error, 956-957
 - architectures, 985-1016
 - binary search, 1003-1005
 - calibrating, 1079
 - charge redistribution, 1005-1007
 - comparator placement, 1061, 1070, 1082
 - coarse conversion, 991
 - cyclic, 1059-1066
 - DFT, see discrete Fourier transform
 - differences of oversampling and Nyquist rate converters, 1008-1009
 - differential nonlinearity (DNL), 950-951, 989-990, 998, 1007
 - digital error correction, 1068
 - discrete Fourier transform (DFT), 218, 956
 - fine conversion, 991
 - flash, 985-990
 - flash accuracy issues, 988-990
 - folding frequency, 955
 - gain error, 953, 992-994
 - higher-order sigma-delta modulation, 1014
 - implementing, 1052-1095
 - integral nonlinearity (INL), 951-952, 989, 997-998, 1007
 - least significant bit (LSB), 940
 - missing codes, 951
 - noise shaping, 1011-1012
 - Nyquist rate, 1007
 - offset, 953, 989-990, 996-998, 1007
 - operational amplifier issues, 992-994
 - oversampling, 1007-1015
 - parallel, feed-forward, 990
 - pipeline, 994-998, 1067
 - pipeline accuracy issues, 996-998
 - pulse-density modulation, 1009
 - quantization error, 948-949
 - quantization levels, 947-949
 - quantization noise, 956
 - residue, 994
 - resolution versus oversampling, 1014-1015
 - sampling function, 954-955
 - SAR, 1003-1005
 - scale factor error, 953
 - sigma-delta modulation, 1009
 - signal-to-noise ratio (SNR), 956
 - specifications, 947
 - successive approximation, 1003-1007
 - successive approximation accuracy issues, 1007
 - successive approximation register, see SAR, 1003-1005
 - transfer curve, 948-953, 987, 994

Analog-to-digital converter (ADC) (continued),
 two-step, 990-992
 two-step accuracy issues, 992
 Analog models, 269-310
 body effect transconductance, 287-288
 transconductances, 279-280, 288
 Analog signal characteristics of, 932
 Anisotropic etch, 171
 Anode, 43, 757, 760
 AOI logic, 364-369
 Aperture error, see sample-and- hold
 Arbiter, 383
 Astronomy, 246
 Autozeroing, 1006, 1051, 1053
 Avalanche breakdown, 143, 154, 253-254
 Averaging noise,
 flicker, 246
 thermal (white), 240-241
 Averaging circuit, 539-540, 873-874, 1078-1079

B

β (transconductance parameter), 142
 Back end of the line (BEOL), 90, 177-178,
 199-208
 Backend processes, 208-211
 Bandgap energy of silicon, 759
 Bandgap voltage references (BGR), 745, 761-770
 Battery, 695, 730
 BCD, see binary coded decimal
 BEOL, see back end of the line
 Beta-multiplier reference (BMR), 624-630, 647,
 650, 750-754
 compensation, 630
 Biasing,
 general long channel analog design, 291-293
 general short channel design, 297-300
 high-speed design, 299-302, 863-866
 long-channel circuit, 647
 push-pull amplifier, 699
 short-channel circuit, 650
 Binary coded decimal, 965
 Bi-phase, 584-585
 Bipolar junction transistor (BJT), 47, 150
 lateral, 758
 parasitic, 2, 37, 56, 341-342, 757-758
 temperature behavior, 758-759
 vertical, 757
 Bird's beak, 181
 BJT, see bipolar junction transistor
 Bloats, 35
 BMR, see beta-multiplier reference
 Body effect, 139, 148-149, 276-277, 691-692, 709
 gamma, γ , 139, 276
 Body transconductance, 287-288
 Bonding pad, 4, 59
 layout, 59-62, 100-102
 Bootstrapped inverter, 546-547

Bottom plate capacitance, 115, 839-840
 Bottom plate sampling, 839-842, 1052
 Breakdown,
 diode model in SPICE, 58
 oxide, 154
 voltage, 58, 143
 BSIM4, 154-157
 Buffers,
 class AB output, 672, 697-701, 709-710,
 727-728, 800, 802-805, 810, 814, 817,
 819-820, 865, 878-891, 900-901
 digital, 344-348
 fully differential input, 920
 input, 534-542
 NMOS only, 350, 546-547
 op-amp, 793-810, 865, 878-891, 900-901
 source follower, 696-698
 Bulk CMOS process, 31, 180
 Buried channel, 304
 Bus, 68, 100-103, 321, 351, 412-419, 427, 527

C

C'_{ox} , 114-115, 123-124, 132-135
 Calibration, 1023-1024, 1035-1038, 1049-1050,
 1061, 1079
 Calma stream format, see GDS, 36
 Caltech intermediate format, see CIF, 36
 Capacitance, 44, 135
 bottom plate capacitance, 115, 839-840
 bottom and sidewall, 117
 depletion, 43-45, 47-49, 58, 94, 100, 117, 122,
 133, 147, 244, 315, 342-343, 398, 478, 546,
 618, 844
 diffusion, 45-47, 117
 metal layer parasitics, 61
 MOSFETs 116-118, 132-135
 sidewall, 44-45, 117
 Capacitive feedthrough, 449, 831-832, 1050
 Capacitor
 common-centroid layout, 980
 depletion, 43
 poly-poly, 113-115
 layout, 113-115, 851-852
 parasitics, 61, 115
 temp co, 116
 voltage coefficient, 116
 Capacitor error averaging, 1068, 1075-1083
 Carrier lifetime, τ_T , see diode, minority carrier
 lifetime
 Carrier transit time, τ_T , see diode, minority carrier
 lifetime
 Cascode,
 amplifier, 686-689, 696-697
 current mirror, 636-652
 differential amplifier, 733-735, 793-794,
 877-891
 origin of the name, 636

- Cathode, 43, 757
CGBO, 135
CGDO, 123-124, 135
CGSO, 123-124, 135
Channel hot electron (CHE), 468-469
Channel-length modulation (CLM), 143-147, 273, 277, 280-281, 289, 613-617, 639, 856
Charge injection, 830-840, 856, 863, 937, 1050
Charge pumps, 329, 461, 542-546, 558-561, 578-580, 591-593, 600, 603
CHE, see channel hot electron
Chemical/mechanical polishing (CMP), 163, 170, 173, 182, 185, 187, 201-207, 211
Chemical vapor deposition (CVD), 176-177, 179, 182, 184-185, 187, 190, 193, 196, 199, 202-207
Chip, 3, 32, 36
 cross-sectional view, 4, 32
 design, 1
 IC design flowchart, 2
 packaging, 4, 211
 layout view, 4, 32
 organization, 447
CIF (Caltech Intermediate Format), 36, 53
Class AB, 672, 697-701, 709-710, 727-728, 800, 802-805, 810, 814, 817, 819-820, 865, 878
CLM, see Channel length modulation
Clock feedthrough, 449, 456, 830, 832-834, 838-840, 860, 863, 937
Clock generation, 577, 1082-1084
 nonoverlapping, 401-402, 843, 850, 853-856, 874, 896, 1084
Clock recovery circuit, 551-552, 584, 588-589, 591, 602-607, 608, 611
 self-correcting, 588-594
Clock synchronization, 383, 551, 591, 596
Clocked logic, 397, 403-408
CMOS, 1
 active pixel sensor, 504-505
 IC design process, 1-2
 passive elements, 105-106
 process flow, 91
 process integration, 161
 scaling, 54, 152
 trends, 152
 twin-tub, 31
 unit processes, 161
CMOS fabrication, 161-212
 APCVD, 176
 back end of the line (BEOL), 90, 177-178, 199-208
 backend processes, 208-211
 BEOL, see back end of the line
 boule, 163
 burn-in, 208, 211
 chemical/mechanical polishing (CMP), 163, 170, 173, 182, 185, 187, 201-207, 211
 chemical vapor deposition (CVD), 176-179, 182, 184-187, 190, 193, 196, 199, 201-207
 CMOS fabrication (continued),
 critical dimension (CD), 179
 contact module, 202-203
 contaminates, 171, 208
 Czochralski (CZ) growth, 162-163
 degree of anisotropy, 170-171
 deposition, 90, 161, 173-177, 179, 191-192, 196, 200-208, 210-211
 depth of focus (DOF), 168-169, 201, 205
 die separation, 3, 211
 diffraction effects, 168-169
 diffusion, 117, 163, 165-167, 211
 doping processes, 52-53, 161, 165-167
 dry etching, 170-171, 208
 electrical coupling, 202, 205
 electronic grade silicon (EGS), 162
 electromigration problems, 203
 etching, 33, 90-91, 93, 170-172, 175-176, 183, 190, 192, 200, 202, 208, 211, 444
 etch rate, 170-171
 etch profile, 171
 EGS, see electronic grade silicon
 epitaxial wafers, 31-32, 180
 FEOL, see front end of the line
 field oxide (FOX), 38, 83-84, 86-87, 90-91, 116-117, 181
 front end of the line (FEOL), 90, 177-178, 180-199
 final test, 208, 211
 gate oxides, 163, 191-192
 IMD, see intra-metal (layer) dielectric
 intra-metal dielectric (IMD), 69, 178, 205-208
 ion implantation, 140, 165-167, 170, 184, 211
 ion implanter, 165
 implant profile, 165-166
 isolation, 90-91, 173, 177, 181-183, 205
 lattice damage, 165, 184
 LOCOS, 181
 mask alignment, 84, 86, 94, 170
 masks, 34-35, 53, 69, 84, 86, 163, 167-168, 170, 173, 179
 metallization, 178, 203-205
 metallurgical grade silicon (MGS), 162
 MGS, see metallurgical grade silicon
 n-wall, 184-186
 n-well, 179, 181, 184, 187-190
 numerical aperture, 168
 p-wall, 184-186
 p-well, 179, 181, 184, 187-191
 packaging, 3-5, 59, 208, 211
 passivation, 62, 173, 178-179, 208-210
 pattern transfer, 168
 PECVD, 176-177
 PECVD reactor, 177
 photolithography, 161, 167-171, 173, 182-193, 196, 202-203, 206, 208-211
 physical vapor deposition (PVD), 175-176, 200, 204, 208

- CMOS fabrication (continued),
 plasma etching, 173-177
 polysilicon, 166, 178-179, 191-194
 pre-metal dielectric (PMD), 178, 200-204
 process description, 89-91, 178-179
 process integration, 177-208
 rapid thermal annealing, 199-201
 rapid thermal processing (RTP), 164
 reactive ion etching (RIE), 171-173
 registration errors, 170
 resolution, 168-169, 171
 reticle, see mask
 salicide module, 199
 scribe lines, 209, 211
 selectivity, 170
 shallow trench isolation (STI), 90-91, 177-178,
 181-188
 silica, 161-162
 silicide, 83, 88-92, 94, 199-201
 SOI wafers, 180
 source drain module, 193-199
 starting material, 180-181
 step coverage, 174
 stepper, 34, 167-168
 straggle, 165
 streets, see scribe, 209, 211
 technology computer assisted design (TCAD),
 179
 thermal oxidation, 34, 161, 163-164, 182, 184,
 190, 192, 211
 thin film deposition, 173-177
 thin film removal, 161, 170-171
 trench liner, 184
 twin tub (well) module, 187-190
 unit processes, 161-177
 via 1 module, 205-207
 wafer manufacture, 161-163
 wafer probe, 208-211
 wet etching, 170-171
 yield, 152, 209-211
- CMOSedu design rules, 53-55, 69
- CMFB, see common-mode feedback
- CMRR, see common-mode rejection ratio
- Common-centroid, 111-113, 618, 724, 851, 916,
 980
- Common drain amplifier, see source follower
- Common gate amplifier, 671, 689-690, 708, 732,
 783
- Common-mode feedback (CMFB), 836-837, 863,
 869-875, 881-885, 888-904, 906-908,
 1057-1058
 compensating, 871-873
 dynamic, 1089-1091
 settling time, 895
 switched-capacitor, 874-875, 896-904, 907-908,
 1089-1091
- Common-mode rejection ratio (CMRR), 721-724,
 742, 773, 789-790, 823, 825, 833
- Common-mode voltage (V_{CM}), 837
- Common source amplifier, 657-658, 666-667,
 671-673, 698-699, 717, 751, 756, 773-774, 793,
 800, 814, 820-823
- Communication system, 582-583
- Comparators, 909-930
 block diagram, 910
 characterizing, 915-918
 clamped input stage, 917
 clocked, 918-919
 dc performance, 915-916
 decision circuit, 910-914
 dynamic, 854-856
 gain and offset, 916, 1061-1062, 1068, 1075
 hysteresis, 912-914
 input slew rate, 918
 inverter based, 854-856
 kickback noise, 448-449, 456, 910, 918, 930
 operation, 909
 output buffer, 913-915
 placement, 1061, 1082-1084
 pre-amp, 910-913
 propagation delay, 918
 self-biased, 920
 sensitivity, 909-910, 930
 transient response, 916
- Compensation, 773-792, 794, 814-815, 819-820,
 892, 895
 beta-multiplier reference, 630
 common mode feedback (CMFB), 871-873
 constant- g_m , 738-740
 high-speed, 783-787
 indirect, 783-787, 825
 gain enhancement, 809-812
 lead, 782
 Miller, 774, 788
 nested Miller, 820
 pole splitting, 674-679, 685, 780, 783, 814, 821
 slew-rate limitations, 787-789
- Conductivity, 39-41
 silicon-dioxide, 468
- Constant- g_m ,
 bias circuit, 625
 diff-amp, 738-740
- Contact resistance, 47, 64, 70-71, 80, 147, 209,
 962
- Contact potentials, 42-43, 124, 137-138
- Convergence help in SPICE, 28, 401
- Complementary to absolute temperature (CTAT),
 745, 759, 761-762, 765, 768
- Counter, 329, 485-486, 506, 998-1002
 as a digital filter, 506-507
- Counter-doped, 52-53
- Coupled noise, 1092-1093
 rejection, 838
- Critical dimension (CD), 179
- Cross-sectional view, 3-5
- Crosstalk, 59, 71-72, 427

CTAT, see complementary to absolute temperature
 Current differential amplifier, 737, 921-922
 Current mirrors, 273-274, 510, 512, 563, 613-656
 biasing, 621-626, 647, 650, 863-866
 cascode, 273-274, 636-646
 design, 615
 dynamic, 856-858
 floating, 647, 651-652, 698-699, 703-704, 710, 804-805, 808, 820, 865
 layout, 616-620, 642
 low-voltage, wide-swing, 639-651
 matching, 616-620
 output resistance, 288, 298, 613, 622, 636-644
 regulated drain, 645-646
 SPICE statement, 620
 subthreshold operation, 635
 supply independant biasing, 624
 temperature coefficient, 632
 V_{THN} mismatch, 616
 KP mismatch, 616-617
 wide swing, 639-651
 Current mirror load, 715-717, 731
 Current-mode DAC, 1018, 1024-1030, 1042
 Current steering DAC, 1042-1044
 Current starved VCO, 329, 561-565, 571, 574
 CVSL logic, 369-370
 Cyclic ADC, 1058-1066
 Czochralski (CZ) growth, 162-163

D

DAC, see Digital-to-analog converter
 Damascene process, 90, 207
 Data conversion
 signal characteristics, 931-935
 DC analysis in SPICE, 13-15
 DC sweep convergence in SPICE, 29
 Decades, 20
 Decoder, 329, 430, 433, 447, 449, 457-462, 480, 966, 985-987
 Decoupling capacitor, 73-74, 81, 417, 419
 Decibels, 20
 Delay time, 49-52, 65, 89, 317-318, 348, 358-359, 362, 526-527, 531-533
 NAND gate, 392
 phase shift, 665
 TG, 376
 word line, 443
 Delay elements, 408, 595-596
 Delay locked loop (DLL), 592-602
 Delay & transition times 317-320
 Delta-sigma modulation, see Sensing using
 delta-sigma modulation (DSM), see also
 Sigma-delta modulation
 Depletion capacitance, 43-45, 47-49, 58, 94, 100, 117, 122, 133, 147, 244, 315, 342-343, 398, 478, 618, 844
 Depletion device, 140

Depletion region, 43
 Depth of focus (DOF), 168-169, 201, 205
 Design rules, 53-54, 69, 75, 98-99
 active and poly, 98-99
 CMOSedu, 53-55, 69
 n-well, 36-37, 53-54
 metal layers, 69
 DFT, see discrete Fourier transform
 DIBL, see drain induced barrier lowering
 Dickson's charge pump, 544
 Dielectric constants, 114
 Die, 3-4, 32, 59-60, 62, 68, 75, 110, 116, 209, 211, 411-412, 427, 429, 443, 746, 958, 960, 998
 Die seperation, 3, 211
 Differential amplifier, 711-744
 ac operation, 718-721
 adaptive biasing, 920-922
 body effect, 730, 742
 cascode, 733-735
 class AB, 727-733
 common-centroid layout, 724
 common mode range (CMR), 713-716, 732-733, 735
 common mode rejection ratio (CMRR), 721-723
 constant transconductance, 738-740
 current, 737, 921-922
 current mirror load, 715-717, 731-733
 dc operation, 711
 gain, 719, 722, 733, 736
 low voltage, 736
 matching, 724-726
 minimum power supply voltage, 717
 noise, 726-727
 output resistance, 719, 733-734
 self-biased, 534-538, 920
 slew rate, 727
 source cross coupled pair, 727-733
 wide swing, 736-740, 918-919
 Differential nonlinearity (DNL), 941-943, 950-951, 963, 967-971, 976-980, 989-990, 998, 1007, 1029-1034, 1040-1041
 improving using segmentation, 1032-1034, 1043
 Differential output op-amp, 836-842, 863-908
 benefits, 838
 simulating, 841, 878-904, 927
 Diffusion,
 capacitance, 45-47, 117
 process, 117, 163, 165-167, 211
 Digital error correction, 1068, see also Analog-to-digital converter (ADC), 1.5 bits/stage
 Digital-to-analog converter (DAC), 931, 938-947, 965-985
 0.5 LSB, 943
 accuracy, 941
 binary switch array, 966-967
 binary weighted, 971, 974-975, 977-980
 calibration, 1035-1038
 charge scaling, 978-982, 1005-1007

- Digital-to-analog converter (DAC) (continued),
 current source mismatch, 976-977
 current steering, 973-975, 1042-1044
 cyclic, 982-983, 1019
 decoder, 966
 differential nonlinearity (DNL), 941-943, 963,
 967-971, 976-980
 dynamic range, 947, 963
 full scale voltage, 939, 941, 963
 gain error, 945-946, 953, 1019
 input combinations, 938
 integral nonlinearity (INL), 943-945, 967-971,
 976-977, 979, 980
 ladder, 967, 971
 latency, 945
 least significant bit (LSB), 940-941
 LSB, see least significant bit
 monotonicity, 943
 most significant bit (MSB), 940
 MSB, see most significant bit
 nonmonotonic, 943
 offset, 943-946
 op-amp issues, 992-994
 pipeline, 984-985, 1098
 R - $2R$, 971-973, 1024-1035, 1038-1040
 reference voltage, 938-941, 956
 resistor string, 966-971
 resistor string mismatch, 967-970
 resolution, 933-934, 937-938, 940-943, 946-947
 settling time, 945
 segmentation, 1032-1034
 signal-to-noise ratio (SNR), 945-946, 956
 specifications, 938-947
 split-array, 980-981, 1019
 transfer curve, 940
 W - $2W$, 1043-1044
 wide-swing, 1026-1032
 without an op-amp, 1038-1044
- Digital models, 311-319
- Digital phase-locked loop (DPLL), 551-612
 active-PI loop filter, 573-574, 581, 588, 591
 block diagram, 552
 charge pump, 558-561, 578-580, 591-593, 600,
 603
 dead zone, 577, 600, 609
 delay elements, 595-596
 examples, 596-607
 jitter, 557, 564, 571, 579, 582, 591-592, 594,
 597, 600
 lock range, 567, 569-570, 573-574, 576-577,
 579-580, 592
 loop filter, 552, 554-557, 559-561, 567-582
 PFD, 552-553, 557-561, 575-580, 591, 600-603,
 608
 pull-in range, 567-569, 571, 574, 576-577, 579,
 592
 static phase error, 572-573, 577, 579, 600, 604,
 610
- Digital phase-locked loop (DPLL) (continued),
 system concerns, 582
 tristate output, 559-560, 575-579, 581
 XOR DPLL, 568-574
 XOR Phase Detector, 552-557, 559, 561
- Diode,
 anode, 43, 757, 760
 breakdown voltage, 58, 253
 carrier transit time, τ_T , see minority carrier
 lifetime
 cathode, 43, 757
 depletion capacitance, 43-45, 117
 diffusion capacitance, 45-46, 117
 drain or source to substrate, 117, 143, 398, 403,
 543, 618
 electrostatic discharge, 100-102
 ESD, see diode, electrostatic discharge
 long base, 45
 minority carrier lifetime, τ_T , 45-48, 242-243
 n-well/p-substrate, 31-32, 39-45, 53, 57-58, 94,
 96, 543
 noise, 242-244, 249, 252-253
 parasitic BJT, 757-759
 photodiode, 249, 504
 reverse recovery time, 46-49
 saturation (scale) current, I_S , 39, 47, 181, 398
 Schottky, 92, 760
 short base, 45
 SPICE modeling, 14-15, 47-49
 storage capacitance, see diffusion capacitance
 storage time, 46-49
 temperature behavior, 759
 t_{rr} , see reverse recovery time
 t_s , see storage time
 τ_T , see minority carrier lifetime
 Zener, 253-254
- Discrete Fourier transform (DFT), 218, 956
- Distortion,
 amplifier, 701, 704-706, 710, 737-740, 807,
 993-994
 common-mode level variation, 740, 790, 807
 multiplier, 923
 pulse width, 531
 signal-to-noise plus distortion ratio (SNDR),
 956
 SPICE modeling, 705-706
 switches, 831
 total harmonic distortion (THD), 704-706, 923
- Distortionless transmission, 582
- DLL, see Delay-locked loop
- DNL, see Differential nonlinearity
- Dominant pole, 680
- Domino logic, 405-407, 409
- Doping processes, 52-53, 161, 165-167
- Doublet, 810
- DPLL, see Digital phase-locked loop
- Drain induced barrier lowering (DIBL), 154
- DRAM, see memory, DRAM

Drawn length, 87, 116-117, 132, 144
 Drawn width, 68, 87, 116-117, 132, 315
 DRC (design rule check), 36
 Drive current, see on current
 Drivers, 344, 449, 459-463, 481, 546
 distributed, 347-348
 DSL logic, 370-372
 DSM, see Sensing using delta-sigma modulation (DSM)
 Dummy elements, 113, 618, 851
 Dynamic circuits, 829-862
 amplifiers, 858
 capacitive feedthrough, 67, 830-832
 charge injection, 830, 856, 830-833
 clock feedthrough, see capacitive feedthrough comparator, 854-856
 current mirrors, 856-858
 dummy switch, 832
 IOS, 856-857
 kT/C noise, 833-834, 856
 logic, 397-410
 OOS, 856-857
 op-amp settling time, 852-853
 reducing charge injection & clock feed-through, 832
 reducing op-amp offset-voltage, 853-854
 sample-and-hold, 838-840
 simulating, 401
 storage capacitors, 852-853, 856
 switch, 829-834
 switched capacitor integrator, 845-850
 switched capacitor resistor, 843-845
 Dynamic logic, 397-410
 charge leakage, 399-400
 clocked CMOS, 403-408
 domino logic, 405-406
 PE logic, 405
 NP logic, 407
 shift register, 402
 simulating, 401
 zipper logic, 407
 Dynamic power dissipation, 339-340
 Dynamic range, 490, 506, 833, 839, 947, 963, 1009, 1014

E

Edge detector, 374, 587
 Effective channel length, 132
 Effective switching resistance, 312-315, 317, 320, 335, 344, 390, 392
 Electrode layer, 115
 Electrical length, 144
 Electromigration, 59, 68, 70
 Electrostatic discharge (ESD),
 diode, 59, 100-103, 530-531, 549
 Energy,
 bands in silicon, 39-43

Energy (continued),
 electrical, 213-215, 217
 implant, 166
 thermal, 225-226, 236
 Energy spectral density (ESD), 217
 Enhancement device, 140
 Epi layer, 31
 Epitaxial wafers, 31-32, 180
 ESD, see electrostatic discharge, see also energy spectral density
 Etching, 33, 90-91, 93, 170-172, 175-176, 183, 190, 192, 200, 202, 208, 211, 444
 Equalizer, 539, 582-583, 610
 Excess gate voltage, see overdrive voltage, 271
 Excess phase shift, 665

F

Fall time, 317-318
 Feature size, F , 444
 Feedback, 1099
 amplifier, 1106
 beta network, 1107
 bandwidth extension, 1101-1103
 closed-loop impedances, 1112
 closed-loop parameters, 1112
 determining signal path, 1107
 equivalent transconductance, 1121-1123
 factor β , 776, 1100
 forward path, 1107
 gain desensitivity, 1101
 gain margin, 781, 1138
 input/output impedance control, 1104
 input mixing, 1106
 inversions around the loop, 1107-1108
 open-loop impedances, 1110
 open-loop parameters, 1110
 output sampling, 1106
 phase margin, 781, 1138
 properties, 1104-1105
 recognizing topologies, 1105
 reduction in nonlinear distortion, 1103
 rules for output sampling, 1107
 series-series, 1109-1110, 1128-1132,
 series-shunt, 1141-1143
 series mixing, 1105
 series sampling, 1105
 shunt-series, 1108-1109, 1132-1135
 shunt-shunt, 1109-1110, 1119-1128, 1145
 shunt mixing, 1105
 shunt sampling, 1105
 stability, 777
 using a gate-drain resistor, 1125-1128
 FEOL (front end of the line), 90, 177-178, 180-199
 Fermi energy level, 42-43
 Field device, 38, 181, 184-185
 Field implant, 38-39
 Field oxide, see FOX (field oxide)

Flash memory, 113, 463, 469-476, 481-482, 487-489

Flatband voltage, 139

Flicker noise, see noise

Flip-flops, 380-389
 data (D), 386-388
 hold time, 388-389
 metastability, 383-385, 396
 setup time, 388-389

Floating current source, 647, 651-652, 698-699, 703-704, 710, 804-805, 808, 820, 865

Floating gate, 113, 466

Floor plan, 412, 958

FNT, see Fowler-Nordheim tunneling

Folded-cascode, 641, 648-649, 714-715, 802-810, 827-828, 872

Fowler-Nordheim tunneling (FNT), 469-474, 487

FOX (field oxide), 38-39, 83-87, 181

FPGA (field programmable gate arrays), 1, 412

Frequency response,
 amplifier, 661-666, 674-688, 696-697
 doublet, 810
 noise, 220-223
 op-amp, 680, 792-793
 pole splitting, 674-679, 685, 780, 783, 814, 821
 transmission channel, 538-541

Frequency synthesis, 577, 591

f_T , unity current gain frequency, 290-292, 297-302, 309, 316, 863, 903, 906

Fully-differential circuits, 833, 836-842, 863-930
 benefits, 833, 838
 bottom plate sampling, 839-842
 common-mode feedback, 836-837, 863, 869-875, 881-885, 888-895, 896-904, 906-908
 delay elements, 595-602
 gain, 836
 noise rejection, 838
 sample and hold, 838-842, 880-881, 901-904
 SPICE model, 841-842

f_{un} , op-amp unity-gain frequency, 260-261, 680-685, 740, 779-781, 785-786, 792-793, 797-799, 852-853, 993
 gain-enhancement, 808-812
 plot (general), 680

G

Gain-enhancement (GE), 808-812, 889-890

Gain- f_T product (GFT), see MOSFET, GFT (gain- f_T product)

Gain margin, 781

Gamma, γ , 139, 276

Gaussian probability distribution function, 248-249

Gate current, see Tunneling, gate current

GDS, 36, 53, 78

Generation, 40

GFT, see MOSFET, GFT (gain- f_T product)

GIDL, Gate-Induced Drain Leakage, 154

g_m , 279-280
 long-channel equation, 280
 short-channel, 293, 297-299
 subthreshold, 292-293

Glitch area, 1041-1042

GM, see Operational amplifier, gain margin

g_{mb} , 289-290

GMIN, 29, 401

GOX (gate oxide), 86-87, 114

Gradual channel approximation, 140, 151

Graphical design format, see GDS, 36

Gray code, 965-966

Ground bounce, 71-74, 81

Guard rings, 110, 343, 757, 851, 957, 960

H

Harmonic distortion, see Distortion, 704-706, 831, 923, 993-994

Hi-Z, 321-322, 350-351, 370, see also Tri-state outputs

High-speed op-amp, 783-787, 891

High impedance node, 397, 629-630, 673, 696, 721, 796, 819

Hold time, 388-389

Hot-carrier effect, 151

Hysteresis, 523-529, 537-538, 547-548, 910-916, 918

I

I_{drive} , see on current

$I_{D,sat}$, 144-145, 158, 271-272

INL, see Integral nonlinearity

Imaging, 504-505
 noise, 246
 sensing, 504-519, 1145-1148

Impact ionization, 153

Inductance, 72

Incomplete settling, 496, 502-503, 520

Input buffers, 531-542, 920

Input offset storage (IOS), 856-857

Input-referred offset, see Offset voltage

Instanced (or placed), 429

Integral nonlinearity (INL), 943-945, 951-952, 967-971, 976-977, 979-980, 989, 997-998, 1007, 1029-1032, 1034-1038, 1040-1041

Integrator,
 ADC, 998-1002
 delta-sigma, 492, 1010-1014
 noise, 245, 267
 offset, 846
 PLL, 573, 575
 switched capacitor, 845-850, 861, 901, 907-908

Inter layer dielectric (ILD), 69, 81

Interconnect burden, 429

Interdigitated layout, 110-113, 960

Intrinsic,
 carriers, 40-41

- Intrinsic (continued),
 propagation delay, 65-66, 81
 silicon, 40-42, 52-53
- Inverter, 331-352
 buffer design, 344-347
 dynamic power dissipation, 339-340
 layout, 341-343, 413, 422-425
 noise margins, 333
 other configurations, 349-351
 power delay product, 340
 switching characteristics, 337-338
 sizing, 344
 transfer characteristics, 332-336
 tri-state output, 351
 VTC, see transfer characteristics
- I_{off} , see off current
 I_{on} , see on current
 Ion implantation, 165
 I_s , see Diode, saturation current
 Isotropic etch, 171
-
- J**
- Jagged plots, 29
 Jitter, 557, 564, 571, 579, 582, 591-592, 594, 597,
 600, 1000
 peaking, 582
 J_s , scale current density, 57
 Junction capacitance, see depletion capacitance, 43
-
- K**
- Keeper MOSFET, 406-407, 461
 Kickback noise, 448-449, 456, 910, 918, 930, 1061
 KP , 142
 kT/C noise, 229, 240, 244, 250-251, 517, 833-834,
 846, 856, 896
-
- L**
- Lambda, λ ,
 channel-length modulation (CLM), 144, 147,
 289, 298, 617, 620
 layout (in the MOSIS rules), 54
 wavelength, 168
- LASI, see <http://CMOSedu.com>
 Latch, 380-386, 400, 403-404
 Latch-up, 2, 46, 180, 341-343, 349-350
 Lateral diffusion,
 MOSFET source/drain, 116-117, 124, 144, 315,
 616, 620
 n-well fabrication, 35-36, 56
 SPICE, 147
- Layout,
 active, 83-85
 adder, 420-421
 binary-weighted capacitor
 array, 980
 bipolar junction transistor, 757-758
- Layout (continued),
 bonding pad, 59-60, 62, 75-77
 capacitor, 113-116, 419, 851,
 capacitor bottom plate, 115, 840
 common-centroid, 111-113, 724
 corners, 38
 design rules, 37, 68, 99
 diff-pair, 724
 diode, 757-760
 DRAM cell, 443-446
 drawing order, 4
 dummy elements, 113, 618, 851
 electrode, 115
 flash memory cell, 466-471
 guard rings, 110, 343, 757, 851, 957, 960
 inverter, 341-343, 413, 422-425
 large-width MOSFETs, 121
 lateral bipolar, 757-758
 long-length MOSFETs, 120
 matching (to improve), 617-620, 724
 MOSFET, 86-87, 95 (NMOS), 96 (PMOS)
 116-124, 617
 MUX/DEMUX, 422
 n-well, 32, 36-37, 94
 NAND and NOR gates, 358, 415
 pad, 60, 75, 102
 parasitic pnp, 757
 power and ground, 417
 resistor, 32, 94, 109-113
 Schottky diode, 760
 serpentine pattern, 57
 SR latch, 416-417
 SRAM, 463-464
 standard-cell, 97-98, 343, 413, 427-431
 standard cell frame, 97, 343
 stick diagram, 422
 TG (transmission gate), 415
 unit cell, 109, 851-852
 view, 3-5
 VLSI, 1, 411
- Layout view, 3-5
 LDD, see lightly-doped drain
 L_{diff} , see lateral diffusion
 L_{drawn} , see drawn length
 L_{elec} , see electrical length
 L_{eff} , see effective channel length
 Leakage current, 93, 181, 184, 200, 244, 249,
 397-403, 547
 Level shifting, 547-548, 692
 pumped output voltage driver, 546
 Lifetime of a minority carrier, τ_T , see diode,
 minority carrier lifetime
 Lightly-doped drain (LDD), 90-91, 116, 151-152,
 179, 193-196
 Linear region, see Triode region
 LOCOS, 181
 Long-channel,
 analog models, 269-296

Long-channel (continued),
 digital models, 312-316
 MOSFETs, xxxi, 132-150
 tables, 292, 317, 320
 Low impedance node, 673
 Low power, 149, 299, 451, 476, 563, 635, 727,
 729, 737
 Low voltage, 476
 current mirror, 637-639
 differential amplifiers, 727, 729, 736-740
 reference, 760, 768-770
 LTSpice, see <http://CMOSedu.com>

M

Manchester NRZ, 584
 Masks, 34-35, 53, 69, 84, 86, 163, 167-170, 170,
 173, 179, 851
 aligning, 84, 86, 94, 170
 CMOS fabrication, 182-209
 Matching, 8
 capacitor, 116, 1075-1081
 common-centroid, 111-113, 618, 724, 851, 916,
 980
 current mirror, 615-618, 636, 642
 diff-pair, 724-726
 interdigitated layout, 110
 layout, 105, 617-620
 NMOS vs PMOS, 440-441
 resistors, 110-113, 1040-1041
R-2R DAC, 1029-1030
 threshold voltage, 616, 726, 856, 867
 transconductance, 616
 Measurements, 246, 267
 currents in SPICE, 10, 274-275
 noise, 213, 219-224
 probe, 326-327
 Memory circuits, 433-482
 array architectures, 434-447
 buried capacitor cell, 446
 chip organization, 447
 decoders, 457-461
 DRAM, 348, 438-446
 EEPROM, 469
 efficiency, 447
 EPROM, 468
 erased, 466, 471
 F, feature size, 443-445
 flash, 113, 463, 469-476, 481-482, 487-489
 folded bit line, 441-446
 floating gate, 466-474
 global decoders, 458
 local decoders, 458
 memory cells, 463
 NAND flash, 471
 NSA, 435-439
 open array, 436
 organization, 457

Memory circuits (continued),
 peripheral circuits, 448
 PE decoder, 461
 PROM, 464-465
 programmed, 466, 471
 PSA, 440-441
 RAM block diagram, 433, 457
 refresh operation, 441
 ROM, 464
 row drivers, 461
 sense-amp design, 448-456
 sensing basics, 435-441
 SRAM, 463-464
 trench capacitor cell, 444-445
 Metal layers, 59-74
 bond pad, 4, 59
 capacitive feedthrough, 66
 cross-sectional view, 64
 delays, 65
 design rules, 69
 electromigration, 59, 68, 70
 inter layer dielectric (ILD), 69
 intrinsic propagation delay, 65
 parasitics, 61, 64-65
 sizing, 68-74
 Metallurgical grade silicon (MGS), 162
 Metastability, 383-385, 396, 450, 452, 478, 918
 Miller,
 capacitance, 311-312, 661-662, 664, 674, 684
 compensation, 774, 788
 effect, 311, 687, 693
 eliminating, 686
 neglected zero, 662-665
 nested, 820
 theorem, 660-661, 676
 Minority carrier lifetime, τ_r , see diode, minority
 carrier lifetime
 Mixed signal, 706, 842, 957, 960
 Mobility, 40, 106, 144, 153
 Monotonic, 943, 966, 1041
 Moore's law, xxxi
 MOSFET, 131
 accumulation, 132-134, 136, 159, 514
 adjusting threshold voltage, 140
 capacitances, 117, 123, 135
 capacitors, 544
 C_{gs} calculation, 145
 channel-length modulation, 144
 depletion, 133
 depletion device, 140
 diode-connected, 272, 534, 542, 545, 579, 624,
 627, 629, 639, 648, 673, 708, 719, 737,
 819-820, 872
 dummy poly strips, 618
 effective width, 116
 enhancement device, 140
 excess gate voltage, see overdrive voltage
 field device, 38, 181, 184-185

MOSFET (continued),
 flatband voltage, 139
 flicker noise, 302-303, 833
 f_T , unity current gain frequency, 290-292,
 297-302, 309, 316, 863, 903, 906
 gain- f_T product (GFT), 300-302
 gate tunnel current, 154, 242, 403, 474-475
 $I_{D,sat}$, 144-145, 271
 I_{off} , 150, 294, 398, 408
 I_{on} , 150, 152-153, 157-158, 297, 314, 316
 IV characteristics, 140, 157
 lateral diffusion, 116-117, 124, 144, 315, 616,
 620
 layout and cross-sectional views, 86-87, 95-96,
 118-122
 linear region, see MOSFET, triode region
 long channel, xxxi, 132-150, 269-296, 312-317,
 320
 NMOS layout, 95
 ohmic region, see MOSFET, triode region
 output resistance, 288
 overdrive voltage, 271, 297-302, 616, 800, 802,
 804, 863-864, 884, 892, 896, 903, 906
 overlap capacitances, 132
 oxide encroachment, 116-117, 132, 181-182
 pad oxide, 182
 parallel connection, 358
 parasitic resistances, 118
 pinch-off, 143
 PMOS layout, 96
 punch-through, 143
 saturation region, 143-145, 271
 scaling, 152
 series connection, 359
 short channel, xxxi, 151-158, 297-302, 314-317,
 320
 SPICE statement, 119-120
 source/drain depletion capacitances, 117
 subthreshold slope, 150
 symbols, 96-97, 131
 temperature effects, 293-295
 threshold voltage, 135-140, 293
 triode region, 141, 271, 278
 $V_{DS,sat}$, 144-145, 271

MOSIS, 3, 53-55
 multiproject wafer, 3
 web address, 3

Multipliers, 923-929
 multiply-by-2, 992, 994, 1060, 1062-1064,
 1071, 1080
 multiplying quad, 924
 simulating, 926-928
 squaring circuits, 928-929

Multivibrator circuits, 529-531, 565-567

MUX/DEMUX, 378-381, 422

N

N-well, 31-58
 cross-section, 32, 36, 39
 design rules, 36, 54
 patterning, 35
 resistor, 32, 38, 94
 n-well substrate diode, 39

N-select (n+ implant), 84-85, 179

NAND gate, 353-356
 layout, 358, 414-415
 switching characteristics, 358-363
 switching point voltage, 354-355

NBTI, Negative Bias Temperature Instability, 153

Negative frequency, 218

Netlists, downloadable at CMOSedu.com

n_i , see Intrinsic, carrier

NMOS, 95-97, see also MOSFET

NMOS clock driver, 546-547

NMOS inverter, 349, 546-547

Noise, 213-268
 1/f, see flicker
 amplifier, 220-223
 analysis, 235
 avalanche, 252-254, 268
 averaging thermal (white) noise, 240-241
 averaging flicker noise, 246
 burst (popcorn), 252-253
 correlation, 256-258
 differential amplifier, 726-727
 diode, 242-244, 249, 252-254
 equivalent bandwidth, 220-223
 estimating RMS value from the time-domain
 amplitude, 249
 excess, 253
 feedback, 259-261
 figure, 233-240
 flicker, 213, 244-253, 261-262, 267, 302-303,
 833
 gate tunnel current, 220, 242
 Gaussian probability distribution function,
 248-249
 generator, 253-254
 imaging chip, 245-246
 input-referred, 220-224, 226-240, 247, 249, 251,
 256-261
 integrator, 245, 267
 kT/C , 229, 240, 244, 250-251, 517, 833-834,
 846, 856, 896
 margins, 333
 mean squared, 214-215, 262
 MOSFET, 302-304
 modeling, 219
 noiseless resistor model in SPICE, 236-238
 op-amp, 247-252, 259-261
 phase noise, 592
 photodiode, 249-250

Noise (continued),
 pink, 244
 popcorn, 252
 power spectral density, 215-218
 random telegraph signal, 252-253
 red, 245
 resistors, 225-229
 RMS, 215, 217, 219-224, 248-249
 root mean squared, see RMS
 shot, 242-244, 268
 signal-to-noise ratio, 230-234, 246, 266-267,
 945-946, 956, 964
 spectrum analyzer, 216-218
 SPICE modeling, 227-228, 237-238, 243-244,
 251-252, 302-304
 noiseless resistor model, 236-238
 standard deviation, 248-249
 substrate, 851
 temperature, 239-240
 thermal, 225
 transimpedance amplifier, 249-251
 variance, see Noise, mean squared
 white, 219-221, 225, 240-242, 253-254
 Zener, 253-254

Nonoverlapping clocks, 401-402, 843, 850,
 853-856, 874, 896, 1082-1085

NOR gate, 353-357
 layout, 358, 414-415
 switching characteristics, 358-363
 switching point voltage, 356-357

NRD and NRS, 118-120, 813

Nyquist criterion, 934

O

Octave, 20

Off current (I_{off}), 150, 294, 398, 408

Offset binary, 965

Offset voltage,
 ADC, 953, 1000, 1005-1007, 1014
 adding to a sense amp, 498
 charge injection, 831, 836, 841
 CMRR, 723, 789-790
 common-mode voltage, 792
 constant- g_m , 740, 792
 DAC, 945-946
 delta-sigma ADC, 1014
 diff-amp, 725-726, 867-868, 875
 flash ADC, 988-990
 gain error, 936
 integrator, 846
 modeling in an op-amp, 776, 827, 867-888
 modeling with SPICE, 654, 867-868, 870-871
 multiplier, 923
 op-amp, 775-776, 804, 813, 818, 825, 853-857,
 863, 867-868, 870-871, 892-895, 902-903
 pipeline, 996-998
 random, 775

Offset voltage (continued),
 removal, 518-519, 853-857
 sensing, 497-500, 502
 systematic, 775, 818, 916, 930

Ohmic contact, 83

Ohmic region, see Triode region

On current (I_{on}), 150, 152-153, 157-158, 297, 314,
 316

One shot, 529

Open circuit gain, 298, 300-302, 668, 673, 678,
 876

Operating point analysis in SPICE, 282-283

Operational amplifiers, 773-828, 863-908
 biasing, 865-866, 876
 CMFB, see common mode feedback
 CMRR, see common mode rejection ratio
 common-mode output voltage, 838
 common mode feedback (CMFB), 836-837,
 863, 869-875, 881-885, 888-895, 896-904,
 906-908
 common mode rejection ratio (CMRR),
 721-724, 742, 773, 789-790, 823, 825, 833
 folded-cascode, 641, 648-649, 714-715,
 802-810, 827-828, 872
 fully-differential, 836-842, 863-904
 f_{un} , op-amp unity-gain frequency, 260-261,
 680-685, 740, 779-781, 785-786, 792-793,
 797-799, 808-812, 852-853, 993
 gain-enhancement, 808-812, 889-890
 gain margin (GM), 781
 high-speed design, 783-785, 806-812, 863
 input common-mode range (CMR), 476, 730,
 732, 741, 743, 774, 787, 701-702, 802, 807,
 870, 872, 889
 layout of differential op-amps, 865
 offset-voltage, 775, 853, 867, 893
 open-loop response, 780, 781, 795, 799,
 801, 804, 805, 806, 811, 812, 822, 823
 OTA with buffer, 800-808
 output voltage swing, 775, 880, 884, 886, 891
 phase margin (PM), 781
 power amplifier, 807-808
 power dissipation, 775
 PSRR, 790-791, 838
 offsets, 775, 892
 RHP zero, 662, 782
 settling time, 852, 895, see also Settling time
 simulation results, 886, 902
 single-ended to differential, 894
 slew-rate limitations, 787, 800
 SPICE (ideal) model, 628, 841
 start-up problems, 887
 switched capacitor CMFB, 874-875, 896-897
 voltage regulator, 812-817

Operational transconductance amplifier (OTA),
 796-808

Optical Proximity Correction (OPC), 79

Oscillator,
 astable, 530-531
 ring, 339-341, 547
 Schmitt trigger, 527-529
 Voltage controlled, 561-567
OTA, see operation transconductance amplifier
Output buffer, see Buffers
Output Offset Storage (OOS), 856-857
Overdrive voltage, 271, 297-302, 616, 800, 802,
 804, 863-864, 884, 892, 896, 903, 906
Overglass layer, 62-63, 75-77, 80, 83
Overlap capacitance, 123-124, 132
Oxide,
 breakdown, 154
 capacitance, 114-115, 132
 encroachment, 116-117, 132, 181-182
 growth, 34, 163-164

P

P-select (p+ implant), 84-85, 179
P-wall, 184-186
P-well, 31, 52-54, 179, 181, 184, 187-191, 469-474
Packaging, 3-5, 59, 208, 211
Pad layer, 62
Parasitics, 1-2
Pass gate (PG), 321-326, 357
Pass transistor, see Pass gate (PG)
Passivation, 62, 178-179, 208-210
Path selector, 378
Patterning, 32-35
PCE, see power conversion efficiency
PE logic, 404-405
Peak detector, 539-540
PECVD (plasma enhanced CVD), 176-177
PG, see Pass gate (PG)
Phase-locked loops, see Digital phase-locked loop
 (DPLL)
Phase margin, 781
Phase shift, 665
Photodiode, 249, 1145
Photolithography, 161, 167-171, 173, 182-193,
 196, 202-203, 206, 208-211
Pinch-off, 143
Pipelining, 407
Pitch, 443
Plasma etching, 173-177
PLL, see Digital phase-locked loops
PM, see Operational amplifier, phase margin
PMD, see pre-metal dielectric
PMOS, 96-97, see also MOSFET
PN junction physics, 39-43
PNP, lateral, 757
 model, 758
Pole splitting, 674-679, 685, 780, 783, 814, 821
Poly (polysilicon), 83, 166, 178-179, 191-194
 design rules, 99
 poly2, 113-115

Polycide, 88
Power and ground, 72-74, 417
Power conversion efficiency (PCE), 699-702
Power delay product (PDP), 340
Power dissipation,
 inverter, 339-340
Pre-metal dielectric (PMD), 178, 200-204
Probe, 326-327
Process characteristic time constant, 316
Process description, 89-91, 178-179
Process flow, 89-91, 161
Process integration, 177-208
Process, voltage, and temperature (PVT), 299, 531,
 745, 867
Proportional to absolute temperature (PTAT), 745,
 762
PSRR, 790-791, 838
PTAT, see proportional to absolute temperature
Pulse density modulation, 1008
Pulse statement, 21
Pumps, 542-550
 driver, 546
Punch-through, 143
Push-pull amplifier, 698-704
PVT, see process, voltage, and temperature

R

Rail, 698
Random offsets, 775
RC circuit, 17-20, 50
 distributed, 49-52, 65, 89, 348
Reactive ion etching (RIE), 171-173
Recombination, 40, 252
References, 745-772
 bandgap, 757-772
 CTAT, 745, 761-762
 diode based, 757-772
 low voltage, 760, 770
 PTAT, 745, 762-765
 thermal voltage, 762-764
Registration errors, 170
Regularity, 412
Regulated drain CM, 645
RELTOL, 28
Resistance, 37
 calculation, 37
 looking into the drain, 668
 looking into the source, 669
 resistivity, 37
 sheet, 37
Resistor,
 common-centroid layout, 111-113
 delay through, 49-52
 dummy elements, 113
 guard rings, 110
 interdigitated layout, 110
 layout, 38, 56-57, 109-113

Resistor (continued),
 layout of corners, 38
 n-well, 32, 38-39, 94
 properties, 88
 sheet resistance, 37
 switched-capacitor, 843
 temp co, 88, 106, 116, 631,
 unit elements, 109
 Reticle, see mask
 Return Ratio, 1139-1141
 Reverse recovery time, 46-49
 RHP zero, 662, 685
 Ring oscillator, 339, 547
 Ringing, 695
 Rise time, 50, 317-320
 Routing, 430
 ROX (recessed oxide), see FOX (field oxide)
 RSHUNT, 29, 401

S

Saturation current, see Diode, saturation (scale)
 current, I_s
 Salicide, 199-200
 Saturation region, 143-145, 271
 S/H, see Sample-and-hold
 Sample-and-hold, 834-836, 838-842, 880-881,
 901-904, 935-938, 1052-1058
 acquisition time, 936
 aperture error, 937
 aperture jitter, 937
 aperture uncertainty, 937
 droop, 937
 gain error, 936
 hold mode, 937
 linearity, 936
 offset, 936
 overshoot, 936
 sampling error, 937
 settling time, 936
 single-to-differential, 1054-1058
 Scale current, see Diode, saturation (scale) current,
 I_s
 Scale factor, 36-37, 44, 53-56, 60-62, 75, 89, 114,
 117, 119-120, 132, 134, 146-147, 154, 157-158
 Scaling theory, 152
 Scanning Electron Microscope (SEM), 55, 79, 124
 Scattering, 52, 106
 Schmitt Trigger, 523-529
 applications, 527-529
 Schottky diode, 92, 760, 772
 Scope probe, 326-327
 Scribe, 75, 209, 211
 Select, 84-85, 179
 Self-aligned gate, 86-88
 Self-biased diff-amp, 534-538, 914, 920
 Self-biasing, 624-626, 750-770
 start-up circuit, 625, 629, 752-754
 Self-correcting phase detector, 588-590
 Sense amplifier design, 448-456
 clock feedthrough, 449
 contention current, 450
 creating an imbalance, 451-455
 kickback noise, 449-451, 456
 increasing input range, 454, 918-919
 removing sense-amp memory, 451
 reducing power, 453
 simulation examples, 454
 Sensing using delta-sigma modulation (DSM),
 483-519
 dynamic range, 490
 examples, 484-486
 feedback signal, 492-496
 Flash memory, 487-496
 incomplete settling, 496
 imagers, 504-519
 low pass filter, 507
 mismatches, 517-519
 noise issues, 506-507, 517
 offset, 497, 517-519
 parasitic capacitance, 492
 pixel, 504
 precision of sense, 485
 programmed state, 487
 resistive memory, 497-504
 sampling, 505
 sensing circuit, 488, 499, 511
 sigma-delta modulation, 484
 voltage to current conversion, 508-510
 Sensitivity analysis, 623, 626
 Series connection of MOSFETs, 322
 delay, 325-326
 Series-shunt feedback, 1045, 1113, 1141-1145
 Series-series feedback, 1128
 Settling time, 663, 782, 788-789, 800, 802, 804,
 810, 819, 840, 852-853, 880, 892, 895, 901-904,
 936, 945, 990, 993, 1000
 incomplete, 496, 502-503, 520
 Setup time, 388-389
 Shallow trench isolation (STI), 90-91, 177-178,
 180-188
 Sheet resistance, 37
 Shielding, 961
 Shift register, 402
 Shotgun shell, 242
 Short-channel,
 analog models, 297-302
 digital models, 314-316
 effects, 153-154
 MOSFETs, xxxi, 151-158
 tables, 300, 317, 320
 Short circuit protection, 826-827
 Shot noise, 242-244
 Shunt-series feedback, 1132
 Shunt-shunt feedback, 1046-1047, 1119,
 1145-1148

- Sigma-delta modulation, 1007-1015, see also
 - Sensing using delta-sigma modulation
 - first-order, 1010-1014
 - higher order, 1014
 - noise shaping, 1014-1015
 - resolution versus oversampling, 1015
- Signal to noise ratio (SNR), 230-234, 246, 266-267, 945-946, 956, 964
- Signal to noise and distortion ratio (SNDR), 956
- Silicide, 83, 88-92, 94, 199-201
- Silicide block, 89
- Silicon bandgap energy, 759
- Silicon on insulator (SOI), 180
- SIN SPICE source, 16-17, 282-287
- Single-ended to differential conversion, 894
- Single-ended to differential converter, Skew, 531-537
- Slew rate, 727, 787, 800, 853, 918, 922
- Small-signal,
 - AC analysis, 280
 - models, 279-288
 - signal parameters, 280, 287-289
- SNDR, see signal to noise and distortion ratio
- SNR, see signal to noise ratio
- SOI, see silicon on insulator
- Source-coupled multivibrators, 565
- Source-coupled pair, see differential amplifier
- Source-coupled VCO, 565
- Source degeneration, 667
- Source follower, 670, 690-698
 - body-effect, 691
 - input capacitance, 693, 1141
 - output stage, 696-698
- Space-charge region, see depletion region
- Spectral density of noise, 216-217
- Spectrum Analyzer, 216
- SPICE, 1, 8-29, 67, 78, 145
 - ABSTOL, 28
 - AC analysis, 19-20, 285
 - bipolar junction transistor, 15
 - breakdown, 58
 - common mistakes, 29
 - convergence, 28, 401
 - DC analysis, 13-15
 - diode breakdown voltage, 58
 - diode model, 14, 47-49, 758
 - distortion, 705-706
 - generating netlist, 8
 - GMIN, 29, 401
 - initial conditions, 24-25, see also UIC
 - integrator, 26-28
 - jagged plots, 29
 - level, 145
 - measuring currents, 274-275
 - mistakes, 29
 - models, parameters for long channel CMOS process, 145-147
 - SPICE (continued),
 - models, parameters for short channel CMOS process, 154, 158
 - MOSFET models, 302-304
 - noise analysis, 227-228, 237-238, 243-244, 251-252, 302-304
 - noiseless resistor model, 236-238
 - op-amp, 12, 841
 - opening a netlist, 8
 - operating point analysis, 9-10, 282-283
 - piece-wise linear (PWL) source, 23
 - problems, 29
 - pulse statement, 21
 - Q of an LC circuit, 25-26
 - RELTOL, 28
 - RSHUNT, 29, 401
 - Schottky diode, 772
 - simulating dynamic circuits, 401
 - SIN source, 16-17, 282-287
 - subcircuit (subckt), 13
 - switches, 24
 - .tran statement, 15, 286, 665-666, 705-706
 - transient analysis, 15-19, 21-25, 27-28, 286
 - transfer function analysis, 10-11
 - UIC, 24-25, 29
 - Voltage-Controlled Voltage Source (VCVS), 11-12, 628, 841
 - Voltage-Controlled Current Source (VCCS), 12
 - VNTOL, 27
 - Squaring circuits, 928
 - Square-law equations, 142-144, 271-272
 - Stability, 776-777
 - Standard-cell, 97
 - Standard deviation, 248-249
 - Start-up circuit, 625, 629, 752-754
 - Static logic, 353
 - Stepper, 34, 167-168
 - STI, see shallow trench isolation
 - Stick diagram, 422
 - Storage node, 397
 - Storage capacitance, 45-46
 - Storage time, 46-49
 - Streaming out, 36
 - Streets, see scribe, 209, 211
 - Strong inversion, 133
 - Student projects, 329
 - Substrate, 31
 - Substrate pump, 547
 - Subthreshold,
 - current, 149, 278
 - current source/sink, 635
 - g_m , 292-293
 - output resistance, 278
 - slope, 150
 - transconductance, 292
 - Switch logic, 369-370
 - Switched capacitor circuits, 492-494, 843-853
 - capacitor layout, 851-852

Switched capacitor circuits (continued),
 filter, 848-849
 integrator, 845-848
 resistor, 488-489, 843-848
 slew-rate requirements, 862

Switches, 311-317, 829-834

Symmetry, 618

Synchronization, 383, 551, 591, 596

Systematic offsets, 775

T

Tail current, 712, 720-722, 798, 803, 865, 868, 873, 882, 894, 898, 903-904, 907, 920-923

Technology computer assisted design (TCAD), 179

Telescopic diff-amp, see Cascode diff-amp

Temperature coefficient,
 bandgap references, 761-770
 diode, 759
 diode self-biasing, 761-762
 MOSFET-only, 633-635
 MOSFET voltage divider, 749-750
 positive, 106-107
 resistors, 88, 105-107
 resistor-MOSFET divider, 631-632, 746-749
 thermal voltage self-biasing, 762-765
 threshold voltage, 293-296, 750
 transconductance multiplier, 634-635, 754-755

Temp co, see Temperature coefficient

Temperature effects,
 bandgap of silicon, 293
 capacitor, 116
 KP (transconductance parameter), 295, 633
 MOSFETs, 293-296
 thermal voltage, 294
 threshold voltage, 293-296

TG (transmission gate), 324, 375, 829-832

THD, see Total harmonic distortion

Thermal (white) noise, 225-229

Thermal oxidation, 34, 161, 163-164, 182, 184, 190, 192, 211

Thermal voltage, V_T (kT/q), 39, 758
 change with temperature, 294

Thermometer code, 965-966, 974-975, 985-986, 988, 992

Threshold voltage, 135-140, 276, 467
 adjusting, 140, 190-192
 determining, 293
 matching, 616
 NMOS, 292, 300
 PMOS, 292, 300
 temperature behavior, 293-296

Timing errors, 583

Total harmonic distortion, 704-706

t_{ox} , 86-87, 114, 292, 300

.Tran statement, 15-16, 286

Transient SPICE analysis, 48, 52, 66-67, 79, 286, 705-706

Transconductance, 280, 297
 parameter, β , 142
 variation with frequency, 695

Transconductance amplifier, 796-798, 835-836

Transimpedance amplifier, 249-250, 261, 267, 666-667, 688-689, 1145-1148

Transmission channel, 538-541

Transmission gate, 324, 375, 402
 applications, 378
 delay through, 376
 layout, 415
 series connection, 377
 static gates, 379

Transit time, 45-47

Transition frequency, f_T , 290-292, 297-302, 309, 316, 863, 903, 906

Tri-state outputs, 351, 370
 buffer, 372-373
 phase detector output, 559

Trimming, 476, 753-755, 766, 769-770, 1007

Triode region, 141, 271, 278
 channel resistance, 278

t_{rr} , see diode, reverse recovery time

True-single phase clocked logic (TSPC), 409-410

t_s , see Diode, storage time

TSPC, see true-single phase clocked logic

τ_p , see Diode, minority carrier lifetime

Tub, 52

Tunneling,
 Fowler-Nordheim, 469-470, 487
 gate current (direct), 153-154, 220, 242, 300, 403, 468-476, 1146-1148
 zener diode, 253

Two's complement, 965-966

Twin well, 31, 52-55
 (well) module, 187-190

U

UIC (SPICE use initial conditions), 24-25, 28

Unbalanced input signals, 894-895

Unity-gain frequency, see f_{un} op-amp unity-gain frequency

Unit processes, 161-177

V

V_{CM} , see common-mode voltage

VCO, see voltage controlled oscillator

$V_{DS,sat}$, 144-145, 271

Velocity,
 carriers, 106-107, 142, 151, 153
 overshoot, 151, 153, 297, 302
 saturation, 151, 291, 299, 634
 speed of light, 65

VLSI, 1, 411

VNTOL, 27

Voltage coefficient, 107, 116
 Voltage-controlled oscillator (VCO), 552, 561, 595
 characteristics, 561
 current starved, 561
 for use with the PFD, 561
 logic based, 567
 source coupled, 565
 use with XOR phase detector, 557
 Voltage dividers, 746-756
 Voltage follower, 1143
 Voltage generators (charge pumps), 542-548
 example, 547-549
 higher voltages (Dickson), 544-545
 Voltage references, 745-772
 Voltage regulator, 812-819
 V_{ov} , see Overdrive voltage
 V_T , see Thermal voltage, kT/q
 VTC, see Inverter, transfer characteristics
 V_{THN} , see Threshold voltage, NMOS
 V_{THP} , see Threshold voltage, PMOS

W

Wafer, 3, 32, 161, 180
 manufacture, 161-163
 probe, 208-211
 production, 162

Waterfowl, 242
 W_{drawn} , see drawn width
 Weak inversion, 132-133, 149-150, 301
 Well, 31-58, 53
 contact, 96
 triple, 53, 187, 278
 White noise, 219-221, 225, 240-242, 253-254
 Wide swing diff-amp, 736-740
 Workfunction,
 gates, 191, 304
 W - $2W$ current mirror, 1043-1044

X

X_d , 136-137
 X_{dl} , 144
 XOR gate, 366, 380
 phase detector, 553, 555-556

Y

Yield, 152, 209, 412

Z

Zener diode, 253-254, 268
 Zero-nulling resistor, 685, 774-782
 Zipper Logic, 407