

# Index

---

## A

AAF. *See* Antialiasing filter.  
Accumulate-and-dump circuit, 129, 132  
Accumulator, 19, 129, 134, 235-236  
Accuracy, 195, 200, 269  
Active-RC Integrator, 73, 75,  
    filter, 80, 82-83, 87-88, 97-98, 101, 103-106,  
        109, 112, 116  
Adaptive filtering, 93  
ADC. *See* Analog-to-digital converter.  
Adder, 94, 126, 145, 147, 151, 156, 158-159, 273,  
    309, 320, 322  
Aliasing, 21, 27-72, 93, 127-129, 140, 143-144,  
    306, 317  
    quantization noise, 169  
Amplitude modulation, 187, 207, 285, 288, 315  
Analog RC filter, 80, 82-83, 87-88, 97-98, 101,  
    103-106, 109, 112, 116  
Analog Sinc averaging filter, 10-11  
Analog-to-digital converter (ADC), 21, 27, 94,  
    164-224, 225-284  
    1-bit, 236  
    bandpass, 134, 287-300  
    gain, 246  
    high-speed, 301-324  
    Nyquist-rate, 43, 63, 220-225, 241, 306-308  
    pipeline, 38  
    SPICE models for, 119-123, 160, 176  
Antenna, 292  
Antialiasing filter (AAF), 27-40, 73, 93, 139, 144,  
    198-199, 203, 205-206, 302  
Aperture jitter, 179, 202, 317  
Autocorrelation function (ACF), 183  
Autozeroing, 57-58, 62, 71  
Average power, 183-187, 198  
Average value, 44, 168, 183-187, 200, 212, 244,  
    315  
Averaging,  
    bandpass filter, 19, 134-139, 160, 290-292  
    clock jitter, 198  
    decimation, 209-211  
    filter, 13-14, 126, 131, 133-134, 201, 220, 223,  
        234, 239-241, 266-267  
    highpass filter, 19, 129, 134  
    improving signal-to-noise ratio (SNR), 13,  
        190-194

Averaging (continued),  
    interpolating filter, 43-50, 71, 139-142, 199,  
        235, 273  
    limiting bandwidth, 13-14  
    linearity requirements, 194-195  
    noise, 250  
    quantization noise, 202, 211  
    without decimation, 132-133

---

## B

$B$ , bandwidth of the input signal, 129-130, 133-134,  
    182, 198-199, 208-209, 212, 220, 229,  
    237-241, 248, 250, 267, 285, 290, 296, 324  
B device. *See* Nonlinear-dependent source.  
Bandpass filter, 19, 96, 103-111, 129, 134-139, 160  
Bandpass modulators, 263, 285-298, 301, 324  
Bennett's criteria, 165-166  
Bilinear transfer function, 95  
Binary offset, 123-125, 204-205, 274  
Biquad filters, 73, 99-101  
Biquadratic transfer function, 99  
Bottom plate of a capacitor, 67  
Bottom plate sampling, 39-40, 54, 219

---

## C

CAI, *See* continuous-time analog integrator.  
Calibration, 322  
Canonic digital filter, *See* Digital filter.  
Capacitance,  
    bottom plate, 54  
    input, 86, 93, 247, 282, 319  
    load, 88-89  
    noise calculation, 307  
    parasitic, 66, 69, 83-84, 219, 279-281  
Capacitive feedthrough, 39, 251, 257  
Cascade of integrators and combs filters (CIC  
    filters), 142  
Cascaded modulators, 233, 264, 275-280  
Charge injection, 39-40, 251, 257, 294  
Charge pump, 120  
Chopper stabilization, 71  
CIC filters, *see* Cascade of integrators and combs  
    filters  
Clock generation, 53, 316-318  
Clock jitter, 178-189  
Coherent sampling, 175-176, 202  
Comb filter, 8-21, 25, 129-131, 133-143, 224  
Common-mode feedback (CMFB), 60-61, 88-89  
Common-mode rejection ratio (CMRR), 87, 252  
Common-mode voltage,  $V_{CM} = 500$  mV in this book  
Comparator,  
    clocked, 163, 319-320  
    gain, 244-246, 259, 262-263, 295  
    hysteresis, 246-247

Comparator (continued),  
 LSB, 204  
 noise, 163, 246-247, 250  
 offset, 246-247  
 placement, 261  
 Constant delay, 10, 31, 145, 171  
 Continuous-time analog integrator (CAI), 73, 75, 95  
 Continuous-time comb filter, 10-11  
 Continuous-time Fourier transform, 23  
 Convolution, 35, 175  
 Correlated double sampling (CDS), 59, 66, 71  
 Cosine window. *See* Hanning window.  
 Counter, 45, 126-129, 130, 270-271

---

## D

DAC. *See* Digital-to-analog converter.  
 DAI. *See* Discrete analog integrator.  
 dBc (decibels with respect to the carrier), 177, 189  
 Dead zones, 215, 217, 232  
 Decimation, 33-34, 127-129, 132, 222-223,  
 306-312, 321-322  
 bandwidth limitations, 34  
 decimating filter, 143-144, 157, 203, 239  
 Delta modulation, 199  
 Delta-sigma modulation, 199, 233-234 *See*  
 noise-shaping.  
 Demodulator, 199-200, 235-236, 271-272  
 Diff-amp, 61, 86, 89, 222  
 Differentiator, 14-15, 119, 275-276  
 Digital averaging filter, 192, 220  
 Digital comb filter, 11-18  
 Digital filter, 119-162  
 biquad, 155-159  
 canonic, 151-155  
 finite impulse response (FIR), 133-134,  
 145-146, 161  
 infinite impulse response (IIR), 134  
 stability, 146-147  
 Digital integrator, 19-21, 235  
 Digital  $I/Q$  extraction to baseband, 297-298  
 Digital resonator, 134-139, 160  
 Digital signal processing (DSP), 27, 32, 203  
 Digital-to-analog converter (DAC), 69, 119-123,  
 204-205, 213-214, 235-236, 272-275  
 Dirac delta impulse, 23, 28  
 Discrete analog integrator (DAI), 66-70, 90-93,  
 233, 251, 260  
 Discrete-time integrator, 90-95  
 Distortion, 35, 37, 49, 65, 71, 176-178, 187,  
 206-208, 213-214, 225-226, 249, 251-252, 269,  
 273, 288-289  
 Dither, 166, 195-198, 242, 282  
 Droop, 37, 39-41, 47-48, 127, 129, 132, 142, 157,  
 209, 212, 223, 241, 267  
 DSP. *See* Digital signal processing.  
 Dynamic range, 83, 177, 251, 276, 279

---

## E

Effective number of bits,  $N_{eff}$ , 173, 176, 179,  
 181-182, 188, 202  
 Error feedback, 235, 271-275, 283  
 Expected value, 186

---

## F

Feedback gains in a DAI, 260  
 Filters,  
 active-RC, 75  
 accumulate and dump, 129  
 bandpass, 19, 96, 103-111, 129, 134-139, 160  
 bilinear, 95  
 biquad, 73, 99-101  
 comb filter, 8-21, 25, 129-131, 133-143, 224  
 decimating filters, 143-144, 157, 203, 239  
 digital. *See* Digital filter.  
 exact frequency response of discrete-time filter,  
 94  
 finite impulse response (FIR), 133-134,  
 145-146, 161  
 $g_m$ -C filters. *See* transconductor-C filter.  
 highpass, 19, 129, 134  
 in a higher-order modulator, 267  
 infinite impulse response (IIR), 134  
 integrating filters, 73-118  
 interpolating filters, 139-142  
 ladder filter, 117-118  
 lowpass, 75  
 MOSFET-C, 83  
 Q peaking and instability, 112  
 Sinc, 133  
 SNR, 82-83, 87  
 stability in digital filters, 146  
 switched-capacitor, 90-95  
 transconductor-C filter, 97  
 tuning, 80, 83, 86, 93, 98  
 Finite impulse response (FIR) filter, 133-134,  
 145-146, 161  
 Finite op-amp gain-bandwidth product, 55-57,  
 78-79  
 First-order noise shaping, 208, 210, 224, 233, 238,  
 254  
 FIR. *See* Finite impulse response.  
 Forward modulator gain, 243  
 Fourier series, 23  
 Fourier transform, 24

---

## G

Gain error term, 176-177, 204, 213-214, 219,  
 247-249, 280  
 $g_m$ -C (transconductor-C) integrators, 86-90  
 Gaussian probability distribution, 187, 197

---

**H**

Hanning window, 175  
 Harmonics,  
   square wave, 189  
 High-frequency transconductor, 89-90  
 Highpass filter, 19, 129, 134  
 Higher order modulators, 267  
 Hold register, 46-50  
 Hysteresis, 246-247

---

**I**

I, in phase or real component, 4-6, 285-286,  
   297-299  
 IIR. *See* Infinite impulse response filter.  
 Impulse sampling, 28-31  
 Infinite impulse response (IIR) filter, 134  
 Integrator,  
   analog. *See* Continuous-time analog integrator.  
   digital, 19-21, 235  
   discrete analog integrator (DAI), 66-70, 90-93,  
     233, 251  
   gain, 113, 244-246, 248, 255, 257-260, 264,  
     276, 303  
   leakage, 247-248, 282  
 Interpolation, 32, 43-46, 48-50, 71, 139-142, 235,  
   273  
 Interpolative modulators, 271-272  
 Inverse Fourier transform, 23

---

**J**

Jitter. *See* Clock jitter.

---

**K**

K, oversampling ratio, averaging factor, or  
   interpolation increase, 33, 43-50  
   clock jitter, 181-182  
 K-Delta-1-Sigma, xvi, 222, 303-304, 320-324  
 K-path,  $K_{path}$ , 50-53, 220-224, 228, 230, 301-302,  
   317

---

**L**

Ladder filter, 117-118  
 Least significant bit (LSB), 119, 204  
 Limit cycle oscillations, 241, 315  
 Linear phase, 25, 30-31, 145  
 Linearity, 212, 214  
 Linearity requirements for averaging, 191-195  
 Lowpass filters, 73-74  
 LSB. *See* Least significant bit.

---

**M**

MASH modulator. *See* Noise-shaping  
 Matching, 53, 55, 94, 200, 211, 212, 230, 279, 323  
 Matlab, 171  
 Mean, 186  
 Miller integrator, 75  
 Mixed-signal system block diagram, 27  
 Modulation noise, 206-208, 212, 237  
 Modulator,  
   bandpass, 287-297  
   cascaded, 275  
   first-order, 233  
   gain, 243  
   higher-order, 265-269  
   interpolative, 271-272  
   multibit, 269  
   noise-shaping, 199-201, 233  
   predictive, 200  
   second-order, 253  
 MOSFET-C Integrators, 83-85  
 Multibit modulators, 269  
 Multiplexer (MUX), 236, 297  
 Multipliers, 34, 64, 94, 291, 297-298  
 Multistage noise shaping modulator (MASH), 275  
 MUX. *See* Multiplexer.

---

**N**

Noise,  
   averaging, 190  
   clock jitter,  
     correlated double sampling (CDS), 59, 66, 71  
     modulation, 206-208, 212  
     quantization noise, *See* Quantization noise.  
 Noise transfer function (NTF), 200-201, 205-208,  
   224, 233, 253-254  
 Noise-shaping (NS), 199-201, 233, 253  
 Non-overlapping clock generation, 51, 53, 304, 317  
 Nonrecursive filters, 133  
 Number representation, 123-126  
 Nyquist,  
   differences between noise-shaping converters,  
     241  
   frequency, 17, 21, 27, 29, 31, 37-40  
   rate ADC, 43, 63, 220-225, 241, 306-308

---

**O**

Offset,  
   autozero, 57-59, 62  
   comparator, 221-222, 224, 246  
   DAC, 214  
   op-amp, 54-55, 58-62, 66, 72, 212, 247-250  
 Offset binary format, 123-125, 204-205, 274

Overflow, 124-126, 143, 145-148, 211, 214-215, 221, 273  
 Oversampling,  
   Oversampling ratio. *See* K, oversampling ratio  
   or averaging factor.

---

## P

Passive noise-shaping, 205-207, 216-219  
 Path settling time, 302  
 Pattern noise, 241  
 PDF, probability density function, 185  
   average value (mean or expected value), 186  
   Gaussian, 186-187, 197-198  
   standard deviation, 186  
   variance, 186  
 Phase-delay relationship, 4  
 Phase,  
   discrete analog integrator (DAI),  
   digital filter, 10-11, 13-15, 17-21, 130, 151  
   linear, 9, 30-31, 145, 171  
   noise, 188-189  
   response, 76, 79-81, 88, 104  
   shift, 4-5, 8, 95-96, 141  
 Phase-locked loop, 180  
 Pipeline ADC, 38, 122, 176, 220, 307  
 PLL. *See* Phase-locked loop.  
 Power  
   average, 183-184, 186-187  
 Power spectral density (PSD), 166, 172, 183, 188,  
   190, 193  
   jitter, 186-189, 198  
   quantization noise, 166, 168, 193  
 Predictive coder. *See* Predictive modulator.  
 Predictive modulator, 199-200  
 Probability density function. *See* PDF.  
 PSD. *See* Power spectral density.

---

## Q

Q (pole quality factor), 99-106  
   high Q, 107-114, 117  
   peaking and instability, 112-113  
 QAM. *See* Quadrature amplitude modulation.  
 Quadrature amplitude modulation, 285  
 Quadrature or imaginary component, 4-6, 285-290,  
   297-299  
 Quantization noise, 122, 163-178, 185-196, 211,  
   224, 233-234, 237, 240, 242-243, 251, 253,  
   266, 273-276, 279, 312-314  
 Quantize, 33  
 Quantizer, 43, 125, 163-164, 203-204, 235-239,  
   269, 271-274, 314

---

## R

Random signals, 185, 196, 216  
   quantization noise, 168-169  
   spectral density, 190  
   standard deviation, 186  
   variance, 186  
 RCF. *See* Reconstruction filter.  
 Reconstruction filter (RCF), 27, 29, 32, 39, 87, 166,  
   139, 185, 187, 235, 273  
 Resolution, 13, 56-57, 83, 176, 191, 194-195,  
   199-200, 203, 209-210, 215, 230, 237-240,  
   253-254, 265, 269, 273, 306-307, 322  
   loss because of jitter, 178-181  
 Return-to-zero (RZ), 35, 37, 39, 42  
 Ripple, 241-242, 282, 288-289  
 RMS quantization noise voltage, 166, 168-170, 211,  
   237, 249, 253, 266-267  
   calculating from a spectrum, 185, 187, 193  
 Root mean square (RMS) voltage, 168  
 RZ. *See* Return-to-zero.

---

## S

Sample and hold (S/H), 27, 35-43, 54-66  
   matching of the capacitors used,  
   single-ended to differential, 65  
   subtraction, 63  
 Sample frequency reduction. *See* Decimation.  
 Sampler, 28-35  
 Sampling and Aliasing,  
   coherent. *See* coherent sampling.  
 Sampling gate, 28  
 Second-order noise-shaping, 227-229, 253  
 Settling time, 57, 60-61, 221, 248-249, 302  
 SFDR. *See* Spurious-free-dynamic range.  
 SFFM. *See* Single frequency frequency modulation.  
 S/H. *See* Sample and hold.  
 Side lobes, 47-48  
 Sigma-delta modulation. *See* noise-shaping  
 Signal-to-noise and distortion ratio (SINAD). *See*  
   Signal-to-noise plus distortion ratio (SNDR).  
 Signal-to-noise plus distortion ratio (SNDR), 93,  
   176-178, 187, 197, 202  
 Signal-to-noise ratio (SNR), 70, 82-83, 87, 137,  
   163-202, 208-229, 238-242, 247-248, 250-253,  
   265  
 Signal transfer function (STF), 200-201, 205-206  
 Sinc filter. *See* digital averaging filter.  
 Sinc function, 32, 36-39, 47-49  
 Sinc-shaped digital filter, 126-144  
 Slew-rate, 57, 179, 248-249  
 Smoothing filter. *See* reconstruction filter.  
 SNR. *See* Signal-to-noise ratio.  
 SNDR. *See* Signal-to-noise plus distortion ratio.  
 Spike, 177

Spurious free dynamic range (SFDR), 177, 242  
 Squarewave, 22, 25, 126-128, 166, 175  
 Stability,  
   digital filter, 146  
   filter, 112  
   noise-shaping modulator, 258-264, 269, 275,  
   293  
 Standard deviation, 186, 198  
 Subtraction, 63, 126, 271  
 Switched-capacitor filters, 91-95, 98-99, 106-111  
 Switches,  
   capacitive feedthrough, 39, 251  
   charge injection, 39-40, 251, 257, 294  
   MOSFET, 318

---

## T

Taylor series, 6  
 T/H, *See* Track-and-hold.  
 Thermometer code, 308  
 Time-domain description of reconstruction, 31-33  
 Time-interleaved ADC, 220-222, 232, 313, 323  
 Track-and-hold, 41-43  
 Transconductor-C filters, 86  
   bilinear, 97  
   biquad, 114  
 Triangular response, 133  
 Tuning, 80, 83, 86  
   orthogonal tuning, 98  
 Two's complement, 123-126, 131, 137, 147,  
   204-205  
   subtraction, 126

---

## U

Unit step function. *See*  $u(t)$ .  
 $u(t)$ , 35-36

---

## V

Variance, 168, 186  
 $V_{CM}$ , ( $V_{DD}/2$  or 0.5 V in this book)  
 $V_{DD}$ , (1.0 V in this book)  
 Von Hann window. *See* Hanning window.

---

## W

White noise, 169, 172, 269  
 Windowing, 175-176  
 Wireless, 285, 291  
   I/Q extraction, 297-298

---

## Z

$z$   
   defined, 7, 12  
   domain, 6-8  
   to s-transform (practical), 51, 149  
 $z$ -plane, 7, 15  
 Zero-Order Hold (ZOH), 27  
 Zero padding, 44-45