

H.W. #19 CpE 100 Spring 2021

Show your work for credit (!) and put a box around each of your answers if possible!

1. Design, and simulate the operation of, a 5-bit row decoder (32 outputs) for a 32 x 32 register file (RF). (5 points)