

H.W. #21 CpE 100 Spring 2021

Show your work for credit (!) and put a box around each of your answers if possible!

1. Design a 4-bit up-counter and simulate its operation. Make sure your counter has a reset input. (3 points)
2. Repeat problem 1 but for a down counter.