

H.W. #5 CpE 100 Spring 2021

Show your work for credit (!) and put a box around each of your answers!

1. Make schematics and corresponding symbol views for 2-input NAND, NOR, AND, and OR gates. Simulate the operation of your gates to show they function properly, see example below. (8 points)

