

H.W. #9 CpE 100 Spring 2021

Show your work for credit (!) and put a box around each of your answers!

1. Work Exercise 2.14. Verify your answers using only inverters, and 2-/3-input logic gates in LTspice. (6 points)