

4/2/09 Lecture 19

$$A = 10$$

$$C = 1 \text{ pF}$$


$$v_{in} = 1 \text{ V}$$

$$f = 10^6$$

$$|i| = 2\pi \cdot 10^6 \cdot 10^{-12} \cdot 11 \cdot 1$$


$$= 6.28 \cdot 10^{-6} \cdot 11$$
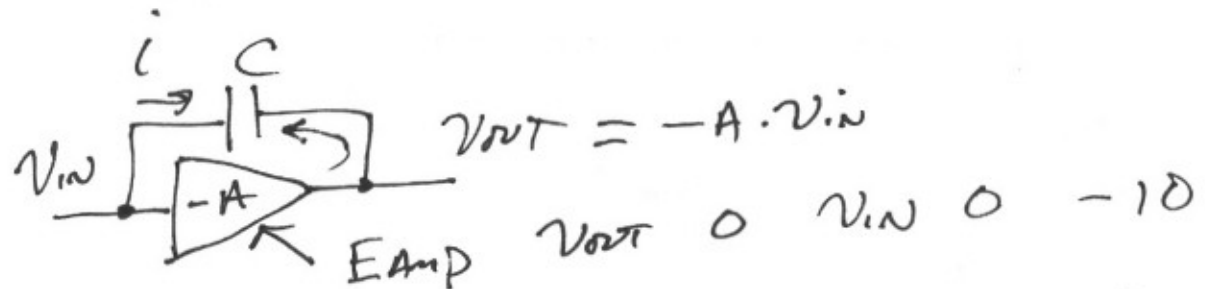
$$\approx \underline{\underline{69.14 \text{ A}}}$$








$$i = \frac{v_{in} - (-A \cdot v_{in})}{\frac{1}{j\omega C}} = j\omega C (1 + |A|) v_{in}$$

$$i = \frac{v_{out} - v_{in} \cdot \frac{-v_{out}}{|A|}}{\frac{1}{j\omega C}} = v_{out} \left(1 + \frac{1}{|A|}\right) \cdot j\omega C$$

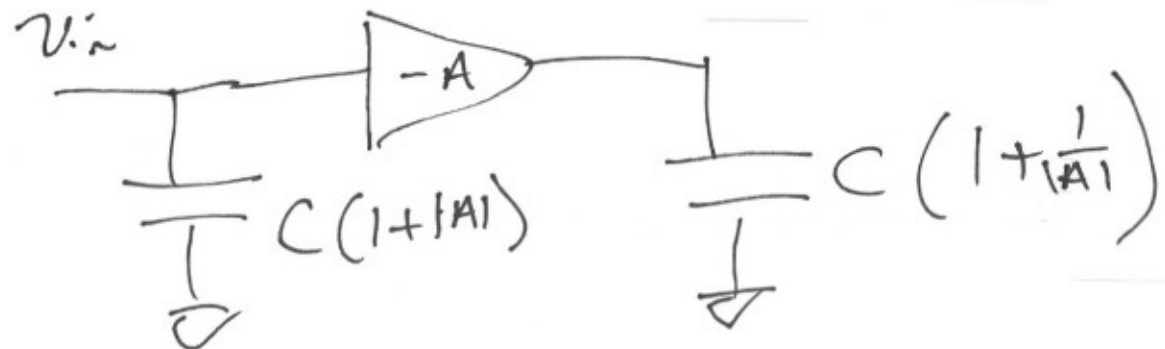


1)

Pass Gates

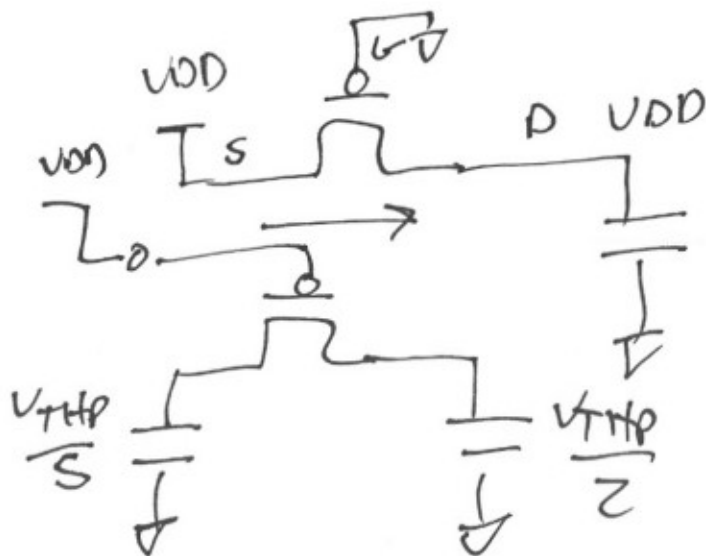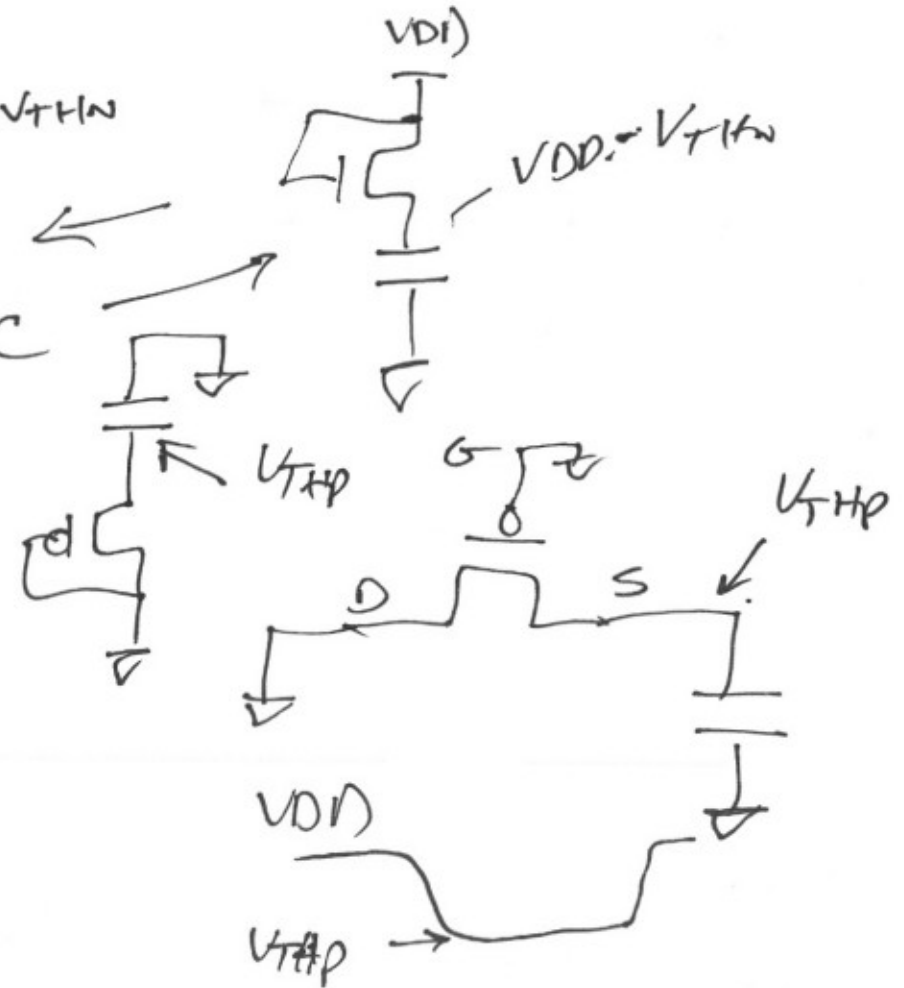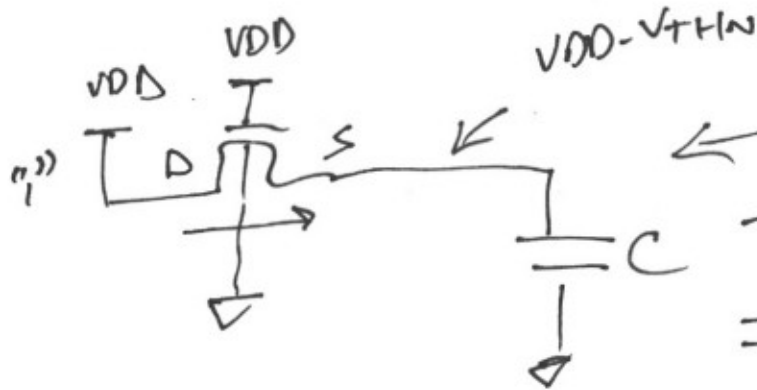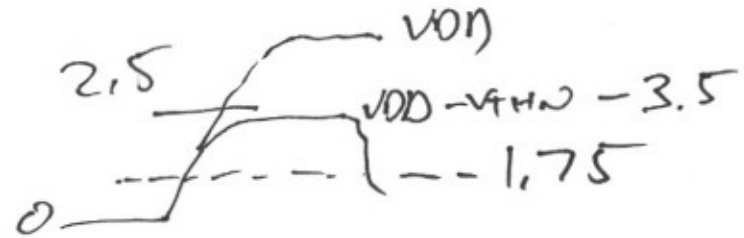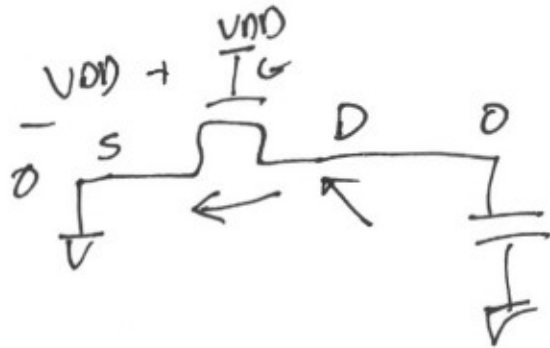


2)

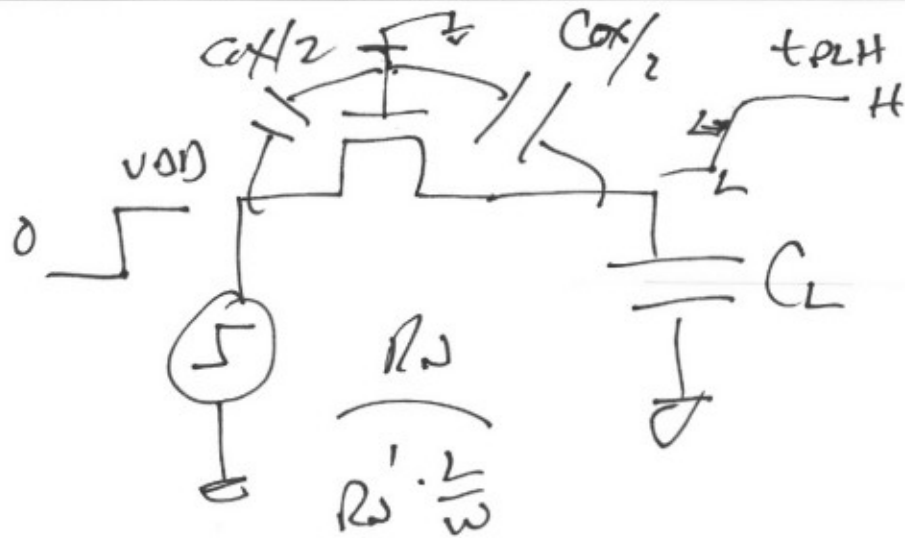

C_L is big

$$t_{PLH} \approx 0.7 R_N C_L$$


C_L is small

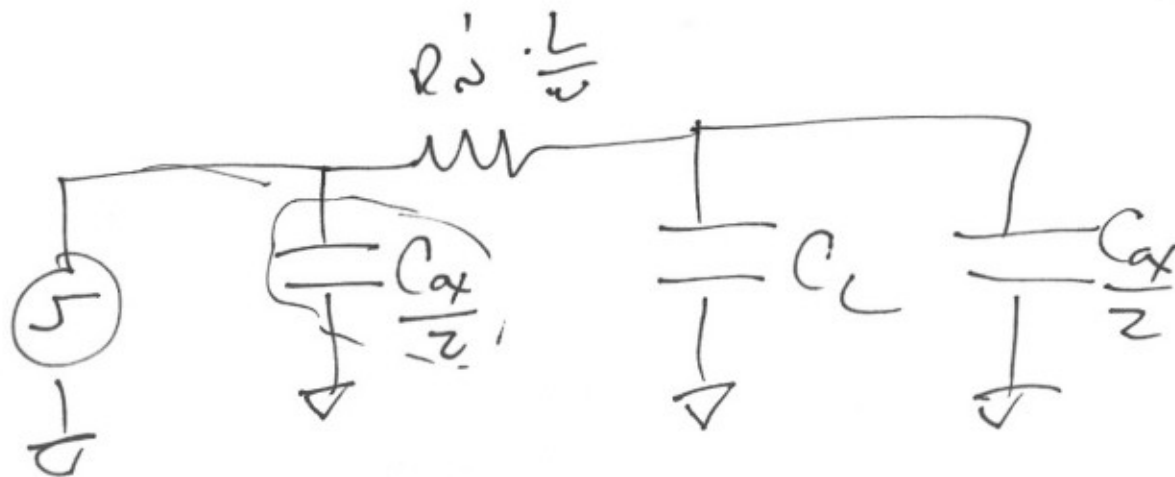

$$t_{PLH} \approx 0.7 R_N \left(C_L + \frac{C_{ox}}{2} \right)$$


3)

Transmission Gate (TG)

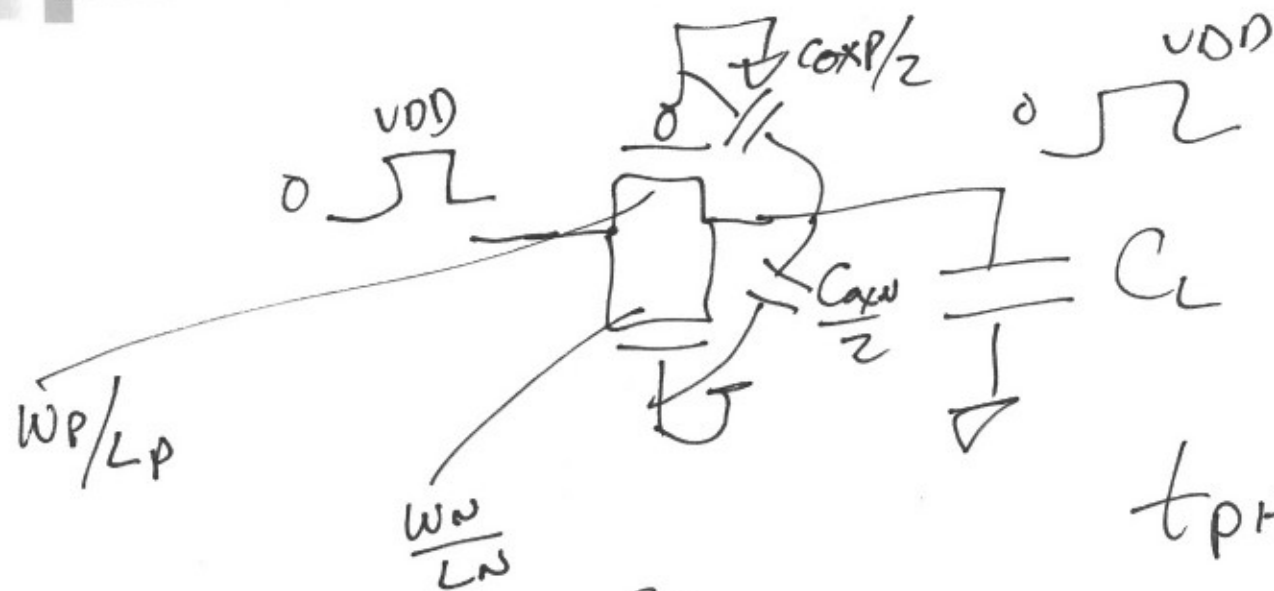

$$t_{pHL} = t_{pLH} =$$

$$0.7 (R_n || R_p) \cdot$$

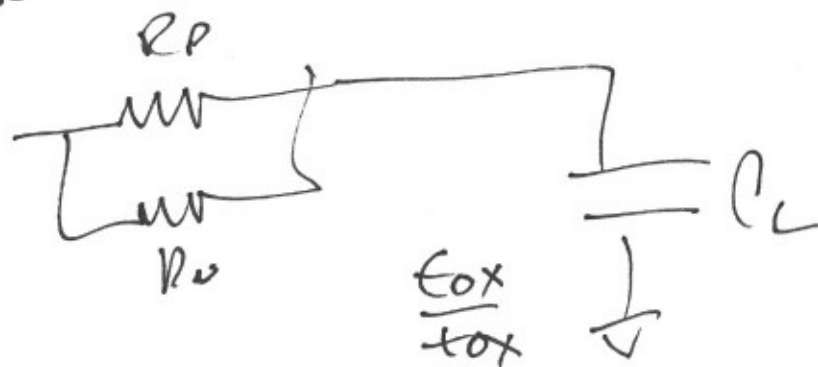





$$\left(C_L + \frac{C_{xp}}{2} + \frac{C_{xn}}{2} \right)$$

$$C_{xp} = C_{ox}' \cdot W_p L_p$$



$$C_{xn} = C_{ox}' \cdot W_n L_n$$

4)


$$V_{DD} = 5V$$

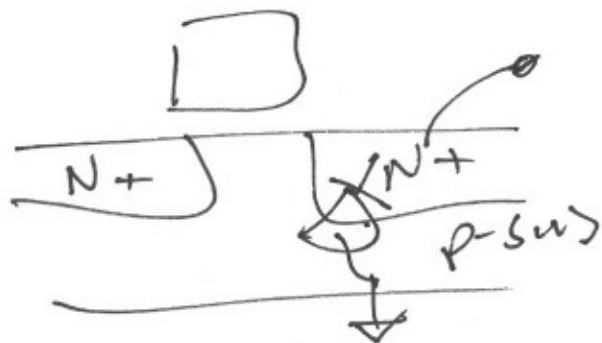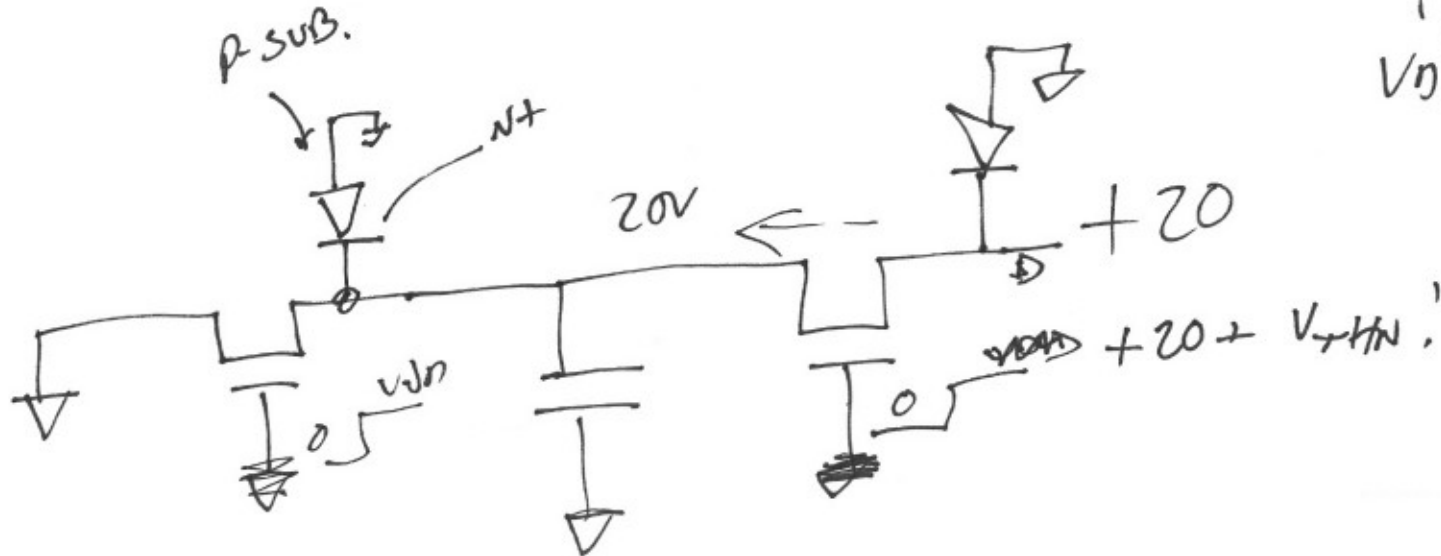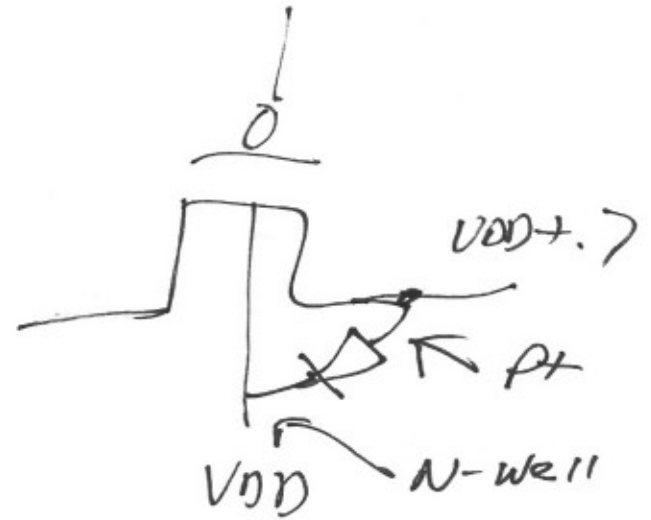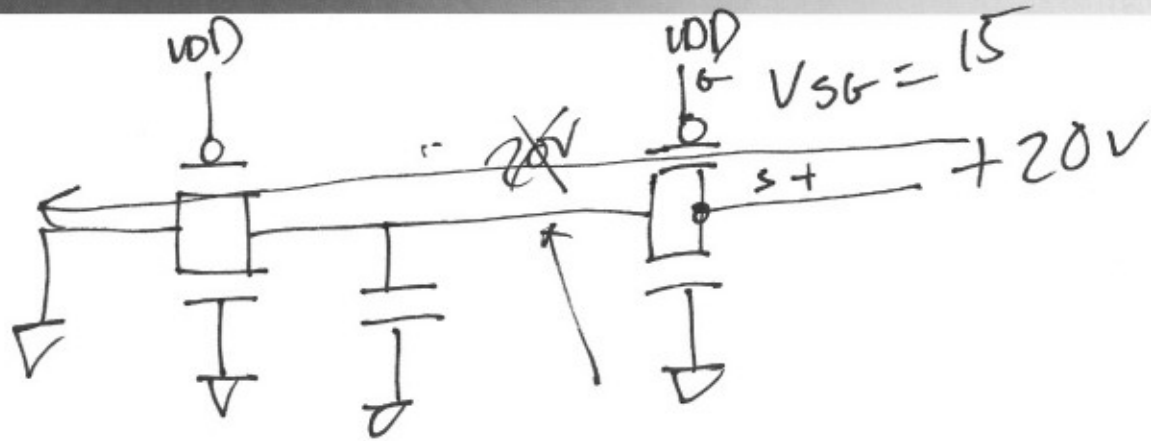


5)

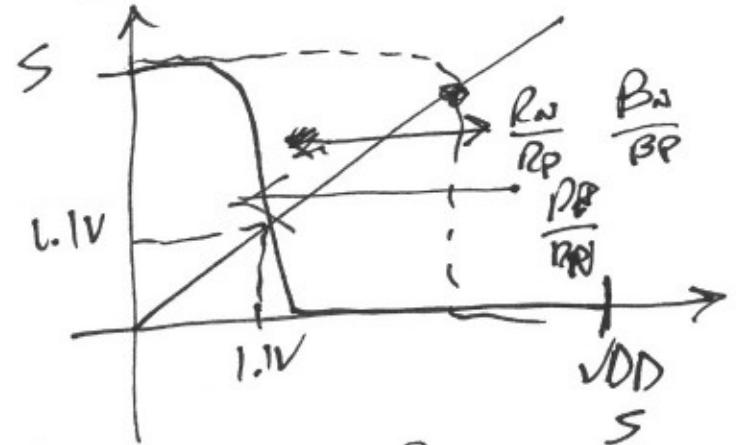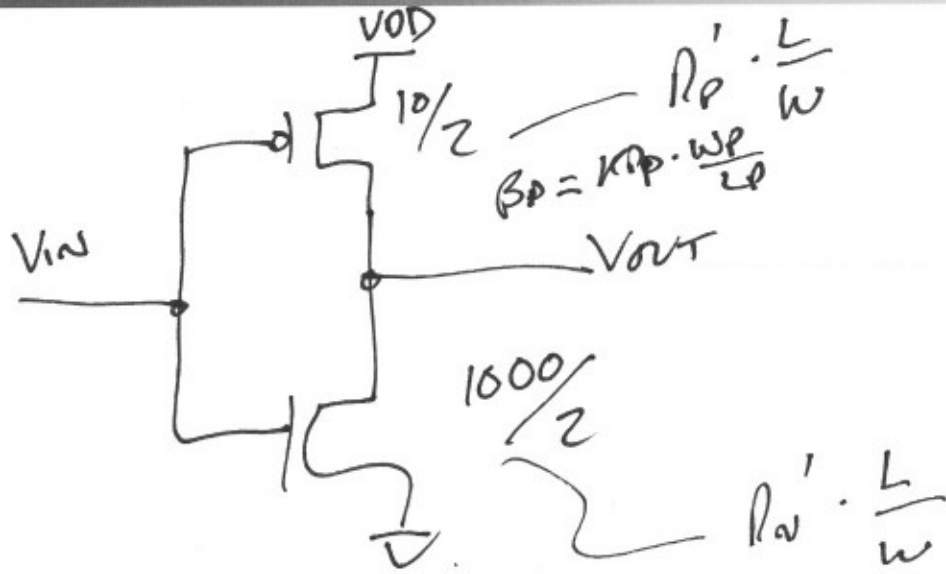

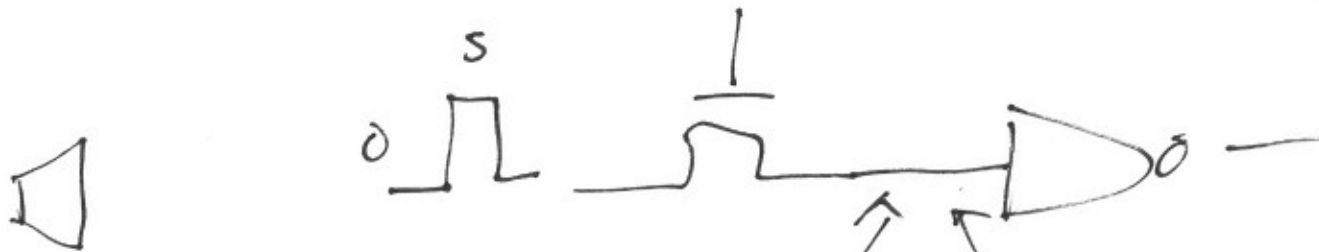$\frac{B_n}{B_p}$
 $\frac{R_n}{R_p}$
 $USP \downarrow$




7)

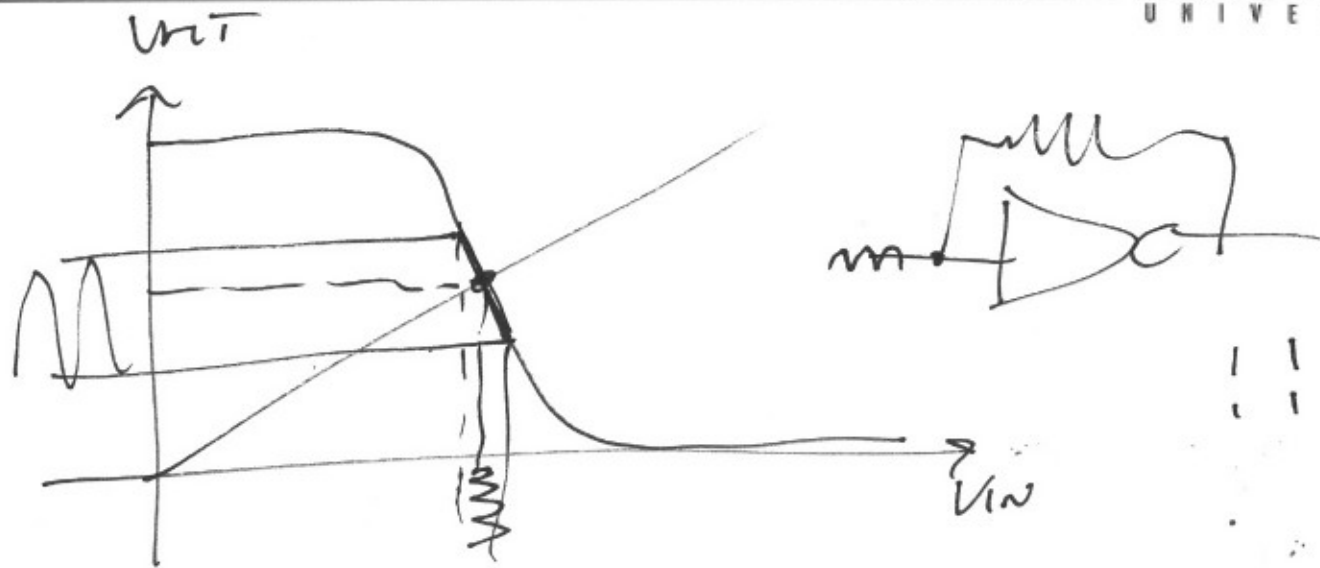

8)

Switching point T

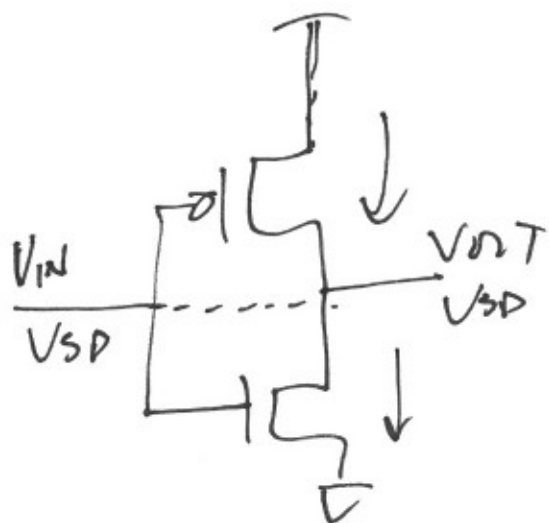

$$V_{OS} \geq V_{GS} - V_{THN}$$

$$V_D - V_S \geq V_G - V_S - V_{THN}$$

$$V_D \geq V_G - V_{THN}$$

$$0 \geq -V_{THN}$$

yes
satisfy.

$$\frac{\beta_N}{2} (V_{SP} - V_{THN})^2 =$$

$$\frac{\beta_P}{2} (V_{DD} - V_{SP} - V_{THP})^2$$

$$\sqrt{\beta_N} V_{SP} - V_{THN} \sqrt{\beta_N} =$$

$$\sqrt{\beta_P} V_{DD} - \sqrt{\beta_P} V_{SP} - \sqrt{\beta_P} V_{THP}$$


$$V_{SP} (\sqrt{\beta_N} + \sqrt{\beta_P}) =$$

$$V_{THN} \sqrt{\beta_N} + \sqrt{\beta_P} V_{DD} - \sqrt{\beta_P} V_{THP}$$

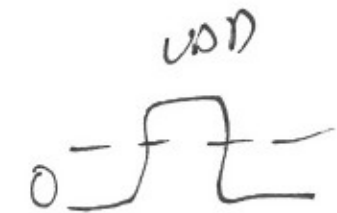9)


$$V_{SP} = \frac{V_{THN} \sqrt{\beta_N} + \sqrt{\beta_P} V_{DD} - V_{THP} \sqrt{\beta_P}}{\sqrt{\beta_N} + \sqrt{\beta_P}}$$

$$V_{SP} = \frac{V_{DD} - V_{THP} + V_{THN} \cdot \sqrt{\frac{\beta_N}{\beta_P}}}{1 + \sqrt{\frac{\beta_N}{\beta_P}}}$$



$$\begin{aligned} V_{THN} &\approx V_{THP} \\ \beta_N &= \beta_P \leftarrow \omega_p = \omega_n \cdot 2 \\ V_{SP} &= \frac{V_{DD}}{2} \end{aligned}$$

10)

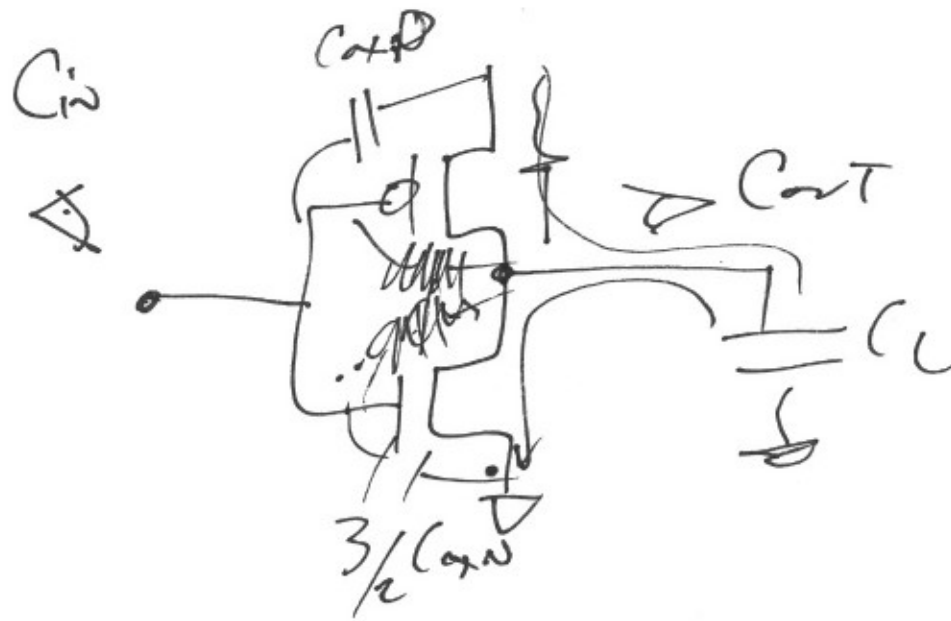

$$t_{pLH} = 0.7 R_o \cdot C_L$$

$$t_{pHL} = 0.7 R_n C_L$$

$$C_{IN} = \frac{3}{2} C_{oxN} + \frac{3}{2} C_{oxP}$$

$$C_{OUT} = C_{oxN} + C_{oxP}$$