
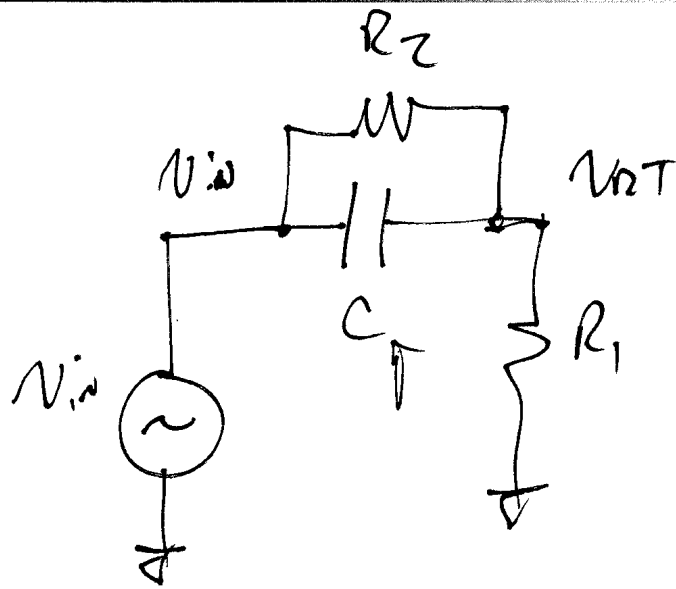


1)

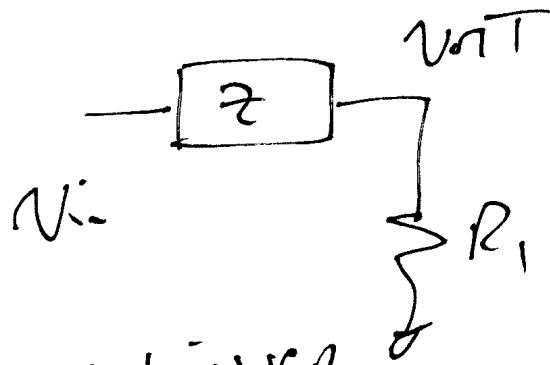

$$z = \frac{R_2 \cdot \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}}$$

$$= \frac{R_2}{1 + j\omega C R_2}$$



$$\frac{v_{OT}}{v_{in}} = \frac{R_1}{R_1 + z}$$

$$\frac{R_1}{R_1 + R_2} \cdot \frac{1 + j\omega C R_2}{1 + j\omega C R_1 \parallel R_2} = \frac{R_1}{R_1 + \frac{R_2}{1 + j\omega C R_2}}$$

$$= \frac{R_1 (1 + j\omega C R_2) \cdot \frac{1}{R_1 + R_2}}{R_1 + R_2 + j\omega C R_2 R_1 \frac{1}{R_1 + R_2}}$$

2)