


## Lecture 19

April 13, 2011

Make-up lecture this



Friday, 5 - 6:15 pm

MEC 206

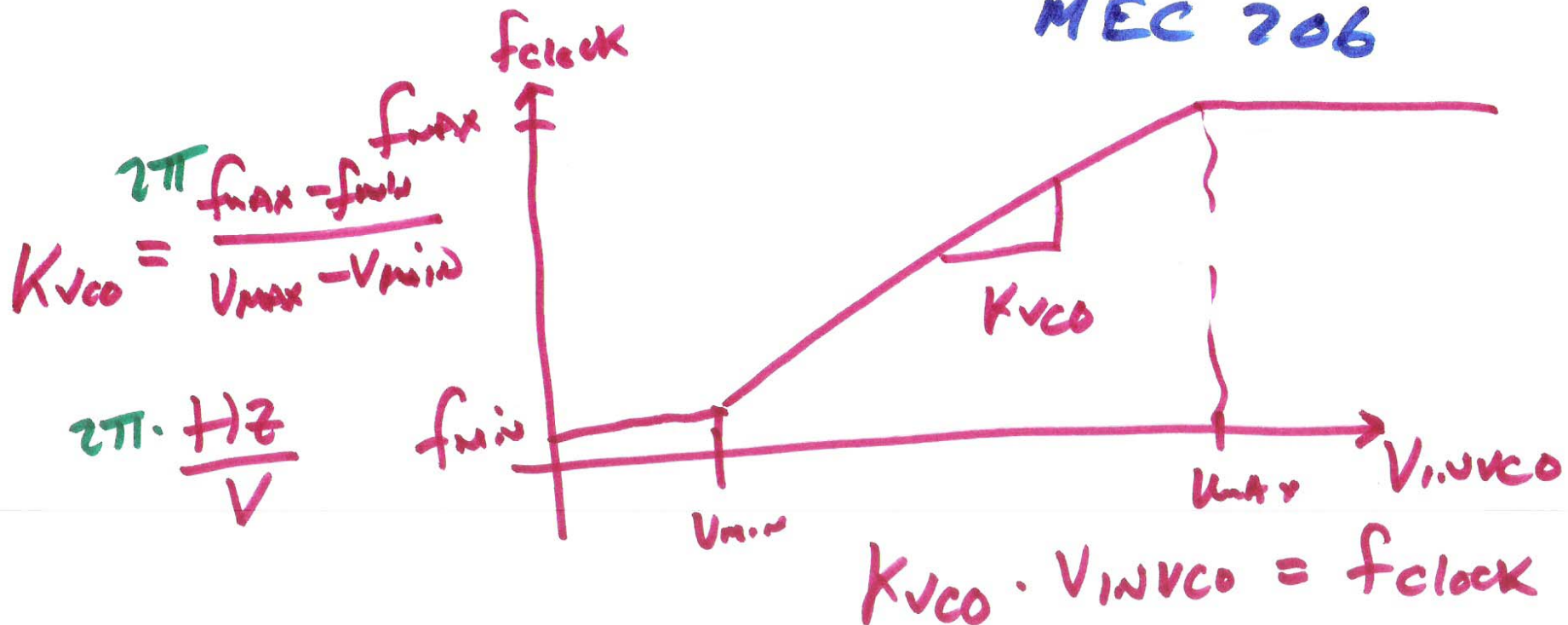

1)

# feeding back phase

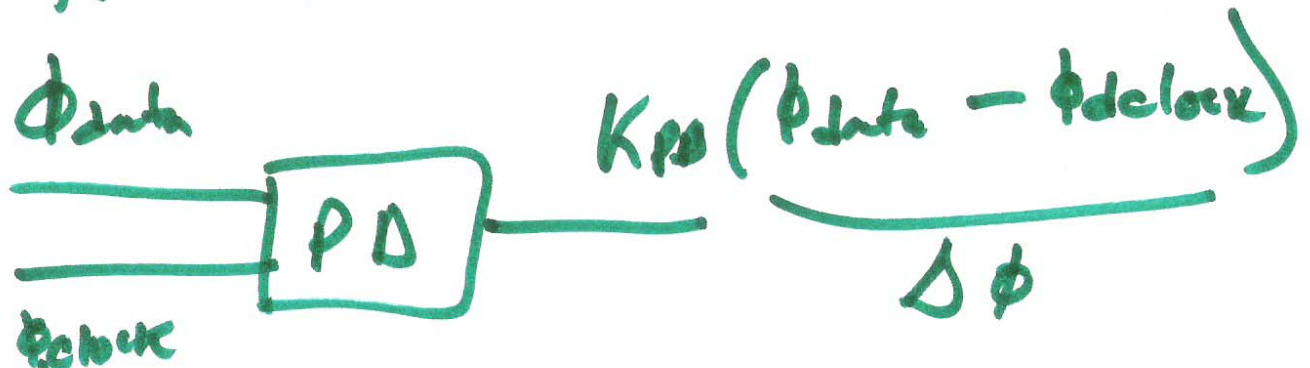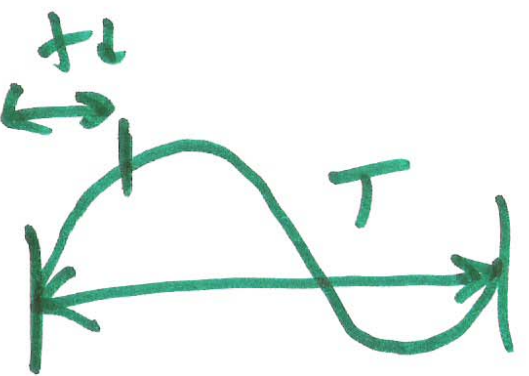

$$\phi = 2\pi \cdot \frac{t_d}{T} = 2\pi f \cdot t_d$$

$$\omega_{clock} = \frac{2\pi}{T_{clock}} = 2\pi f_{clock}$$

$$\phi_{clock} = \int_0^{t_d} \omega_{clock} \cdot dt = \frac{2\pi}{T_{clock}} \cdot t_d$$

2)  $\int dt \rightarrow \frac{1}{s}$  time domain

$$= \frac{1}{s} \cdot \frac{K_{VCO} \cdot V_{inVCO}}{\omega_{clock}}$$

$$\int dt \rightarrow \frac{1}{s}$$

$$\int \cos \omega t dt = \sin \omega t$$

$$\text{let } x = \omega t$$

$$\frac{dx}{dt} = \omega$$

$$dt = \frac{dx}{\omega}$$

$$\int \cos x \cdot \frac{dx}{\omega} = \frac{\sin \omega t}{\omega}$$


3)

$$\int \frac{\cos \omega t + \frac{t}{T}}{f(t)} = \frac{e^{j\omega T} + e^{-j\omega T}}{2} \cdot \frac{1}{j\omega}$$

$$= \frac{1}{s} \cdot f(t)$$


$s = \cancel{\sigma} + j\omega$   
for Sinusoidal Analysis

$$\frac{\sin \omega T}{\omega}$$


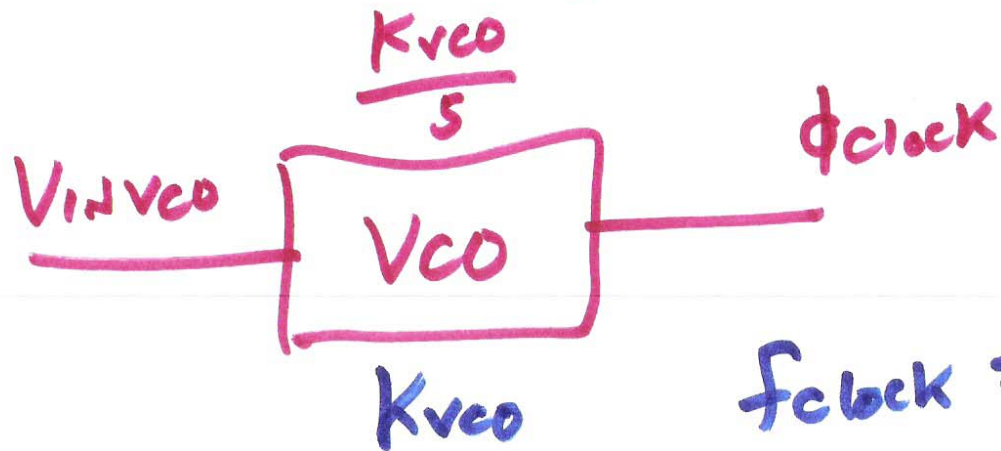


$$f_{clock} = K_{vco} \cdot V_{inVCO}$$

4)

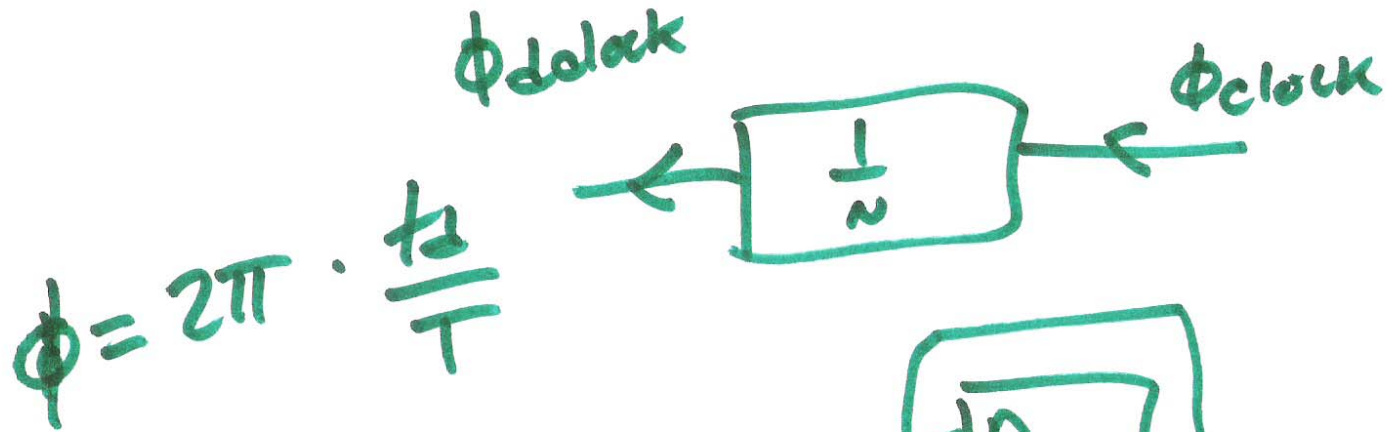

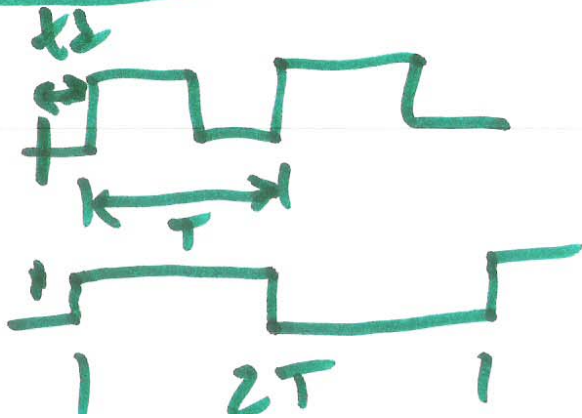
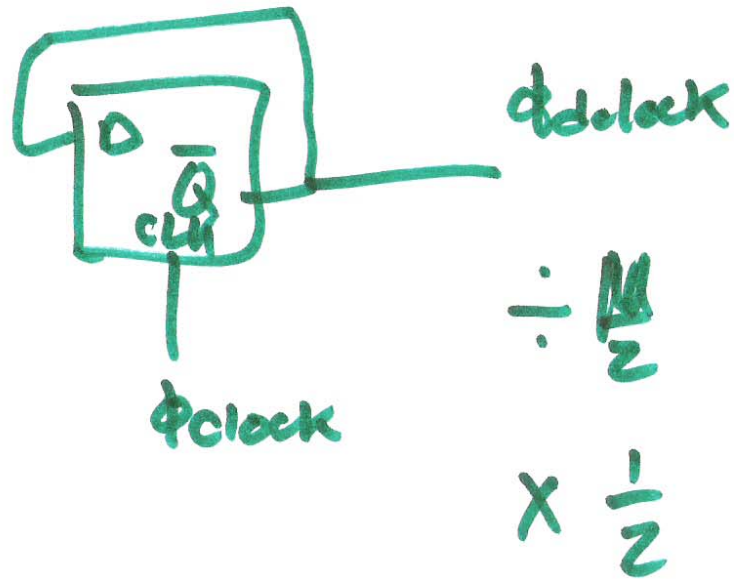
$$\phi_{dlock} = \frac{1}{N} \cdot \phi_{clock}$$



$$2\pi \cdot \frac{t_d}{2T} = \frac{\phi}{2}$$

5)

# PLL Block diagram

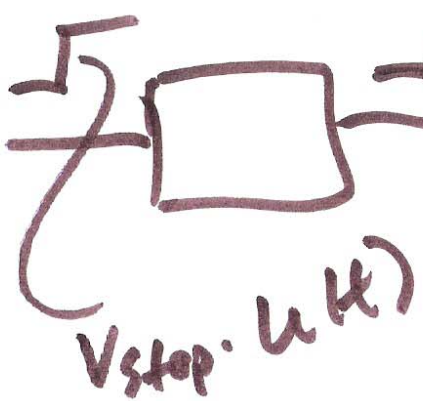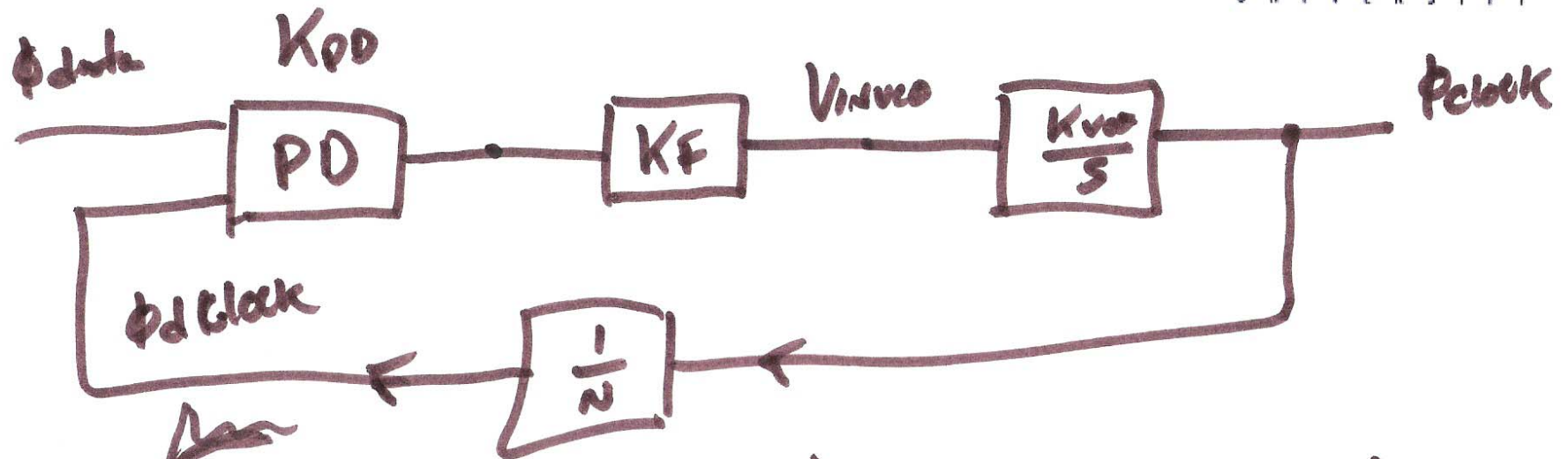

$$K_{PD} \left( \phi_{data} - \frac{\phi_{clock}}{N} \right) \cdot K_F \cdot \frac{K_{VCO}}{s} = \phi_{clock}$$


$$\frac{V_{stop}}{s} \phi_{data} \cdot K_{PD} \cdot K_F \cdot \frac{K_{VCO}}{s} = \phi_{clock} \left( 1 + \frac{K_{PD} K_F K_{VCO}}{N s} \right)$$

$$\phi = \frac{f}{s}$$


$$\left( \frac{\phi_{data}}{\phi_{clock}} \right)^{-1} = \frac{K_{PD} \cdot K_F \cdot K_{VCO}}{s + \frac{K_{PD}}{N} \cdot K_F \cdot K_{VCO}}$$

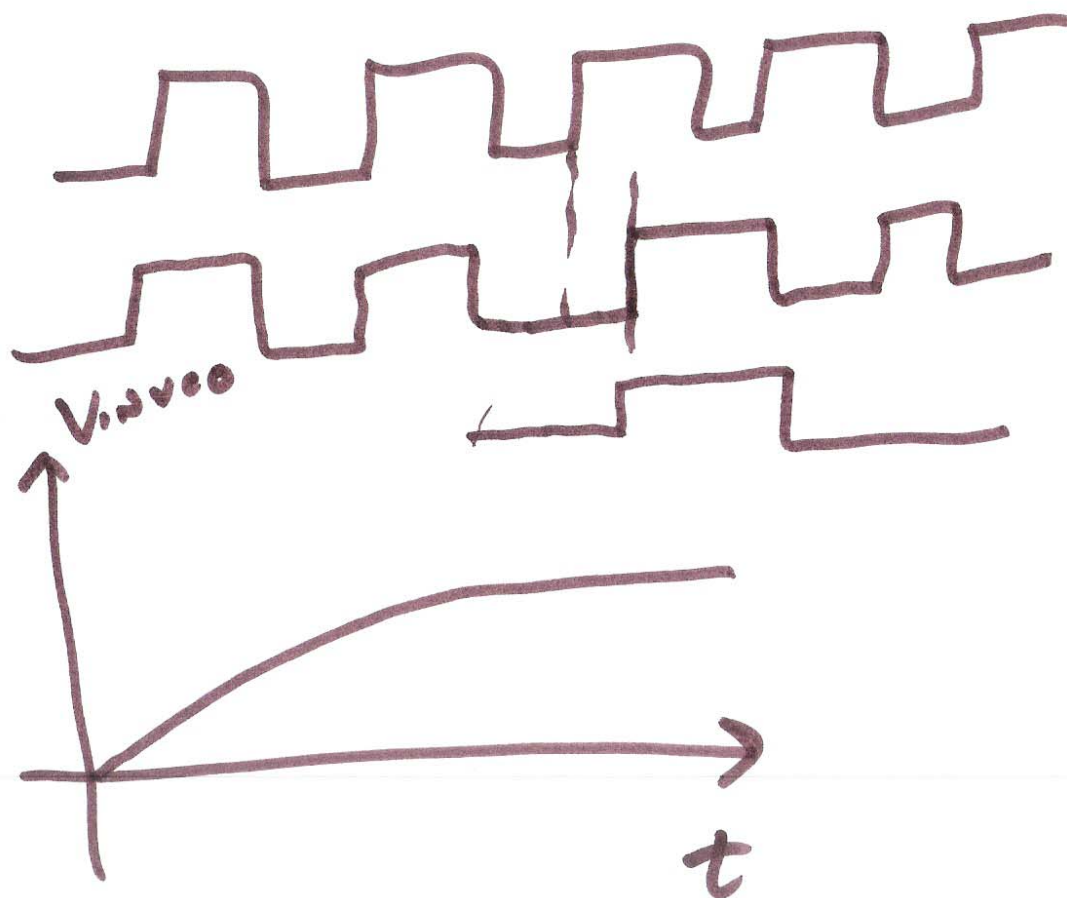6)

Step in frequency  
 step in phase  
 or a step in both




→

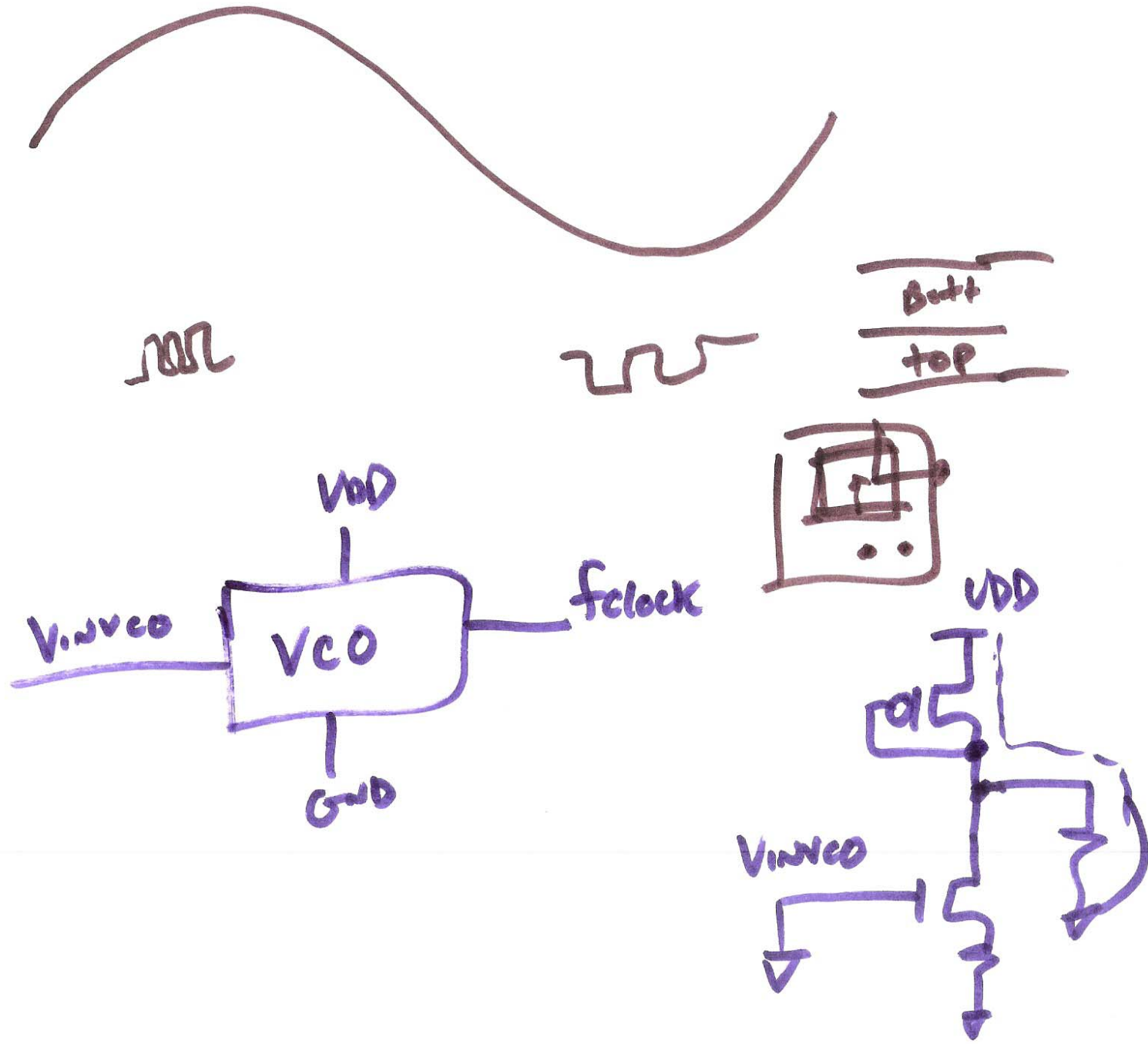


8)





# Linear voltage to current conversion

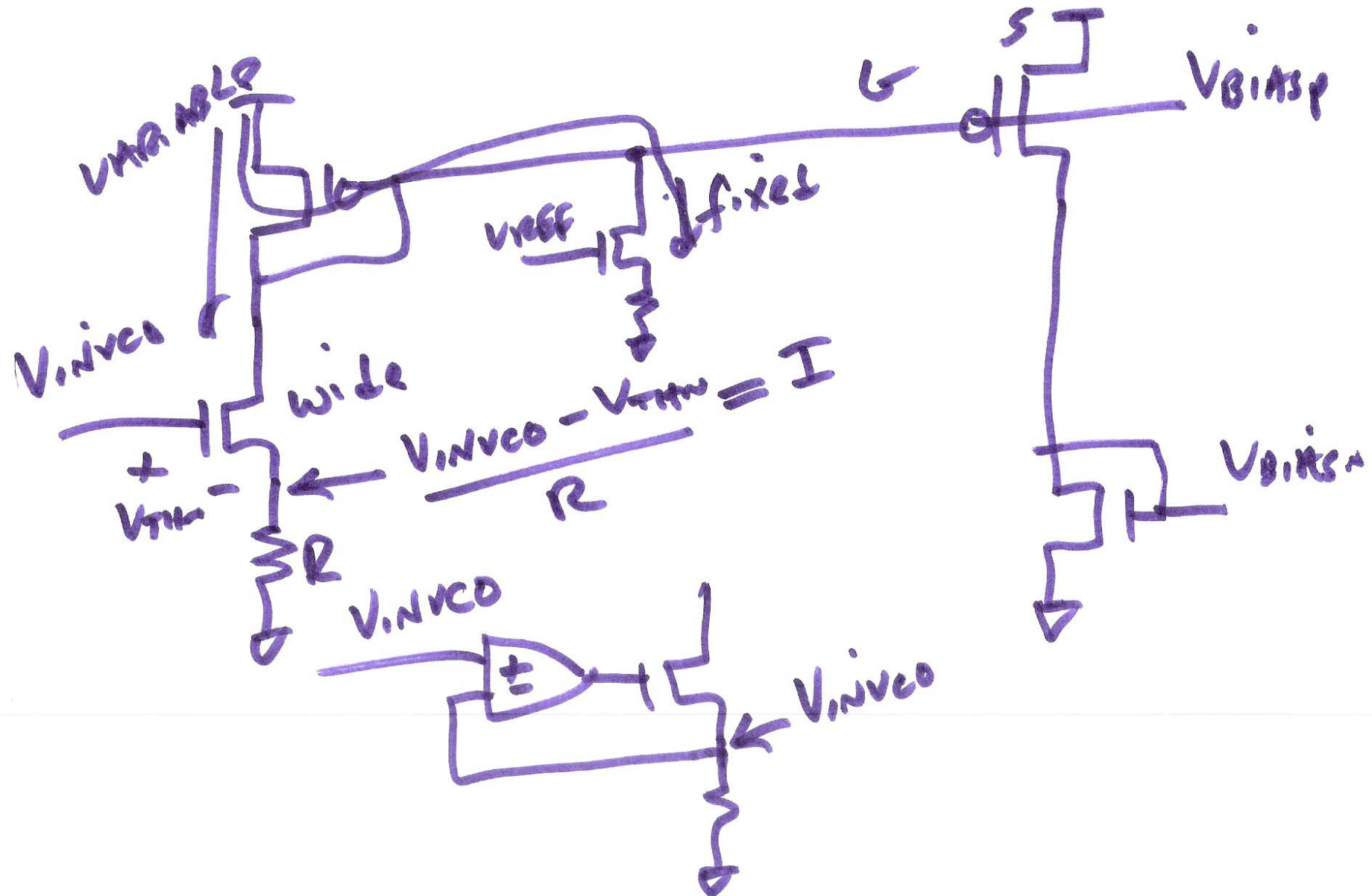

a)

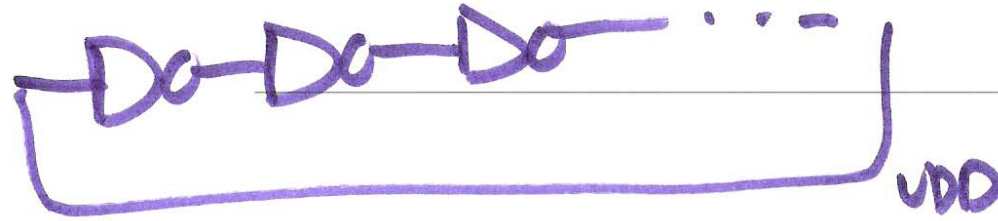

d

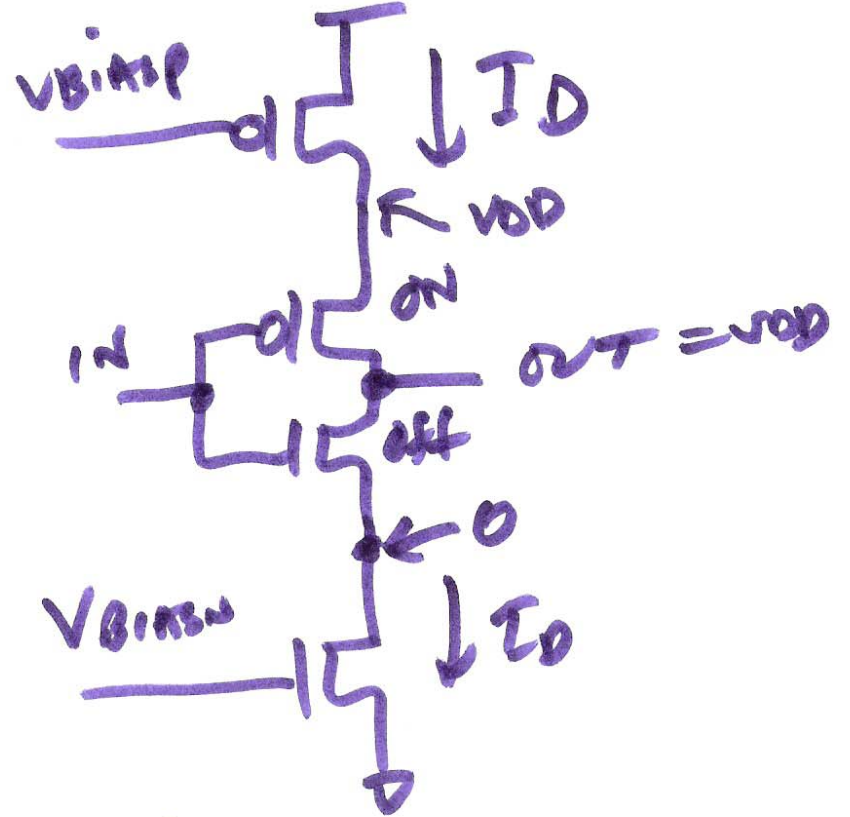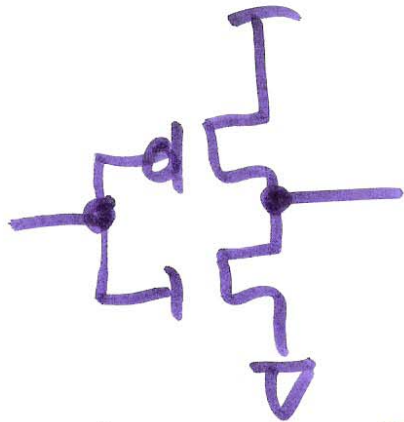

due manday  
 design a current  
 Staved VCO in  
 180nm process  
 100 → 200 MHz  
 VS.

VDD  
 TEMP  
 Show linear feedback  
 vs  
 $V_{inVCO}$

10)