
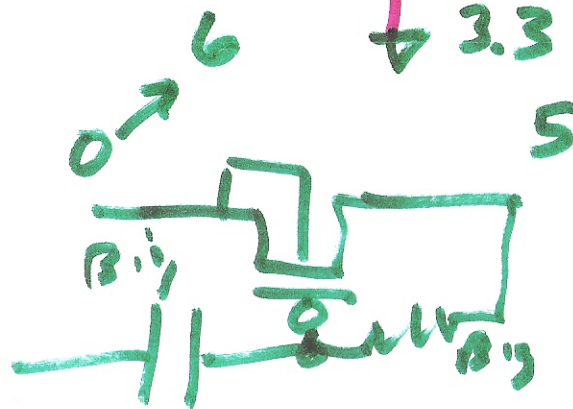
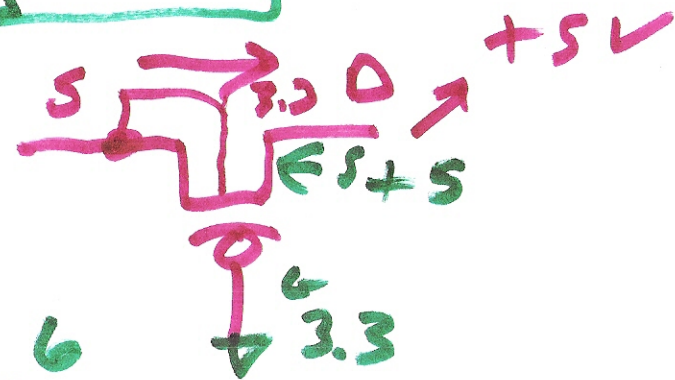
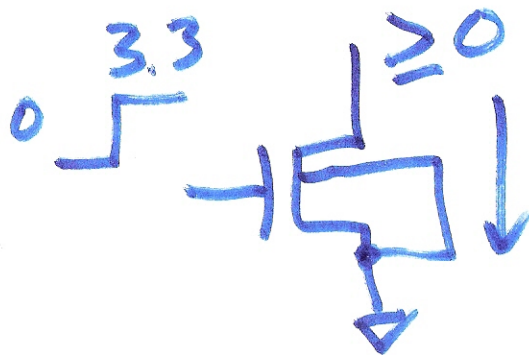


# ECE 5/472 Power Electronics




## Lecture 13

Sept. 24, 2010

Boost

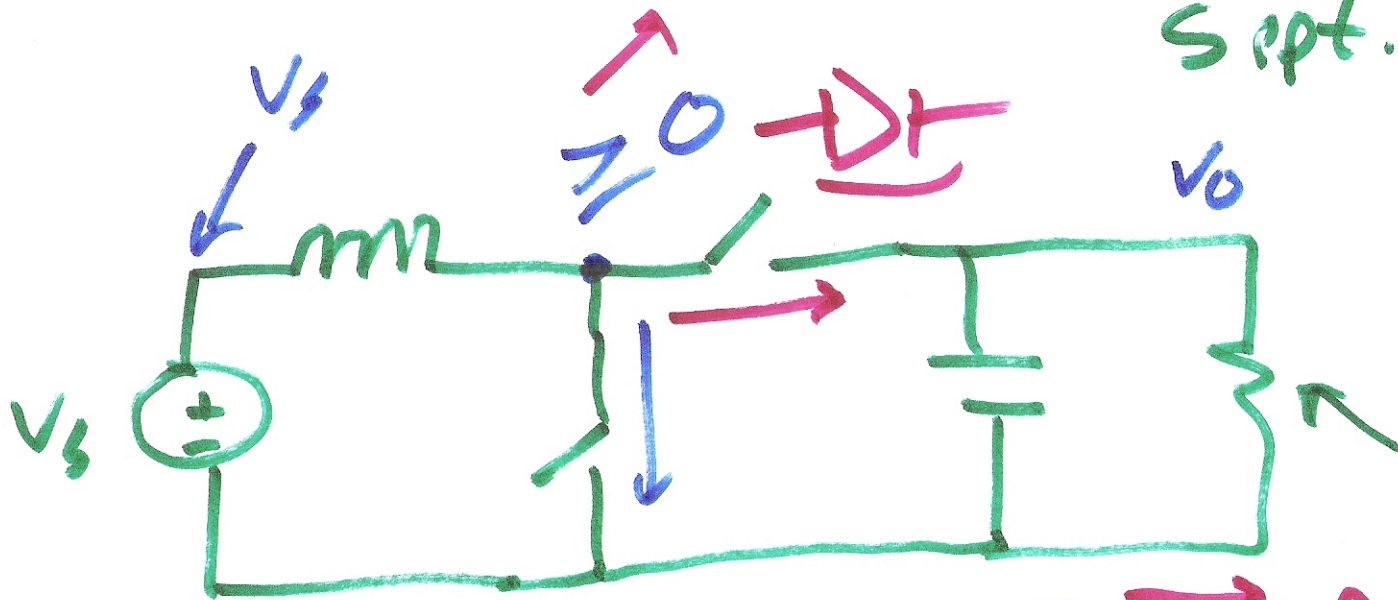


1)

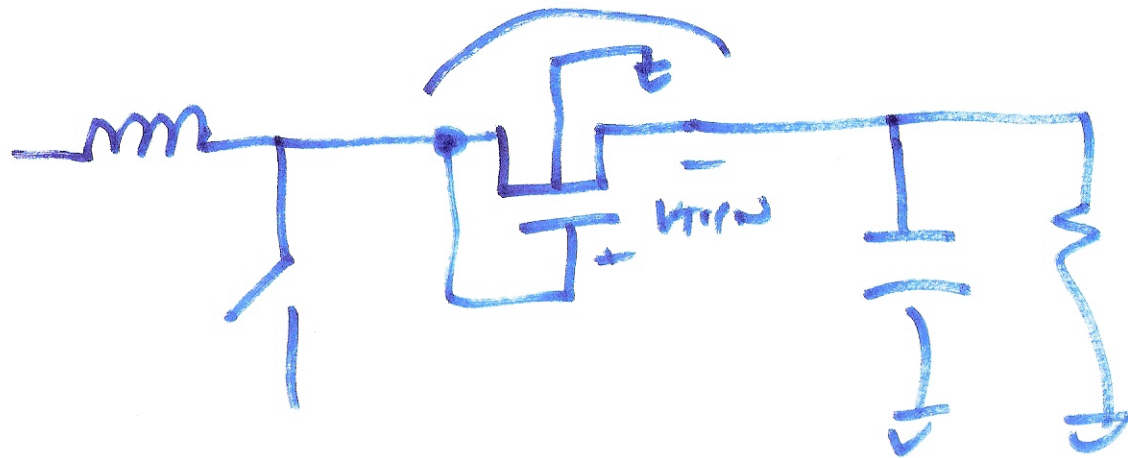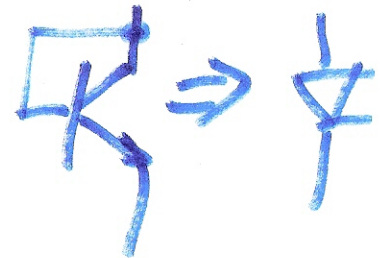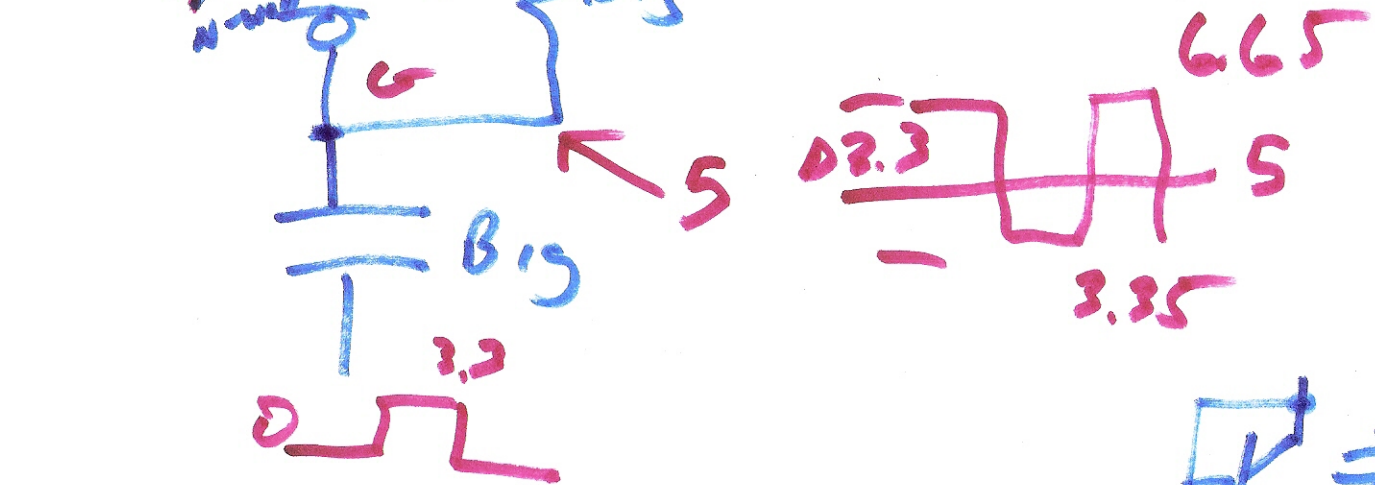

2)

# Study Review

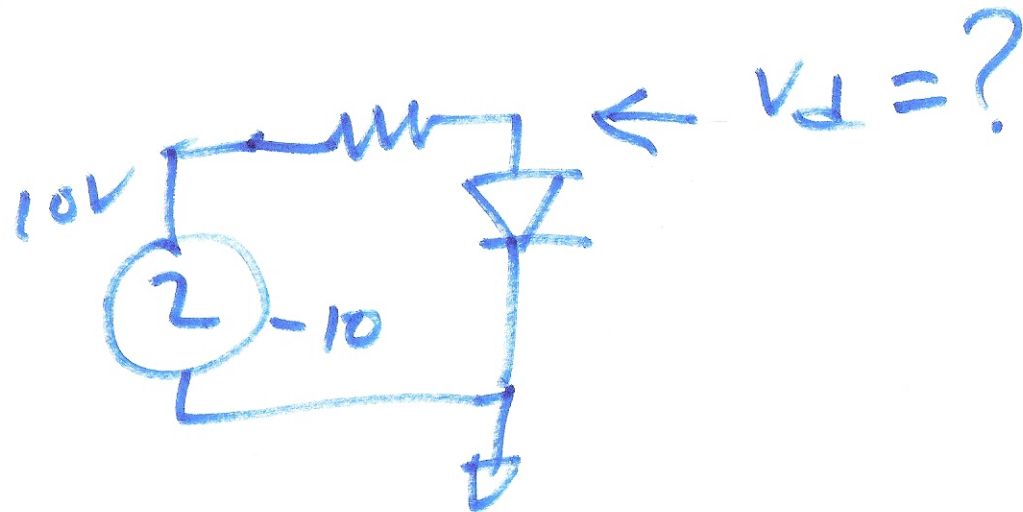- 1) Know H.W. problems
- 2) Basic devices



MOSFETS  
Diodes

LTspice questions

3) instantaneous power  $p(t) = i(t) \cdot v(t)$   
Average power  $P = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) \cdot dt$

3)




# ELI the ICE man

Ex. Show average power diss. by an inductor is zero. Show instantaneous power delivered to inductor is NOT zero.

USE SINWAVE

(study squarewave)

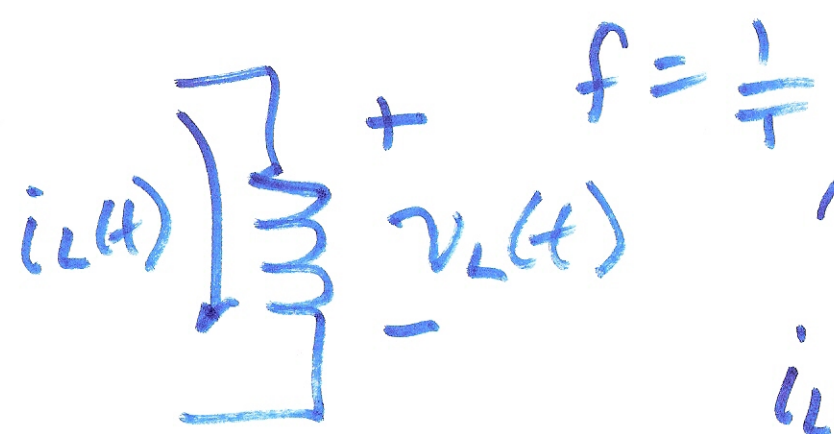


$$v_L(t) = V_p \sin 2\pi f \cdot t$$

$$i_L(t) = \frac{1}{L} \int_0^t V_p \sin 2\pi f t \, dt$$

$$\int \sin x \cdot dx = -\cos x$$

$t=0, x=0$      let  $x = 2\pi f t$   
 $t=t, x=2\pi f t$       $\frac{dx}{dt} = 2\pi f$

$$dt = \frac{dx}{2\pi f}$$

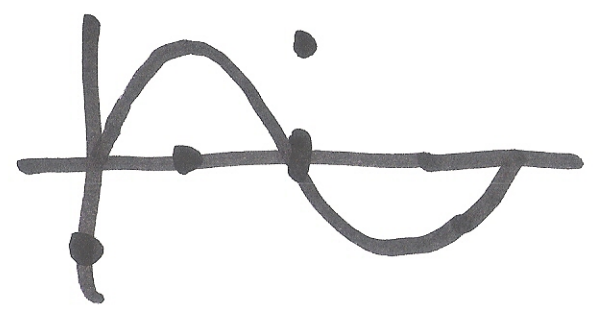

4)

$$i_L(t) = \frac{V_P}{L} \int_0^{2\pi f t} \sin x \cdot \frac{dx}{2\pi f}$$
$$= \frac{V_P}{L \cdot 2\pi f} \cdot \left( -\cos x \right) \Big|_0^{2\pi f t}$$

$$i_L(t) = \frac{V_P}{L \cdot 2\pi f} \left( -\cos 2\pi f t + 1 \right)$$

$$P(t) = v_L(t) i_L(t) = V_P \sin 2\pi f t \cdot$$

$$\frac{V_P}{L \cdot 2\pi f} (1 - \cos 2\pi f t)$$

s)



$$P = \frac{1}{T} \int_0^T \frac{V_p^2}{L \cdot 2\pi f} (\sin 2\pi f t - \cos 2\pi f t) dt$$

$$P = \frac{V_p^2}{L \cdot 2\pi} \left[ \int_0^T \sin 2\pi f t dt - \int_0^T \sin 2\pi f t \cos 2\pi f t dt \right]$$

$\frac{1}{2\pi f} (-\cos x) \Big|_0^{2\pi}$

$\frac{1}{2 \cdot 4\pi f} (-\cos x) \Big|_0^{4\pi}$

$\frac{1}{2} \int_0^{2\pi} \sin(4\pi f t) dt$

$\frac{1}{4\pi f} (-\cos x) \Big|_0^{4\pi}$

b)


Energy stored

Study!!

$$W = \int_0^{T/2} p(t) \cdot dt \quad 2.2$$

Study → Ex. 2-5

Effective rms

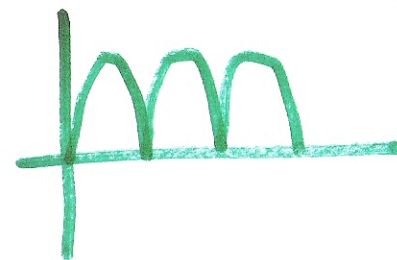

Energy Recovery.

1)

# Buck & Boost

topologies and operation

det.


$\Delta i_L$  open

$\Delta i_L$  closed

Show how

$$V_s \cdot D = V_o$$

Show.

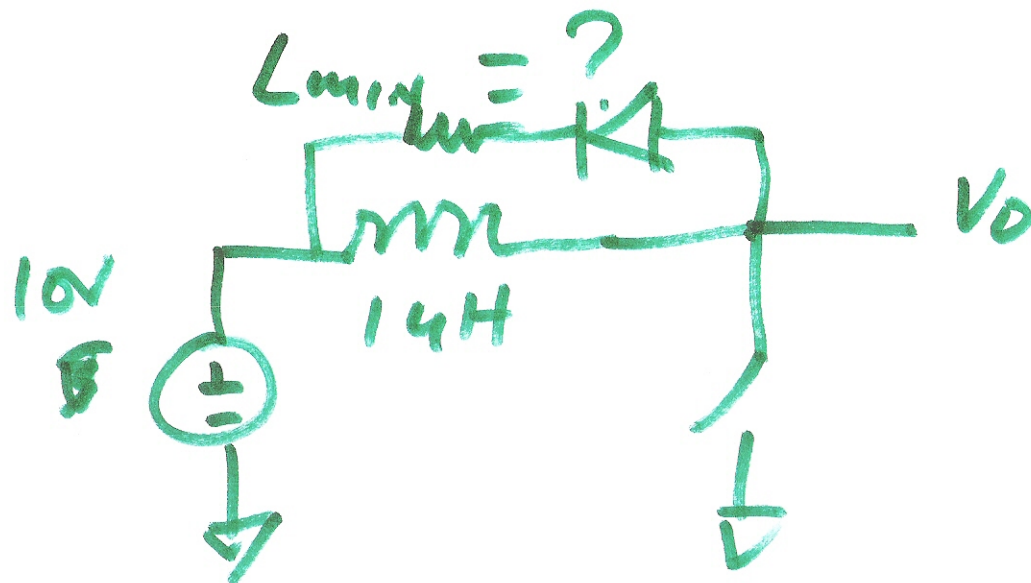

Sketch  $i_L$

Know

8)