
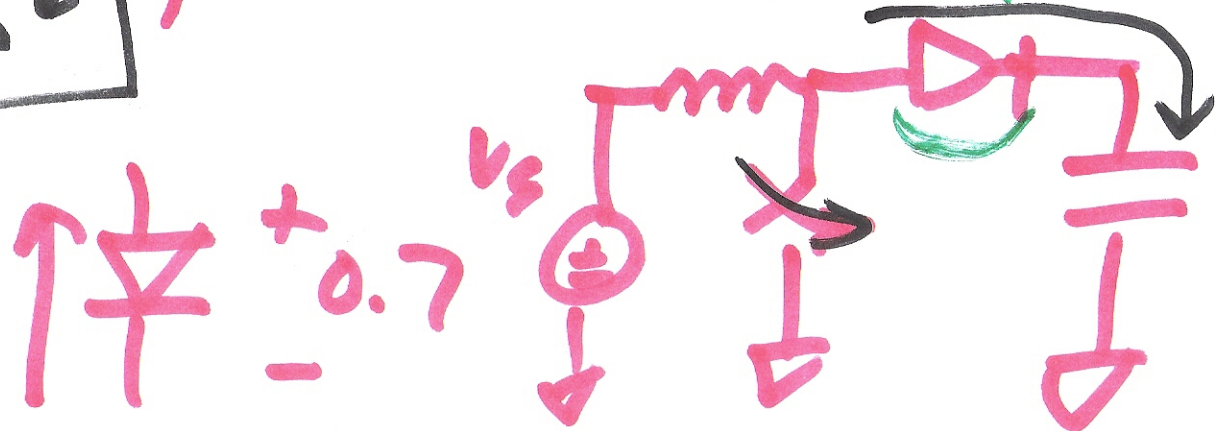
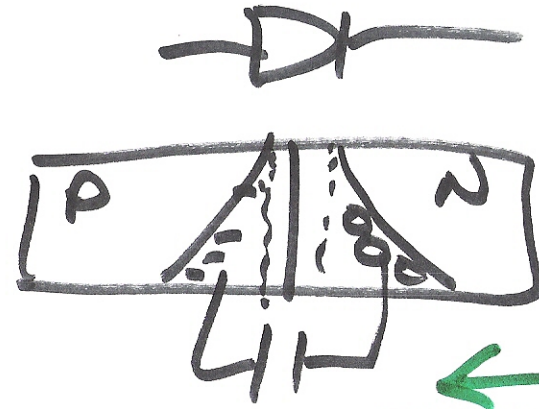


## Lecture 14 (study/review)

15 JA

Sept. 26, 2010

### Reverse Recovery

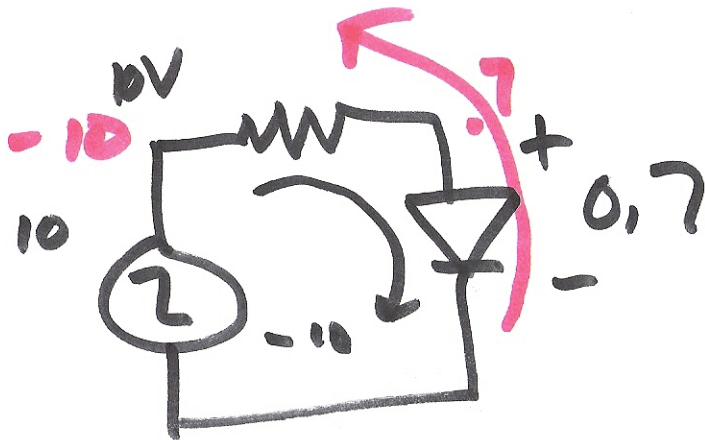


1)

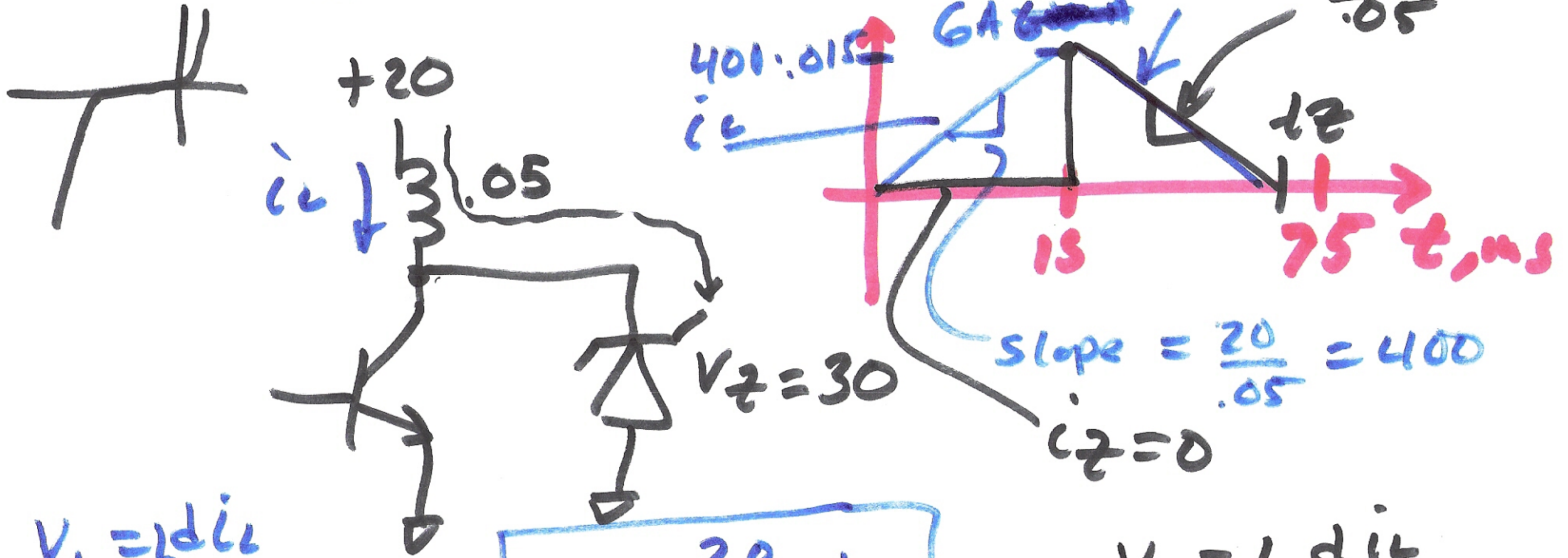2-14)

$V_{CC} = +20V$      $L = 50mH$      $V_Z = 30V$

$t_{ON} = 15ms$      $t_{OFF} = 60ms$      $i_Z = i_L - \frac{10}{.05}$



$V_L = L \frac{di_L}{dt}$

$20 = .05 \cdot \frac{di_L}{dt}$

$i_L = \frac{20}{L} \cdot t$



$V_L = L \frac{di_L}{dt}$

$20 - 30 = L \cdot \frac{di_L}{dt}$



$6 = \frac{10}{L} (t_2 - .015)$

$i_L = \frac{6 - 10}{L} (t - 15ms)$

2)

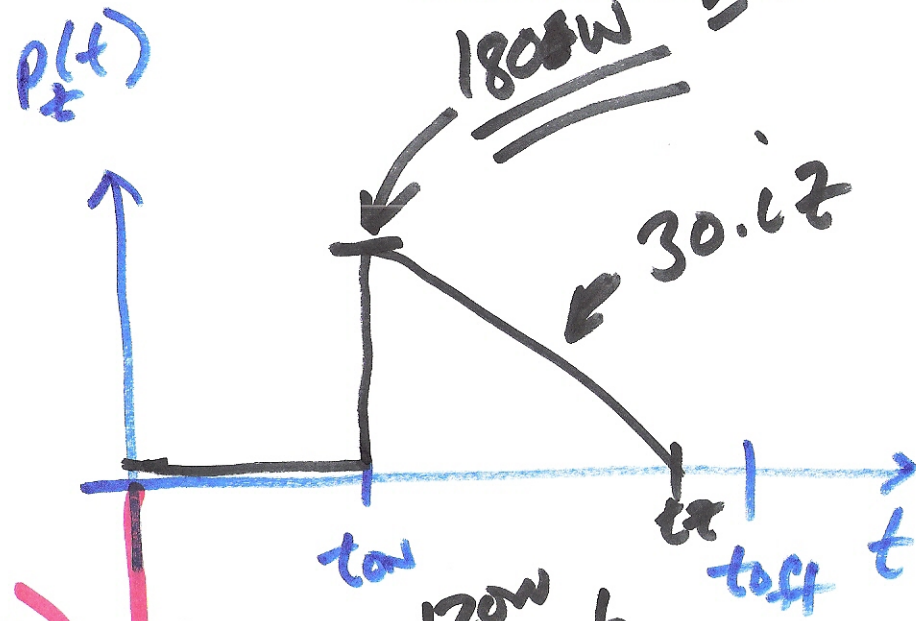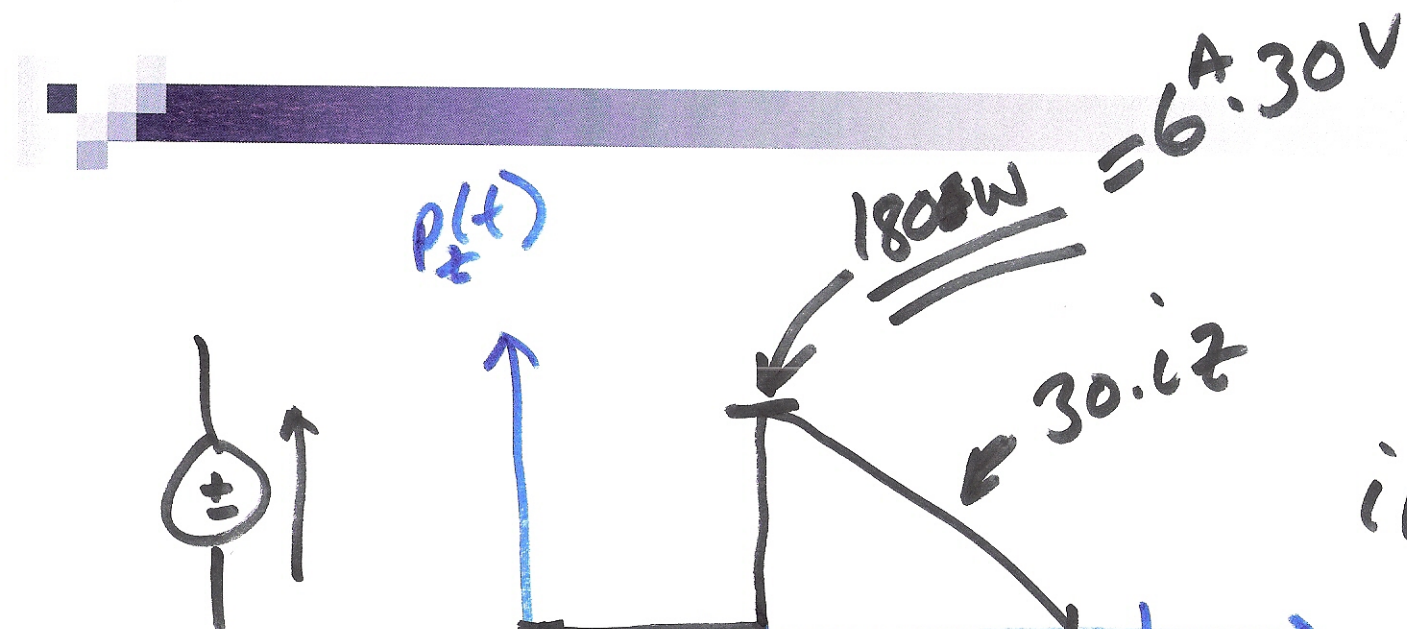


$P_L(t)$

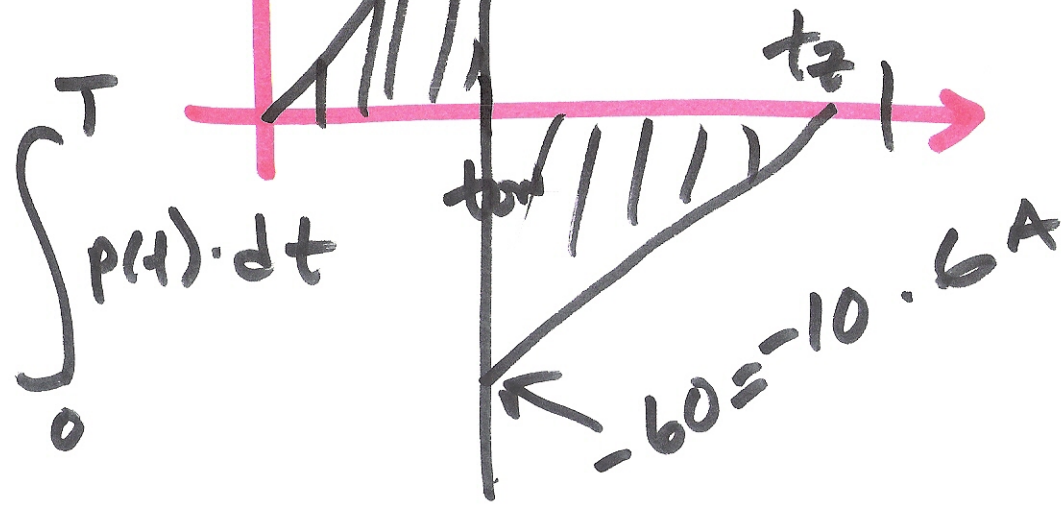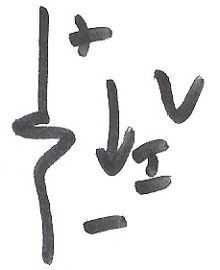

$$P = \frac{1}{T} \int_0^T P(t) \cdot dt$$

$i_L \downarrow \begin{matrix} + \\ 3 \\ - \end{matrix} \begin{matrix} + \\ 2V \\ - \end{matrix}$   
 $\leftarrow +20$   
 $i_L \downarrow \begin{matrix} + \\ 3 \\ - \end{matrix} \begin{matrix} + \\ v_L \\ - \end{matrix}$   
 $\leftarrow 30V$   
 $P_L(t) = v_L \cdot i_L$   
 $v_L = -10$

3)

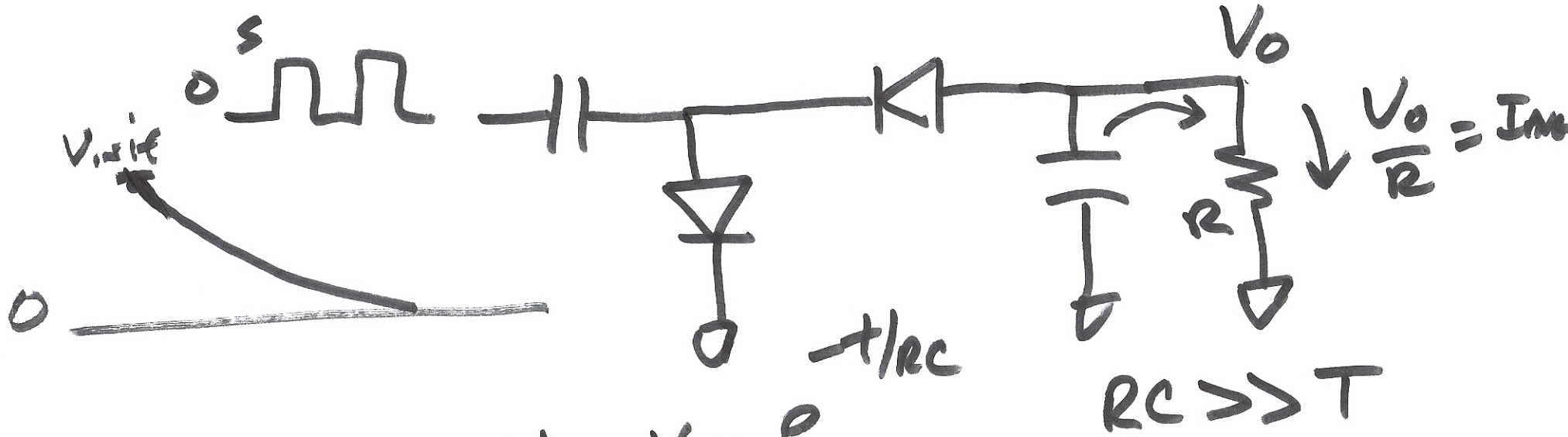

$$V_o(t) = V_{init} e^{-t/RC}$$


$$= V_{init} \left( 1 + \left( -\frac{t}{RC} \right) + \frac{\left( -\frac{t}{RC} \right)^2}{2!} + \dots \right)$$

$$\approx V_{init} \left( 1 + -\frac{t}{RC} \right)$$



4)

$$C V = Q$$

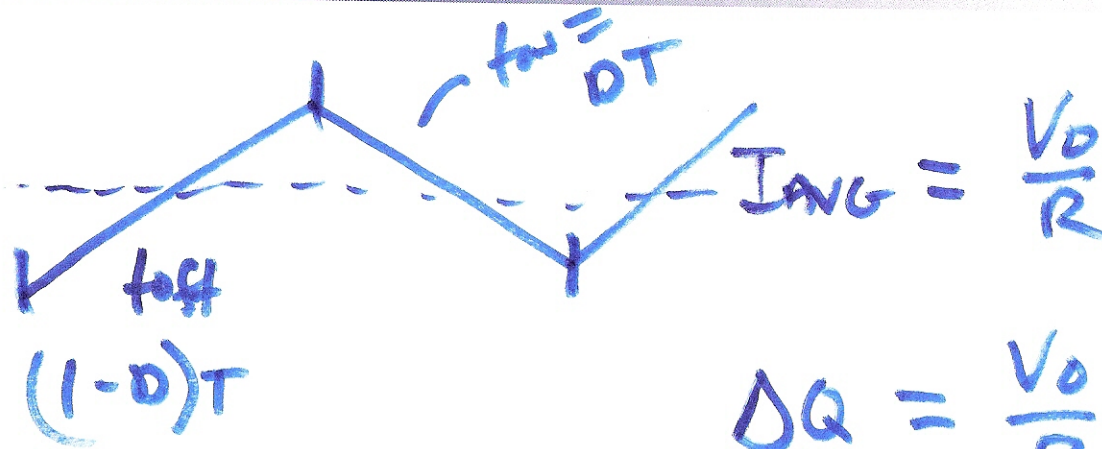


$$\Delta Q = \frac{V_0}{R} \cdot DT = C \cdot \Delta V_0$$

$$V_0 \gg \Delta V_0$$


$$\frac{\Delta V_0}{V_0} = \frac{DT}{RC} = \frac{D}{RC \cdot f}$$
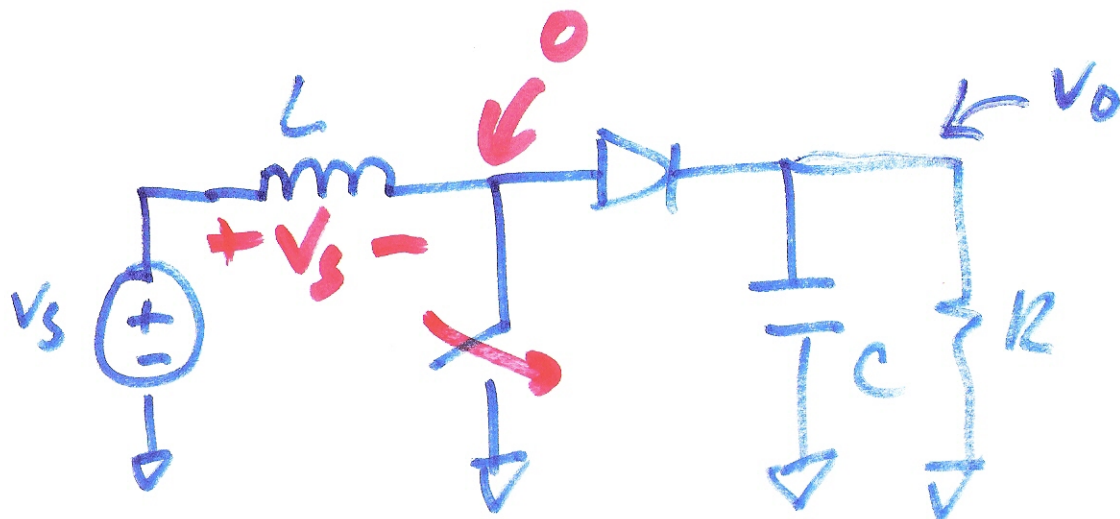
$$\Delta V_0 = I_{avg} \cdot \frac{D}{f \cdot C}$$



5)

# Buck

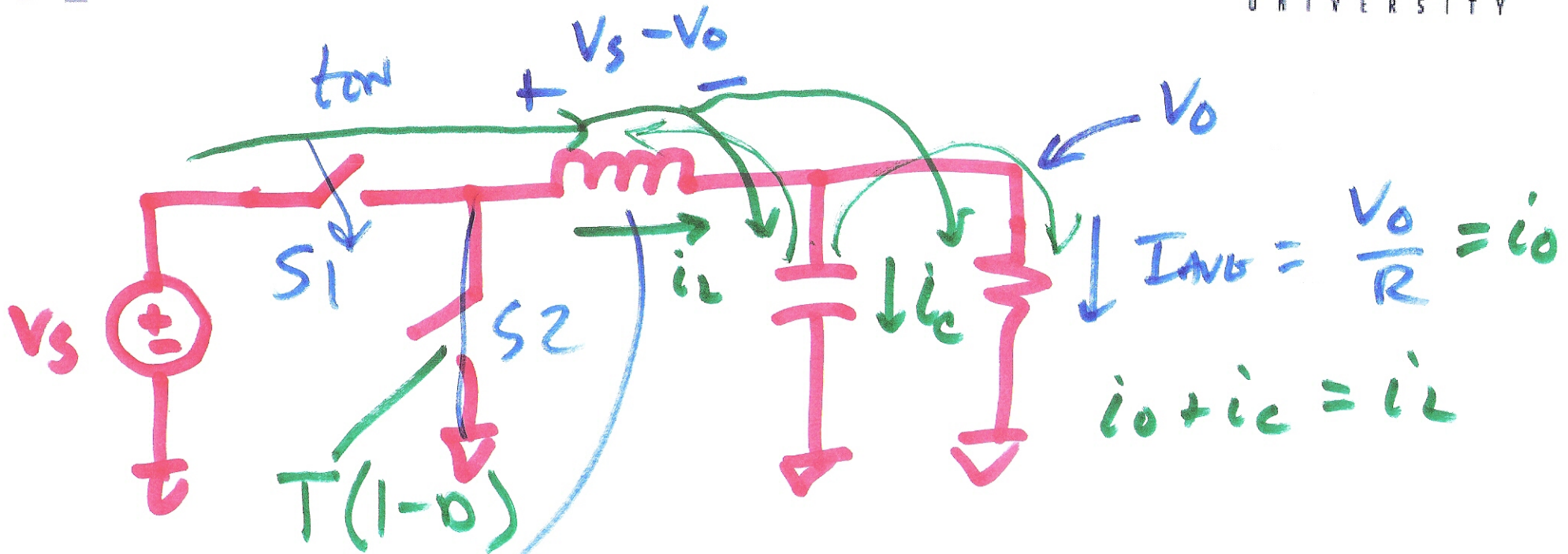


$$i_L(t) = \frac{V_s - V_o}{L} \cdot t$$

$$i_L(t) = -\frac{V_o}{L} \cdot t$$

~~ON~~ S1 is on


S2 is on

6)

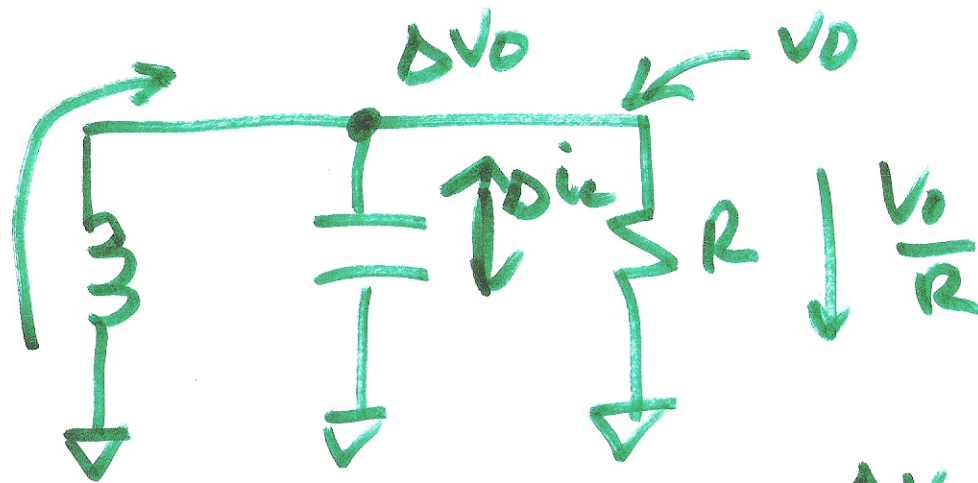

$$\Delta i_c = C \cdot \frac{\Delta V_o}{(1-D)T}$$
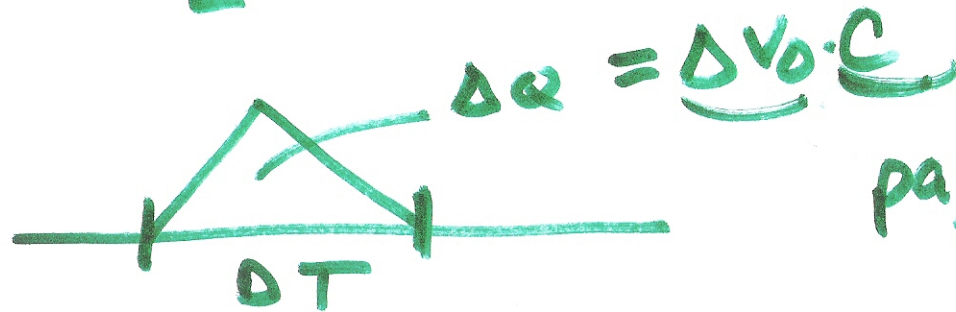
$$I_{L,init} - \frac{V_o}{L} \cdot (1-D)T = i_L$$




7)

$$V_s \cdot I_s = V_o \cdot I_o$$

ASSUMES

100% efficiency.

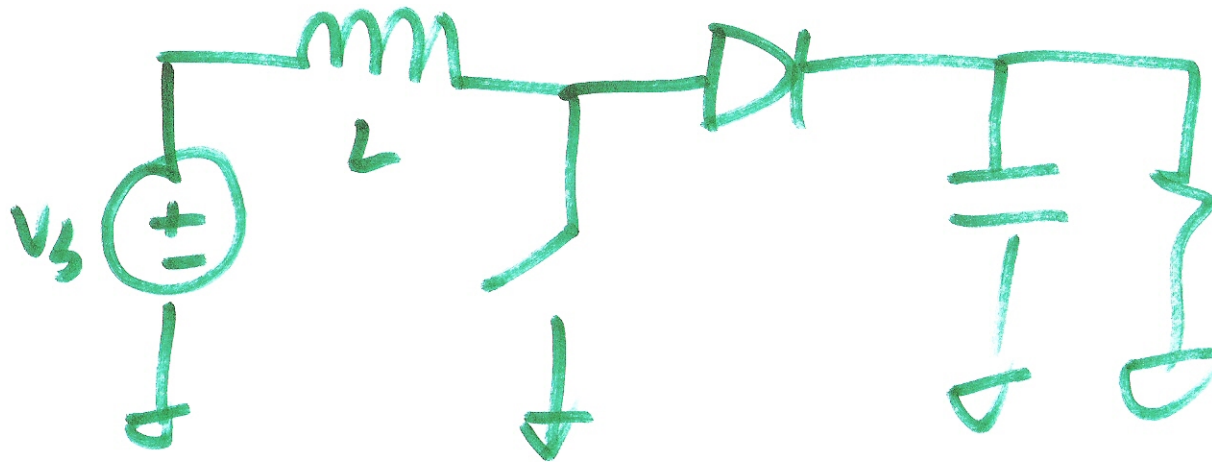

8)