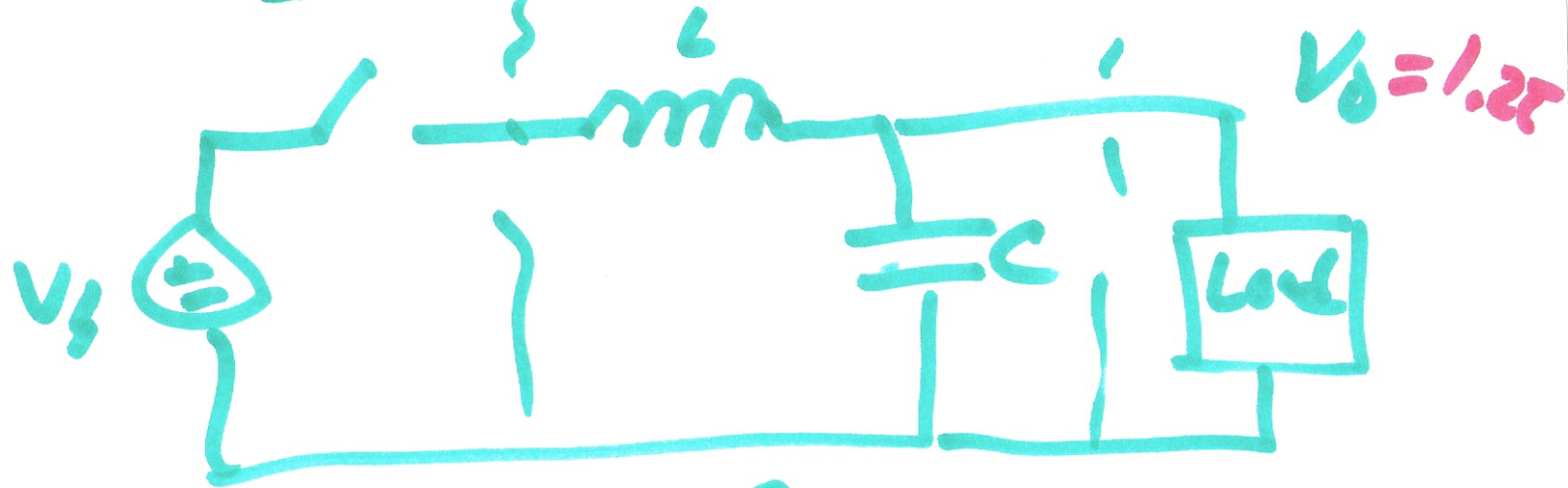



## Lecture 19


 $\omega_1 = 0.7$   

Oct. 8, 2010




filter

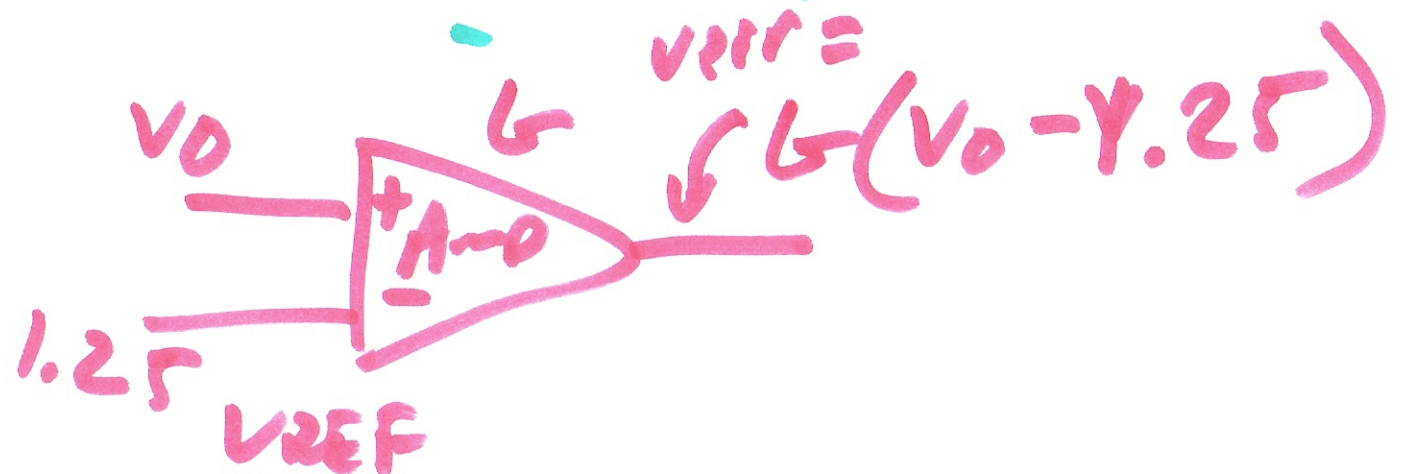

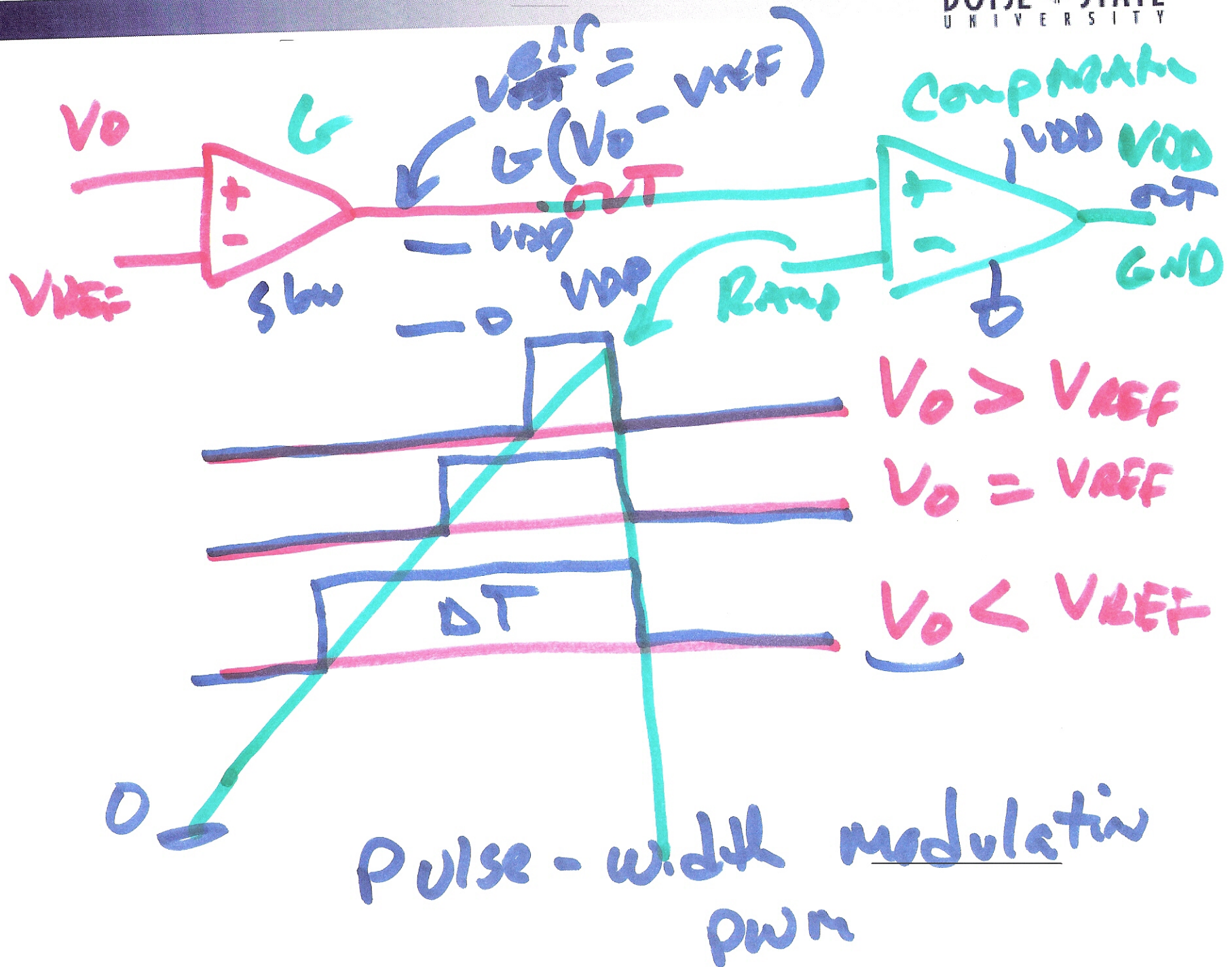


# pwm control

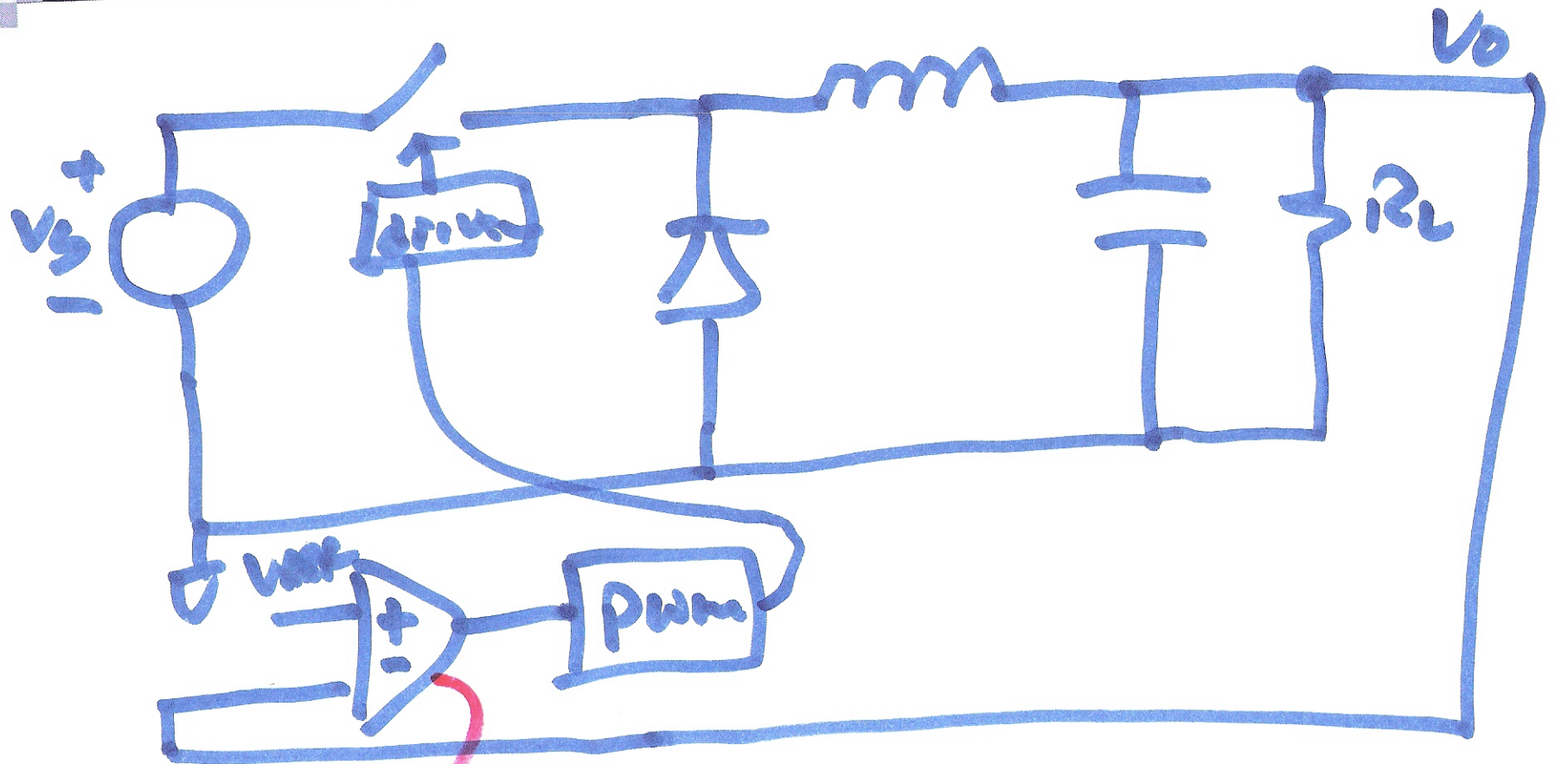

Compensated Error Amplifier



# Basic f.b.

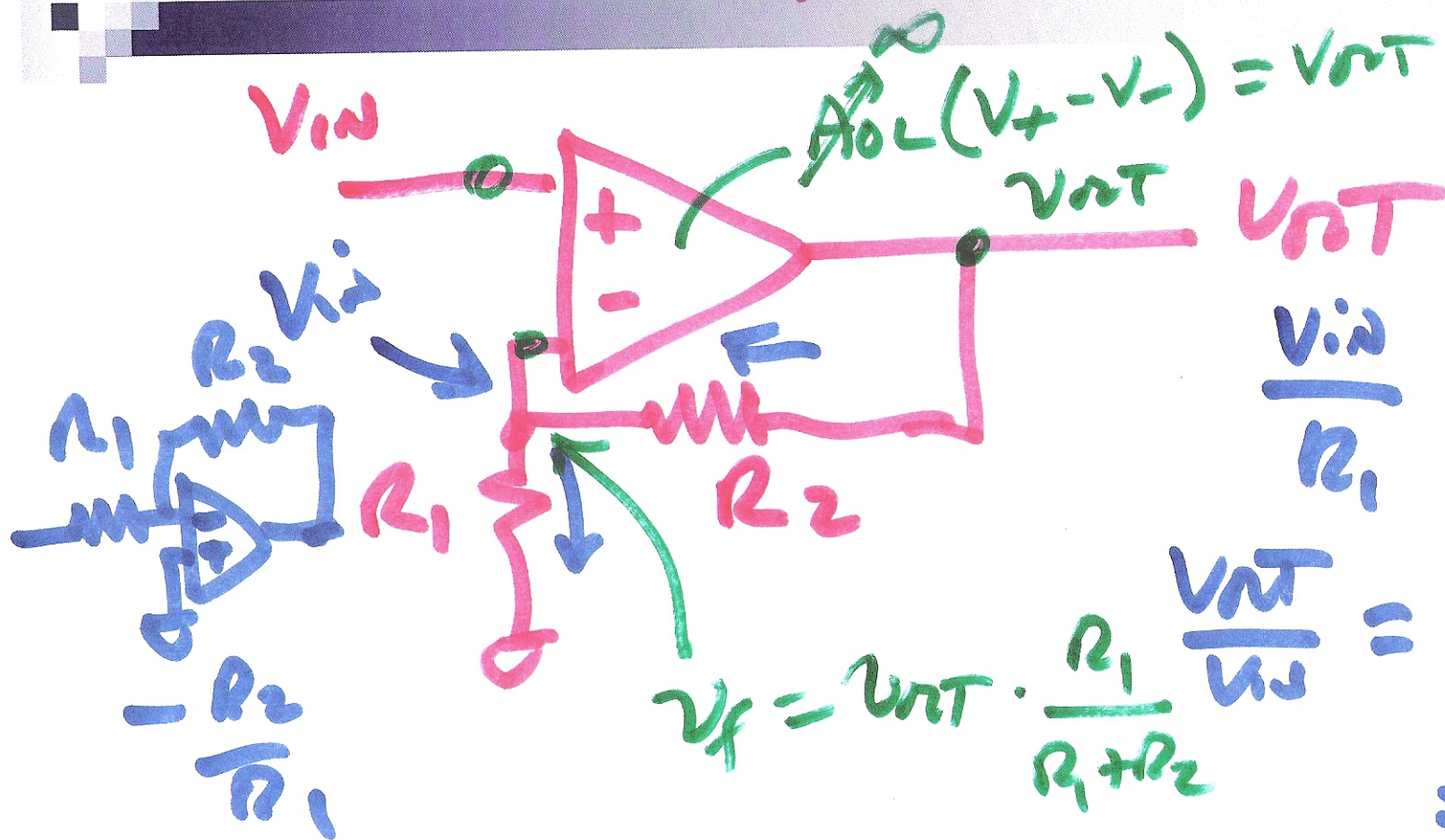


$$A_{OL}(V_+ - V_-) = V_{out}$$

$$\frac{V_{in}}{R_1} = \frac{V_{out} - V_{in}}{R_2}$$
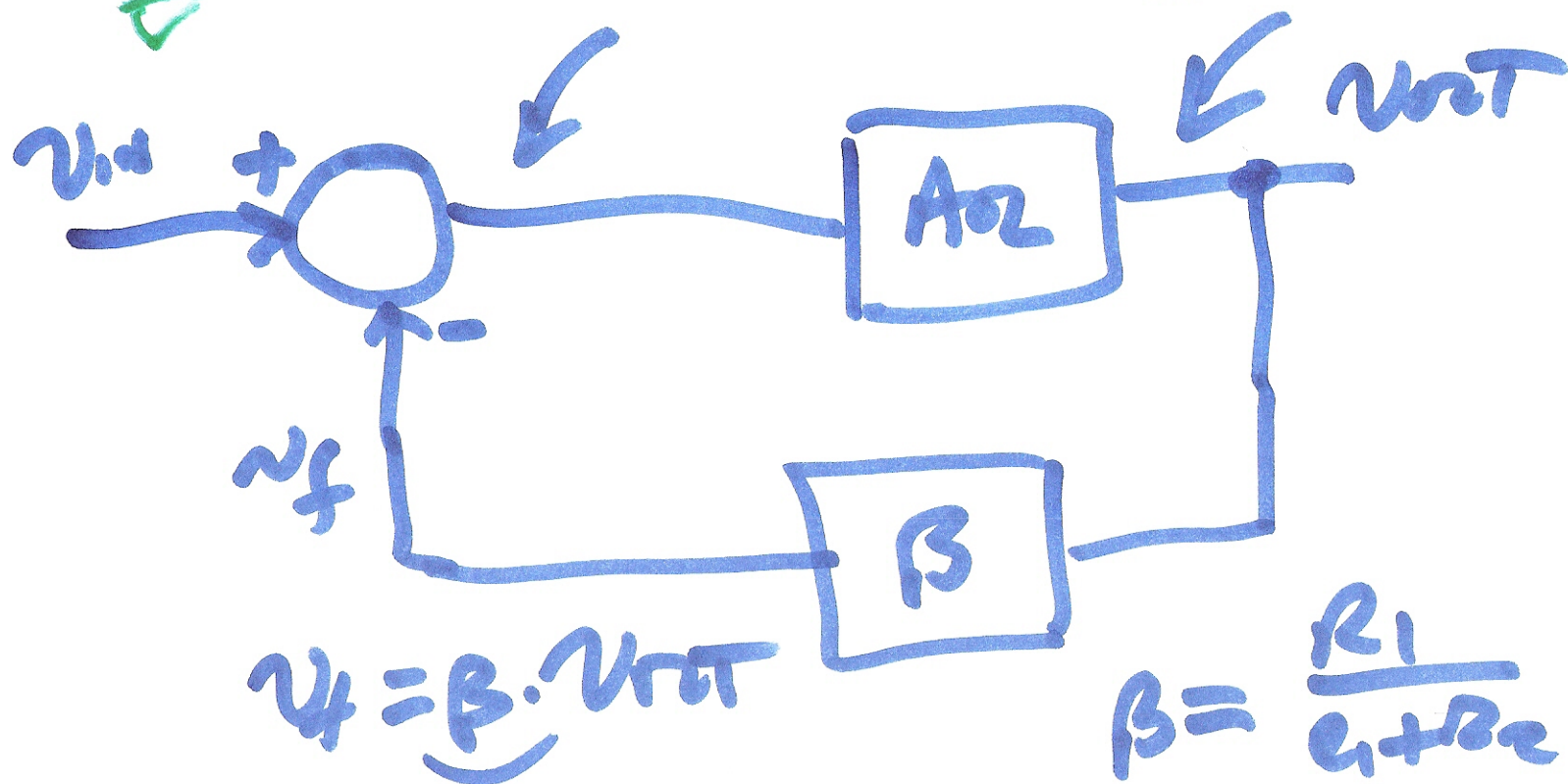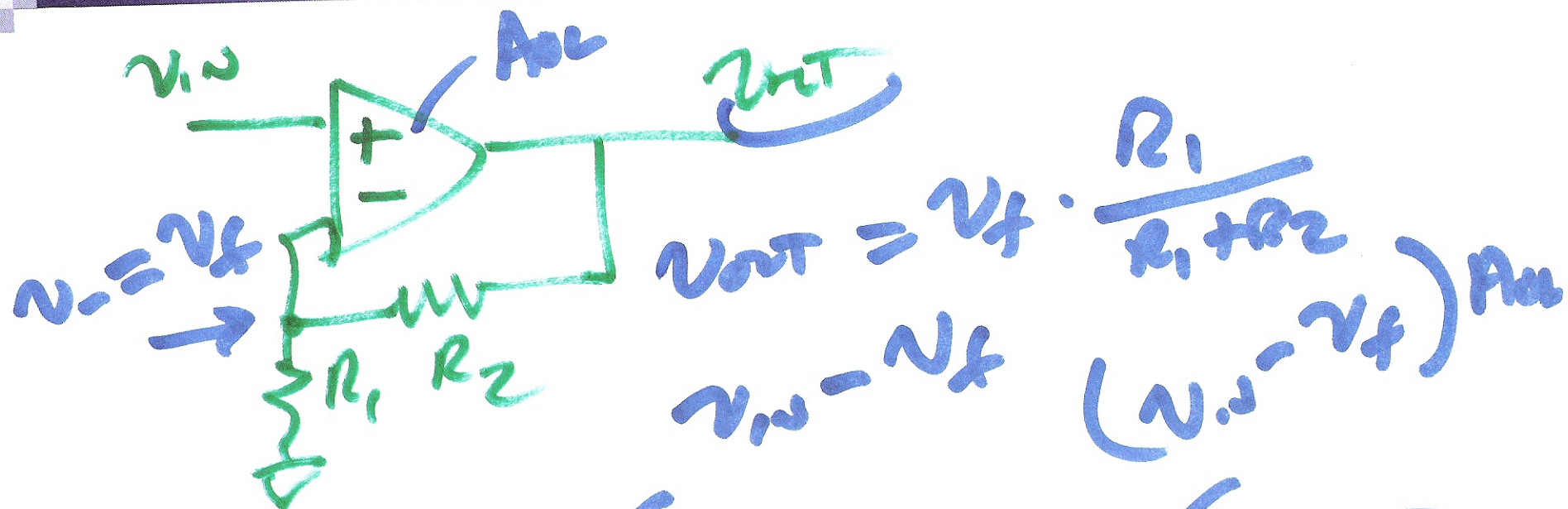
$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1} = \frac{R_2 + R_1}{R_1}$$



5)

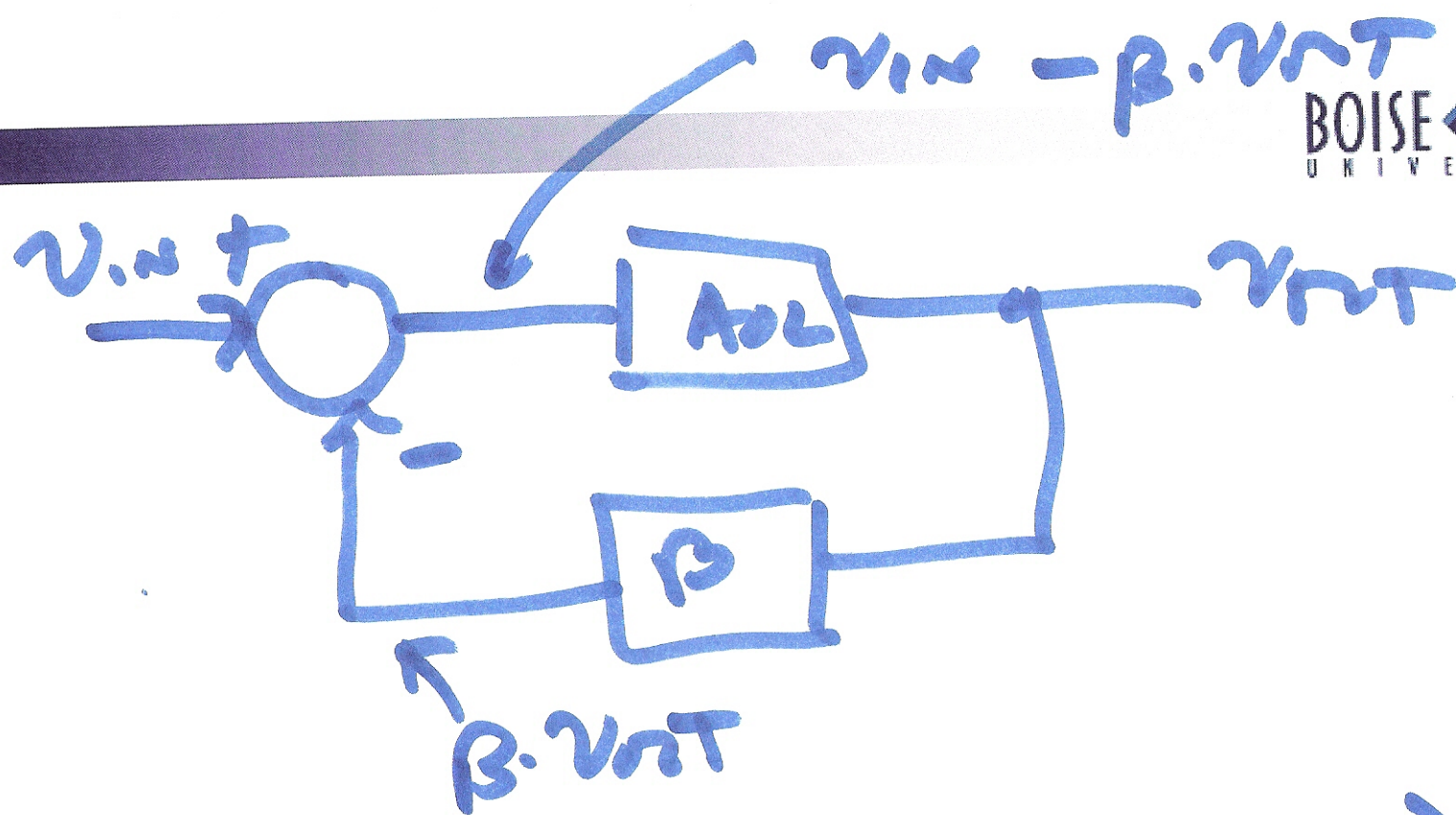

$$v_{out} = A_{OL} (v_{in} - \beta v_{out})$$

$$v_{out} (1 + \beta A_{OL}) = A_{OL} \cdot v_{in}$$

$$A_{CL} = \frac{v_{out}}{v_{in}} = \frac{A_{OL}}{1 + \beta \cdot A_{OL}}$$

b)


$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}}$$

$$= \frac{1}{\frac{1}{A_{OL}} + \beta}$$


$A_{OL} \rightarrow \infty$

$$A_{CL} = \frac{1}{\beta}$$

$v_{in}$

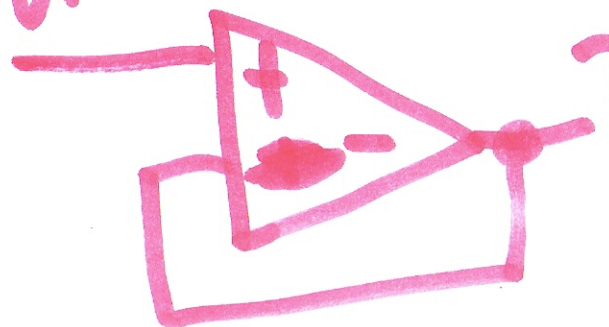


$$v_{out} = 1 + \frac{R_2}{R_1}$$

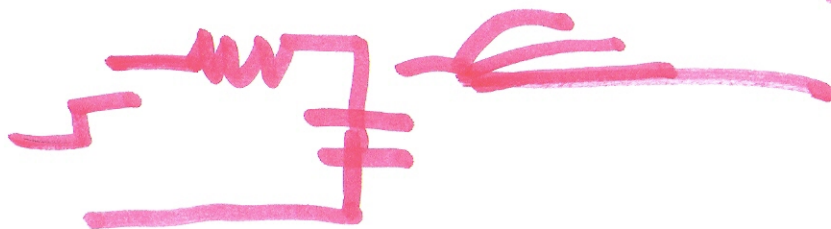

77

$A_{OL}$

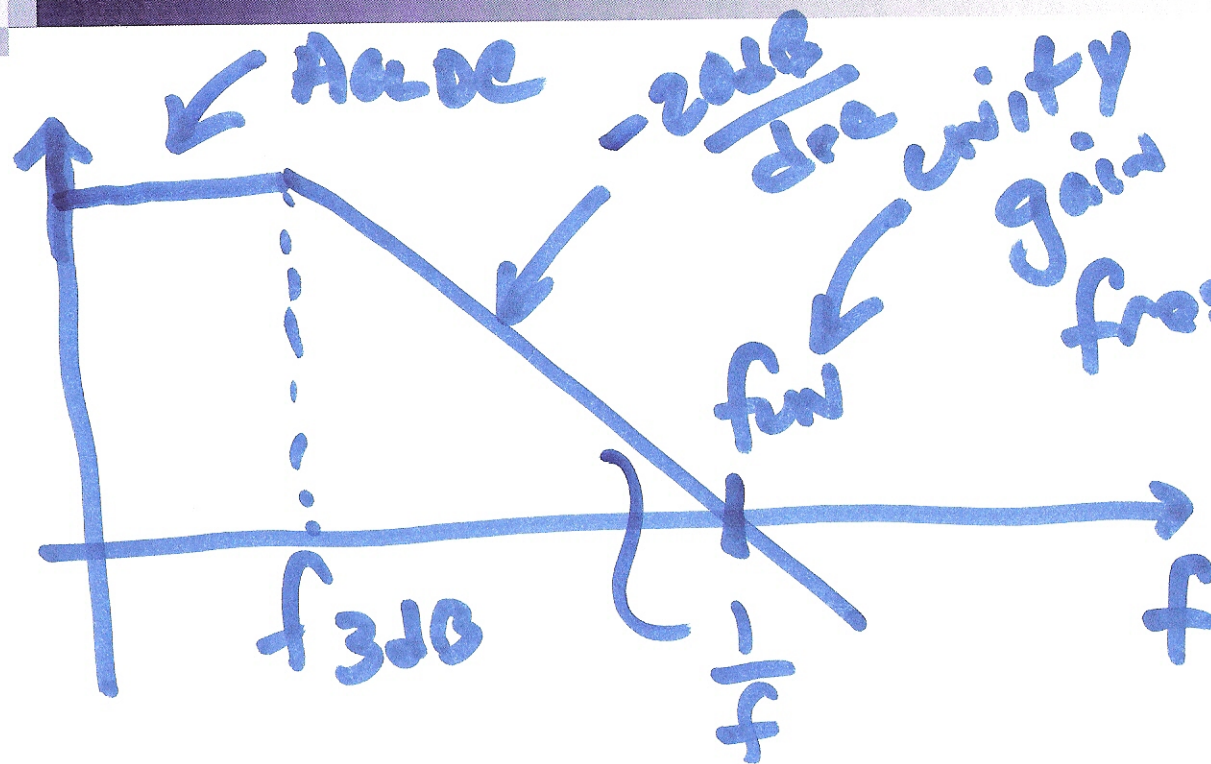

$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}}$$

$$|\beta A_{OL}| = 1$$

$$\angle \beta A_{OL} = 180^\circ$$

$$1.2 \text{ kHz} \Rightarrow 12 \text{ K}$$

$$12 \text{ dB} \times 4 \quad \beta = 1$$




$$\begin{array}{l} 1.2 \text{ kHz} \xrightarrow{1 \text{ dec}} 2.4 \text{ K} \\ 6 \text{ dB} \xrightarrow{10 \text{ CT}} \times 2 \\ \qquad \qquad \div 2 \end{array}$$

$$32 \text{ dB} \times 40 \quad |A_{OL}| = 1$$

$$\times 10 \times 2 \times 2 \quad \angle A_{OL} = 180^\circ$$


$$8) \quad 6 \text{ dB} \rightarrow \times 2 \\ -6 \text{ dB} \div 2$$

# phase marg.

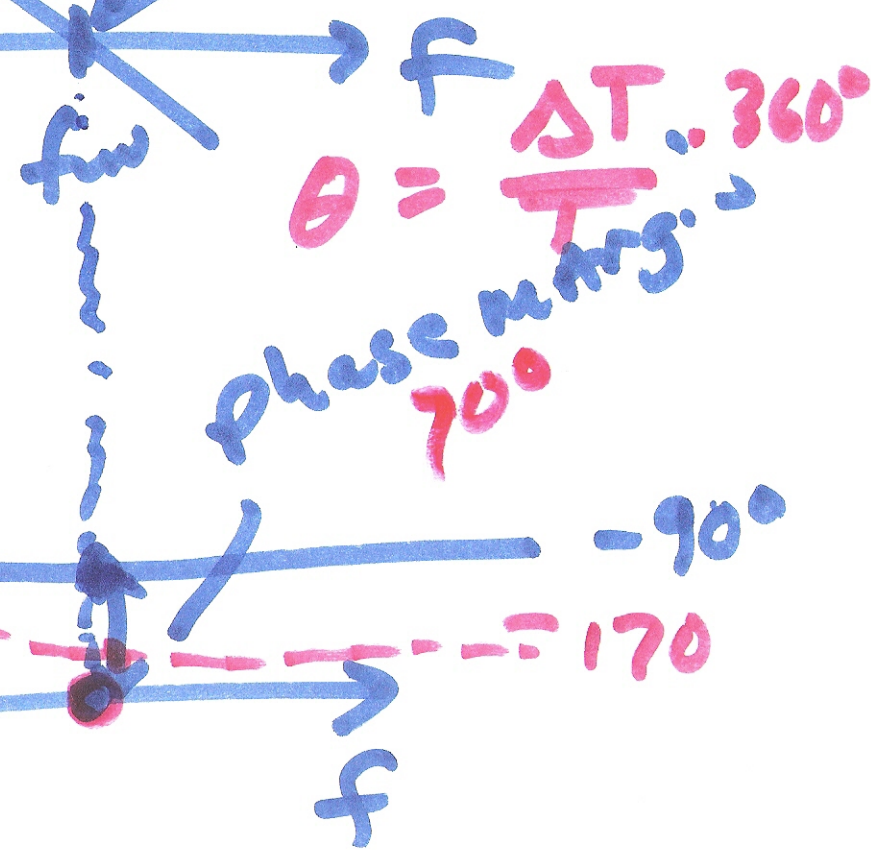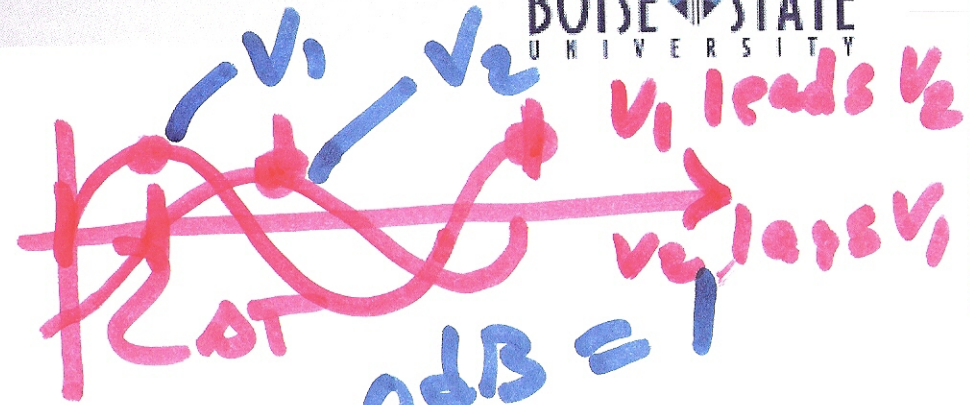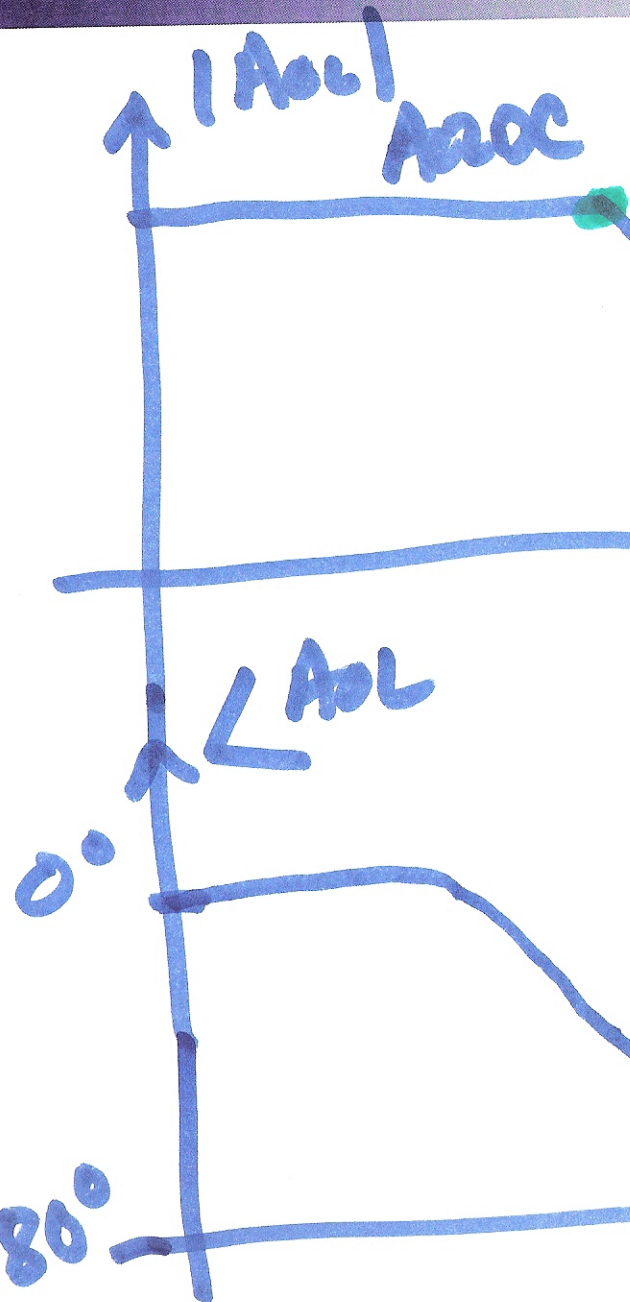


9)

# GAIN MARG:-

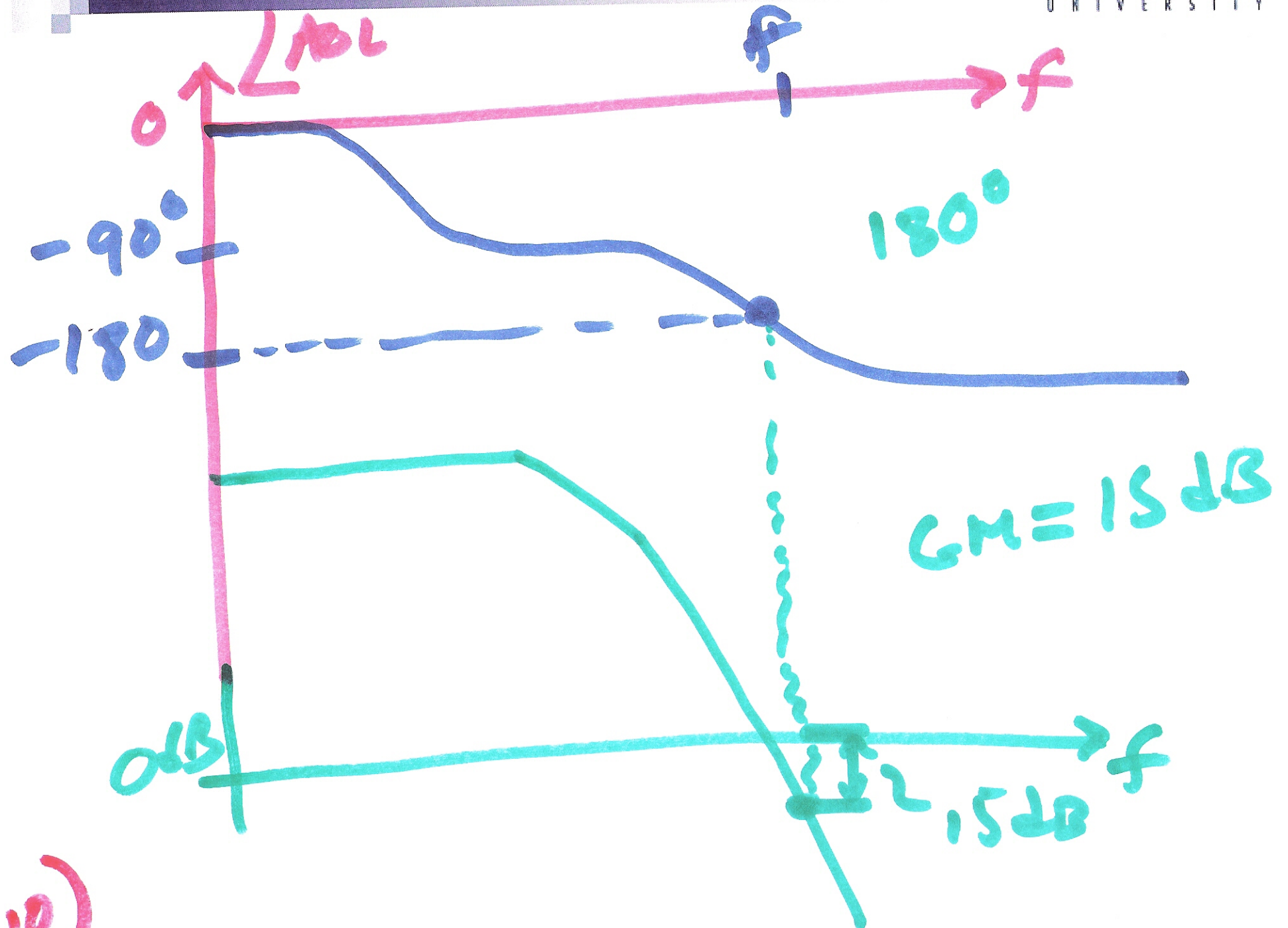

10)


# pwm Block diagram

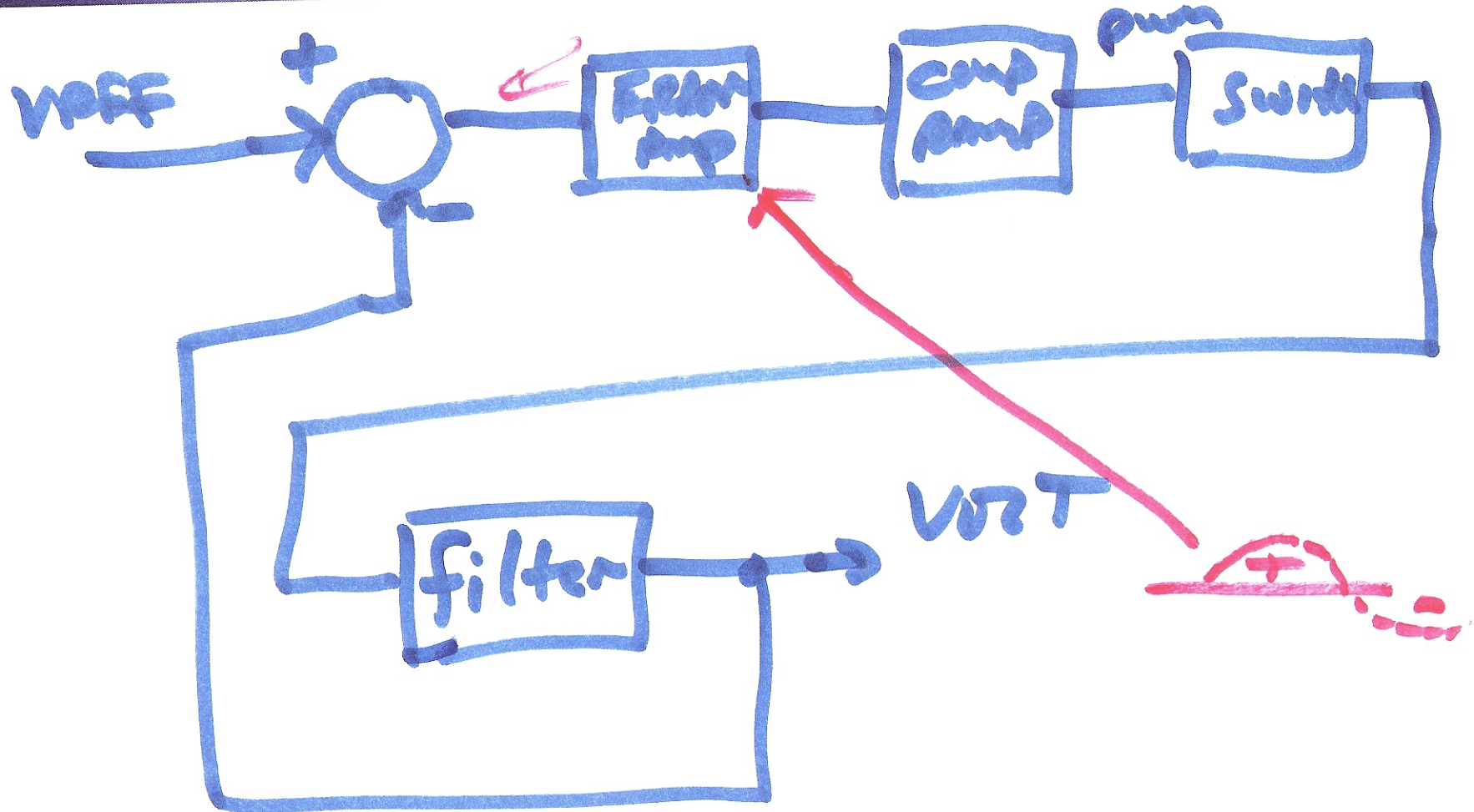

11)

# Simple error Amp

Integrator

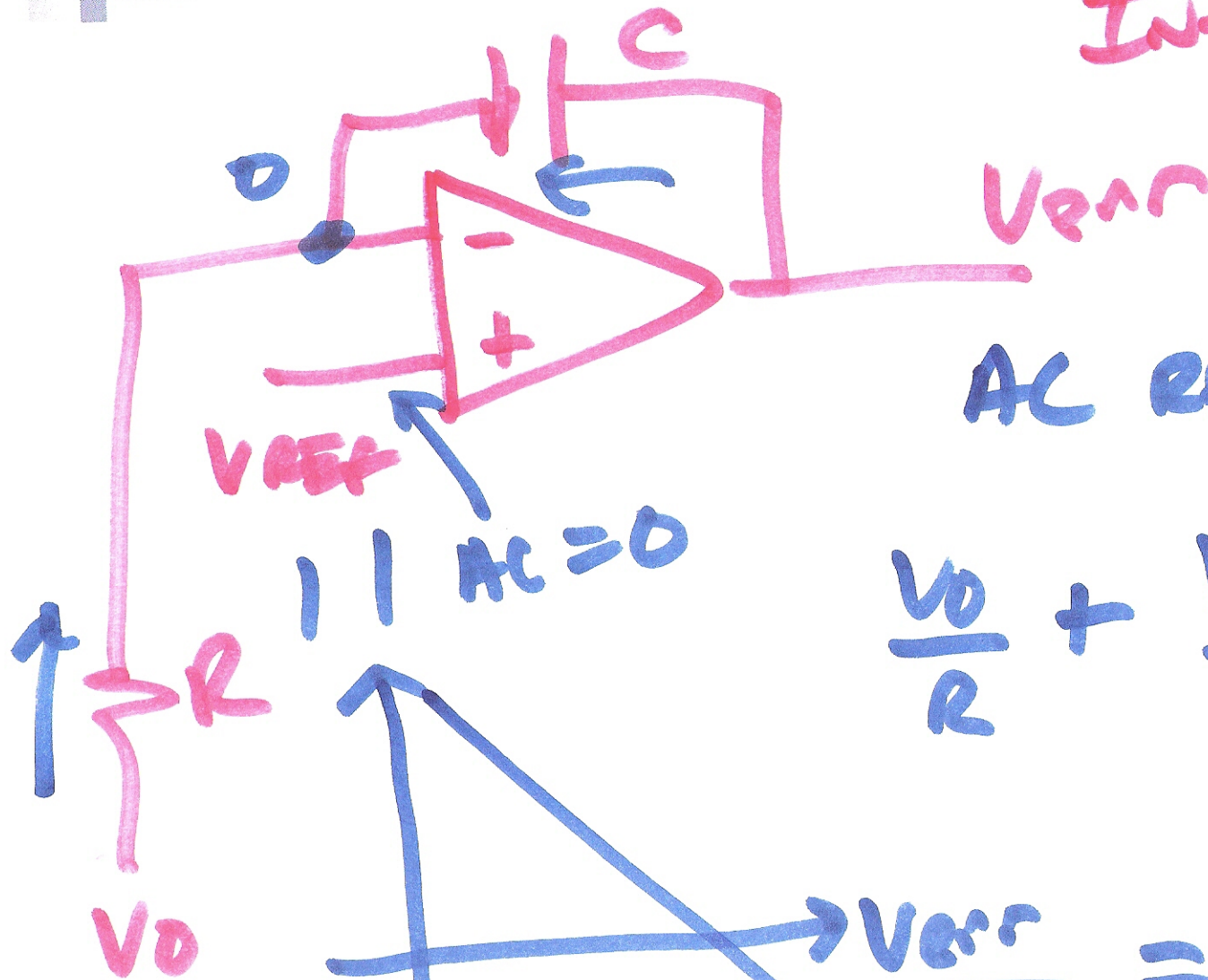

AC RESPONSE

$$\frac{V_0}{R} + \frac{V_{err}}{1/j\omega C} = 0$$

$$\frac{V_{err}}{V_0} = -\frac{1}{j\omega RC} = \frac{j}{\omega RC}$$

(2)