
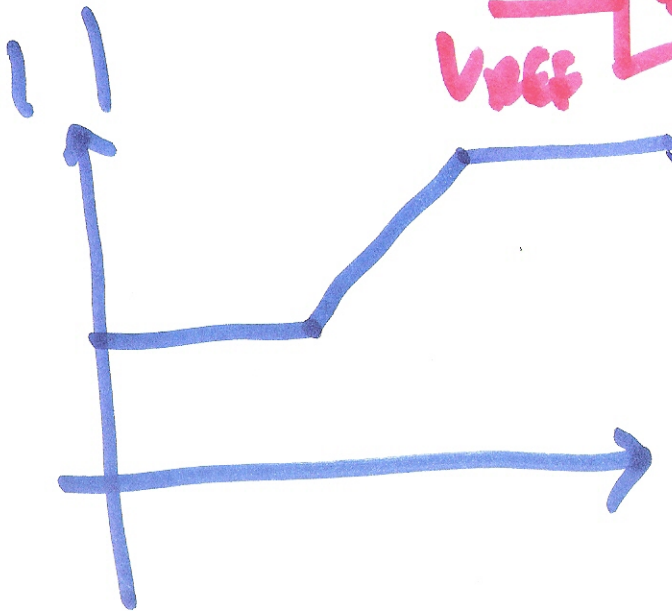


# ECE 51472 Power Electronics

Lecture 22

OCT. 22,



2010

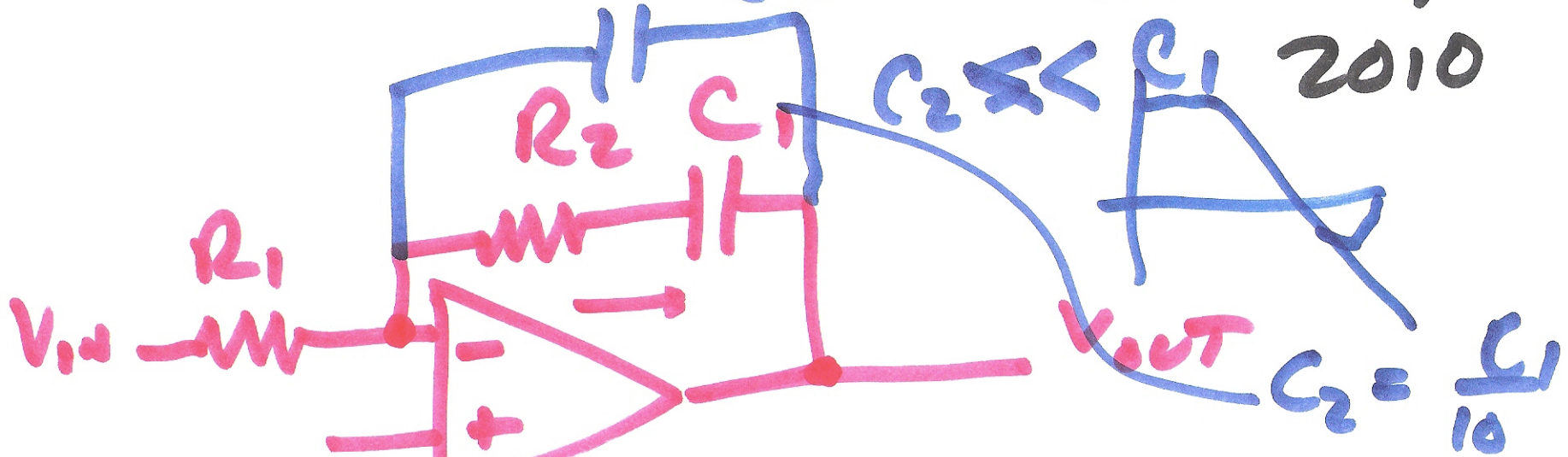


$$\frac{V_{in}}{R_1} = \frac{0 - V_{out}}{R_2 + \frac{1}{j\omega C_1}}$$

$$\frac{V_{out}}{V_{in}} = - \underbrace{\frac{R_2}{R_1}}_{\text{PROP.}} + \underbrace{\frac{1}{j\omega C_1 R_1}}_{\text{INT.}}$$

1)

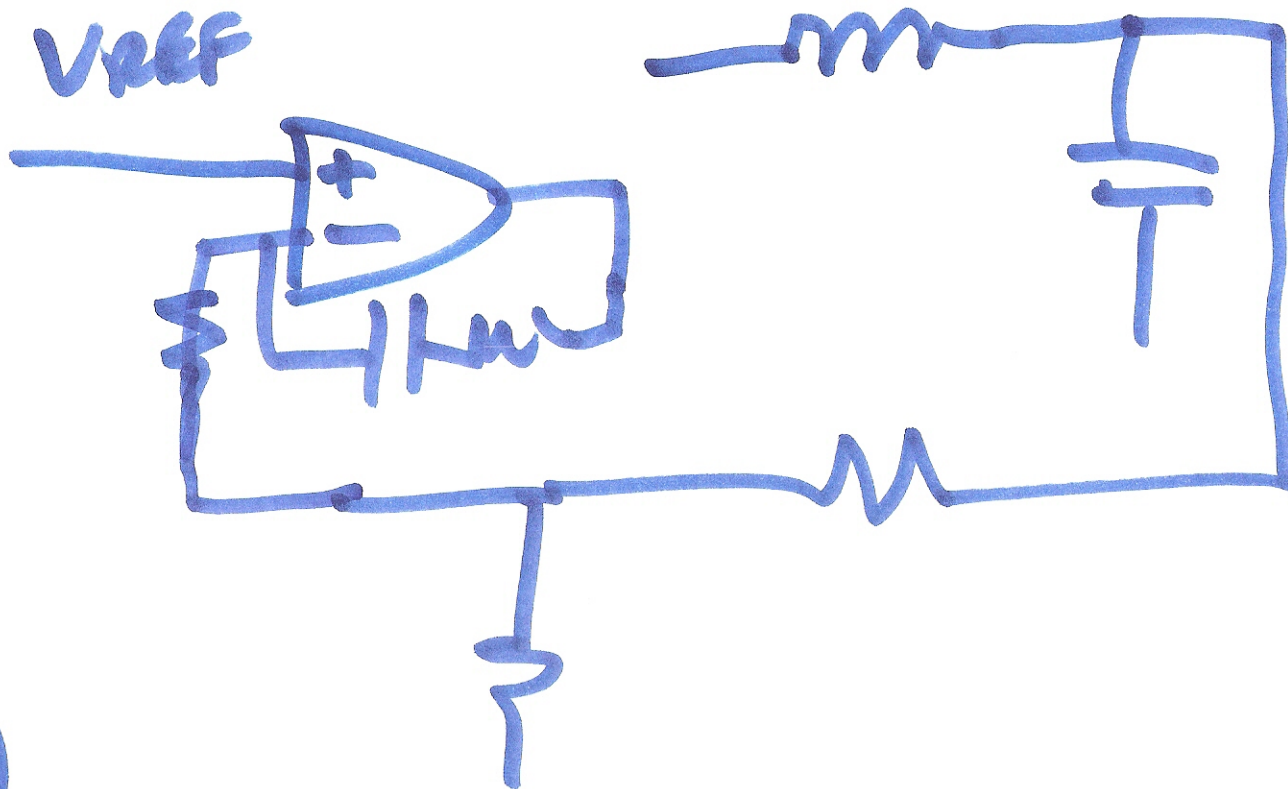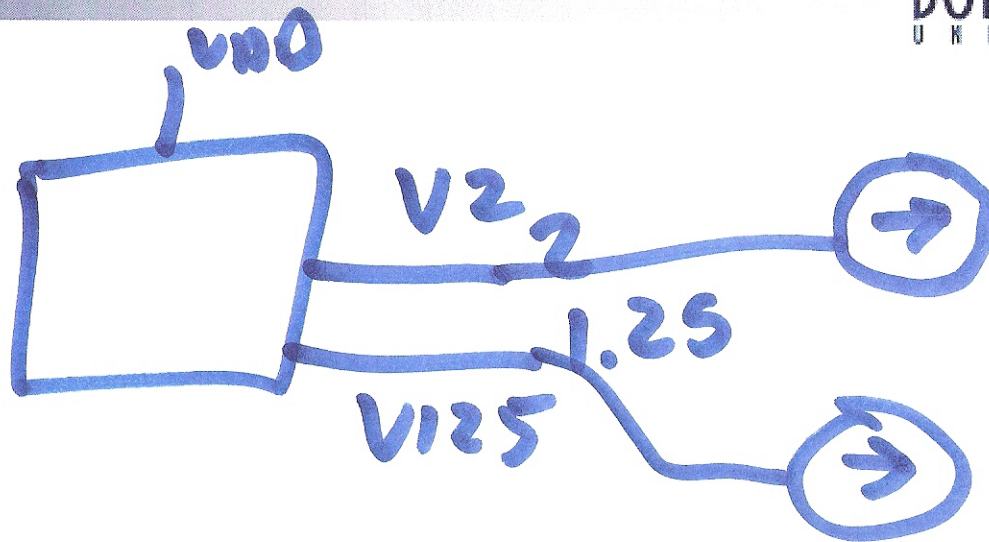


2)

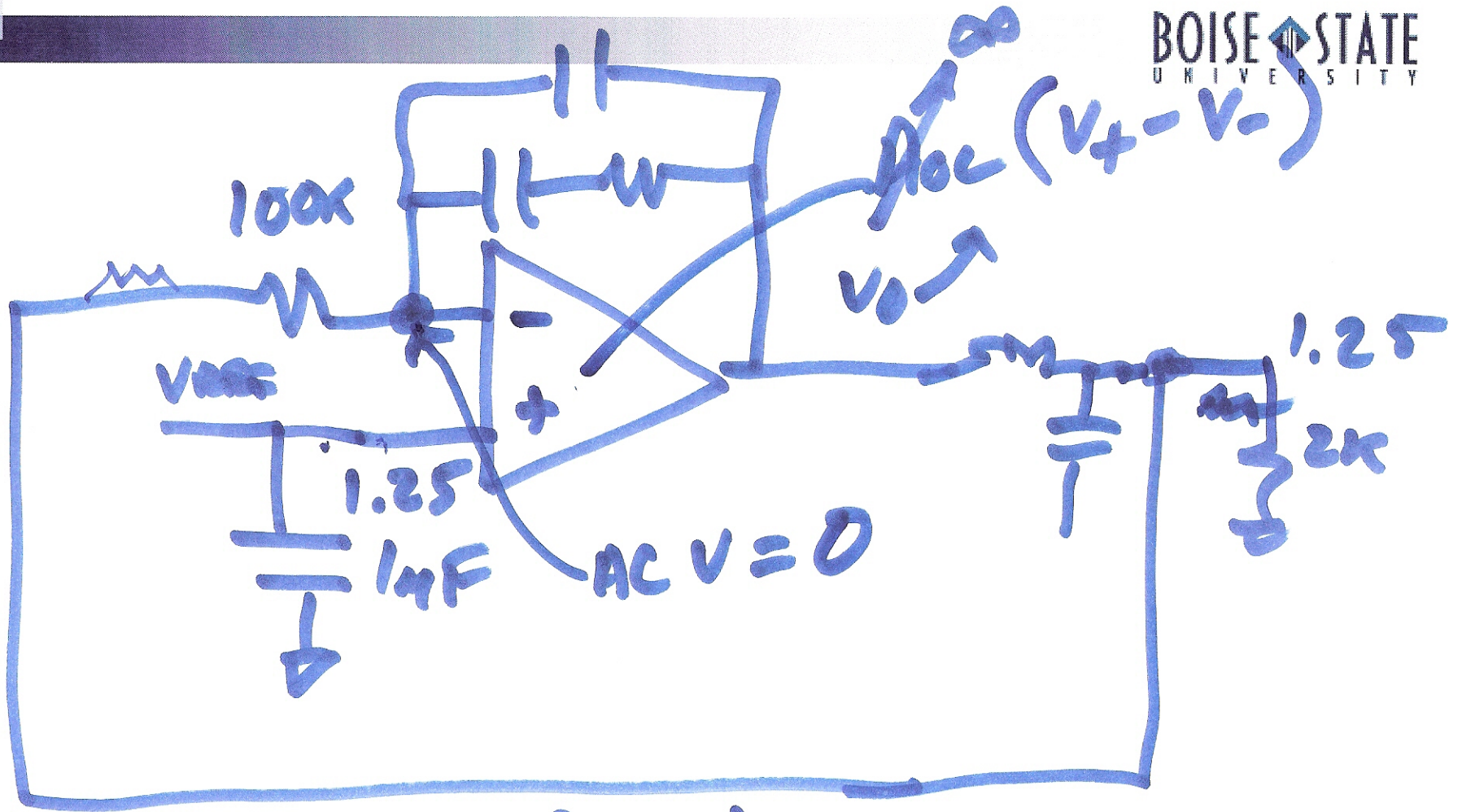

$$B = 1$$

3)


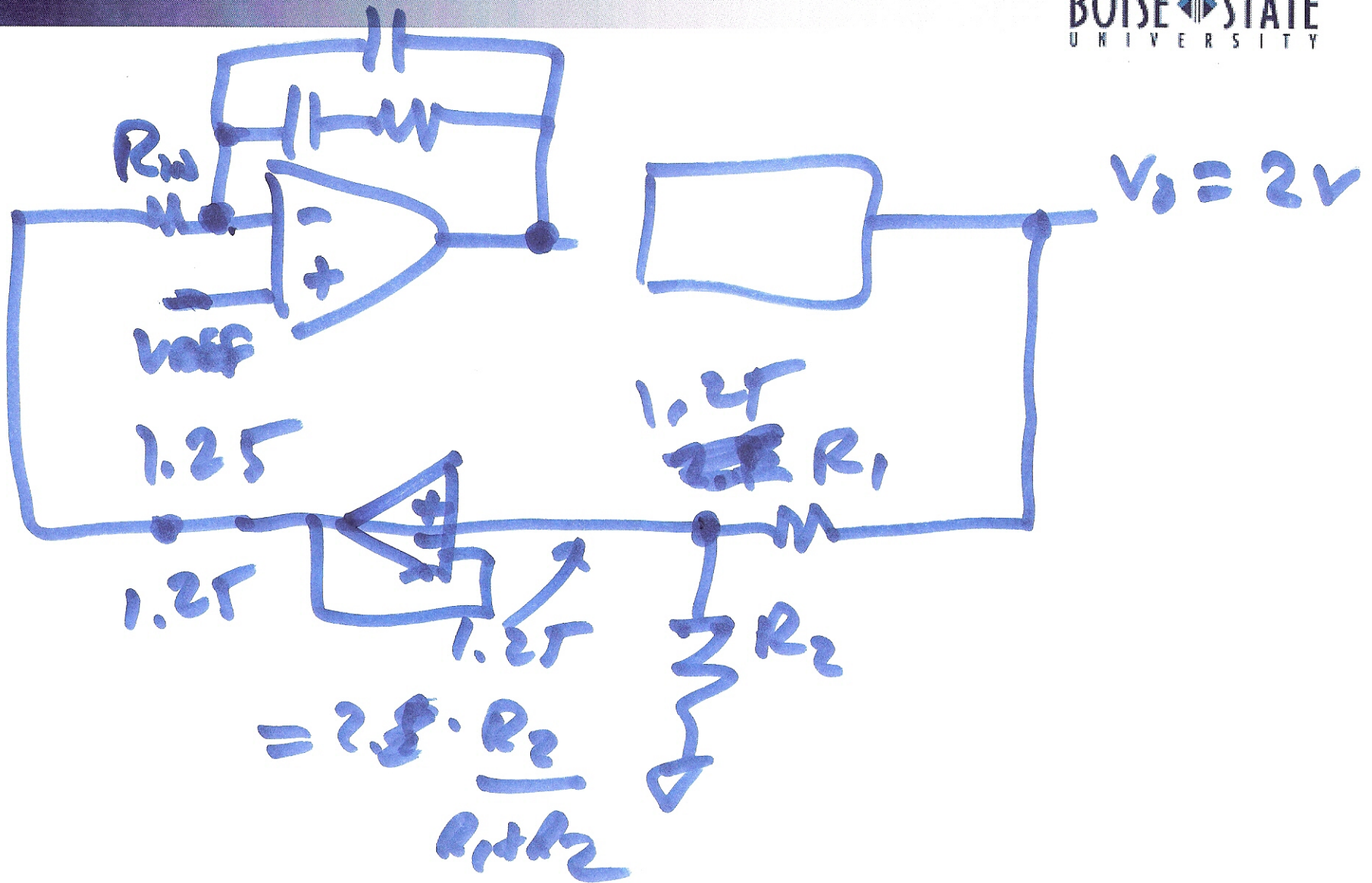


4)


mm

$$Q = \frac{\text{energy stored}}{\text{energy lost}}$$

$$Q = \frac{f_0}{BW}$$

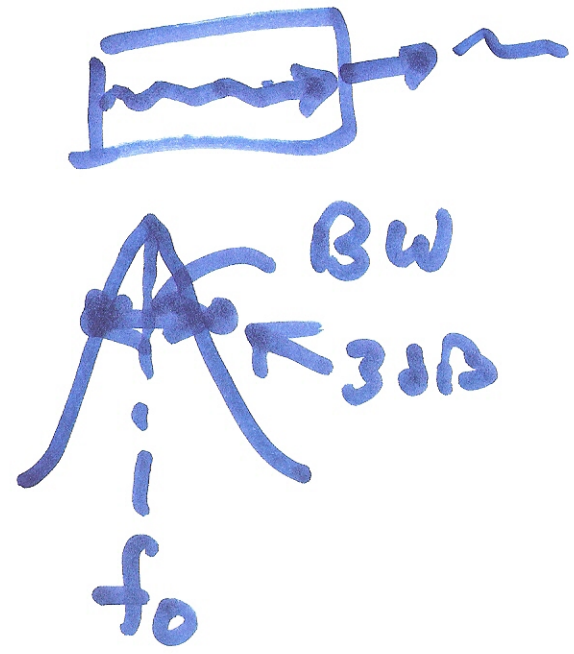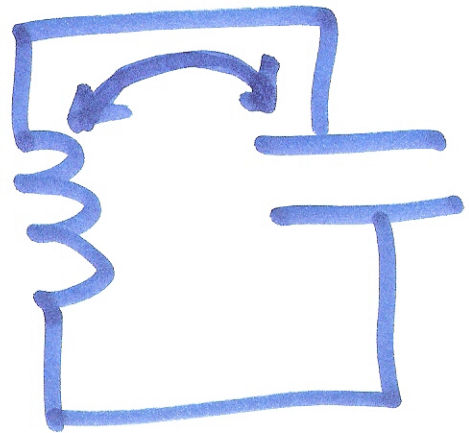

s)

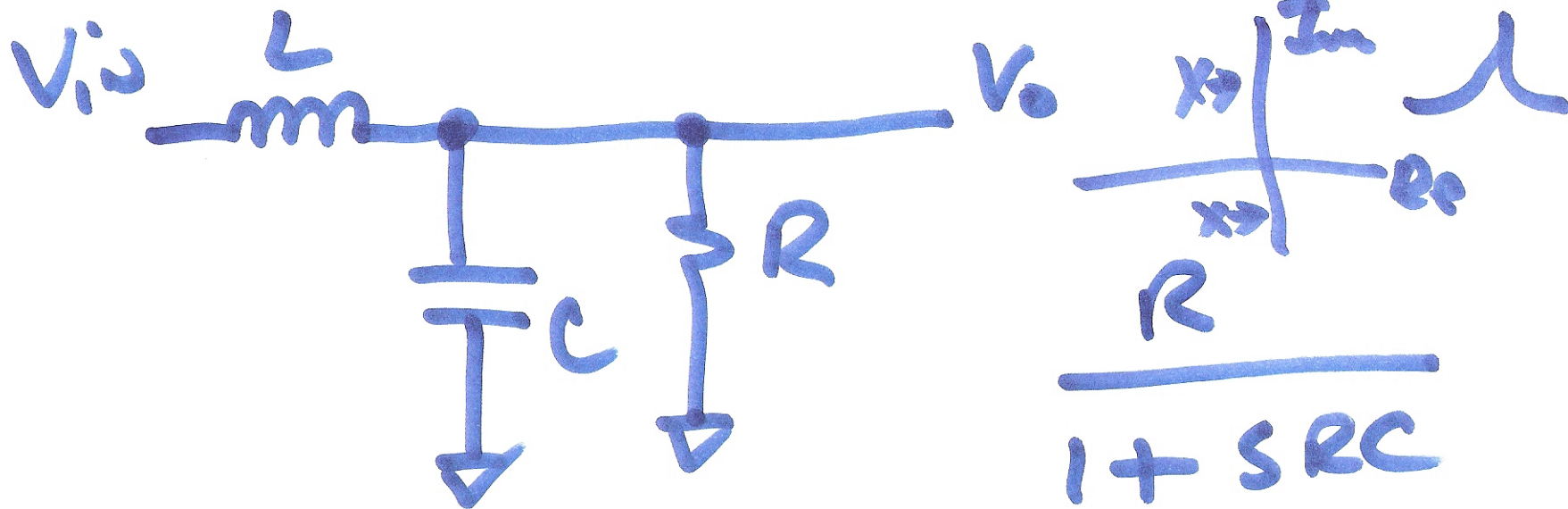

$$\frac{V_o}{V_{in}} = \frac{R}{1 + sRC}$$

$$\frac{R}{1 + sRC} + sL$$

6)

$$\frac{V_o}{V_{in}} = \frac{R}{R + sL + s^2 RLC}$$

$$= \frac{1}{LC} \cdot \frac{1}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

$$= \frac{1}{LC} \cdot \frac{1}{(s + p_1)(s + p_2)}$$

$$p_1, p_2 = \frac{-\frac{1}{RC} \pm \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}}{2}$$

→

$$1 \mu s \rightarrow \frac{1}{2\pi \cdot 10^{-6}} = 159 \text{ Hz}$$

$$P_1, P_2 = \frac{-1}{RC} \pm \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}$$

$$f_0 = \frac{1}{2\pi \sqrt{LC}}$$

$$= \frac{1}{2\pi \cdot 10^{-6} \cdot \sqrt{100 \cdot 400}}$$

$$= \frac{1}{2\pi \cdot 2 \cdot 100 \cdot 10^{-6}} = \frac{1}{2} \cdot 1.59 \text{ K} = \underline{\underline{.79 \text{ kHz}}}$$

8)