
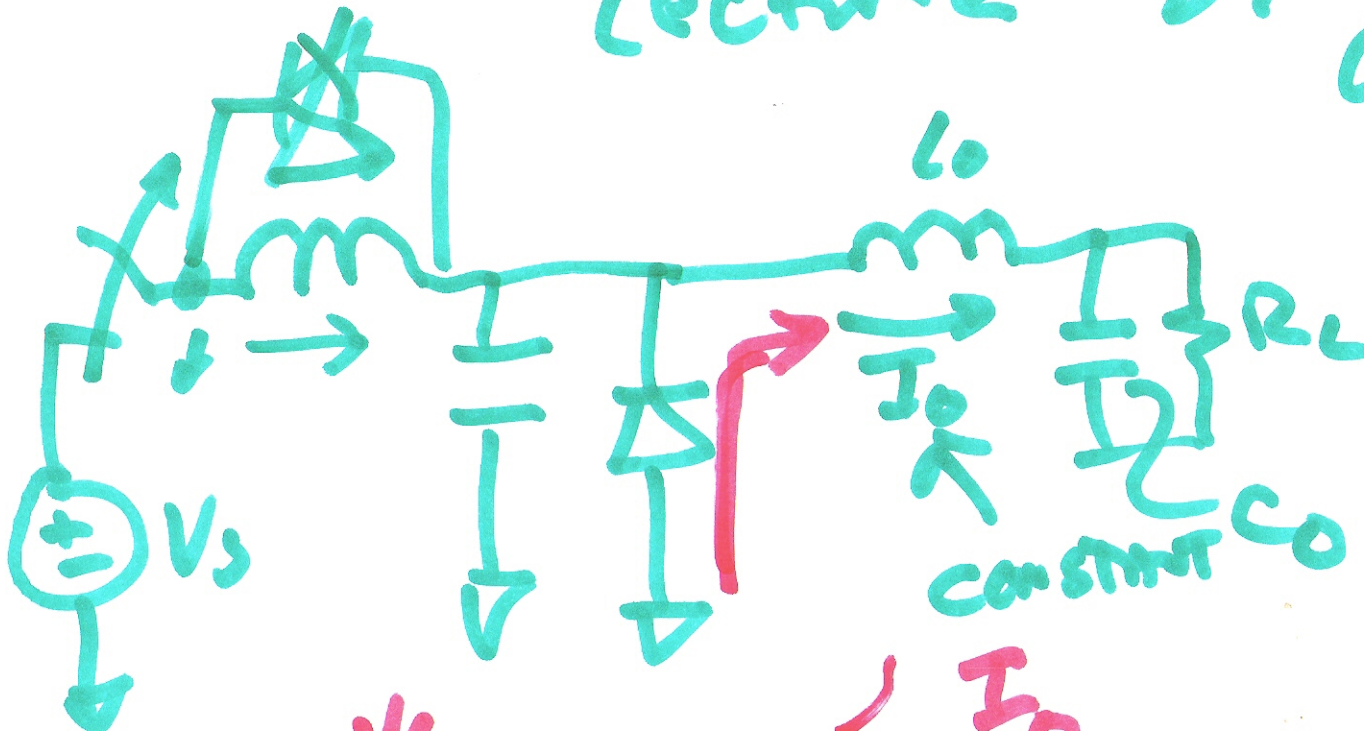


Lecture 27

OCT. 27
2010

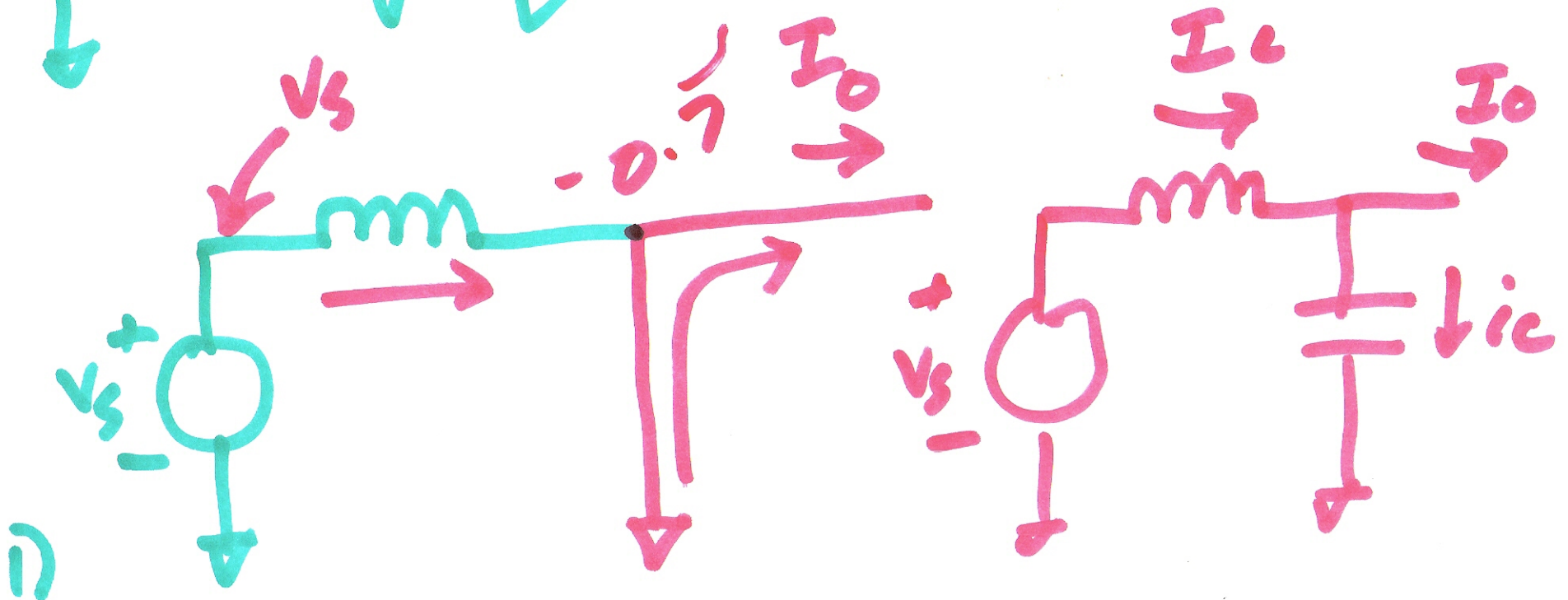

$$v = L \cdot \frac{di}{dt}$$




(1)

$0 < t < t_1$, diode is on

$$I_0 = I_L + I_D$$
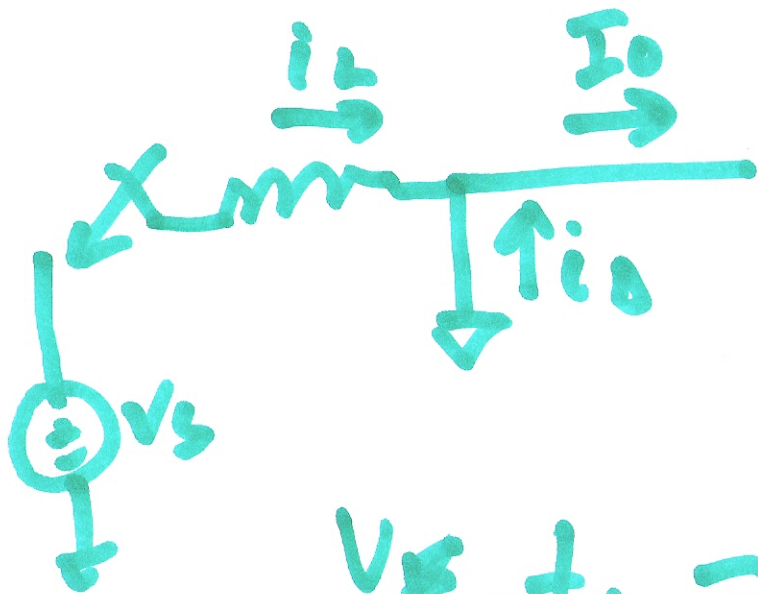
$$i_L(t) = \frac{1}{L} \int_0^t v_s \cdot dt = \frac{V_s}{L} \cdot t$$



$$I_0 = I_0 - I_L$$

t_1 occurs when

$$\frac{V_s}{L} \cdot t_1 = I_0$$

$$I_0 = I_L$$


$$t_1 = \frac{I_0 \cdot L}{V_s}$$

2)

$t_1 < t_0 < t_2$

inductor, L_r ,
 i_L and supplies

charges C_r
 current to load

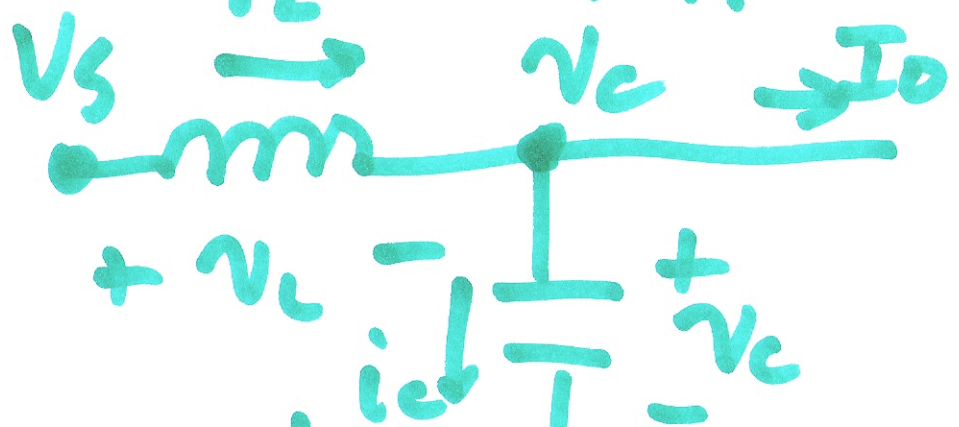

$$v_L(t) = V_s - v_c(t)$$

$$i_L = \frac{1}{L} \int_{t_1}^{t_2} v_L(t) \cdot dt$$

$$\frac{1}{L} \int_{t_1}^{t_2} v_L \cdot dt = C \frac{dv_c}{dt}$$

$$i_c = C \frac{dv_c}{dt}$$

(9-7)

$$L_r \frac{d^2 i_L(t)}{dt^2} + \frac{i_L}{L_r C_r} = \frac{I_o}{L_r C_r}$$


$$i_L = i_c + I_o$$

$$= \frac{I_o}{L_r C_r}$$

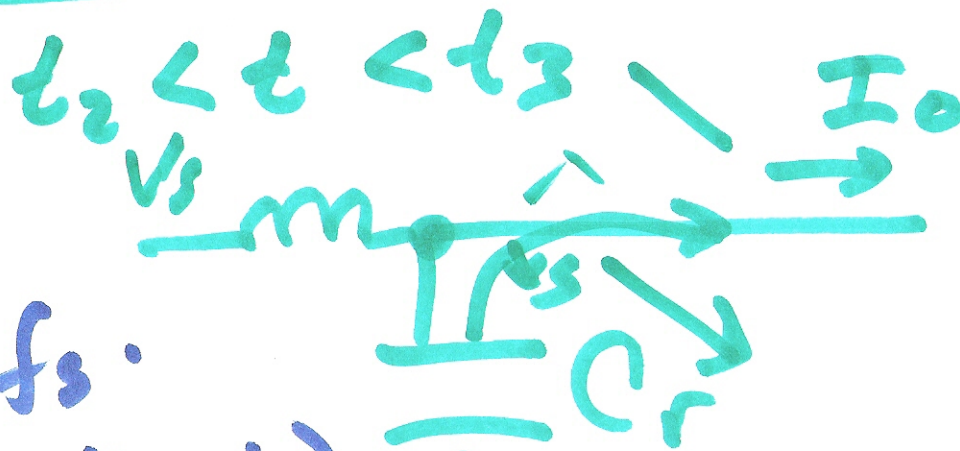3)

$$t_2 - t_1 = \frac{1}{\omega_0} \cdot \left[\sin^{-1} \left(\frac{I_0 \cdot Z_0}{V_S} \right) + \pi \right]$$

$$\omega_0 = \frac{1}{\sqrt{L_r C_r}} \quad Z_0 = \sqrt{\frac{L_r}{C_r}}$$



$$I_0 = C_r \frac{dv_c}{dt}$$

$$v_c(t) = \frac{I_0}{C_r} \cdot t$$

$$v_c(t) = \frac{I_0}{C_r} \cdot (t - t_2) \quad t < t_2$$

$$v_o = V_S \cdot f_s$$

$$4) \left[\frac{t_1}{T} + (t_2 - t_1) + t(t_3 - t_2) \right]$$