

Lecture 41


Dec. 10, 2010

Review for the final


- 1) Know how to do all HW problems
- 2) Know how to do problems on tests 1 & 2
- 3) Project questions!

1)

Sketch PI loop filter


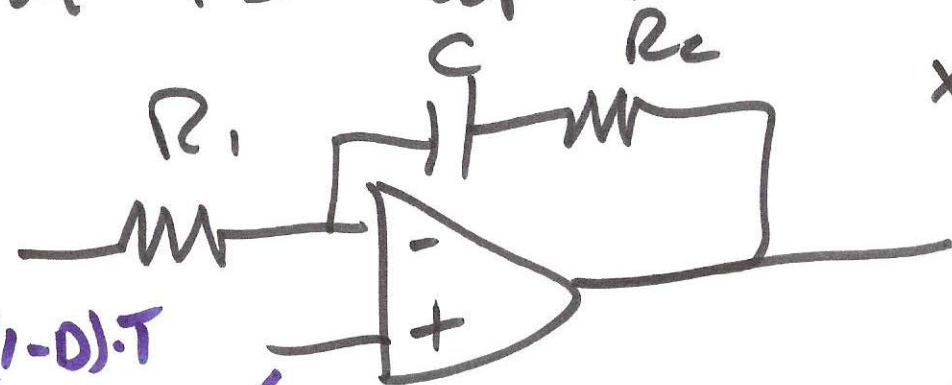


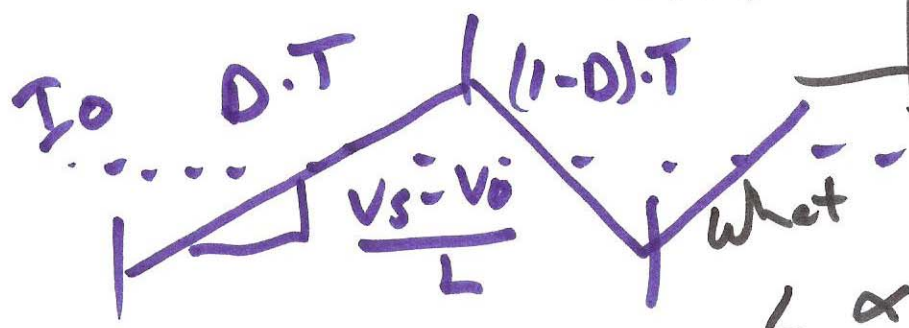xfer function
 \hookrightarrow cross-over freq.



what sets $L \propto \frac{R}{f_s}$
 what sets C value


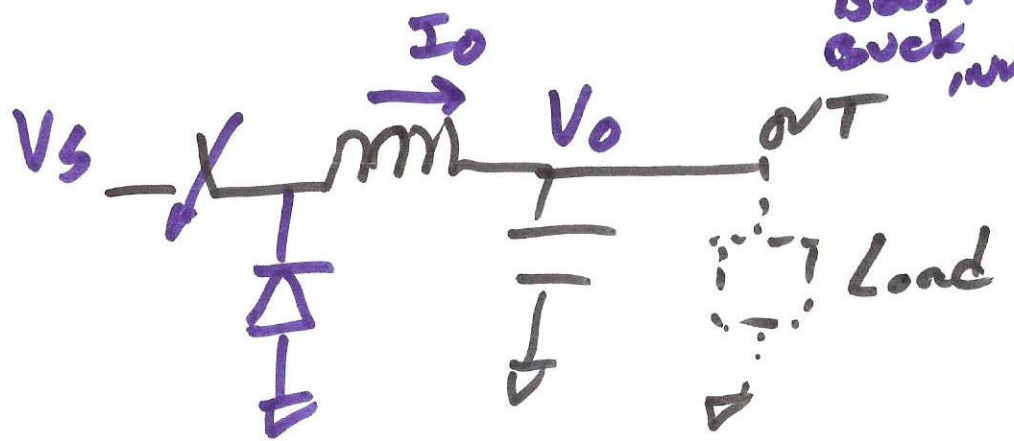
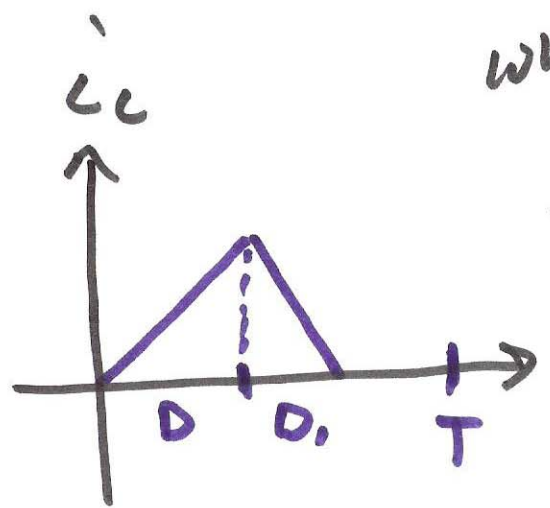
L in a buck converter switching & load
 Buck-Boost
 Cuk
 Boost
 Buck, inv.?



2)

Projects cont'd

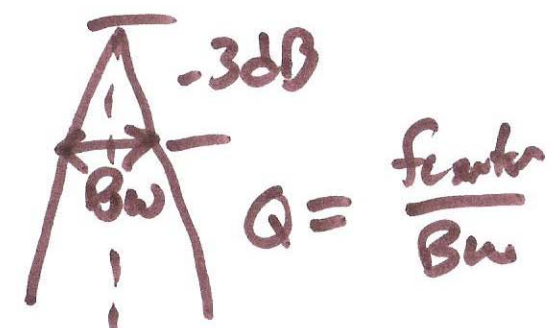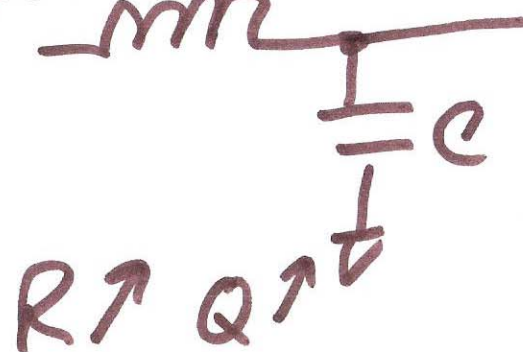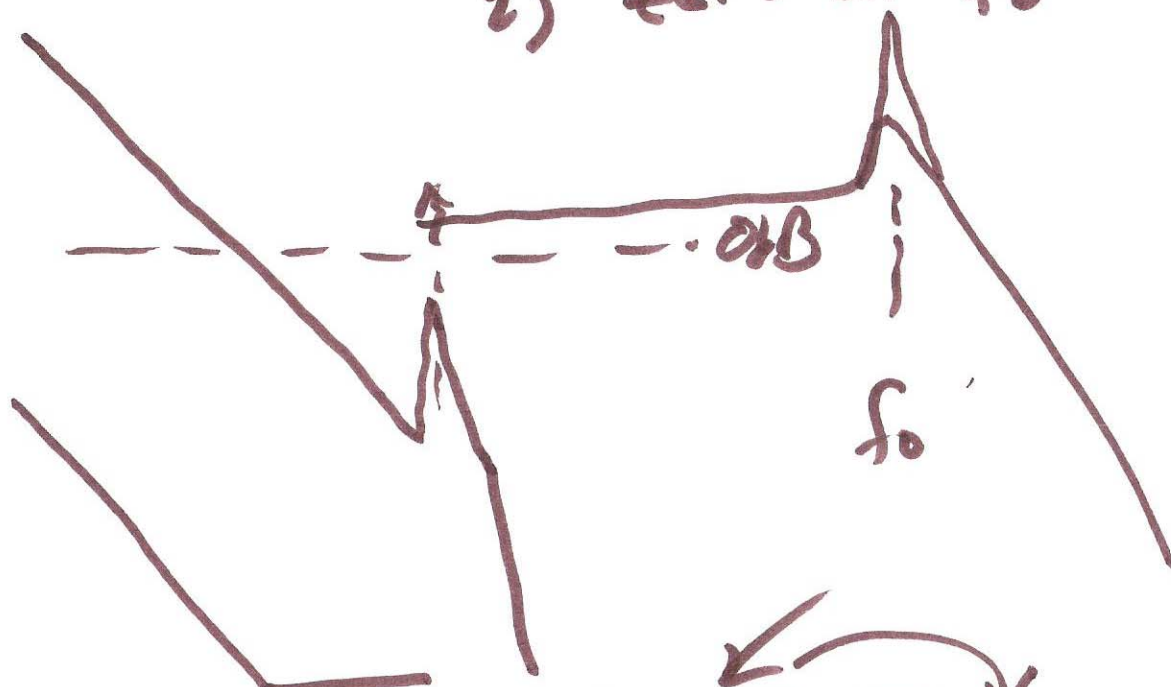- 1) Determine $f_0 = \frac{1}{2\pi\sqrt{LC}}$
- 2) zero at f_0




$$Q = \frac{\text{Energy stored}}{\text{Energy lost}}$$

3)

sketch half-bridge
 ZVS Buck converter
 non-overlapping clock generation

open-loop PWM

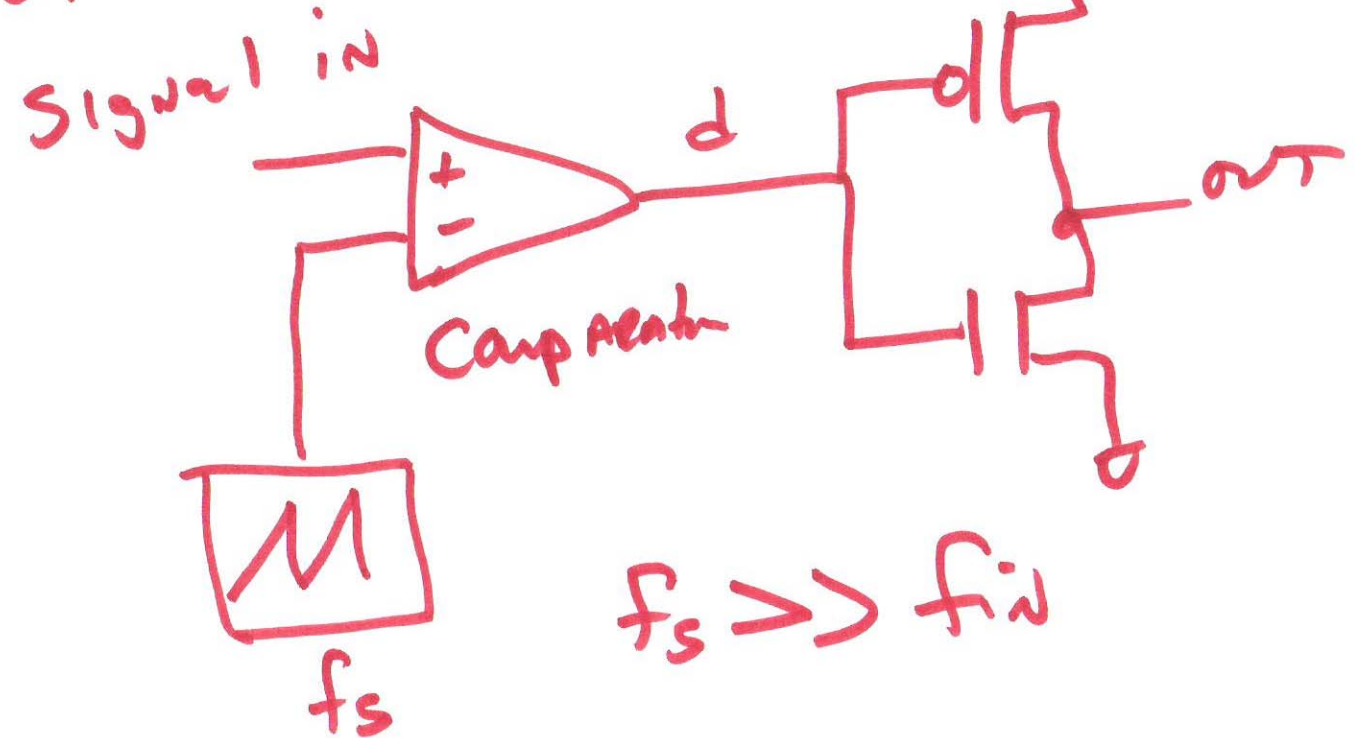

→ Tests ←

$$L_2 = 100 \mu H$$

$$N = 100$$

$$L_1 = \frac{100 \mu H}{10K} = 6 \mu H$$

→ H.W. ←

$$\frac{N_1}{N_2} = \sqrt{\frac{L_1}{L_2}} = \frac{1}{N} \text{ Charge}$$

pump operation

Topology


Sketch neg. V C.P.

Fly back converter

Magnetizing induct.

modeling / operation


x furs.

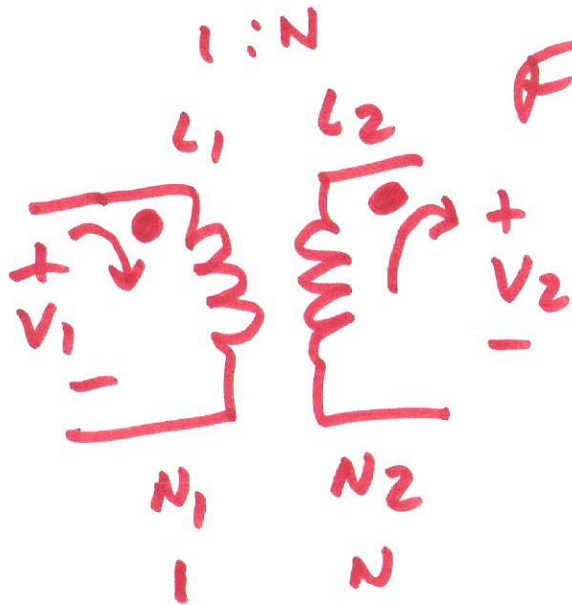

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}, \quad \frac{I_1}{I_2} = \frac{N_2}{N_1}$$

5)

N1 N2

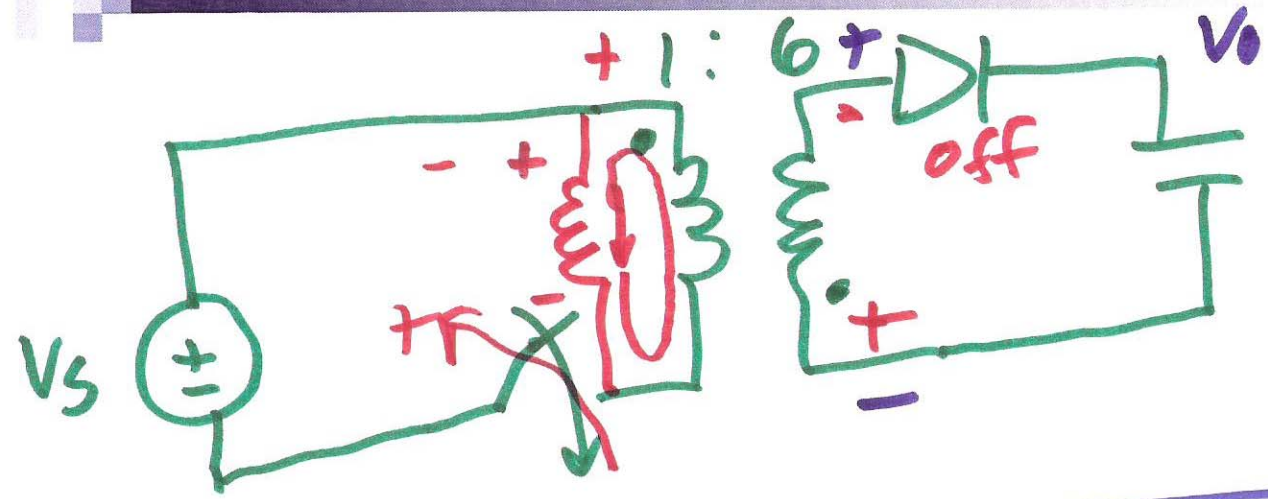

flyback
 Buck
 Boost
 Buck-Boost
 ZVS -

$$V_0 = N V_1 \dots$$

$$V_1 = \frac{V_2}{N}$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{1}{N}$$

$$f_0 = \frac{1}{\sqrt{LC}} \cdot 2\pi$$

6)