
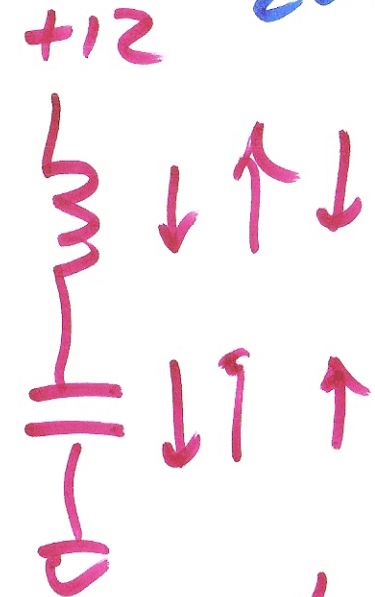
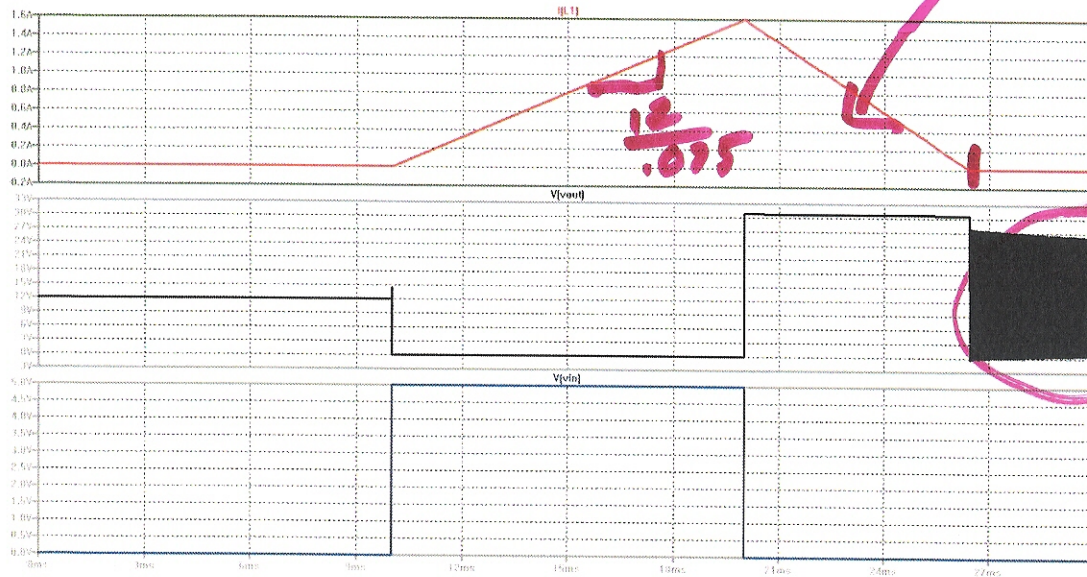




Lecture 8

Sept. 13, 2010

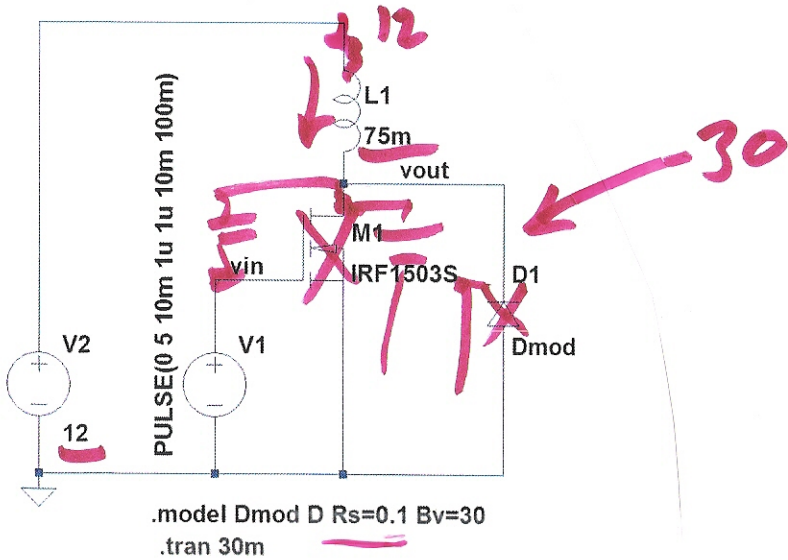

$$f_{res} = \frac{1}{2\pi\sqrt{LC}}$$


11

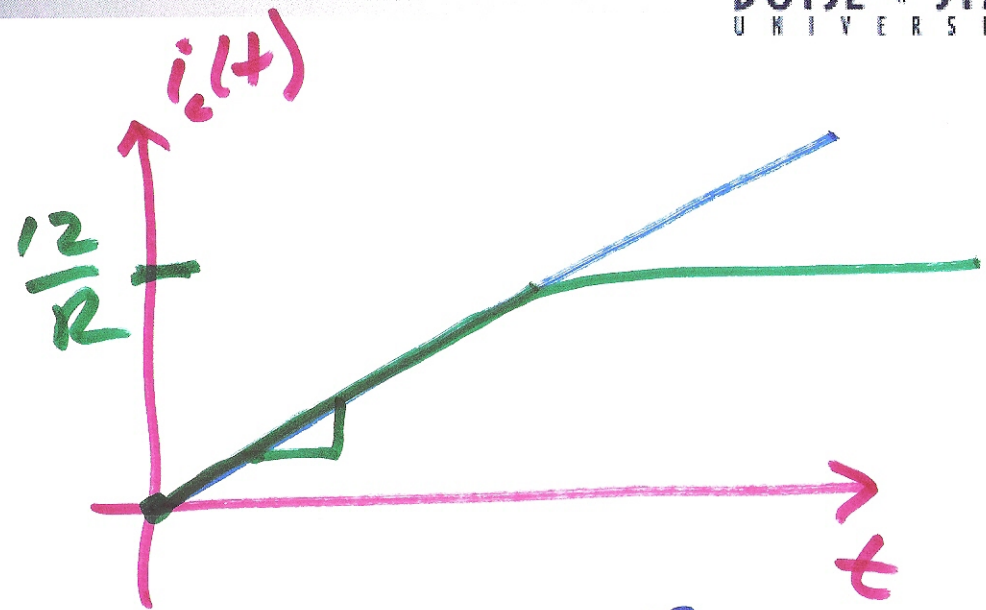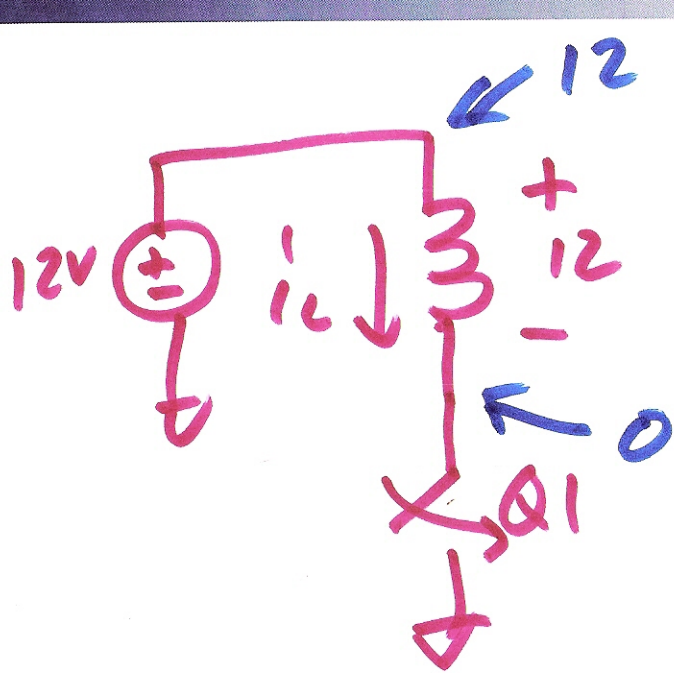


$$V_L = L \cdot \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{V_L}{L}$$

$$i = \frac{V_L}{L} \cdot t$$

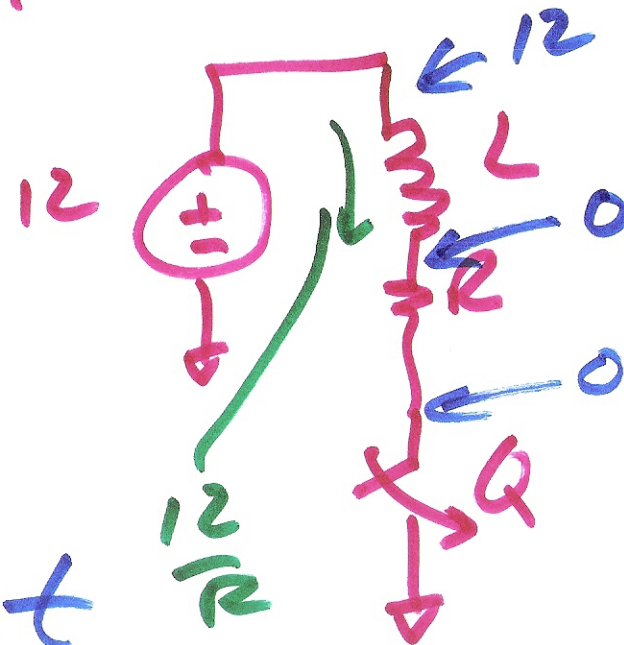

2)

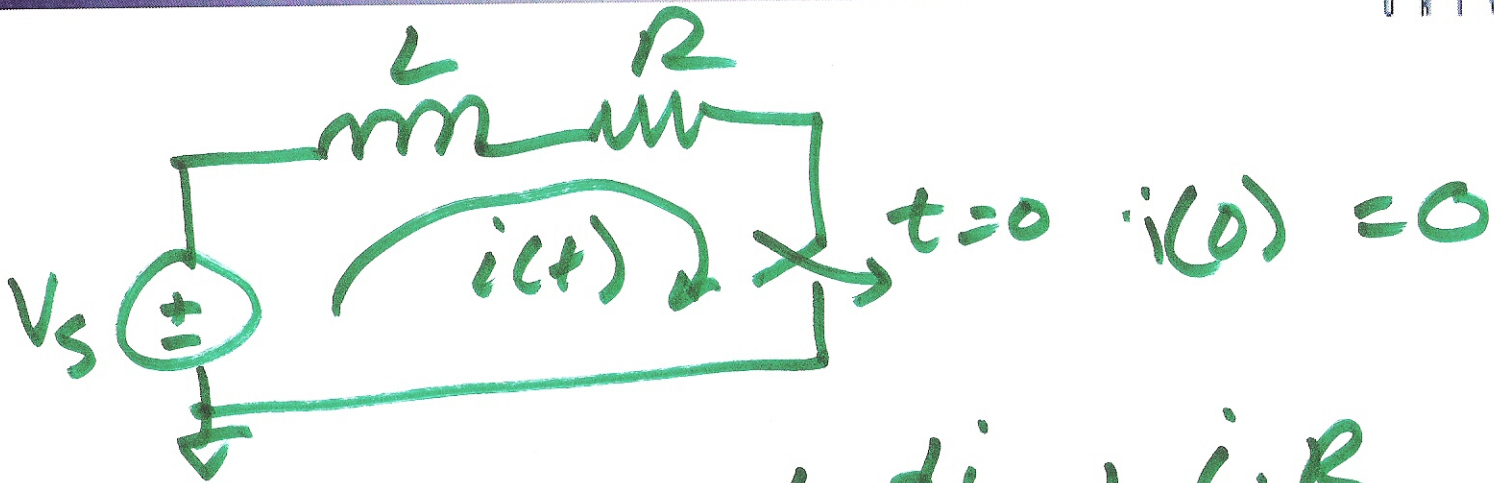

$$V_s = L \cdot \frac{di}{dt} + i \cdot R$$

$$V_s = L s I(s) + I(s) \cdot R$$

$$V_s = I(s) (L \cdot s + R)$$

$$i(t) = \frac{V_s}{R} \left(1 - e^{-t/\tau} \right)$$

$$i(t) = \frac{V_s}{R} \left(1 - e^{-t/\tau} \right)$$

$$I(s) = \frac{V_s}{s \cdot L + R}$$

$$= \frac{V_s}{L} \cdot \frac{1}{s + R/L}$$

$$i(0) = 0$$



$$i(\infty) = \frac{V_s}{R}$$

3)

$$i(t) = \frac{V_S}{R} (1 - e^{-t/\tau})$$


$$= \frac{V_S}{R} \left(1 - \left(1 + \left(\frac{-t}{\tau} \right) + \dots \right) \right)$$

$$= \frac{V_S}{L} \cdot t$$

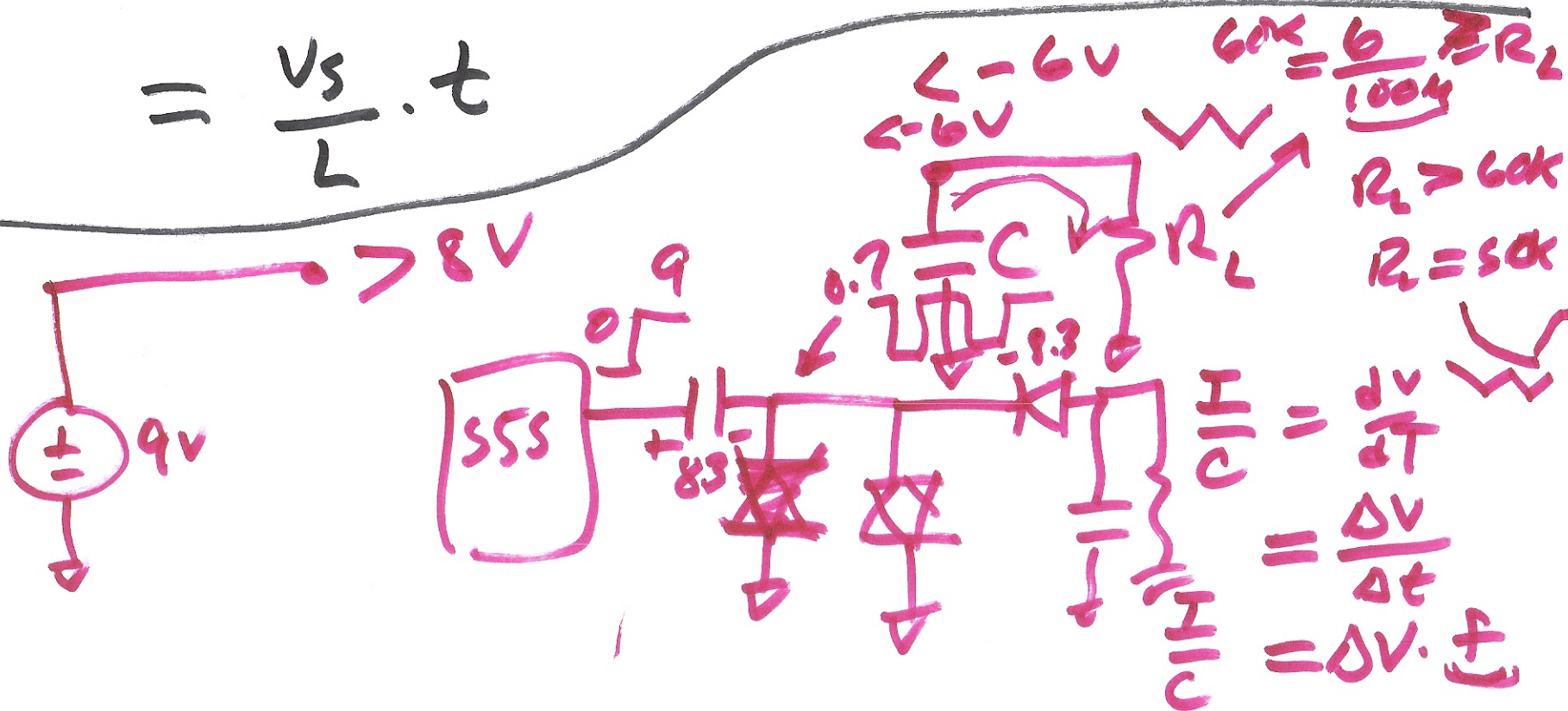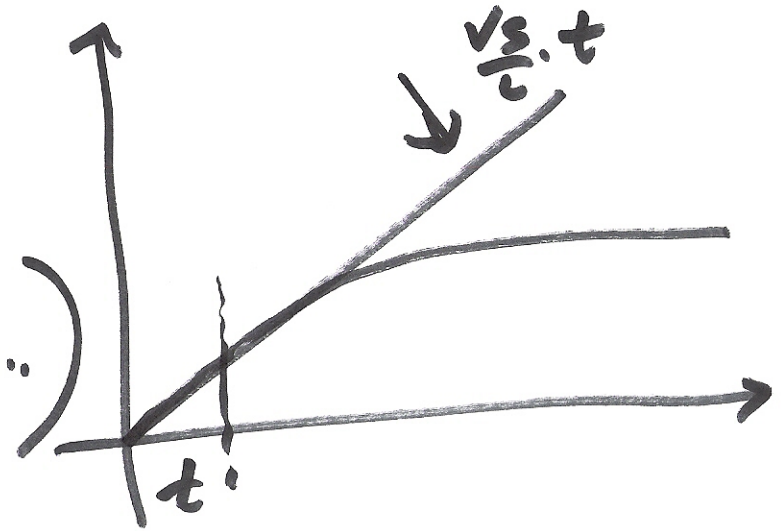


4)

$$CV=Q$$

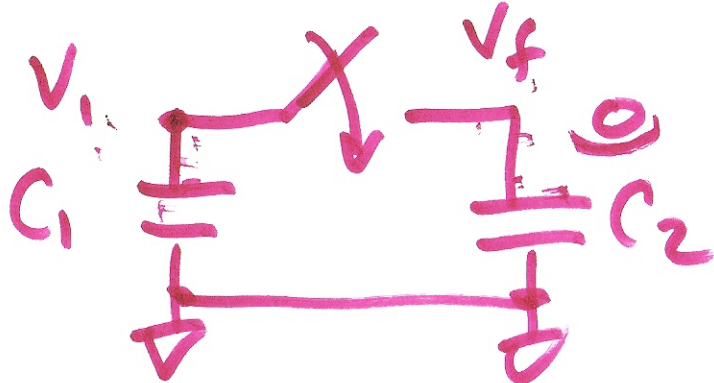
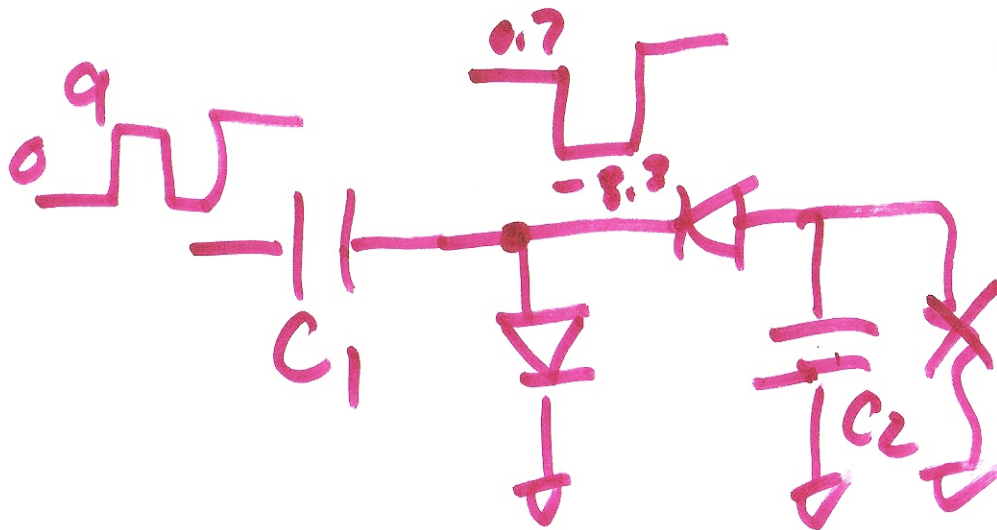
$$C_1 \cdot V_1 + 0 \cdot C_2 = V_f (C_1 + C_2) \quad qv$$



$$V_f = \frac{C_1}{C_1 + C_2} \cdot V_1$$


$C_1 = C_2$

$$V_f = 4.5V$$

$$C_1 \gg C_2$$

s)

Ex. 6.1 ←

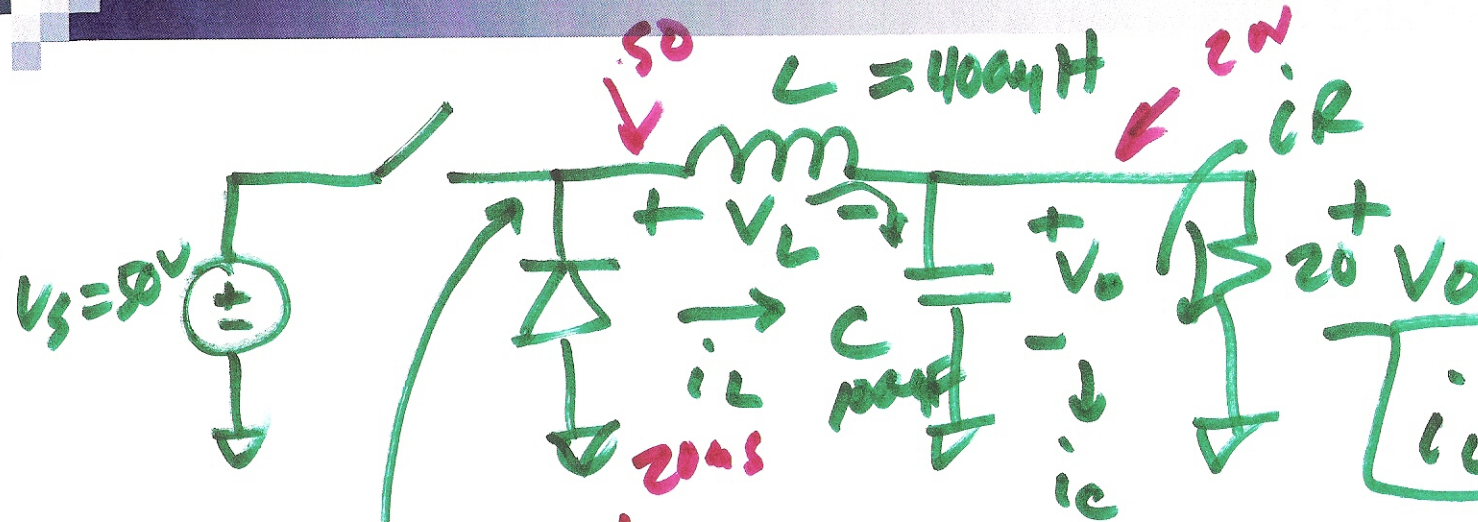


$$i_L = i_R + i_C$$

$$D = 0.4$$

$$V_o = 0.4 \cdot 50 = 20V$$

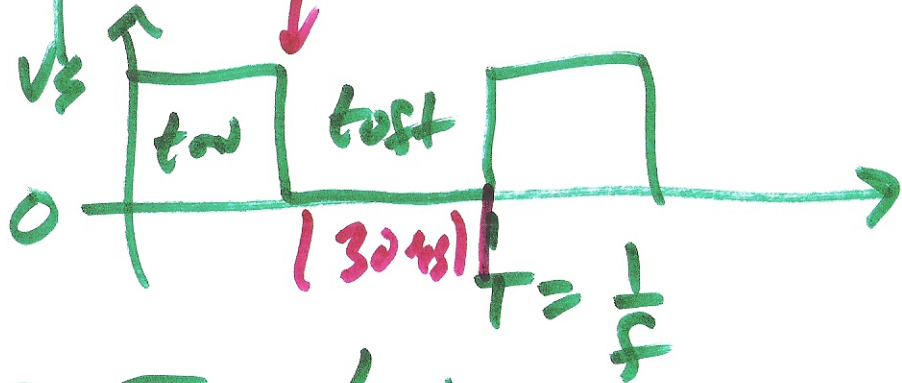
$$i_L = \frac{V_o}{R} = \frac{20}{20} = 1A$$




$$D \cdot T = t_{on}$$

$$(1-D) \cdot T = t_{off}$$


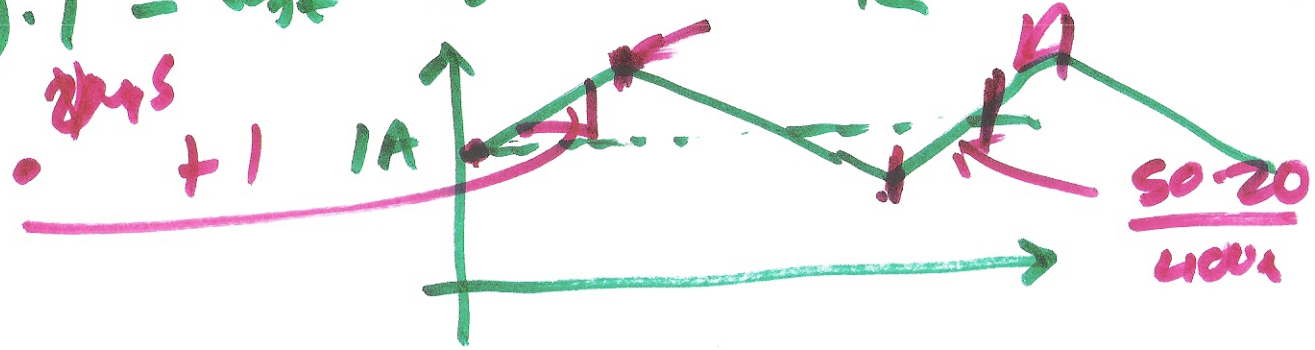
$$\frac{50-20}{400 \mu H} \cdot 20 \mu s$$



6)

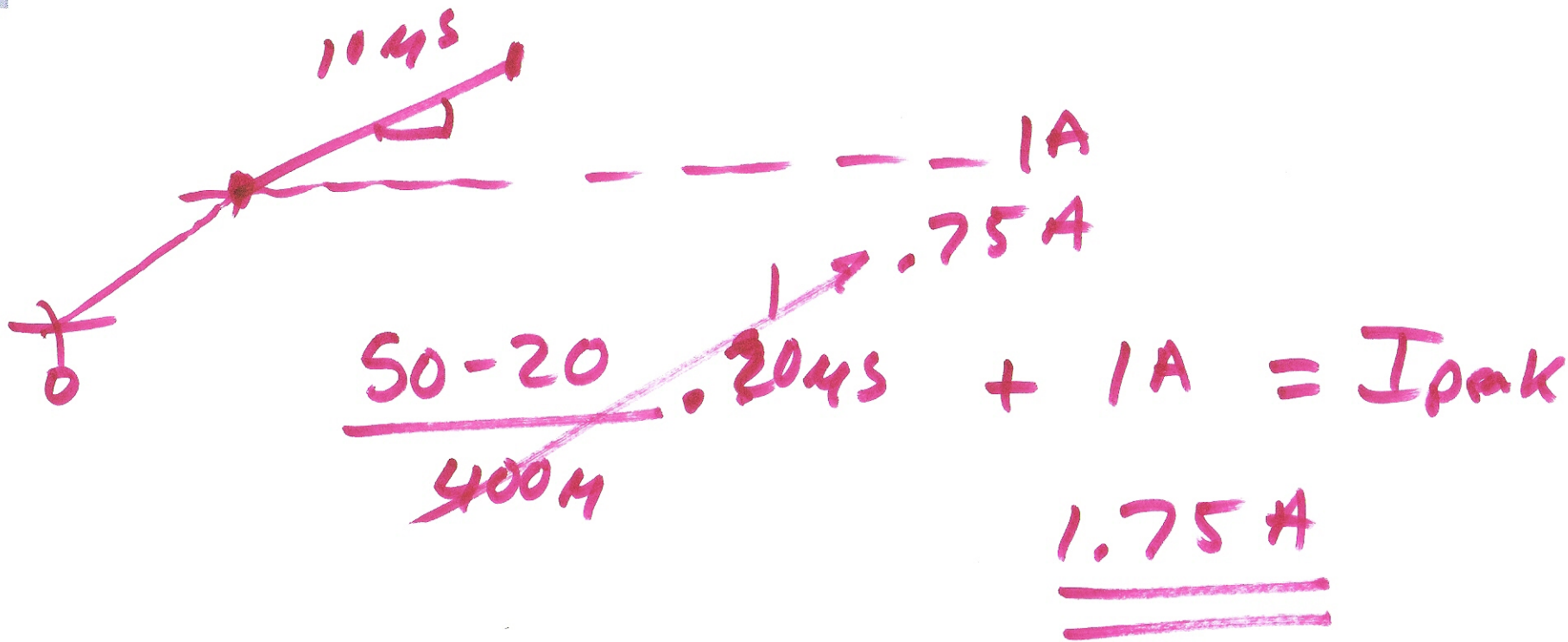

7)

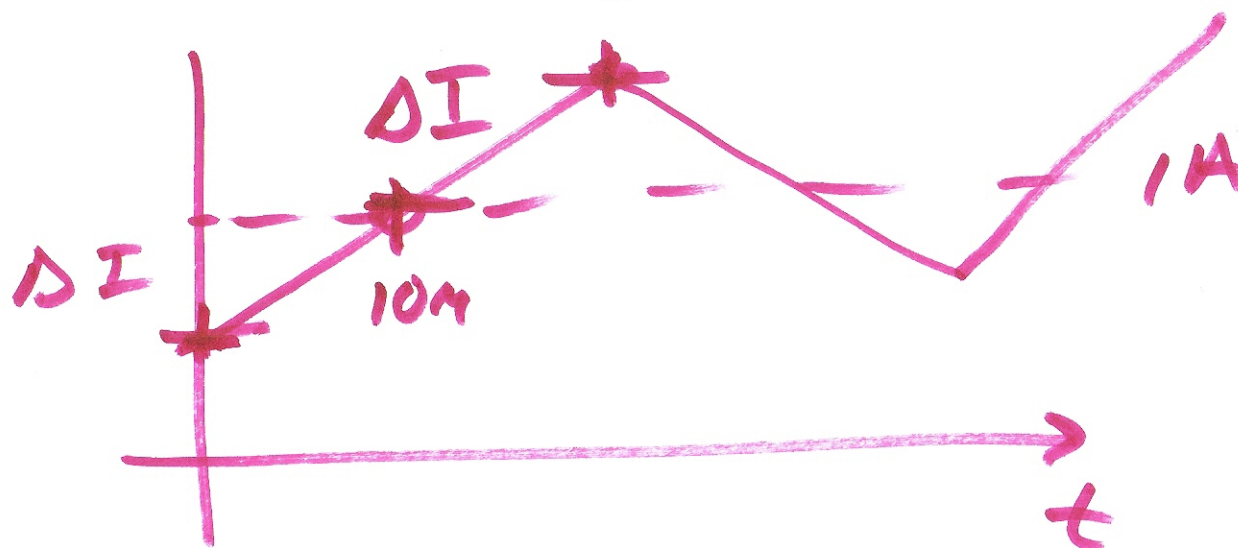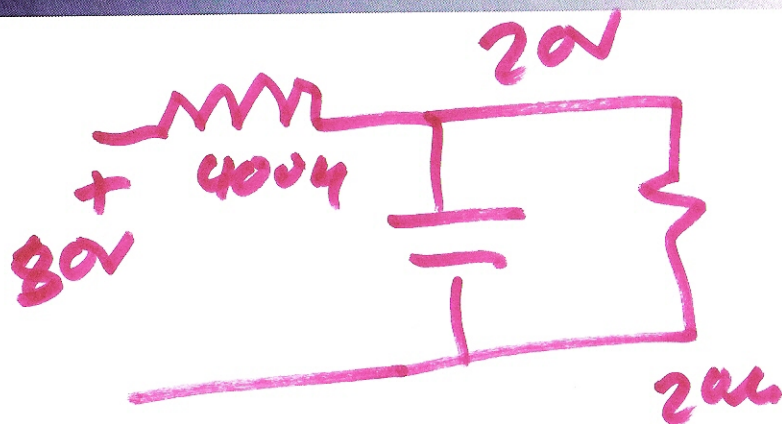

$$\frac{50-20}{40\Omega} \cdot (10\Omega) + 1A = I_p$$

$$I_m = .25 A$$

8)