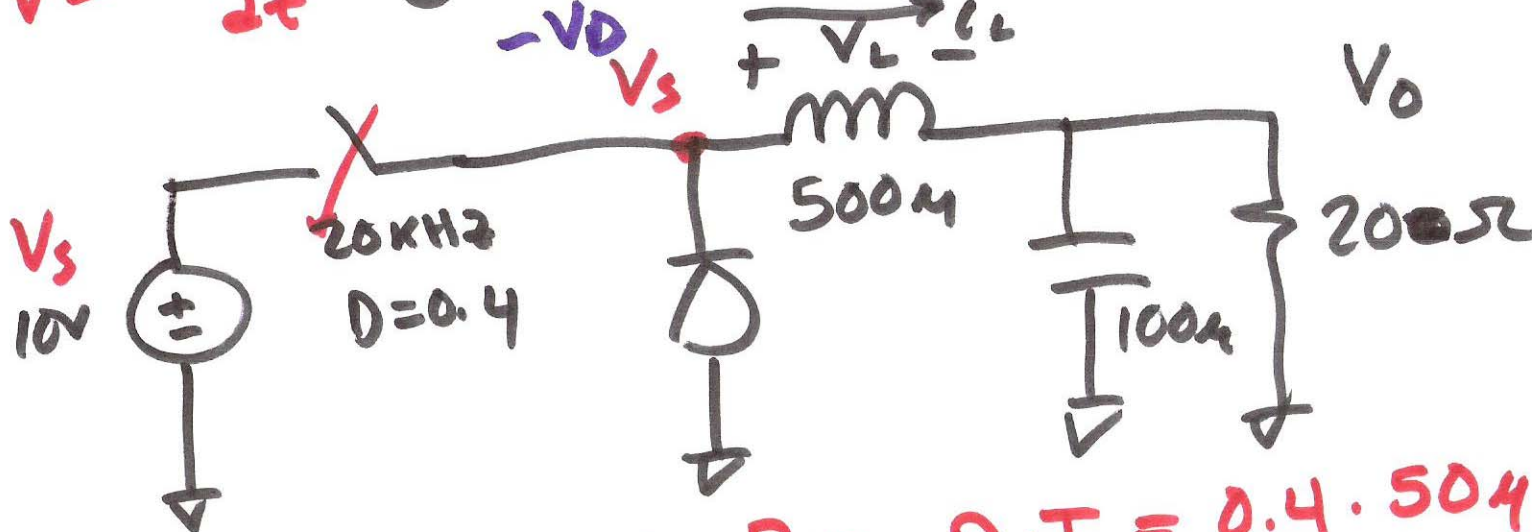


$v = L \cdot \frac{di}{dt}$

Give DC-DC converter



- $V_o = ?$
- $\frac{\Delta V_o}{V_o} = ?$
- $\Delta i_L = ?$
- $I_{MAX} = ?$
- $I_{min} = ?$

switch closed for $D \cdot T = 0.4 \cdot 50\mu s = 20\mu s$

$$\frac{V_s - V_o}{L} = \frac{\Delta i_L}{D \cdot T}, \quad \Delta i_L = 20\mu s \cdot \frac{10 - 3.5}{500\mu H}$$

switch open for $(1-D)T = 0.6 \cdot 50\mu s = 30\mu s$

$$\frac{-V_o - V_o}{L} = \frac{\Delta i_L}{(1-D)T}$$

$$\frac{20 \cdot 6.42}{50 \cdot 25} \approx \frac{1}{4} A$$

$\Delta i_L = \frac{1}{4} A$

2)


Buck $V_s > V_o$

$$\left(\frac{V_s - V_o}{L}\right)(DT) + (1-D)T \cdot \frac{-V_o - V_o}{L} = 0$$

$$V_s \cdot D - V_o \cdot D - V_o(1-D) - V_o(1-D) = 0$$

$$V_s \cdot D - V_o(1-D) = V_o$$

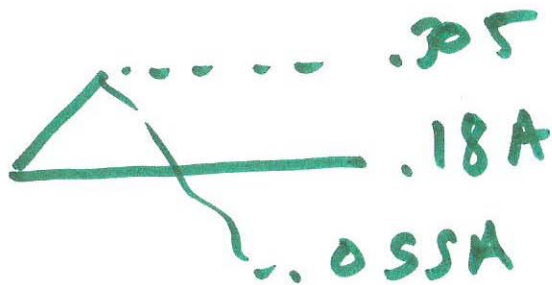
$$V_o = 10 \cdot 4 - 0.7(0.6) \\ = 4 - .42 = \underline{\underline{3.58V}} = \underline{\underline{V_o}}$$



$$I_{MAX} = \frac{\Delta i_c}{2} + \frac{V_o}{R} = \frac{1}{8} A + 1.08A = \underline{\underline{.305A}}$$

$$I_{min} = .18 - \frac{1}{8} A = .055A = \underline{\underline{.055A}}$$

3)

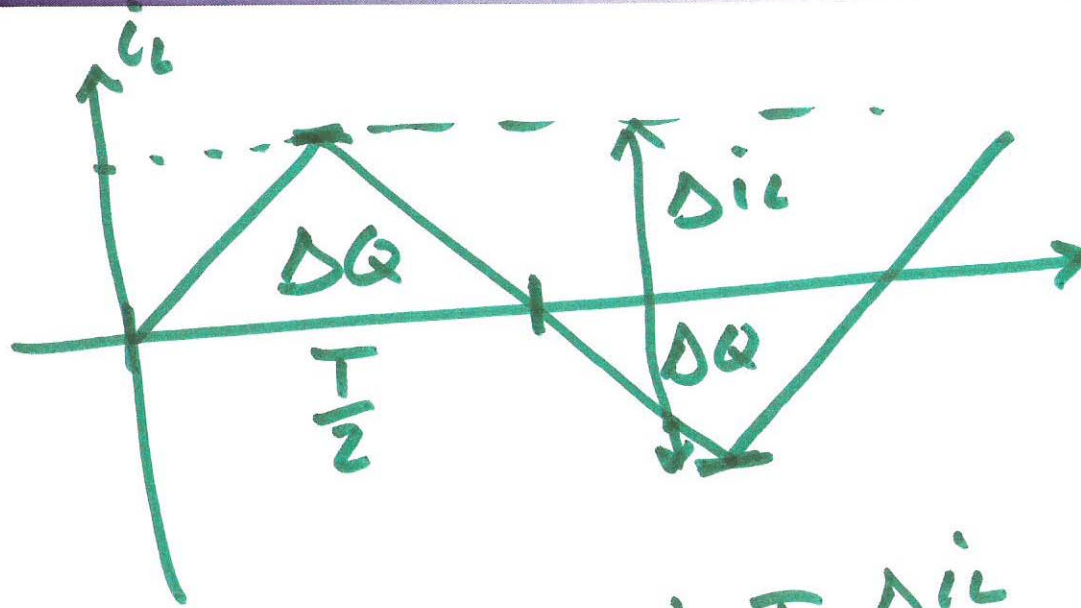

$$CV = Q$$

$$\Delta V_0 = \frac{\Delta Q}{C}$$

$$C = 100 \mu\text{F}$$

$$\Delta Q = \frac{1}{2} T \frac{\Delta i_L}{2} = \frac{T \cdot \Delta i_L}{8}$$

$$\Delta i_L = DT \cdot \left(\frac{V_S - V_0}{L} \right)$$


$$\Delta V_0 = \frac{T}{8} \cdot \frac{DT}{C} \cdot \frac{V_S - V_0}{L} = \frac{50 \mu\text{s} \cdot 50 \mu\text{s} \cdot 4 \cdot 6.42}{8 \cdot 100 \mu\text{s} \cdot 500 \mu\text{s} \cdot 2}$$

$$= \frac{2.5}{160} \approx \frac{1}{64} \approx 18 \text{ nV}$$

$$\frac{\Delta V_0}{V} = \frac{.18}{3.58} \approx .05$$

4)

$$V = L \cdot \frac{di}{dt}$$

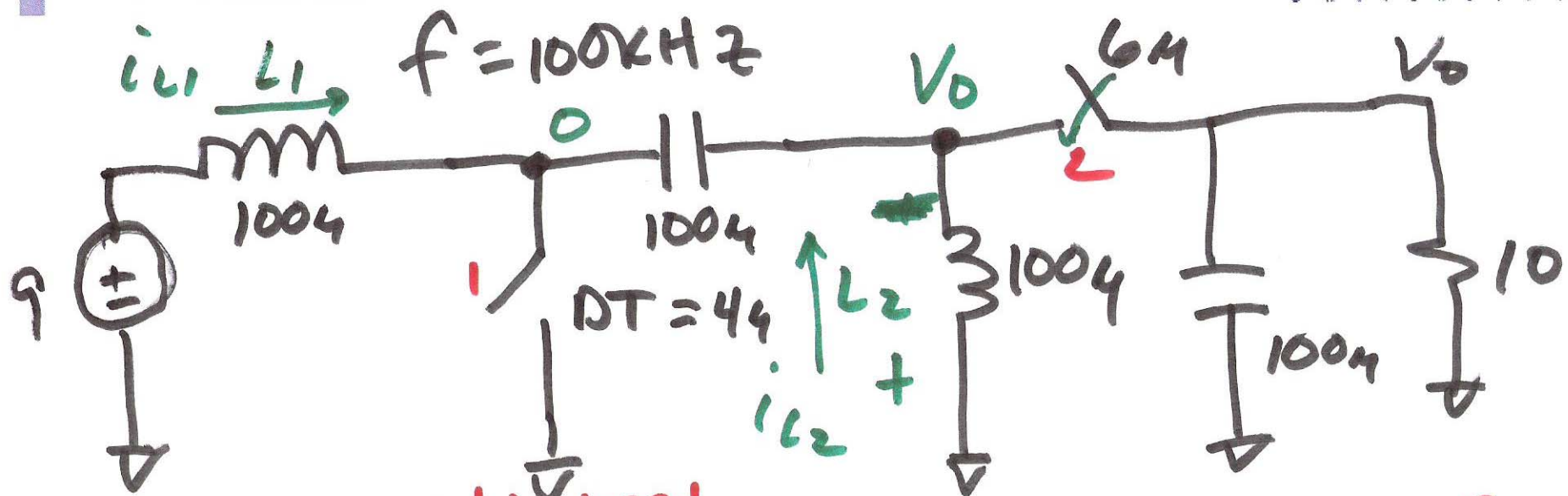

$V_o = ?$

Switch 1 closed

$$\Delta i_{L1} = \frac{V_s}{L_1} \cdot DT = \frac{9}{100\mu\text{H}} \cdot 44 = \frac{9}{25} \text{ A}$$


Switch 2 closed

$$\Delta i_{L2} = \frac{-V_o}{L_2} \cdot (1-D)T =$$

$$V_s \cdot i_{L1} = \frac{V_o^2}{R}$$

$$\frac{V_s}{L_1} \cdot DT + \frac{-V_o}{L_2} \cdot (1-D)T = 0$$

5)

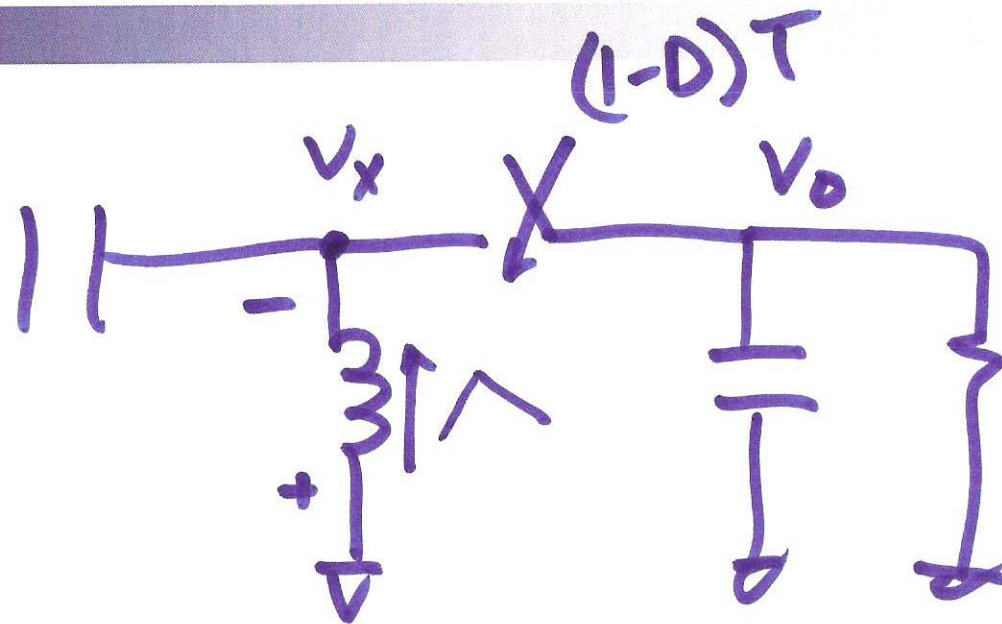


$$\Delta i_L = (1-D)T \cdot \frac{V_o}{L}$$

$$-\Delta i_L = DT \cdot \frac{-V_x}{L}$$


b)

$$\frac{v}{L} = \frac{di}{dt}$$

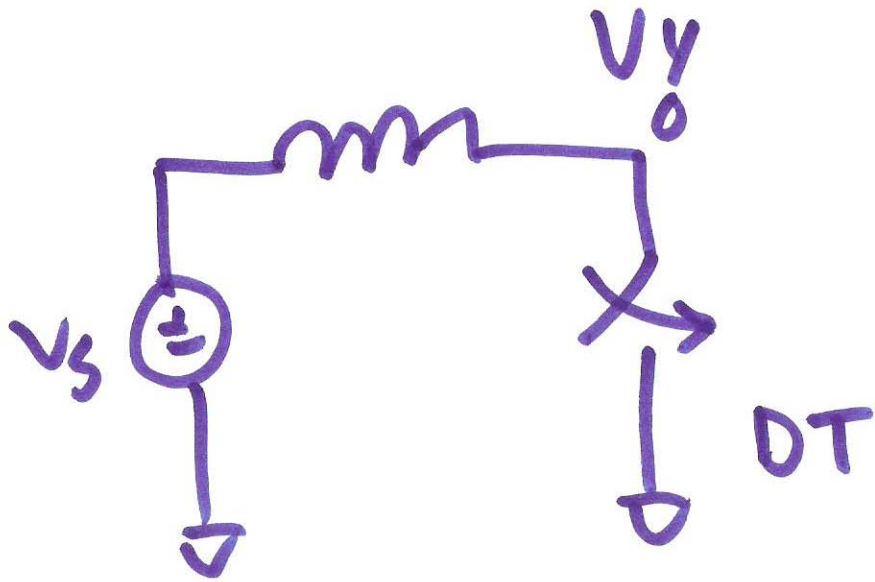


$$\begin{aligned}\Delta i_L &= DT \cdot \frac{v_s}{L} \\ &= (1-D)T \cdot \frac{v_s - v_y}{L}\end{aligned}$$

$$I = C \frac{dv}{dt}$$

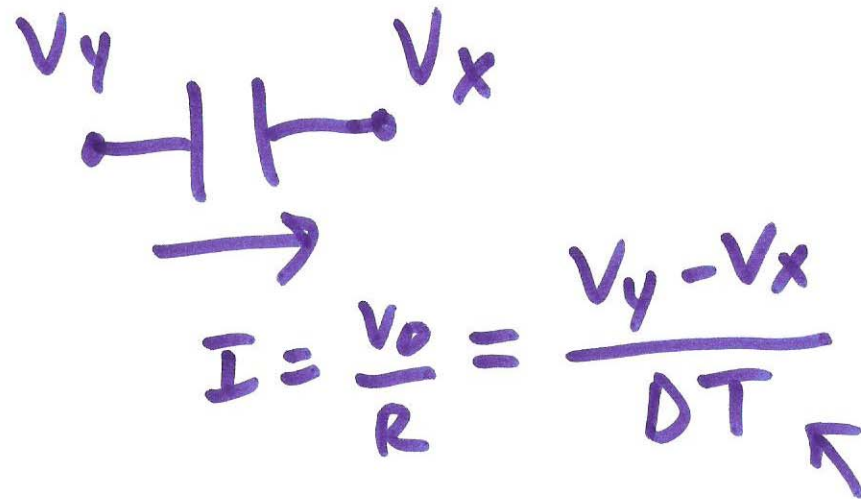

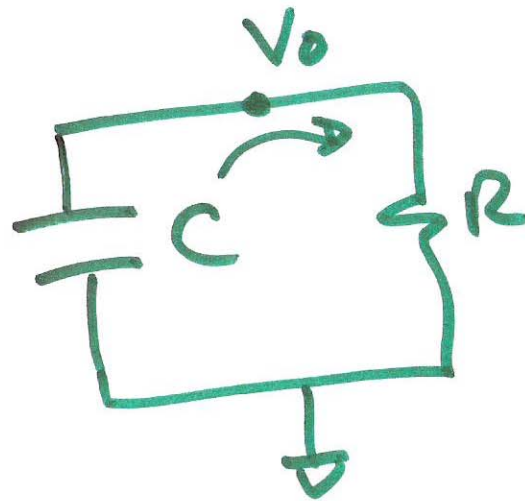2)

- * Energy problems
- * Study Ex. 6-1 to 6-9
- * Really understand Buck & Boost
- * Questions about operation of converters.
- * Study homework problems
- * Derive relationship between V_o and V_s for Buck or Boost operating in discontinuous with current inductor



estimate the ripple

$$I = C \frac{dv}{dt}$$

$$\frac{V_o}{R} = \frac{\Delta V_o}{\Delta T} \cdot C$$

9)