
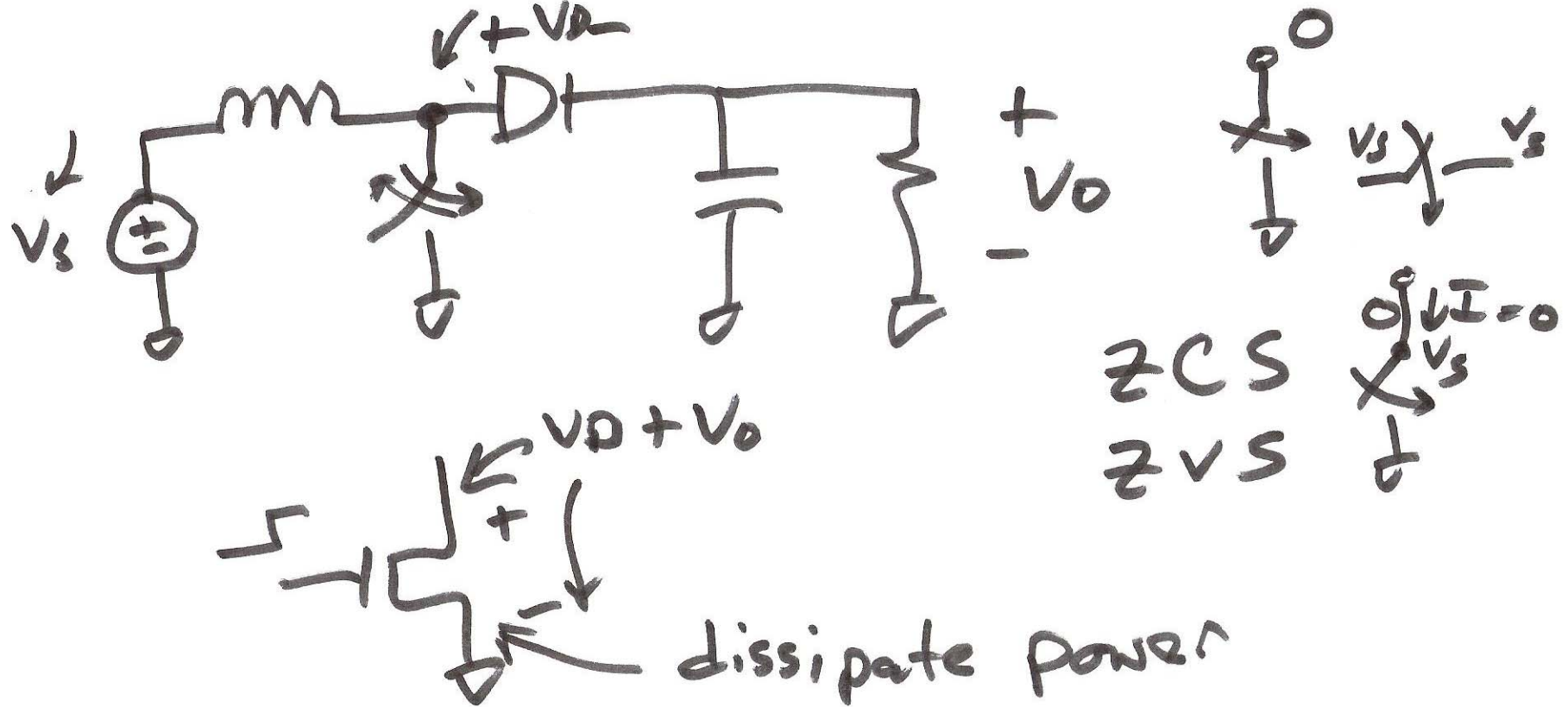


Sept. 29, 2011

$v_o + v_D$ Lecture 11

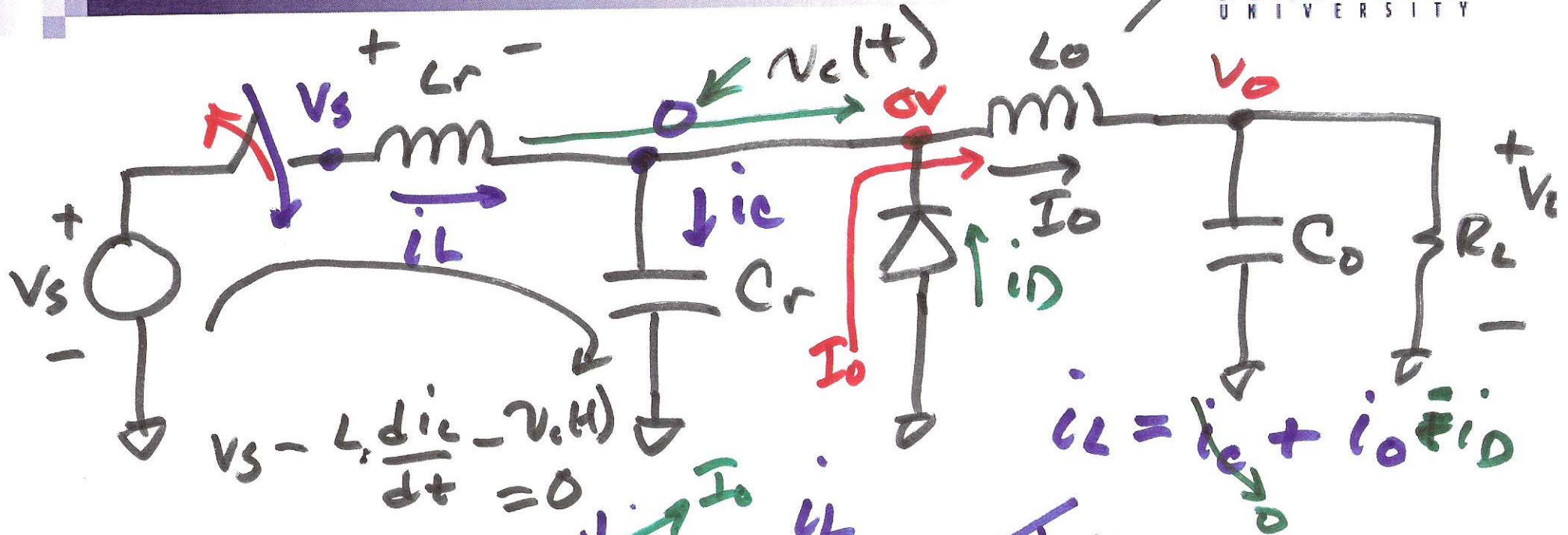


RESONANT CONVERTERS ZVS, ZCS



$$\frac{V_s}{L} = \frac{\Delta i_L}{dt} \rightarrow t_1$$

$$t_1 < t < t_2$$

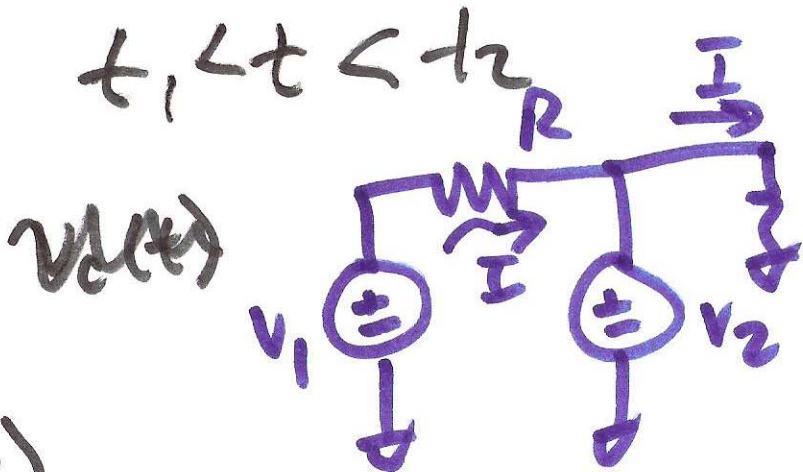

$$\frac{I_0 \cdot L}{V_s} = t_1$$

diode shuts off

$$V_1 - IR - V_2 = 0$$

2)

$$t_1 < t < t_2$$

$$v_c(t) = V_s - L \frac{di_c}{dt}, \quad i_c(t) = i_L(t) - I_0$$

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

$$\frac{dv_c(t)}{dt} = -L \frac{d^2 i_c}{dt^2} = \frac{i_c(t)}{C}$$

$$L \frac{d^2 i_c}{dt^2} = \frac{I_0 - i_c}{C}$$


$$\frac{d^2 i_c(t)}{dt^2} + \frac{i_c(t)}{LC} = \frac{I_0}{LC}$$

3)

$$i_L(t) = I_0 + \frac{V_s}{Z_0} \sin \omega_0 (t - t_1)$$

$$Z_0 = \sqrt{\frac{L}{C}} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$
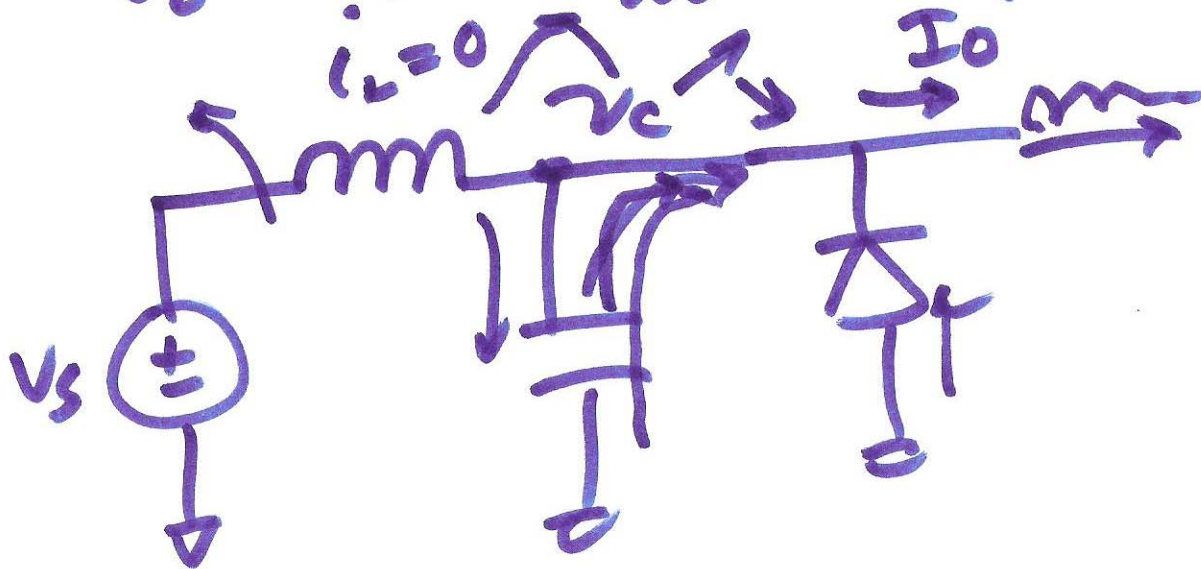
$$t_2 - t_1 = \frac{1}{\omega_0} \sin^{-1} \left(\frac{-I_0 Z_0}{V_s} \right)$$




4)

$t_2 < t < t_3$

CAP discharges

diode off

$t_3 \rightarrow$ diode on!

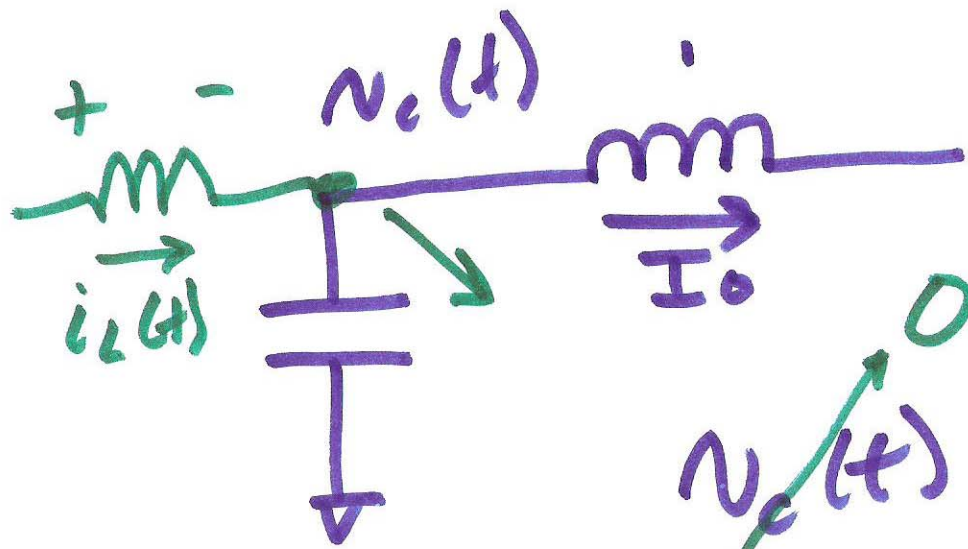

$$v_c(t) = \frac{1}{C} \int_{t_2}^{t_3} i_L(t) \cdot dt + v_c(t_2)$$

$$v_c(t) = V_s - L \cdot \frac{di_L}{dt}$$


$$= -\frac{I_o}{C} (t_3 - t_2) + v_c(t_2)$$

$$t_3 - t_2 = \frac{v_c(t_2) \cdot C}{I_o} \quad \frac{L \cdot \sqrt{L}}{\sqrt{L} \cdot \sqrt{L}}$$

$$= \frac{C V_s}{I_o} \left(1 - \frac{L \omega_0}{Z_0} \cos(\omega(t - t_1)) \right)$$

5)


$t_2 < t < t_3$

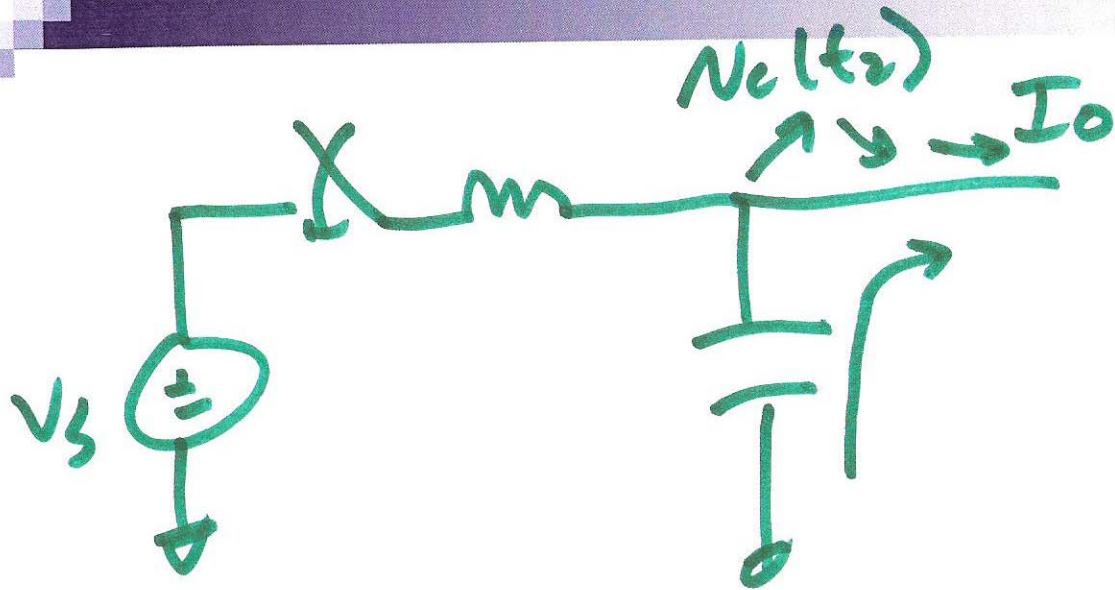

$$v_c(t_2) = v_s - L \frac{di_L}{dt}$$

$$v_s - L \left(\frac{v_s \omega_0}{Z_0} \cos(\omega_0(t-t_1)) \right)$$

6)

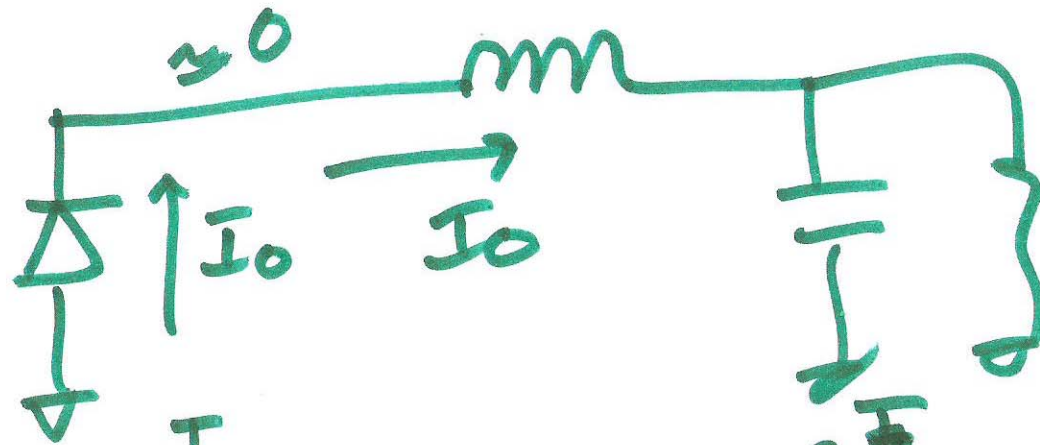

$$\mathcal{E}_s = \int_0^T P_s(t) dt = V_s \int_0^T i_L(t) \cdot dt$$



$$\mathcal{E}_L = \int_0^T P_o(t) \cdot dt = V_o \cdot I_o \cdot T = \frac{V_o \cdot I_o}{f}$$

$$\int_0^T i_L(t) dt = \int_0^{t_1} \frac{V_s \cdot t}{L} \cdot dt + \int_{t_1}^{t_2} \left(I_o + \frac{V_s}{Z_o} \sin \omega(t-t_1) \right) \cdot dt$$

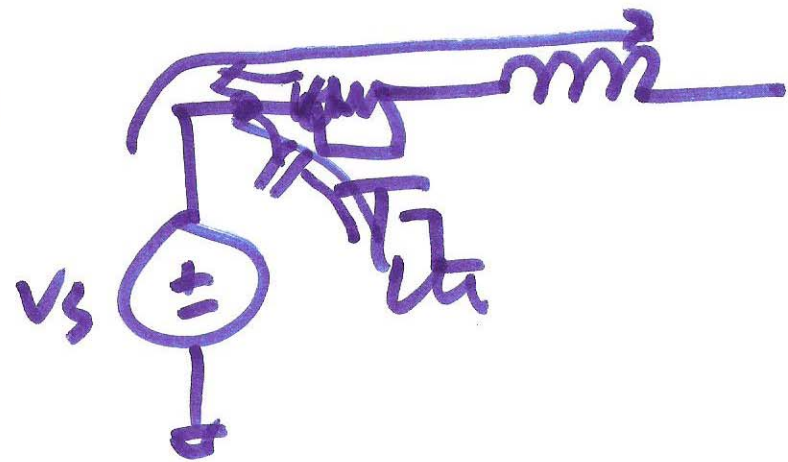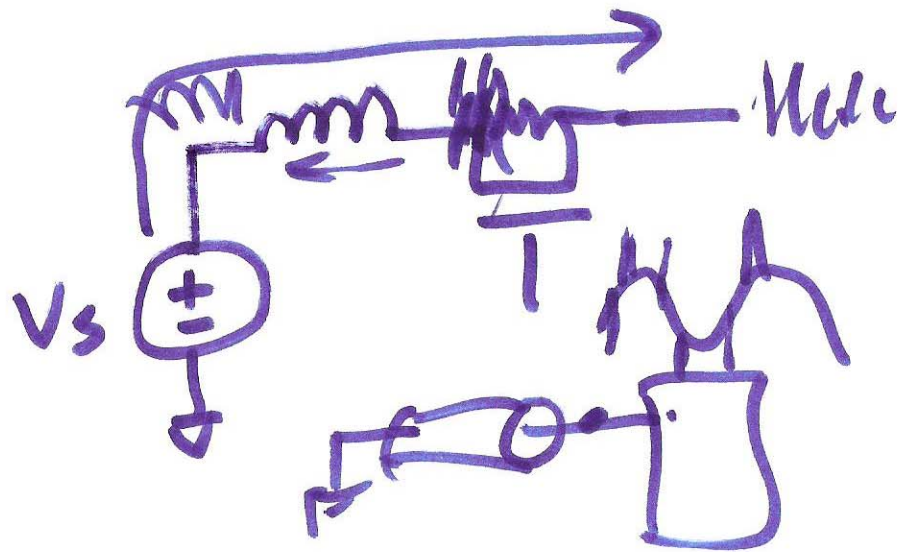
7)

$$V_o = V_s \cdot f_s \left[\frac{t_1}{2} + (t_2 - t_1) + \frac{V_s C_r}{I_o} \right]$$

$$\left[1 - \cos(\omega_o (t_2 - t_1)) \right]$$



How to measure zero current

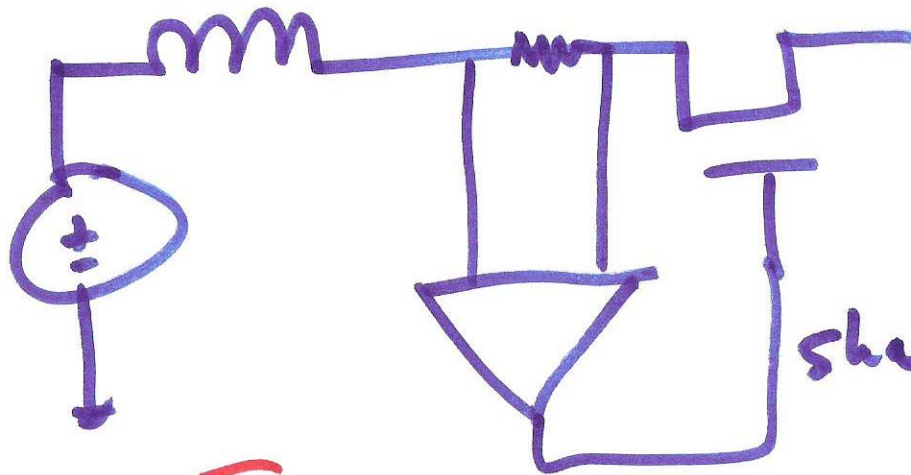

zero ~~current~~ voltage switching

$$V_0 = V_s f_s \left[\frac{t_1}{2} + (t_2 - t_1) + (t_3 - t_2) \right]$$

ZVS
ZFS
↑
field

9)