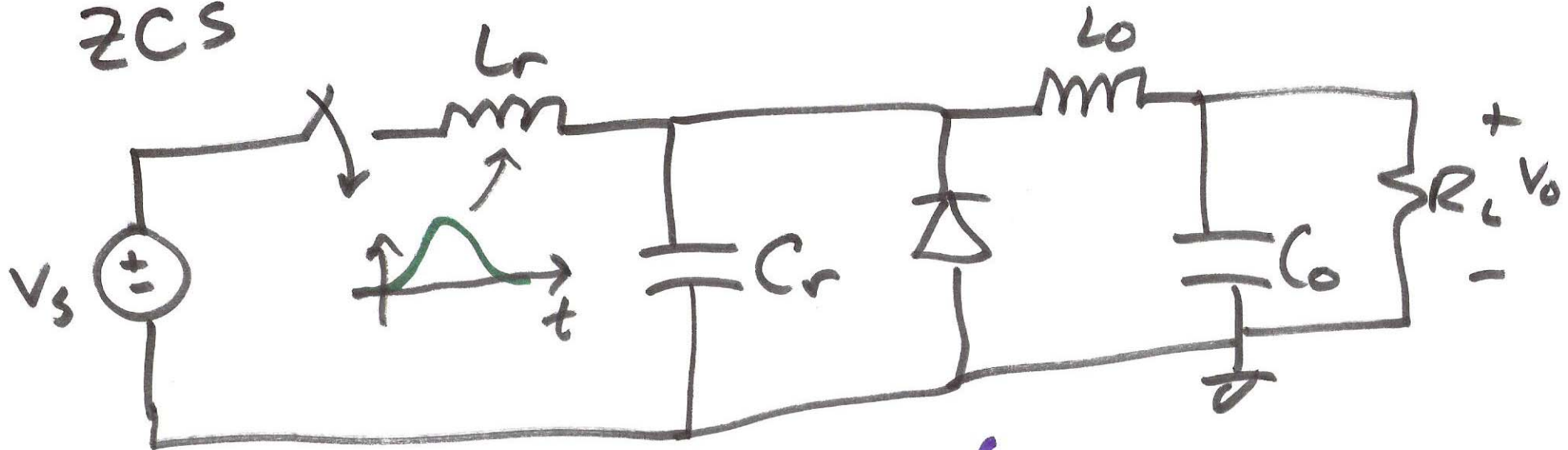



OCT. 4, 2011

Lecture

ZCS




ZVS

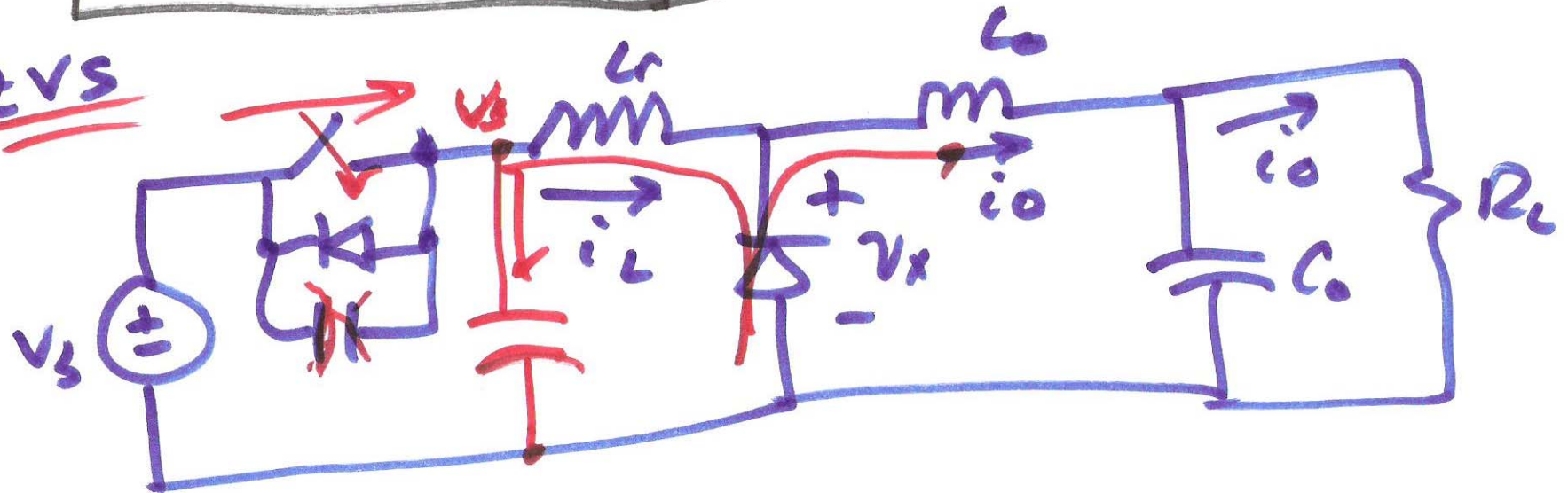

1)

# Buck converter

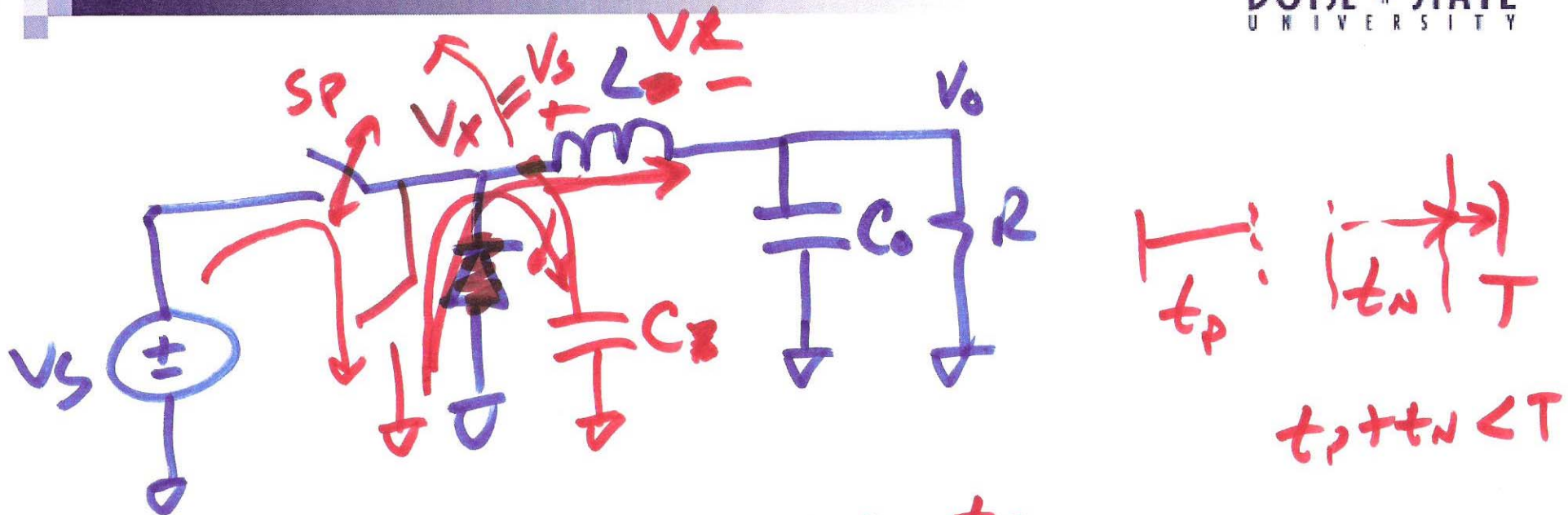

$S_P$  - closed switch  $t_p$   


$$\frac{V_s - V_o}{L} = \frac{\Delta i_L}{t_p}$$

$S_N$  - switch closed  $t_n$   

$$\frac{0 - V_o}{L} = \frac{\Delta i_L}{t_n}$$

2)

# Buck ZVS Converter

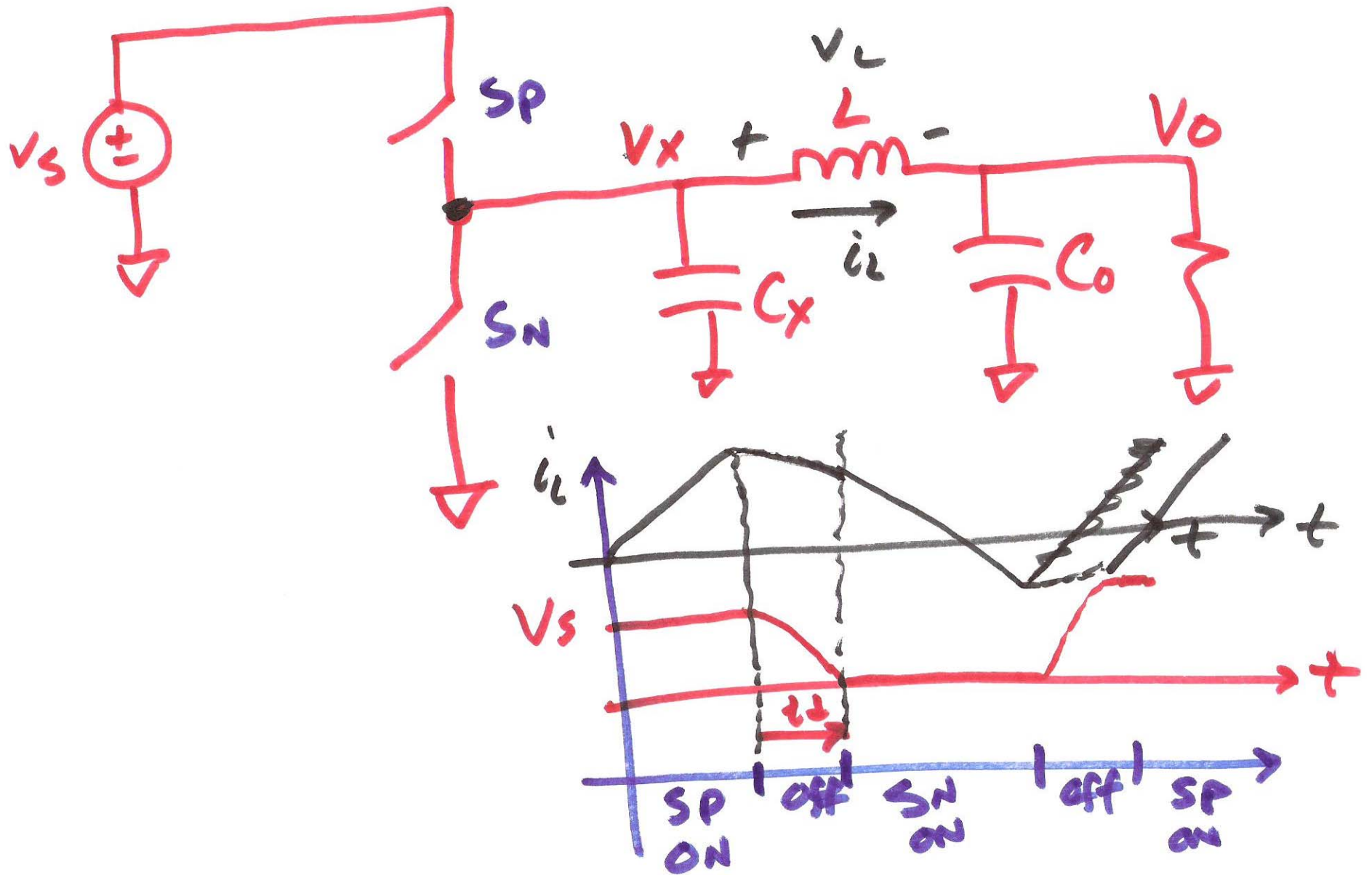


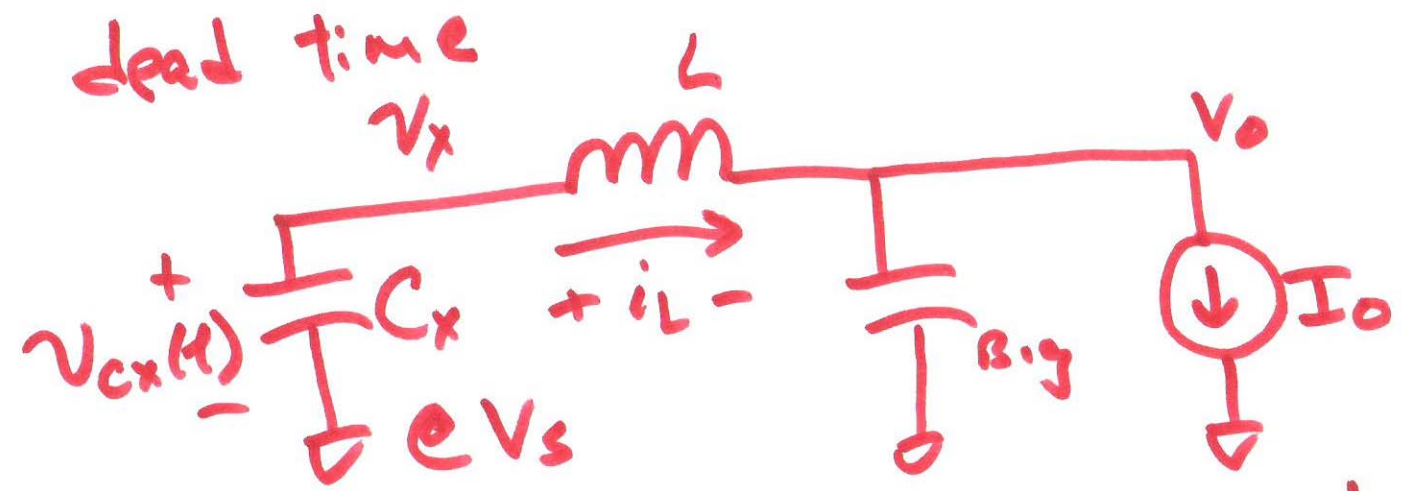3)



\* SP is closed

$$\frac{V_s - V_o}{L} = \frac{\Delta I_L P}{t_P}$$



$$v_{cx}(t) = L \frac{di_L}{dt} + v_o = \frac{1}{C} \int_0^t i_L \cdot dt + v_c(t)$$

$$\frac{dv_c}{dt} = L \frac{di_L}{dt^2} = \frac{i_L L}{C}$$


4)

$$\left\langle \frac{d^2 i_c}{dt^2} \right\rangle = \frac{1}{C}$$


$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{T}$$

$$L = C = 10^{-6}$$

$$f_0 = 159 \text{ kHz}$$

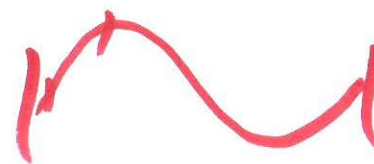

~~4.5~~  
6.284 s

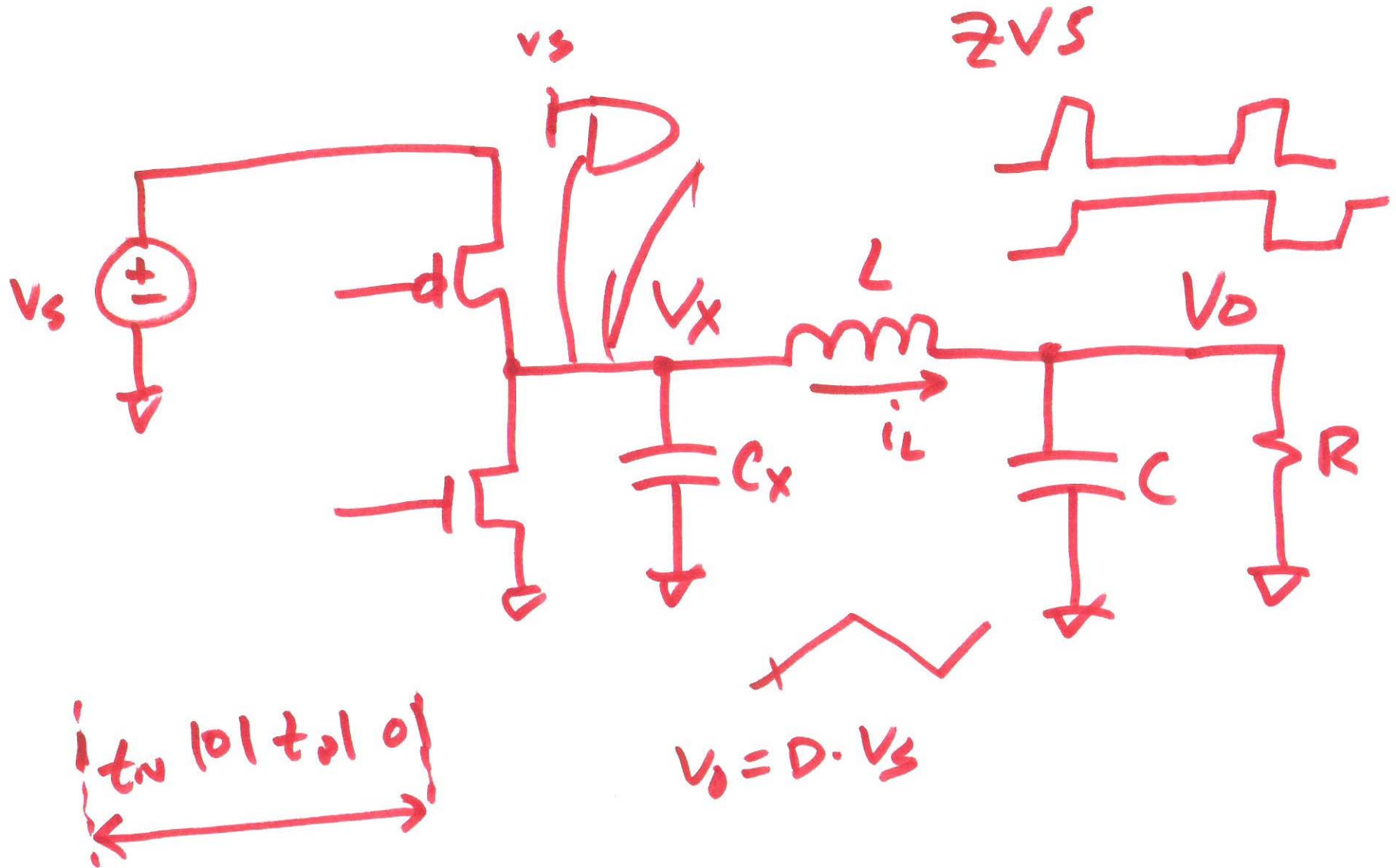

6)