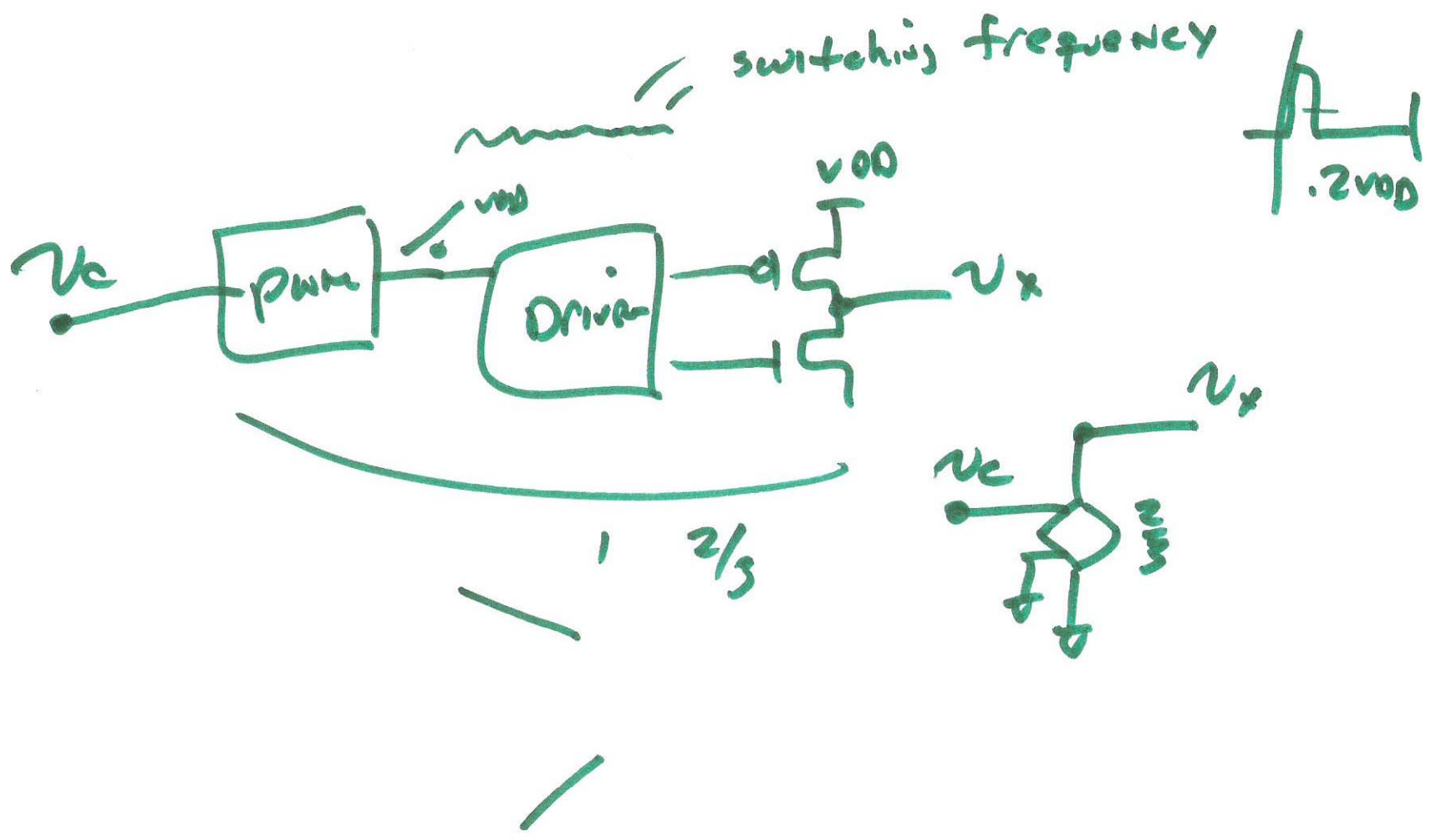


NOV. 1, 2011

11/1/11



## Lecture 20



11

Switching frequency  $\approx 2 \text{ MHz}$

$$f_0 = 1000 \text{ kHz} = \frac{1}{2\pi\sqrt{LC}}$$

$$f_{sw} = 15.9 \text{ kHz}$$

$$\frac{1}{2\pi RC_1}$$

$$(RC_1)^{-1} = 100 \cdot 10^3$$

$$RC_1 = \frac{10^{-5}}{\underline{\underline{\quad}}}$$

$$C_1 = 1 \text{ nF}$$

$$R_1 = \frac{10^{-5}}{10^{-9}} = 10^4$$

$$2) C_2 = \frac{C_1}{10} = \frac{100 \text{ pF}}{\underline{\underline{\quad}}} = \underline{\underline{10 \text{ k}}}$$

$$\sqrt{LC} = 6.28 \cdot 159 \cdot 10^3$$

$$\sqrt{LC} = 10^6$$

$$LC = 10^{12}$$


$$L = \frac{100 \text{ nH}}{10^{-7}}$$

$$C = \frac{10^{12}}{10^{-7}} = \underline{\underline{10 \text{ pF}}}$$


$$f_2 = \frac{1}{2\pi R_2 \cdot 10^{-9}} = 159 \text{ kHz}$$

$$\frac{1}{R_2 \cdot 10^{-9}} = 10^6$$
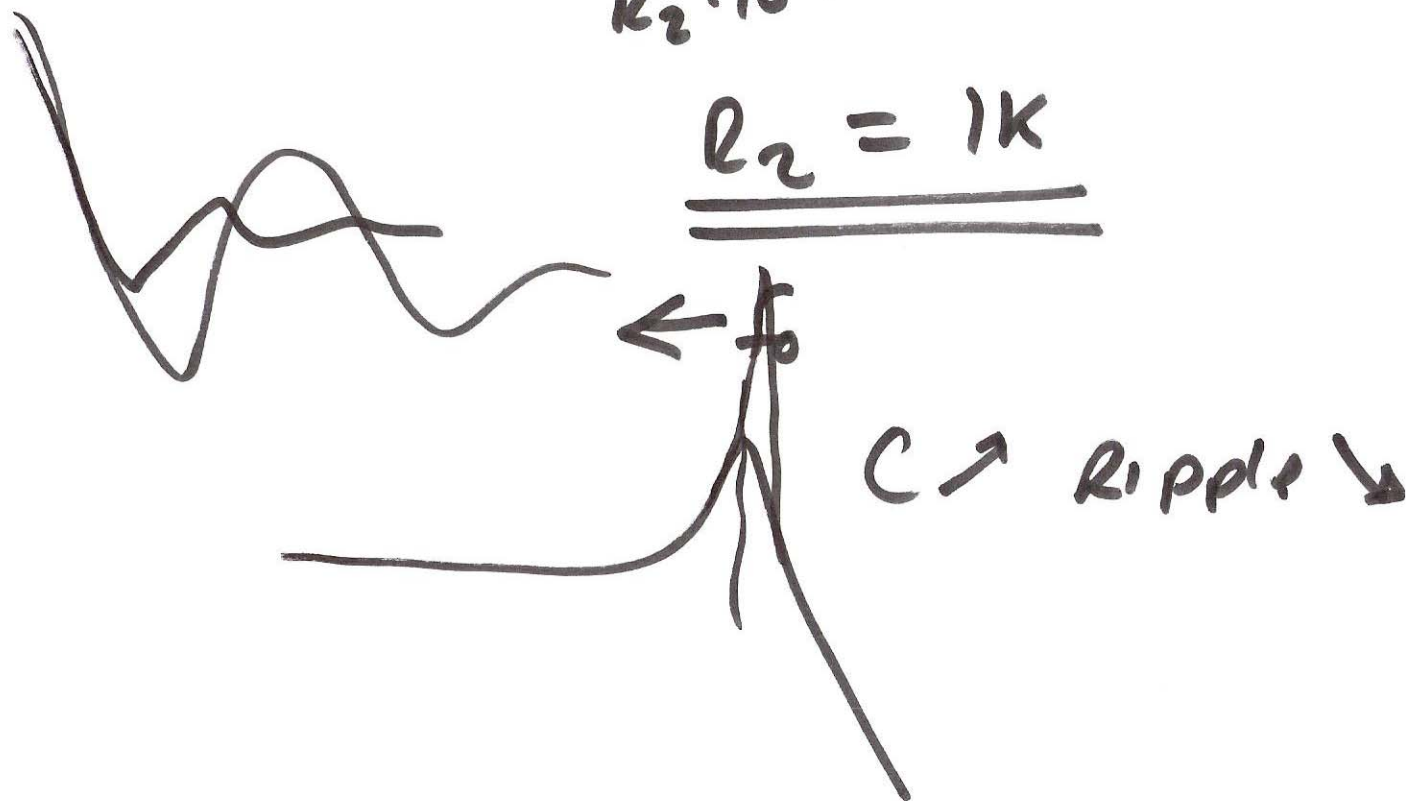
$$\underline{\underline{R_2 = 1 \text{ k}}}$$





3)

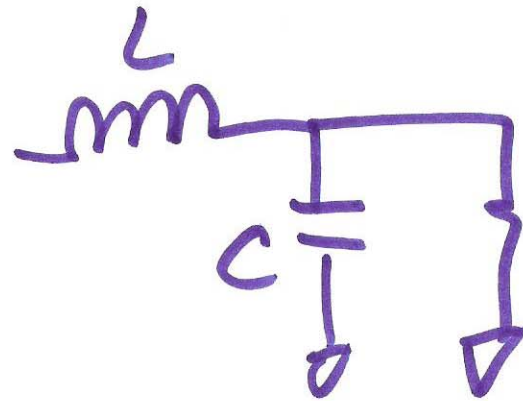

$$Q = R \cdot \sqrt{\frac{C}{L}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

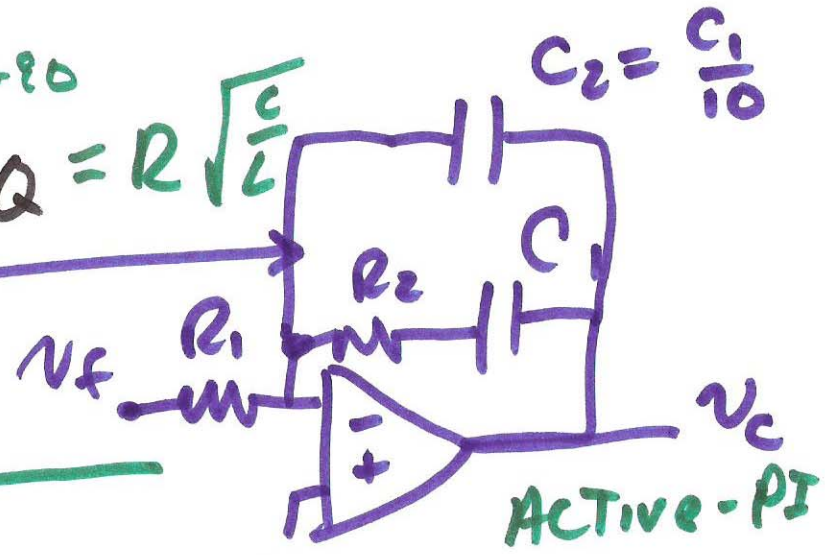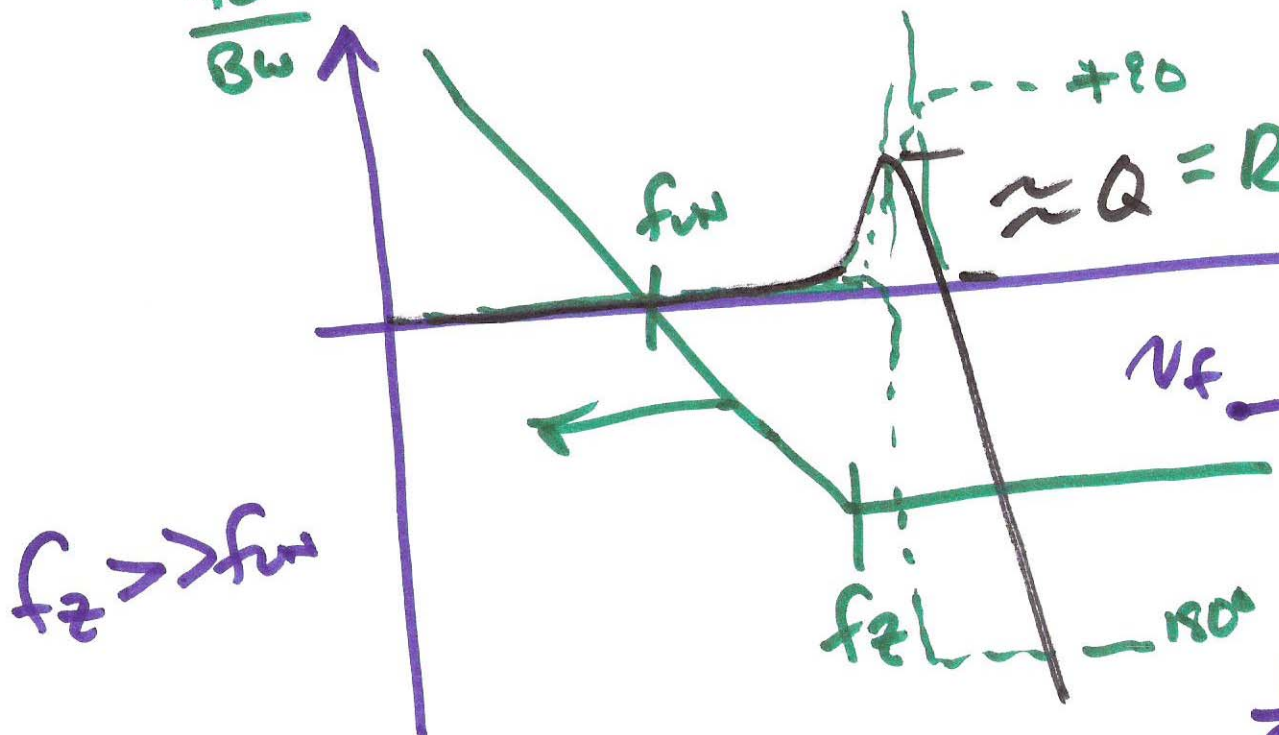

$$= \frac{\frac{1}{sC_1} + R_2}{R_1} = \frac{1 + sC_1R_2}{sC_1R_1}$$

4)

$$f_z = \frac{1}{2\pi C_1 R_2}$$