

NOV. 10, 2011 Lecture 22

Review for Exam


ON Tuesday, Nov. 15!

Zero voltage switching

Zero current switching

How is the resonant freq. related to the dead time between on switches?

→ ZVS ←
ZCS


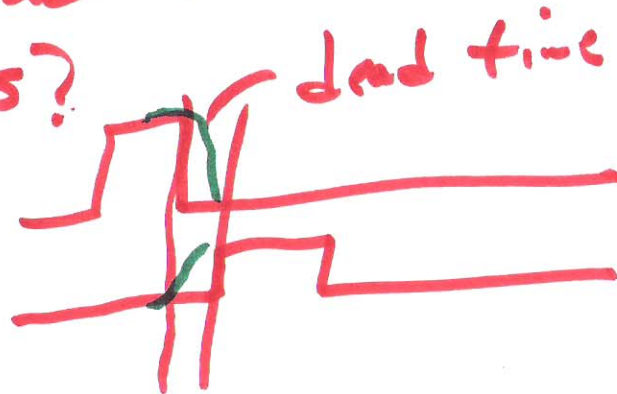


Bode plots

$$\frac{1}{s^2 + x \cdot s + y}$$

energy stored


energy lost

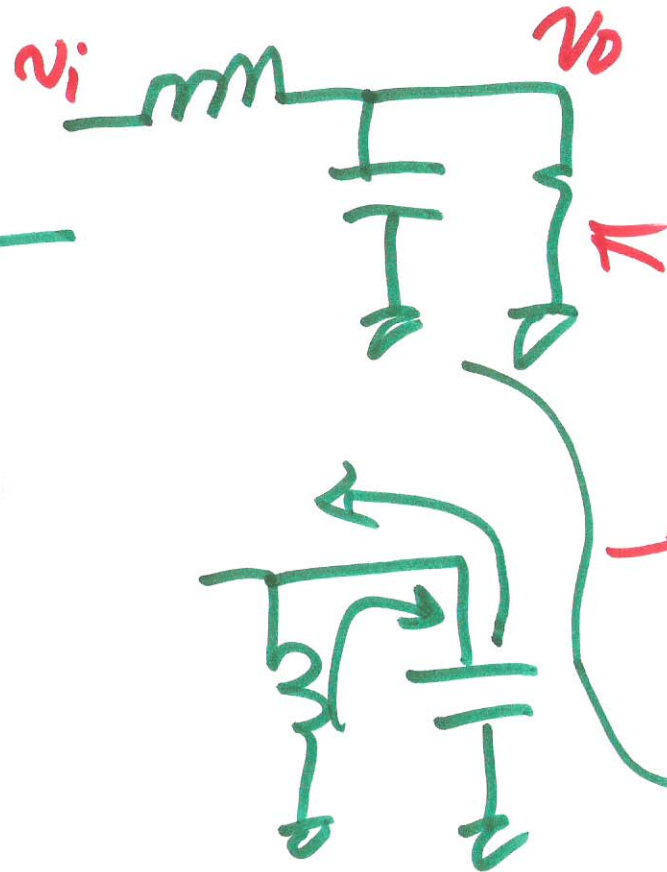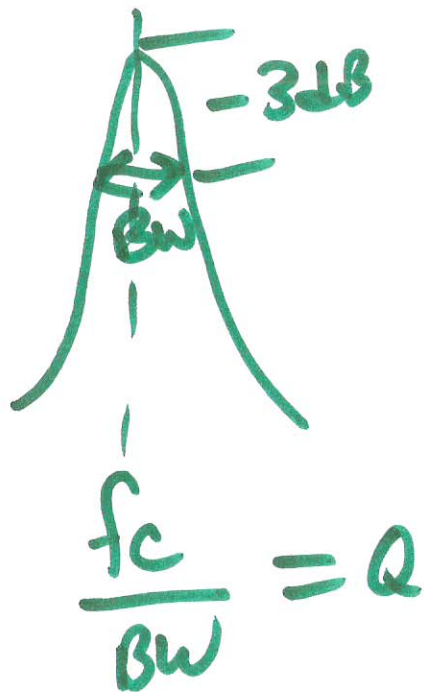



Where are the poles?

freq. $Q = R\sqrt{\frac{C}{L}}$

$f_0 = ?$
 $Q = ?$

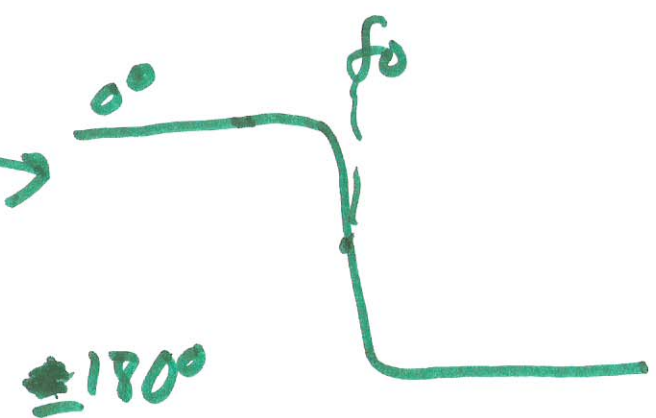

2)

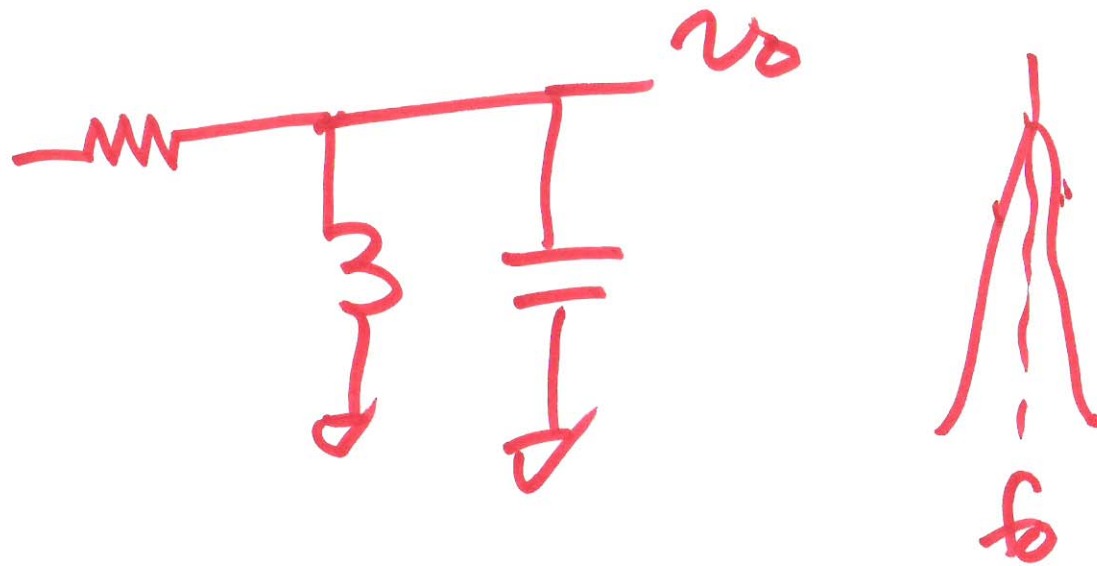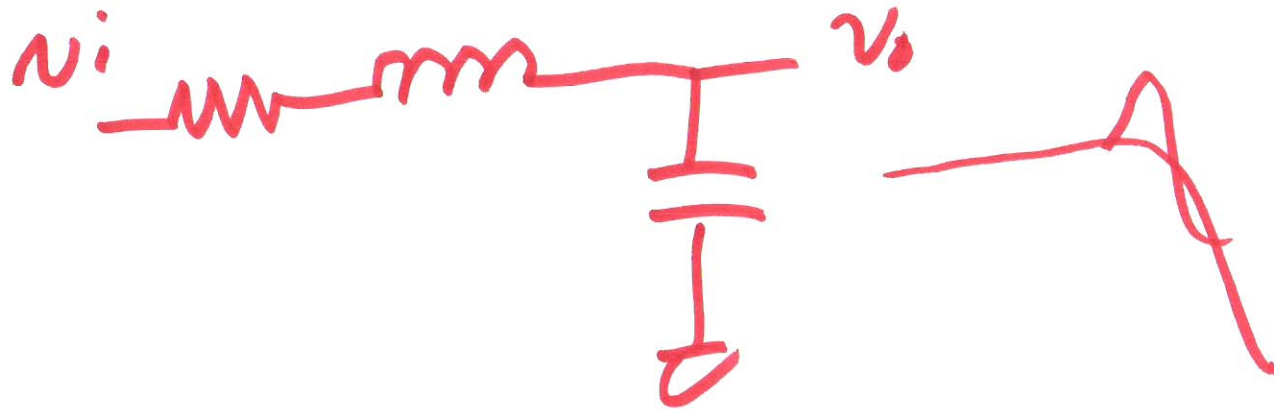

3)



Active - PI filter

$$\frac{1}{2.5 \cdot \frac{2}{3}} = \text{Gain}$$

$$\frac{1}{3.5 \cdot \frac{2}{3}} = \text{Gain}$$

1.25
2. 1.22

$$K < 1$$

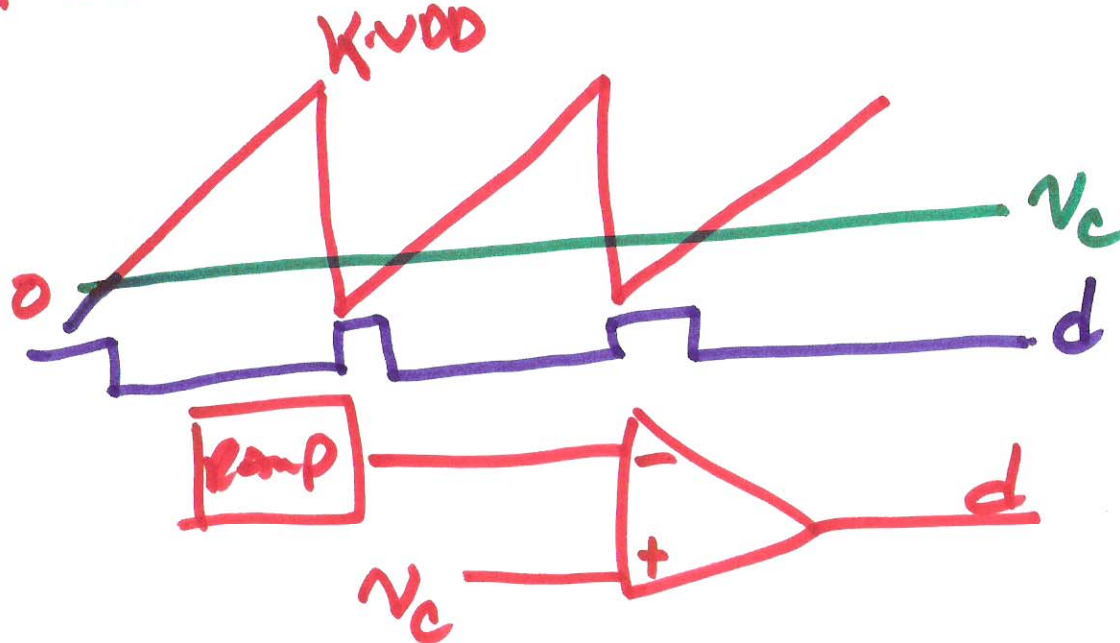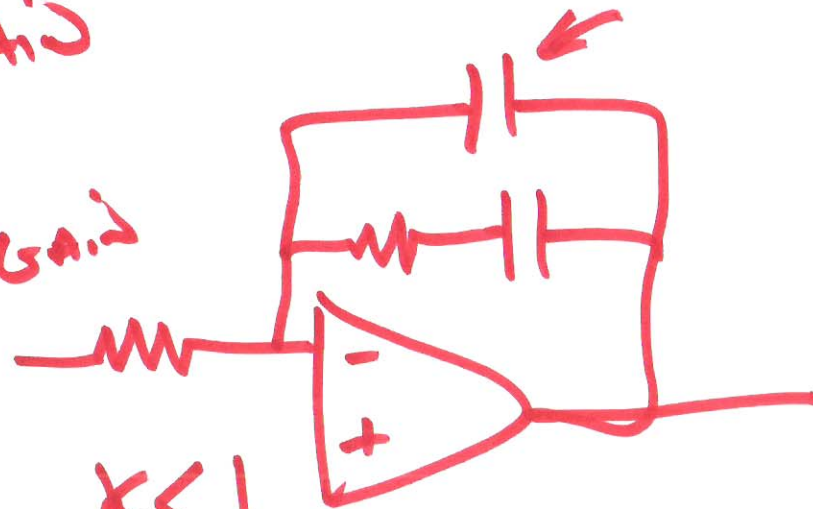

$$\frac{d}{V_c} = \text{Gain}$$


$$d = \text{Gain} \cdot V_c$$

$$V_c = K \cdot V_{DD}$$

$$d = 1 = \text{Gain} \cdot K \cdot V_{DD}$$

$$\text{Gain} = \frac{1}{K \cdot V_{DD}}$$

4)

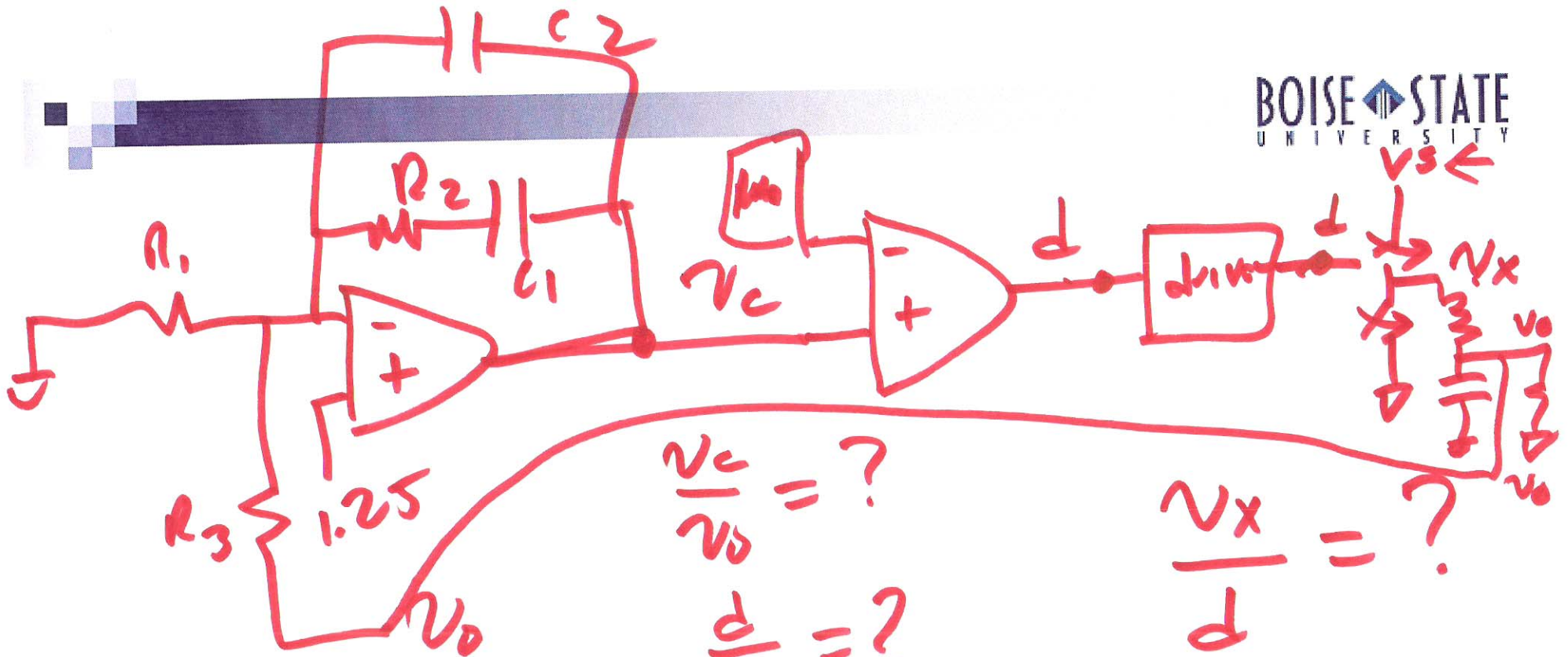

$$\frac{V_c}{V_o} = ?$$

$$\frac{d}{V_o} = ?$$

$$\frac{d}{V_o} = ?$$

$$\frac{V_o}{V_x}$$

$$\frac{V_x}{d} = ?$$

$$d = 0 \text{ or } V_{DD}$$

$$d = 0, V_x = 0$$

$$d = V_{DD}, V_x = V_s$$

$$\boxed{\frac{V_x}{d} = \frac{V_s}{V_{DD}}}$$

transfer function
mag & phase

Bode response

$$f_w = ? \quad f_o = ?$$


$$f_p = ? \quad f_z = ?$$

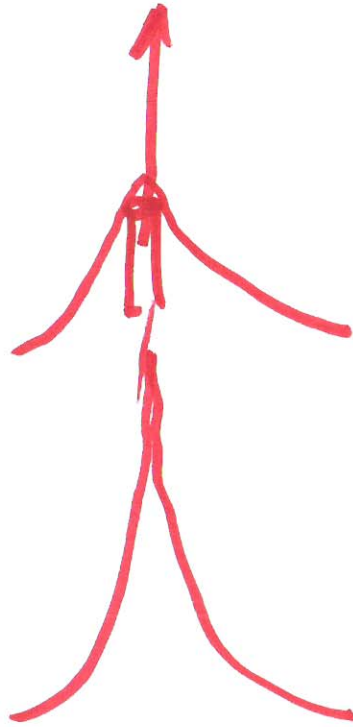5)

$$s = \sigma + j\omega$$




$$\frac{X}{0 + sR_1C_1} = \frac{X}{0 + j \cdot 2\pi f \cdot R_1C_1}$$



1.25

$$0 = 2\pi f R_1C_1$$


$$f_p = 0$$

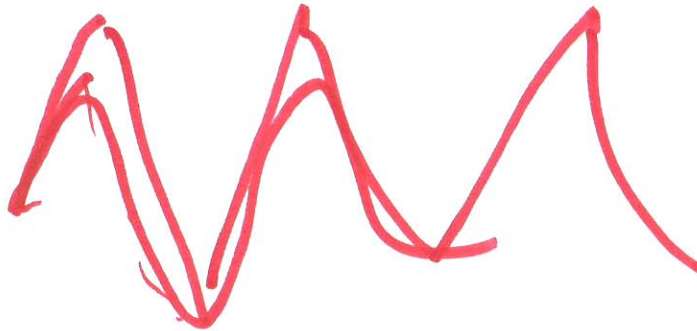

$$\frac{1}{\sqrt{12+12}}$$

$$\frac{1}{0} = \frac{1}{\sqrt{2}} = 0.707$$
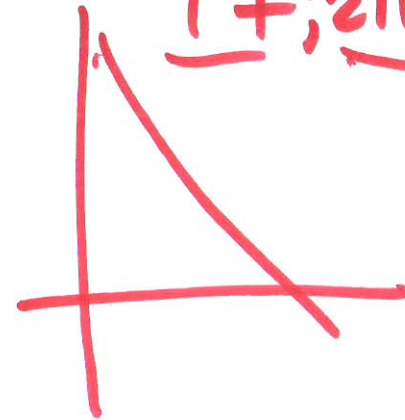
$$\frac{1}{1 + sC_1R_2} = \frac{1}{1 + j2\pi f C_1R_2}$$



$$2\pi f C_1R_2 = 1$$



$$f = \frac{1}{2\pi C_1R_2}$$

$$\frac{1}{2\pi C_1R_2}$$

b)

Buck \rightarrow Review, ZVS

Boost \rightarrow

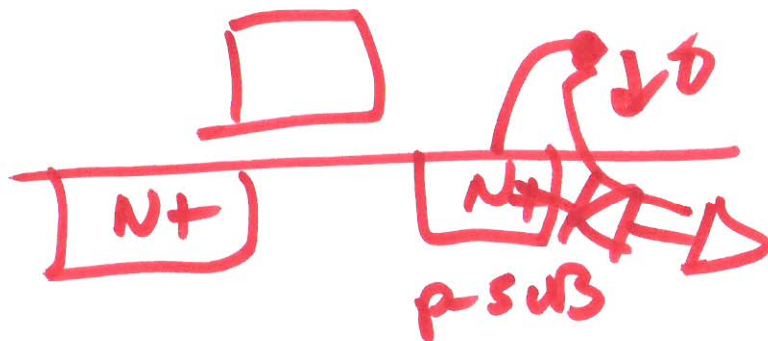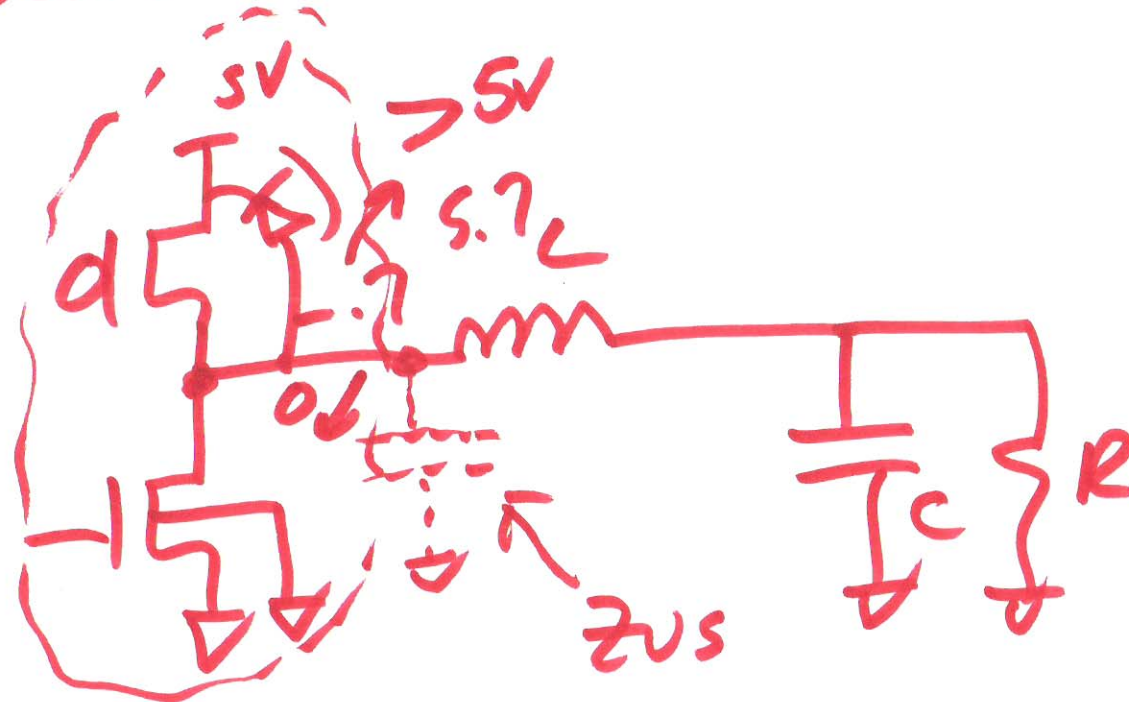

7)