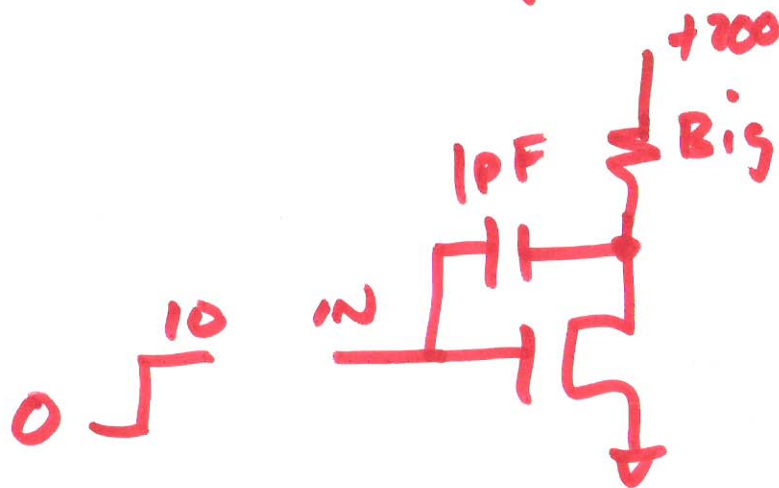


## Lecture 27

Dec. 8, 2011

\* operation & schematics of basic charge pumps

\* understand power MOSFET capacitances especially Miller Capacitance




How much charge does the input supply?  $Cv=Q$   
What is the input capacitance?

1)

# Driving Power MOSFETs

see lecture

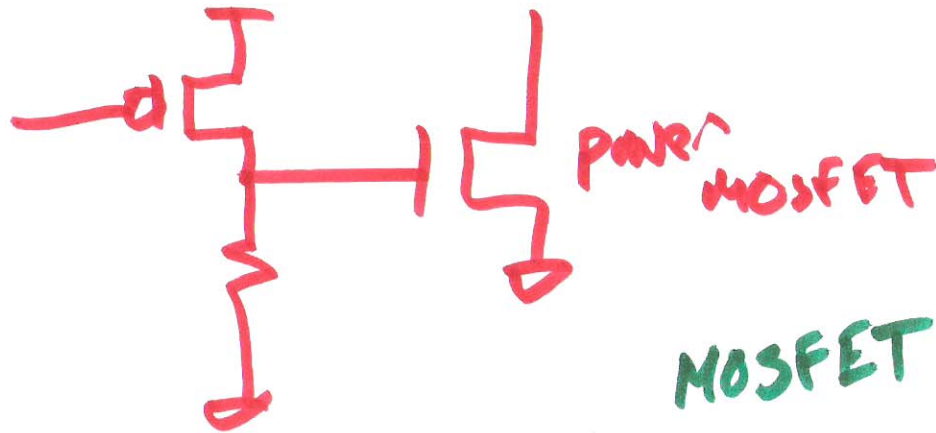

## MOSFET CAPACITANCES


Model an SCR  
using BITS

discuss its operation

$C_{iss}$   
 $C_{oss}$  How meas.

$C_{oss}$

$$C_{iss} = C_{gd} + C_{gs}$$

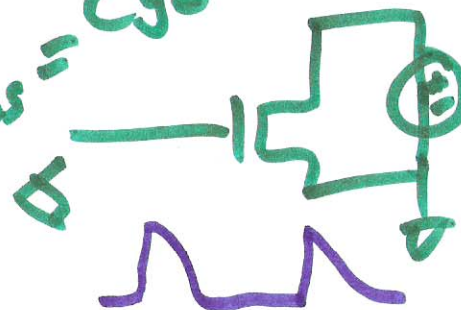

AC short.

Use in a light dimmer

2)

Triac operation

its use in an application

Thyristor  $\left\{ \begin{array}{l} \text{SCR} \\ \text{TRIAC (ANTI-parallel} \\ \text{SCRs)} \end{array} \right.$

study your H.W.s, Tests, And  
your project (!)


ZVS, ZCS, Buck, Boost,

discontinuous current operation,  
ripple in the inductor (max, min, etc.)

OUTPUT voltage ripple.

$V_o = DV_s \rightarrow$  derive operation of  
converter

3)

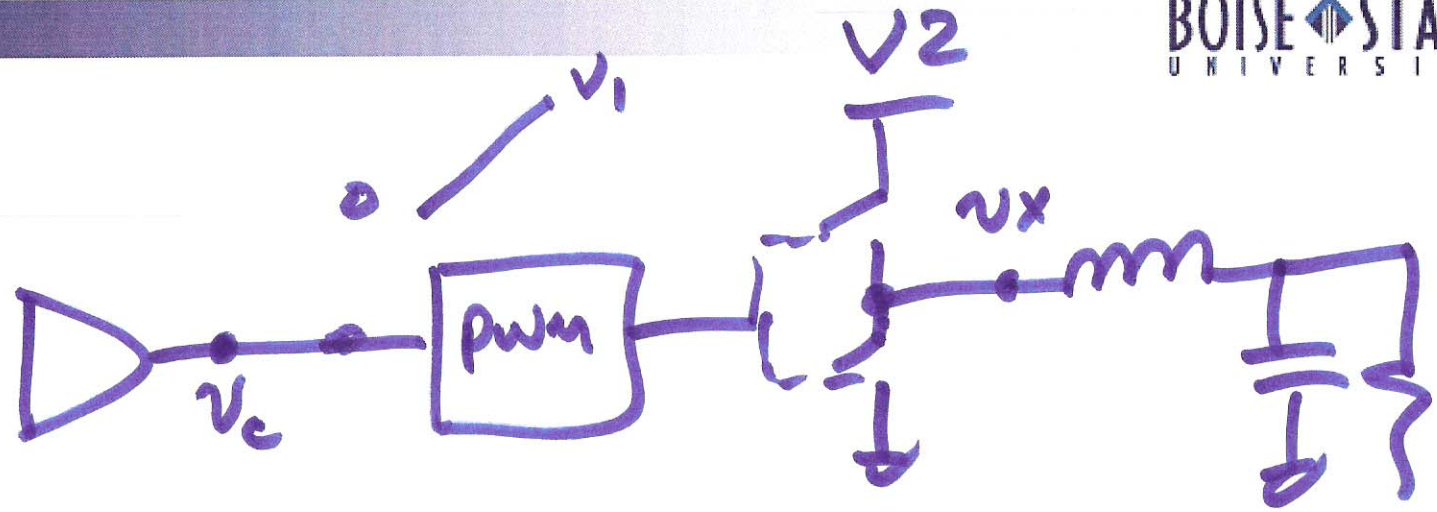

Modeling  
transformers  
with  
SPICE

$$\frac{v_x}{v_c} = ?$$

Reverse Recovery time?  
Storage time?

study the ch. 6 & ch. 2  
examples

4)

SEPIC operation