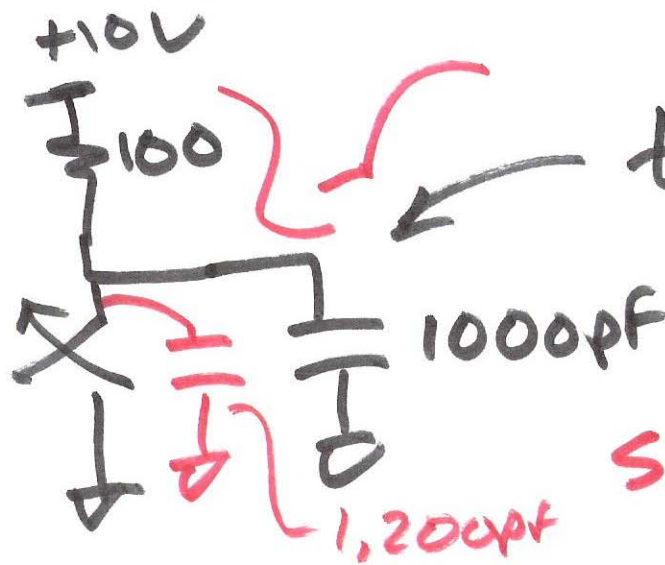



ECE 5/472 Power Electronics

Lecture 3 Aug. 30, 2011



$$t_r = 2.2RC = 220 \text{ ns}$$

Sim $\rightarrow t_r = 500 \text{ ns}$

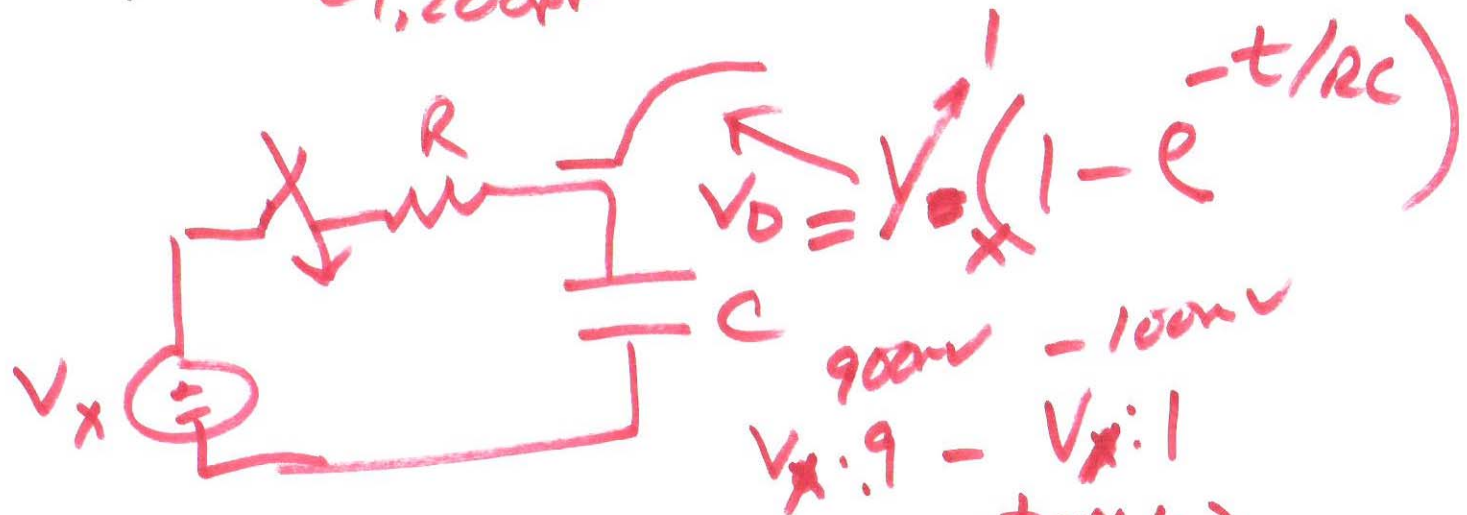

$$V_x \cdot 0.9 - V_x \cdot 0.1 = V_x (1 - e^{-t_{90\%}/RC}) - V_x (1 - e^{-t_{10\%}/RC})$$

$$V_x \cdot (0.9) - V_x (0.1) = V_x (1 - e^{-t_{90\%}/RC}) - V_x (1 - e^{-t_{10\%}/RC})$$

))


$$0.8 = -e^{-t/RC} + e^{-t/RC}$$

$$\ln 0.8 = \ln \left(e^{-t/RC} - e^{-t/RC} \right)$$

$$\ln \left(\frac{a}{b} \right) = \frac{\ln a}{\ln b} = \ln a - \ln b$$

$$\ln a \cdot b = \ln a + \ln b$$

2)

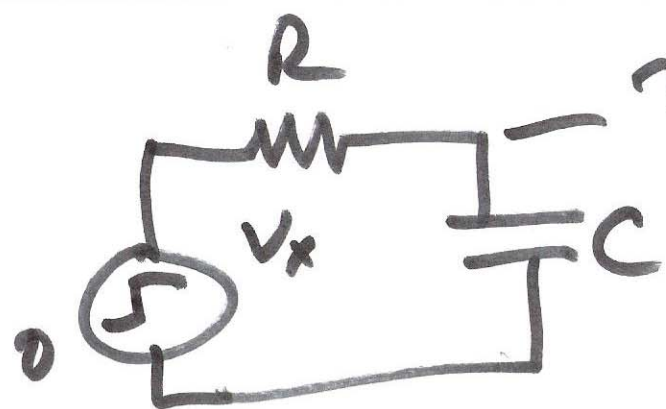

$$v_o(t) = V_x (1 - e^{-t/RC})$$

$$t_{90\%} - t_{10\%} = \text{rise time} = \underline{\underline{2.2 RC}}$$

$$0.9 V_x = V_x (1 - e^{-t_{90\%}/RC})$$


$$0.1 V_x = V_x (1 - e^{-t_{10\%}/RC}) \quad -2.3$$

$$+ 0.1 = e^{-t_{90\%}/RC} \rightarrow t_{90\%} = (\ln 10) RC$$

$$+ 0.9 = e^{-t_{10\%}/RC} \rightarrow t_{10\%} = (\ln 10) RC$$

3)

Buck Converter

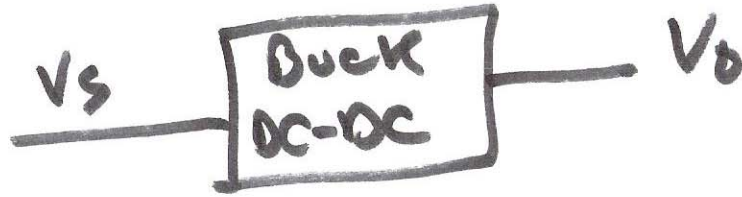


$$L \cdot \frac{di}{dt} = V$$

$$V_s > V_o$$


$$V_o = D \cdot V_s$$

$$\frac{V_s - V_o}{L} = \frac{di}{dt}$$

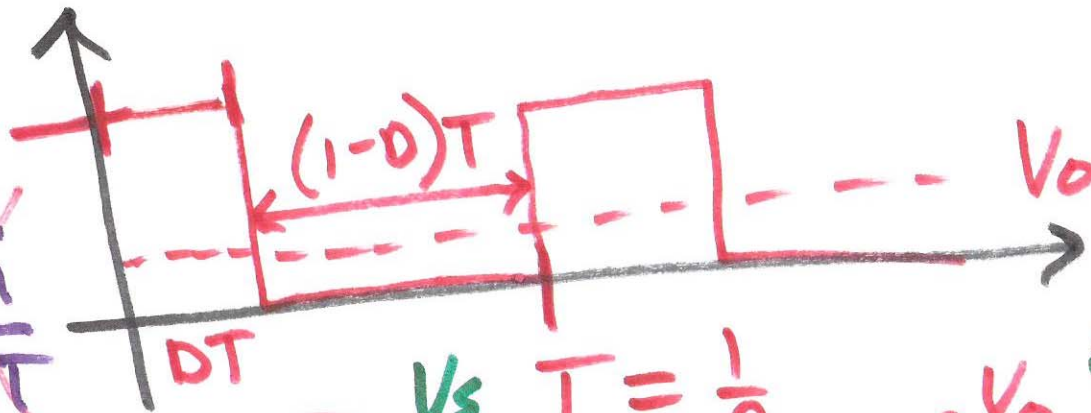


$$\Delta i = DT \cdot \frac{(V_s - V_o)}{L}$$

$$i_{avg} = \frac{V_o}{R_L}$$

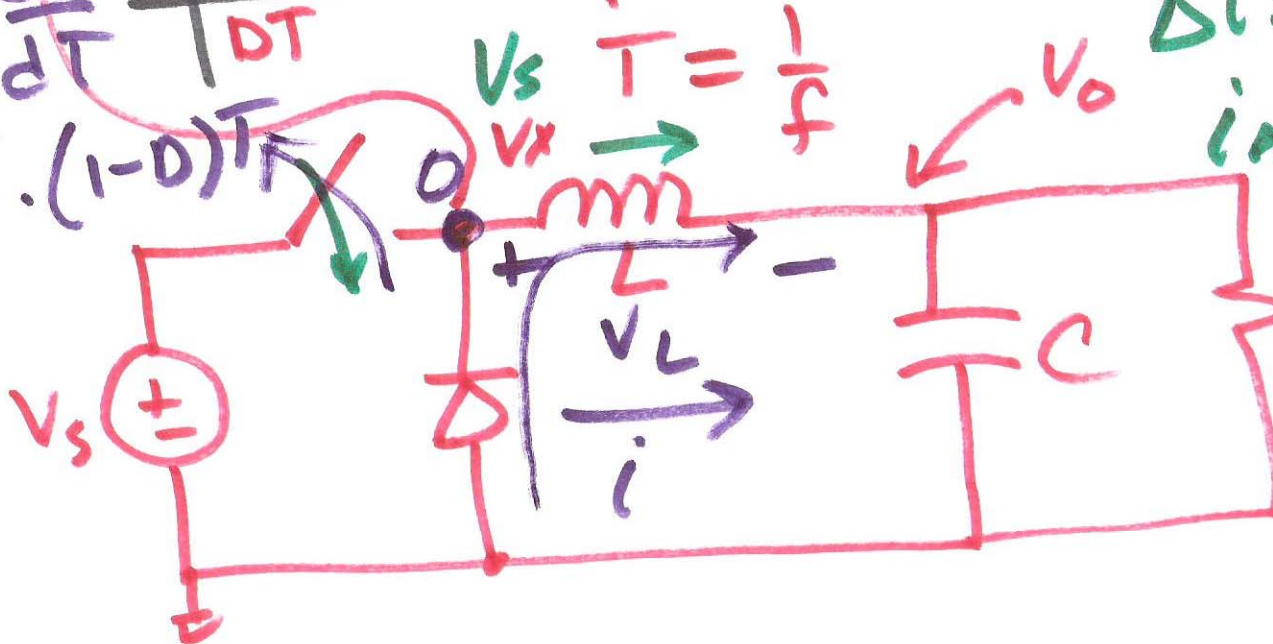

$$\frac{di}{dt} = \frac{V_o}{R_L}$$

4)

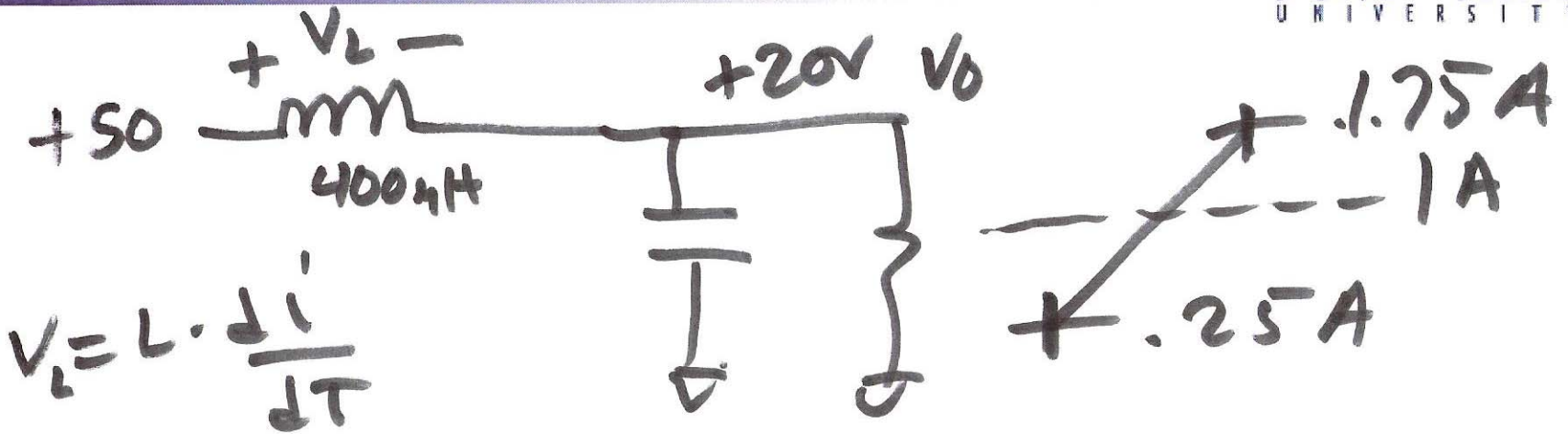

$$V_L = L \cdot \frac{di}{dt}$$

$$\frac{V_L - V_O}{L} = \frac{di}{dt}$$

$$\frac{50 - 20}{400m}$$

$$\frac{di}{dt} = \frac{1.5A}{20m}$$


$$\Rightarrow \Delta i = \frac{di}{dt} \cdot \Delta t$$

$$\Delta i = \frac{V_S - V_O}{L} \cdot \frac{D}{f}$$

$$= \frac{30}{400m} \cdot \frac{.4}{20K}$$

$$= \frac{12}{8} = \frac{3}{2} = \underline{\underline{1.5A}}$$

5)

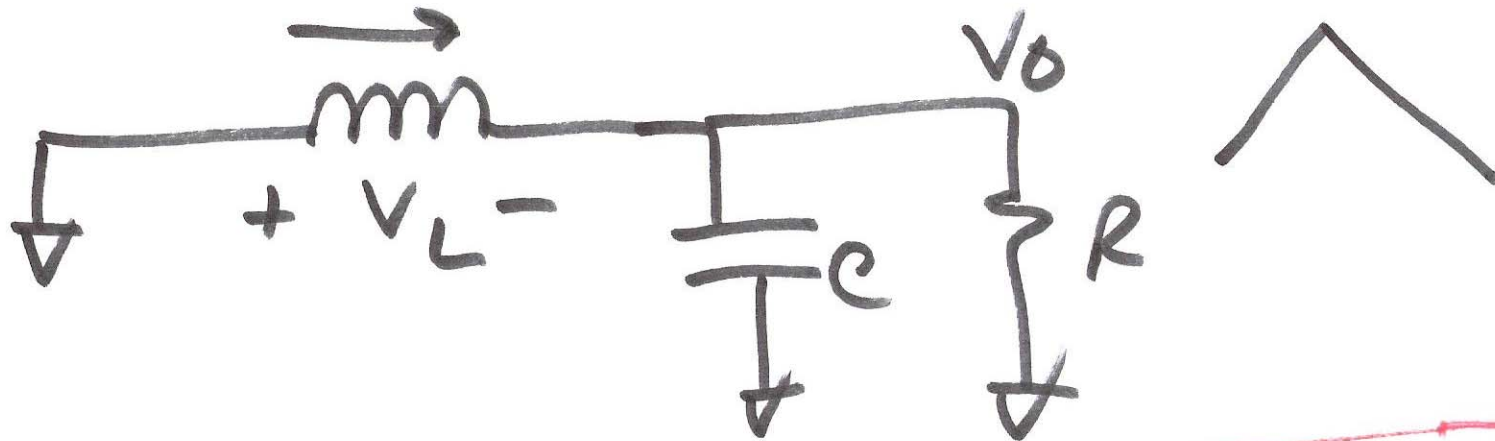

$$\frac{0 - v_O}{L} = \frac{di}{dt} \Rightarrow \Delta i = \frac{-v_O (1-D)}{fL}$$

$$\Delta i = \frac{-20}{400\mu} \cdot \frac{0.6}{20K} = \frac{-12}{8} = -1.5A$$

$$\frac{di}{dt} = \frac{-1.5A}{30\mu}$$


6)

$$\frac{V_s - V_o}{L} \cdot \frac{D}{f} - \frac{V_o}{L} \frac{(1-D)}{f} = 0$$

$$D(V_s - V_o) + D V_o - V_o = 0$$

$$D V_s = V_o$$
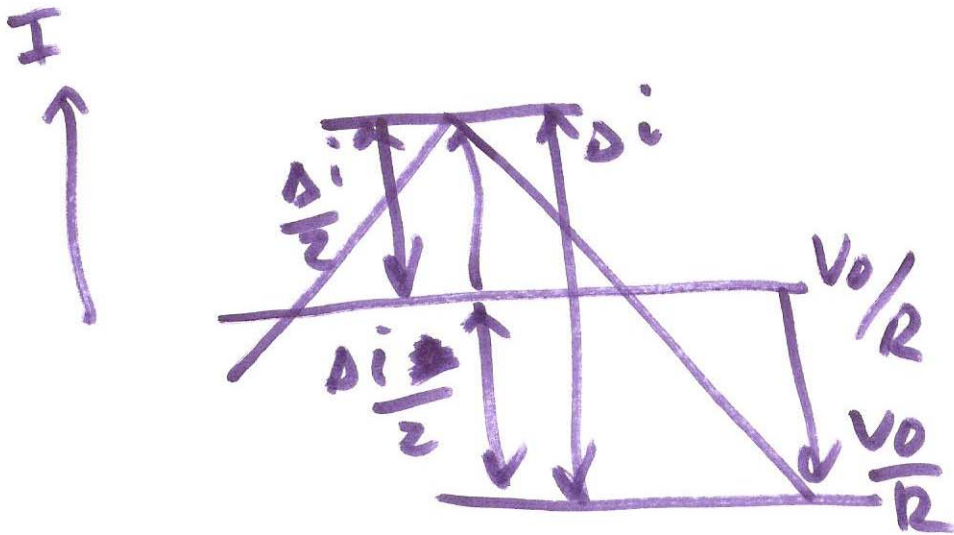
$$\frac{V_o}{R} = \frac{1}{2} D i_a = \frac{V_s - V_o}{2 L_{min}} \cdot \frac{D}{f}$$



8)

$$V_s \cdot D = V_o$$


$$V_s = \frac{V_o}{D}$$

$$\frac{V_o}{R} = \frac{V_s - V_o}{2L_{min}} \cdot \frac{D}{f}$$

$$V_o = V_s$$




$$\frac{1}{R} = \frac{1-D}{2L_{min}f}$$

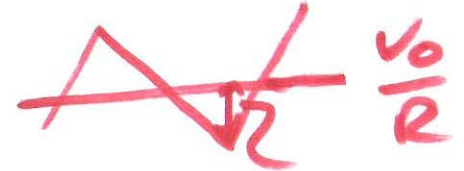

$$\frac{di}{dt} = \frac{V}{L}$$


$$L_{min} = \frac{R \cdot (1-D)}{2f}$$

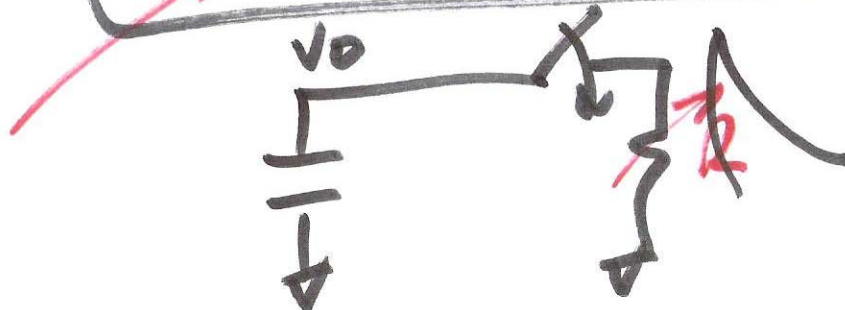

$$R \downarrow$$


$$\gamma = RC$$

9)

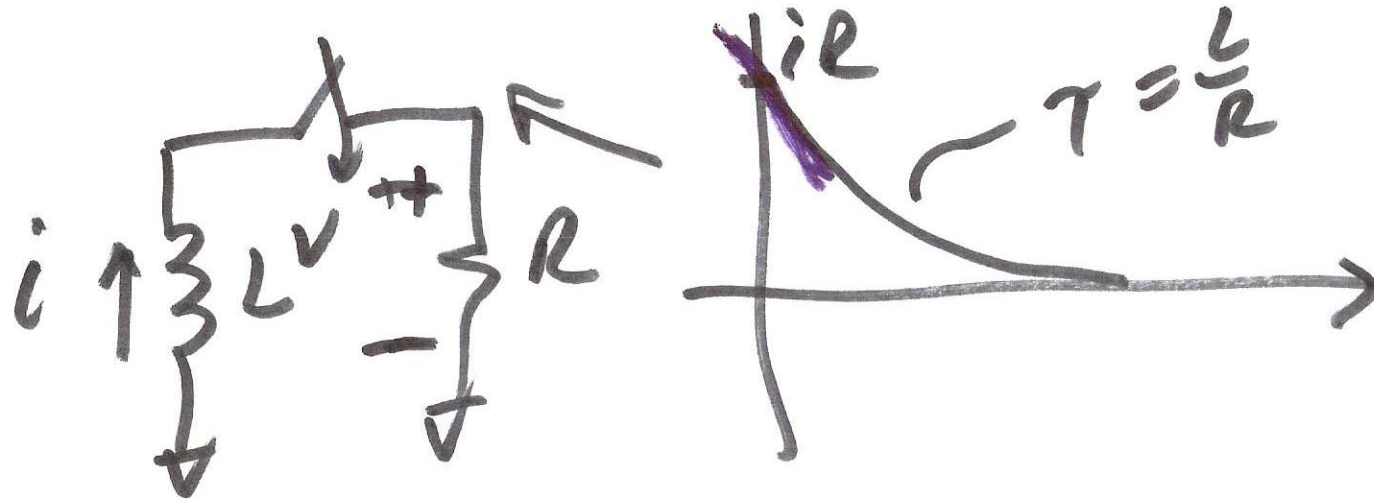

$$\frac{v}{L} = \frac{di}{dt} \quad i^2 R = P$$

10)

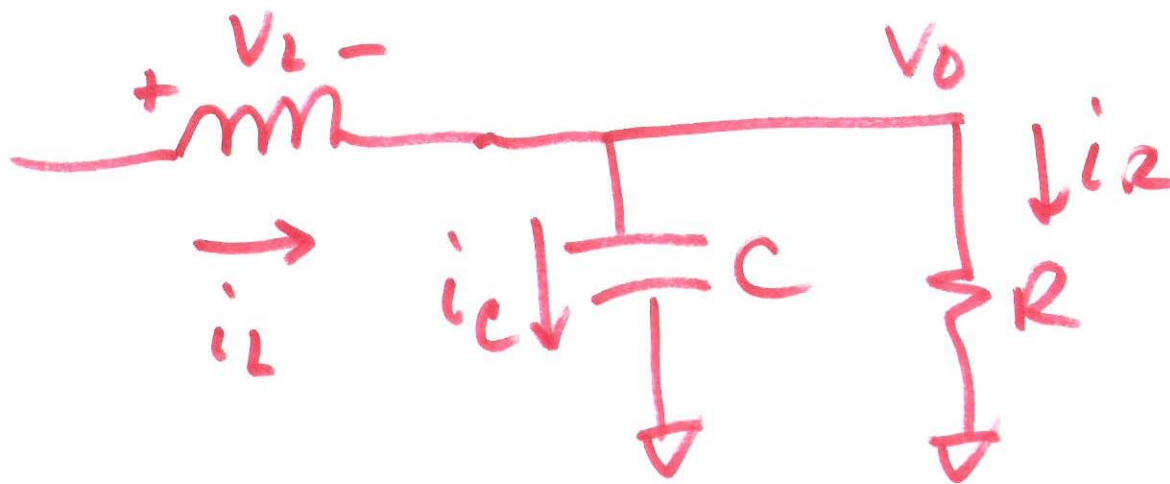

$$i_C = i_L - i_R$$

11)