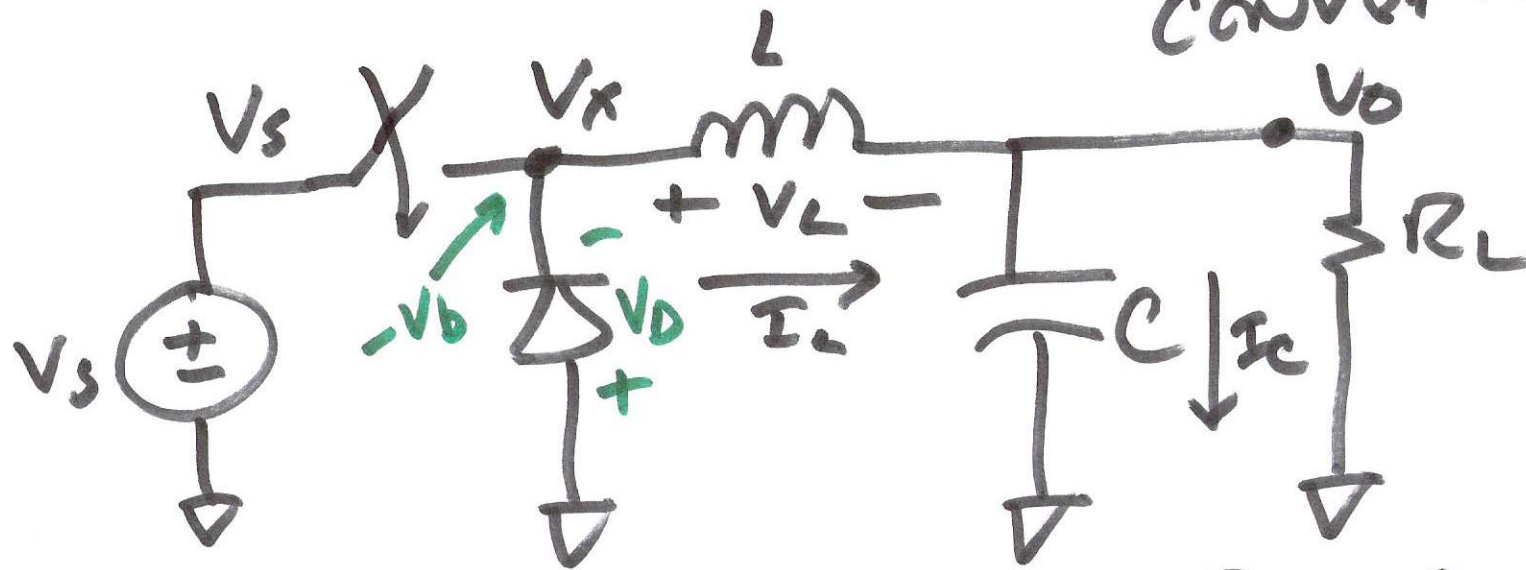


Lecture 4


Sept. 1, 2011

Design of

Buck converters



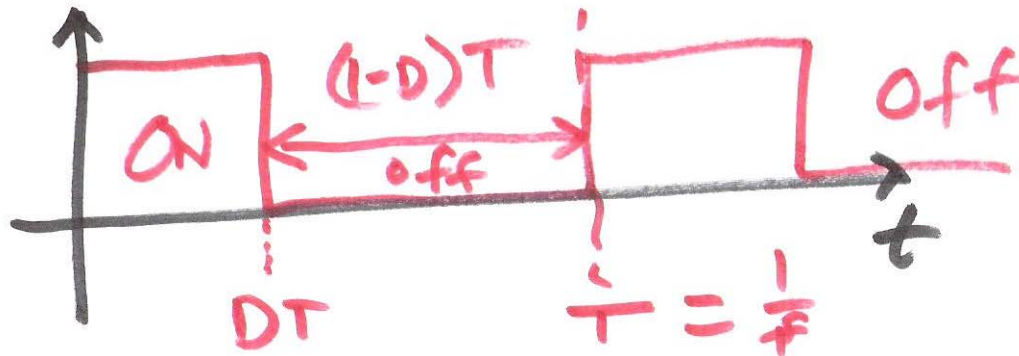
Assume $V_o = \text{CONST.}$ so $I_C = 0$



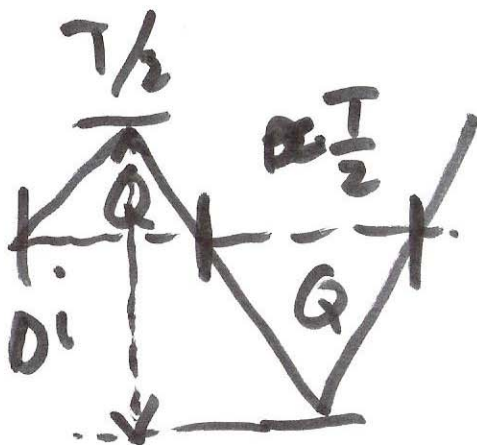1)

Switch on $V_x = V_s$, diode is off


$$I_{AVG} = \frac{V_o}{R} \quad v = L \cdot \frac{di}{dt}$$



$$V_L = L \cdot \frac{di_L}{dt} = V_x - V_o = L \frac{di_L}{dt}$$

$$\frac{V_s - V_o}{L} = \frac{\Delta i_L}{DT}, \quad \Delta i_L = DT \cdot \frac{(V_s - V_o)}{L}$$

Switch off

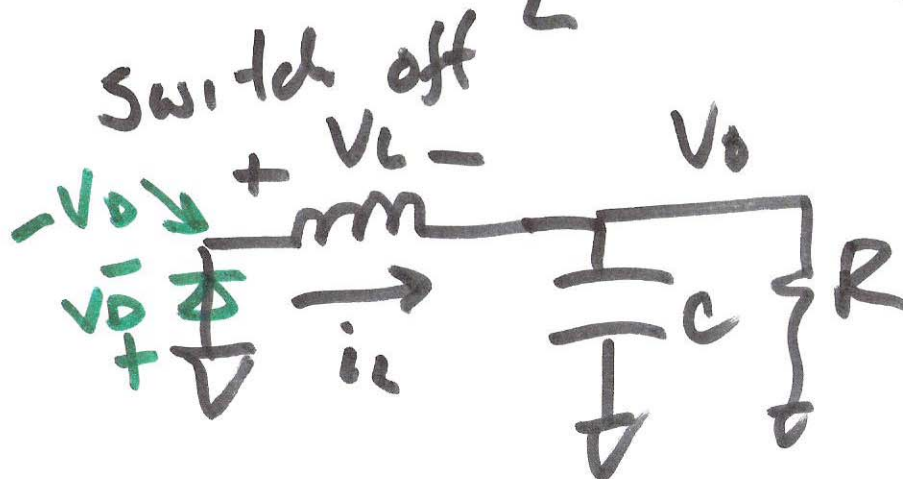

$$\frac{-V_o - V_o}{L} = \frac{\Delta i_L}{(1-D)T}$$

$$\Delta i_L = (D-1)T \frac{(V_o + V_o)}{L}$$


2)

$$DT \frac{(V_s - V_o)}{\downarrow} = -(D-1)T \cdot \frac{V_o}{\downarrow}$$

$$DT \uparrow V_s - \cancel{DT \uparrow V_o} = \cancel{-DT \uparrow V_o} + \uparrow V_o$$

$$\boxed{D \cdot V_s = V_o}$$


OUTPUT Voltage Ripple

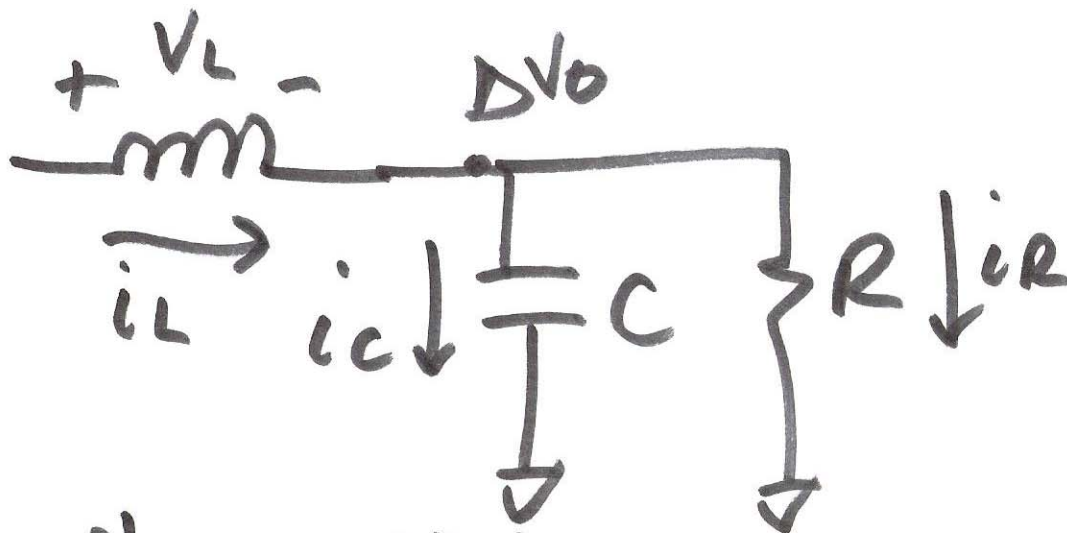

$$i_L = i_c + i_r$$

$$i_c = C \cdot \frac{\Delta V_o}{T/2}$$

$$i_r = \frac{\Delta V_o}{R}$$

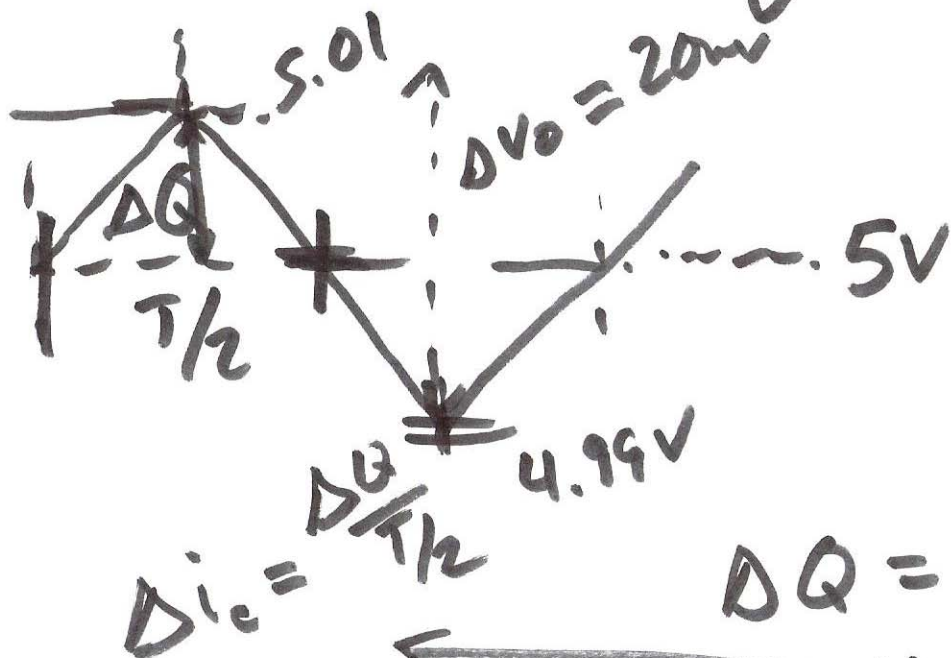

$$C \cdot \Delta V_o = \Delta Q$$


$$\Delta V_o = \frac{\Delta Q}{C}$$


$$\Delta Q = \frac{1}{2} \left(\frac{T}{2} \right) \left(\frac{\Delta i_L}{2} \right) = \frac{T \cdot \Delta i_L}{8}$$

$$\Delta V_o = \Delta i_c \cdot C \cdot \frac{T}{2} = \Delta Q \cdot C = T \cdot \frac{\Delta i_L}{8}$$

4)

$$\Delta V_c = \Delta V_o$$

$$i_c = C \frac{\Delta V_c}{dt}$$

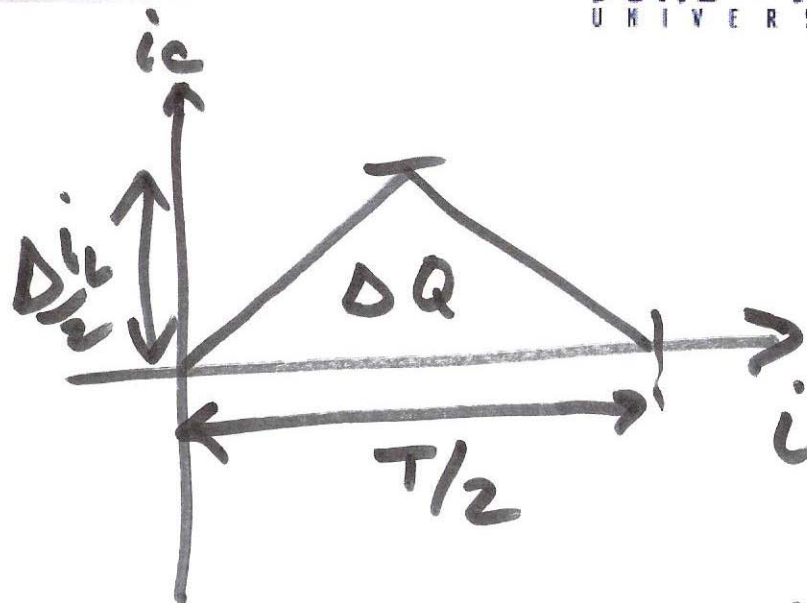


$$Cv = Q$$

$$C \cdot \Delta V_c = \Delta Q$$

$$\Delta V_o = \frac{\Delta Q}{C}$$

$$\Delta Q = \frac{1}{2} \left(\frac{T}{2} \right) \left(\frac{\Delta i_c}{2} \right)$$

$$= \frac{T \cdot \Delta i_c}{8}$$

$$\Delta V_o = \frac{T \cdot \Delta i_c}{8C}$$

$$T = \frac{1}{f}$$


$$= \frac{T}{8C} \cdot \frac{DT(V_s - V_o)}{L} = \boxed{\frac{(1-D)V_o}{8CLf^2}}$$

5)

$$V_s = 24V \quad V_o = 5V$$

$$f = 1 \text{ MHz} \quad I_{\text{min}} = 1A$$
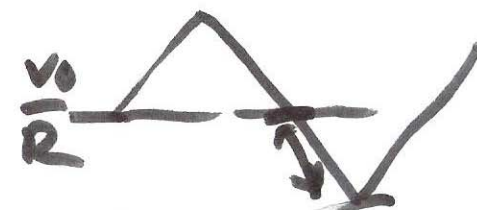
$$L_{\text{min}} = \frac{(D-1)T \cdot V_o}{\frac{V_o}{R} - \frac{\Delta i_L}{2}}$$



----- $I_{\text{dc}} = \frac{V_o}{R}$

$$\frac{V_o}{R} - (D-1) \frac{1 \cdot V_o}{f L_{\text{min}}} = 0$$

b) $L_{\text{min}} = \frac{(D-1)R}{f \Delta i_L / 2}$

$$0 = \frac{1}{R} + \frac{(1-D)}{f L_{\text{min}}}$$



$$V_s = 24 \quad V_o = 5$$

$$f = 10^6 \text{ Hz} \quad I_{\text{min}} = 1 \text{ A}$$

$$\underline{\underline{R = 5 \Omega}}$$

$$.01 = \frac{D V_o}{V_o} \quad D = \frac{5}{24} = 0.2$$
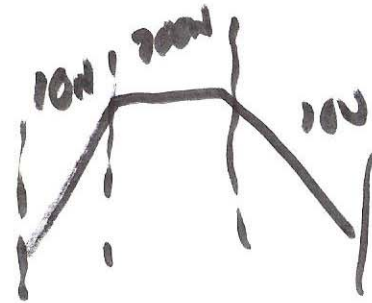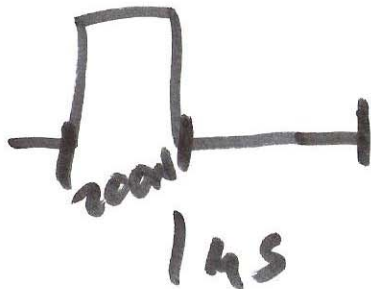
$$.01 = \frac{1 - .2}{8 \cdot 24 \cdot C \cdot 10^6} L_{\text{min}} = \frac{(0.2 + 1) \cdot R}{f \cdot 2} = \frac{4}{2 \cdot 10^6} = \underline{\underline{2.4 \mu\text{H}}}$$



C_{min}

$$= \frac{.8 \cdot 100}{16 \cdot 10^6 \cdot 10^{12}} = 50 \cdot 10^{-6} = \underline{\underline{50 \mu\text{F}}}$$

7)

$$D \cancel{V_s - V_o} = \frac{(1-D) \cancel{V_o + V_D}}{\cancel{V_o}}$$

$$DV_s - \cancel{DV_o} = V_o + V_D - \cancel{DV_o}$$

$$DV_s + \cancel{DV_D} - V_o = V_o$$

$$V_o = DV_s - V_o(1-D)$$

$$= \underbrace{0.2 \cdot 24}_{4.8} - \underbrace{0.7 \cdot (.8)}_{.56}$$

$$V_o = 4.24V$$

8)