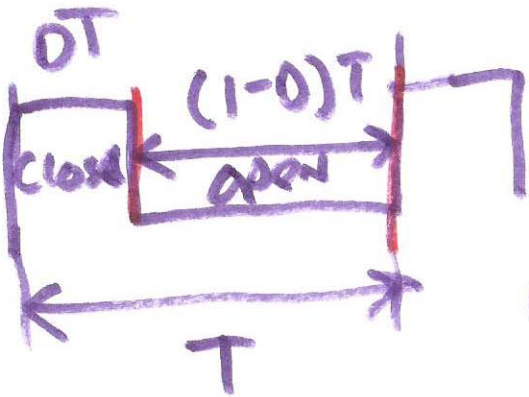



Lecture 5 Sept. 2, 2011



$$V_o > V_s$$

Boost Converter

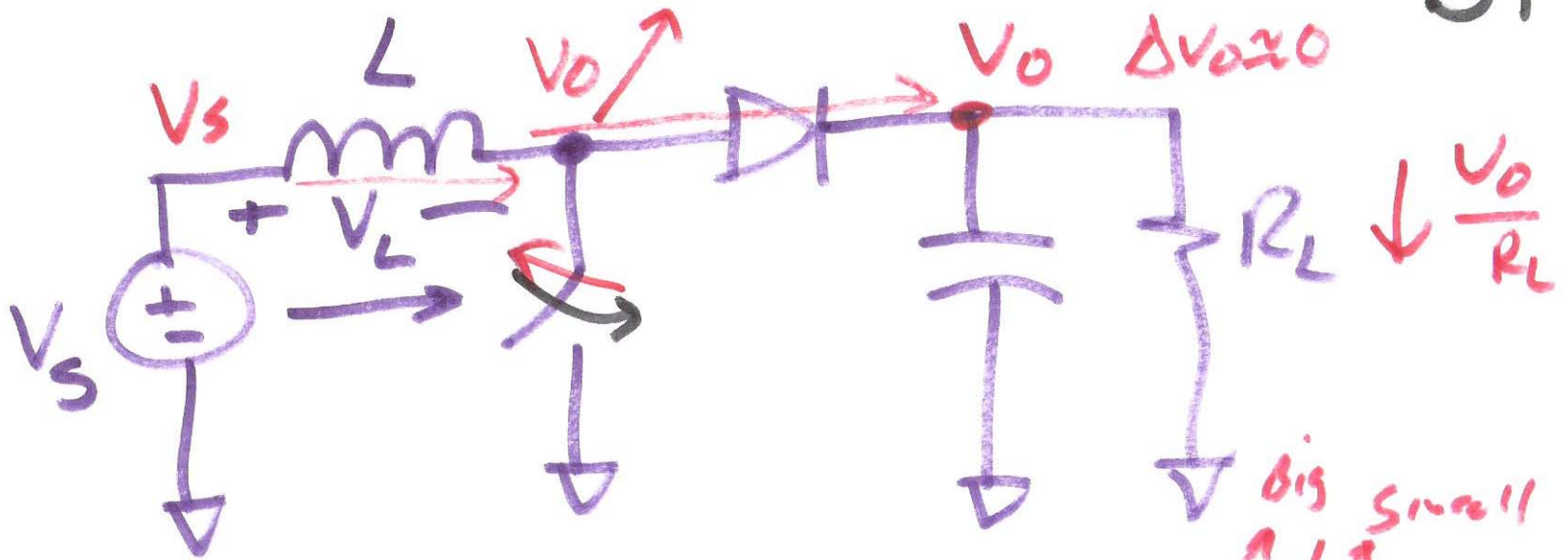
$$\Delta i_L = L \cdot \frac{\Delta i_L}{DT}$$



$$\Delta i_L = \frac{V_s \cdot DT}{L}$$

$I = C \frac{dV}{dt}$
 ↓ $\frac{V_o}{R}$ ↑ $\frac{dV}{dt}$
 big small

11

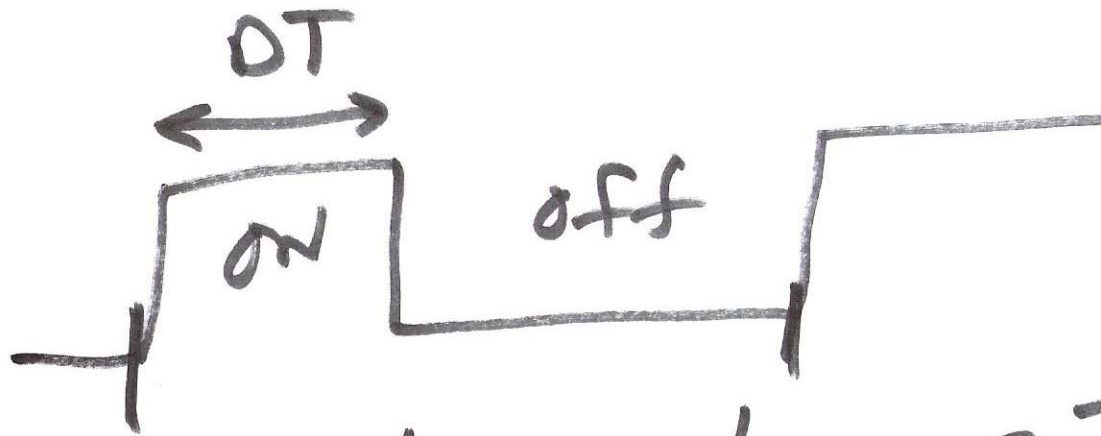


$$404 = \frac{1}{25\text{kHz}} = T$$

$$D = 0.6 \cdot \cancel{T}$$

$$TD = 0.6 \cdot 404 \\ = 244\text{s}$$

2)

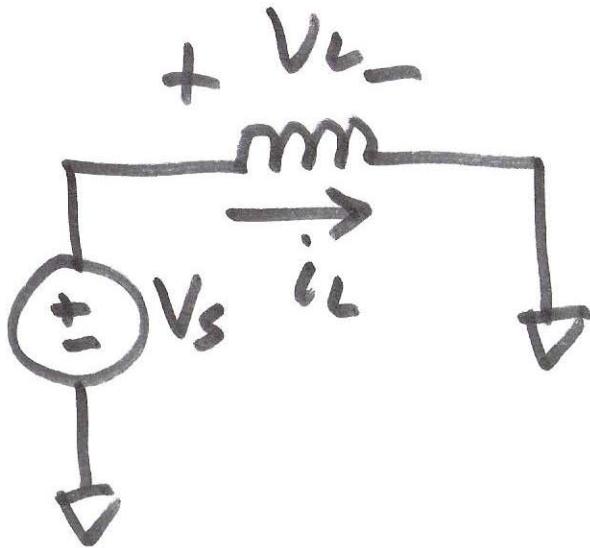

$DT =$ time switch
closed $\ddot{}$

$$V_L = V_s$$

$$V_L = L \cdot \frac{di_L}{dt}$$


$$V_s = L \cdot \frac{\Delta i_L}{D \cdot T}$$

$$\Delta i_L = \frac{V_s \cdot D \cdot T}{L}$$

EQ 6.25

3)

Switch open

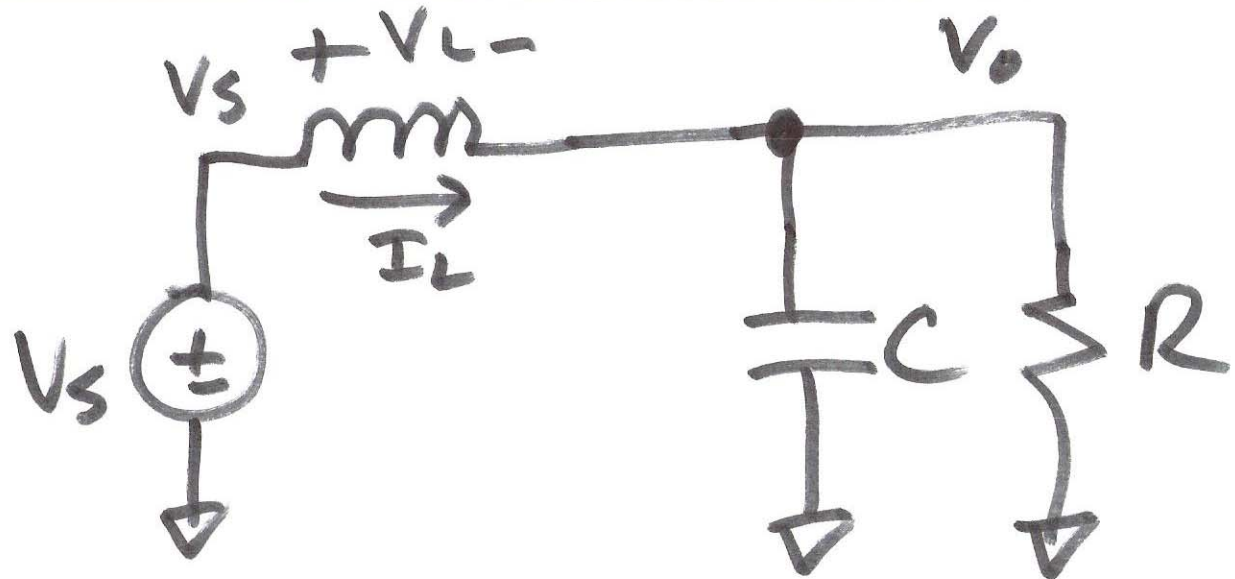

$$V_L = L \cdot \frac{di}{dt}$$

$$V_s - V_o$$

$$= L \cdot \frac{\Delta i_L}{(1-D)T}$$

$$I_{AVG} = \frac{V_o}{R}$$

$$\text{peak} = \frac{\Delta i_L}{2} + I_{AVG}$$

$$\text{valley} = I_{AVG} - \frac{\Delta i_L}{2}$$

$$(1-D)T =$$

$$\Delta i_L = \frac{(V_s - V_o) \cdot (1-D)T}{L}$$

$$T = \frac{1}{f}$$

Time switch closed

4)

$$\frac{V_s - V_0}{K} \cdot (1-D)T = \frac{-V_s \cdot D \cdot T}{K}$$

$$V_s - V_0 - DV_s + DV_0 = -DV_s$$

$$(D-1)V_0 = V_s(D+D-1)$$

$$V_0 = \frac{V_s(2D-1)}{D-1}$$

$$V_s = V_0 \cdot (1-D) \quad \boxed{(V_0) = \frac{V_s}{1-D}}$$

5)

100% Efficient

$$V_s \cdot I_s = V_o \cdot I_o$$

$$V_o = \frac{V_s}{1-D}$$

$$\frac{V_o}{V_s} = \frac{1}{1-D}$$

$$I_s \cdot \cancel{V_s} = \cancel{V_s} \cdot \frac{I_o}{1-D}$$

$$I_L = I_s = \frac{I_o}{1-D}$$

$$\frac{I_o}{I_s} = \frac{V_s}{V_o} = 1-D$$

6)


Return to Ex 6.4

$$\frac{30V}{50\Omega} = I_0 = 0.6A \quad \text{AVG.}$$

$$I_s = I_L = \frac{I_0}{1-D} \quad \text{AVG.}$$

$$= \frac{0.6}{1-0.6} = \frac{0.6}{0.4} = \underline{\underline{1.5A}}$$

$$I_{\text{AVG}} = 1.5$$

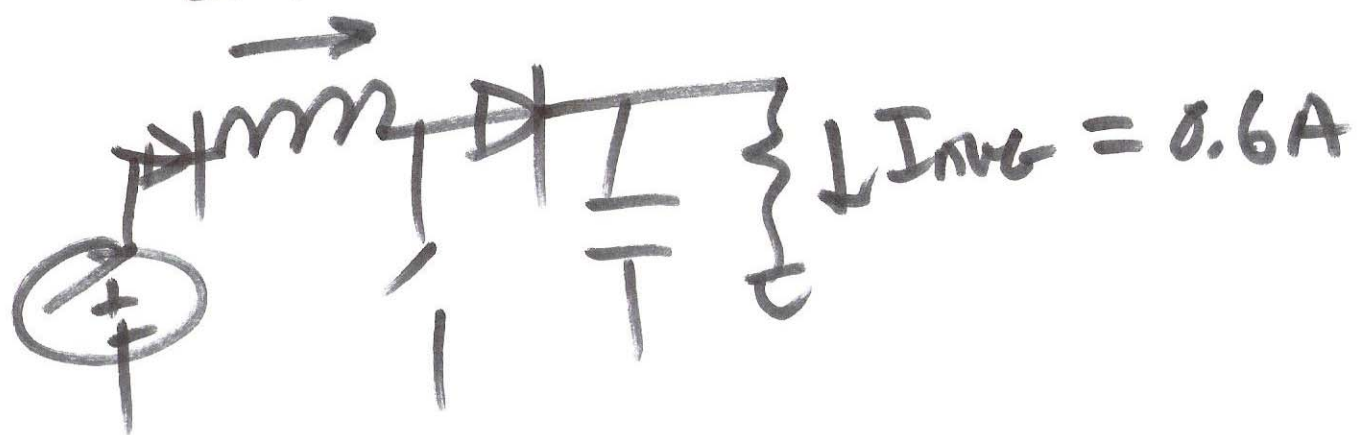


7)

L_{min}

$$\frac{\Delta i_L}{2} = \frac{V_s \cdot D}{f \cdot L \cdot 2}$$

$$V_o = \frac{V_s}{1-D}$$
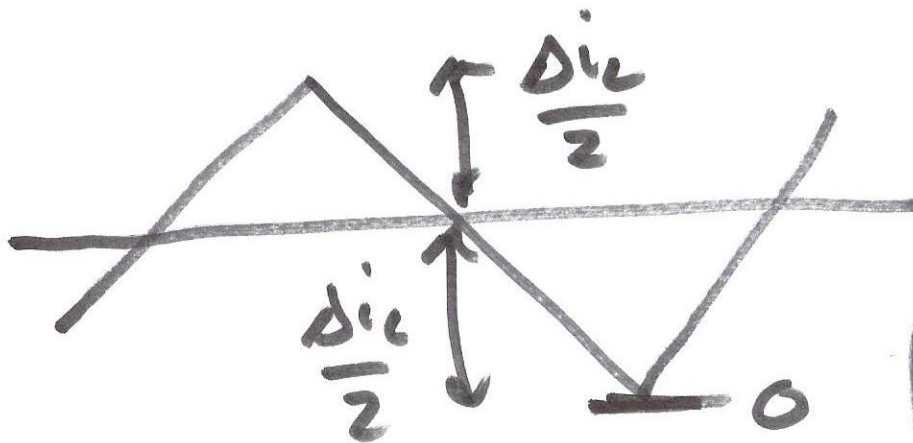
$$I_L = \frac{I_o}{1-D} = \frac{V_o}{(1-D)R} = \frac{V_s}{(1-D)^2 R}$$




$$\frac{V_s \cdot D}{f L_{min} \cdot 2} - \frac{V_s}{(1-D)^2 R} = 0$$

$$L_{min} = \frac{(1-D)^2 R \cdot D}{2f}$$

EQ. 6.32

8)

Buck

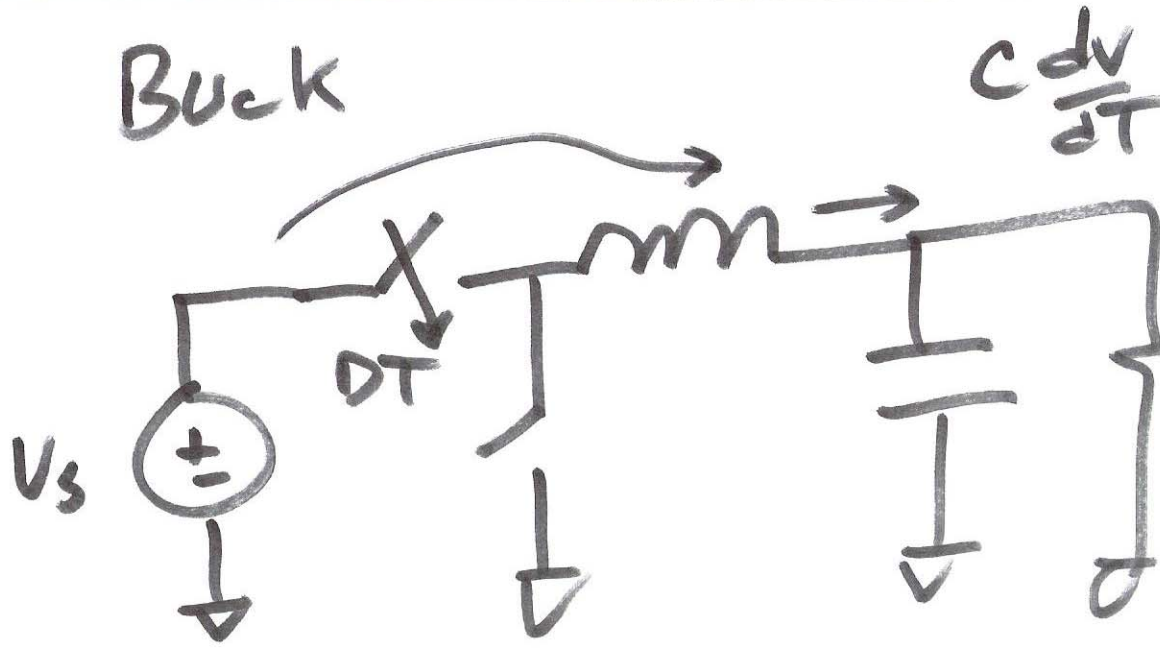

$$C = \frac{1-D}{8L \cdot \left(\frac{\Delta V}{V}\right) f^2}$$

$$\Delta Q = \frac{V_o}{R} DT$$


$$CV = Q$$

$$\Delta Q = C \cdot \Delta V_o$$

$$\Delta V_o = \frac{R \cdot \Delta Q}{DT}$$

$$V_o = \frac{R \cdot C \cdot \Delta V_o}{DT}$$

Boost

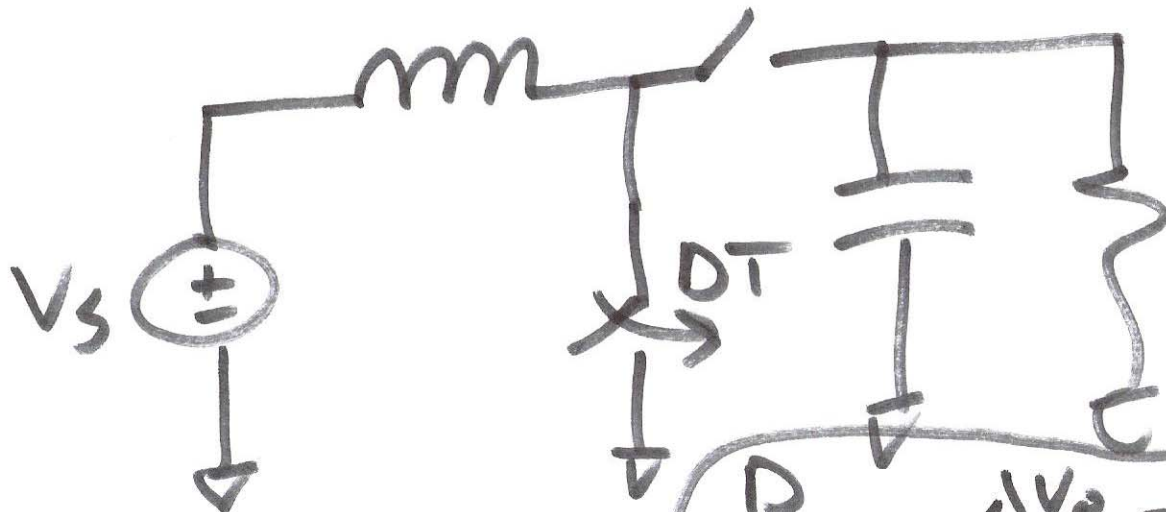

$$\frac{D}{RCf} = \frac{\Delta V_o}{V} = \frac{DT}{RC}$$

a)