
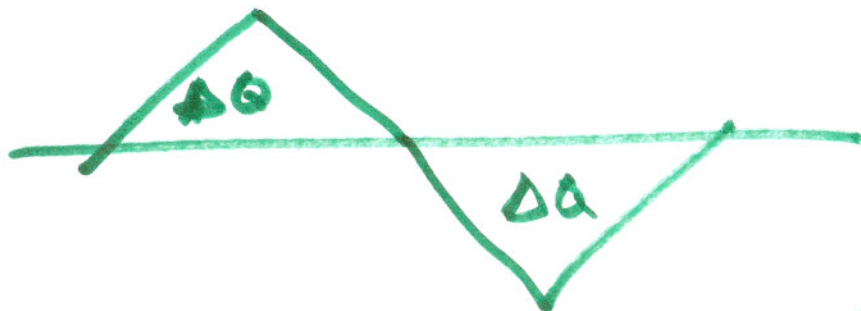


Lecture 6, Sept. 6, 2011

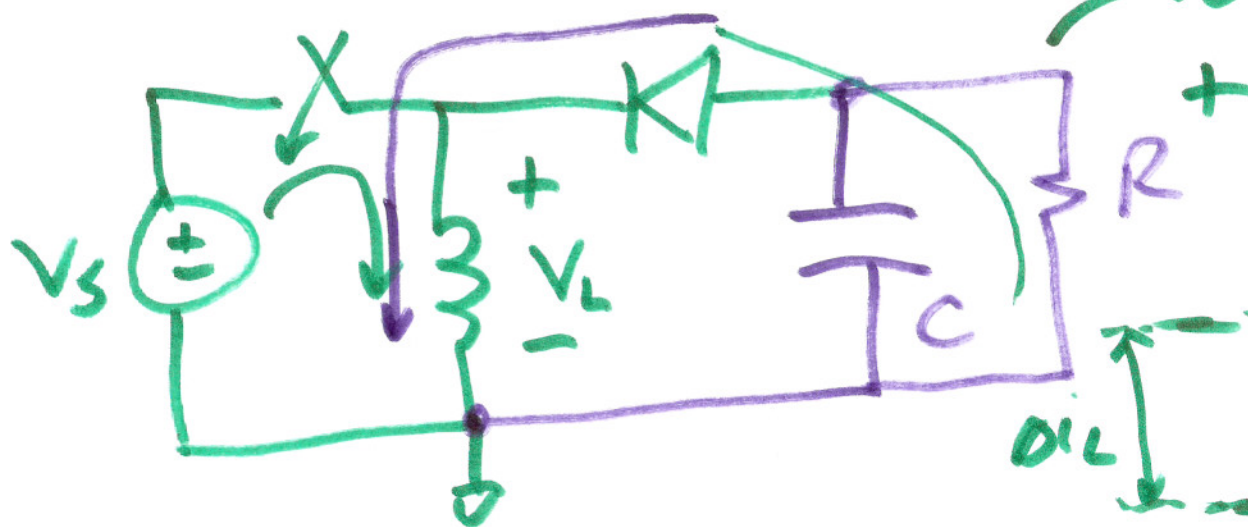


Buck-Boost



$V_o$  is negative


$$I_{AVG} = \frac{V_o}{R}$$

switch closed?

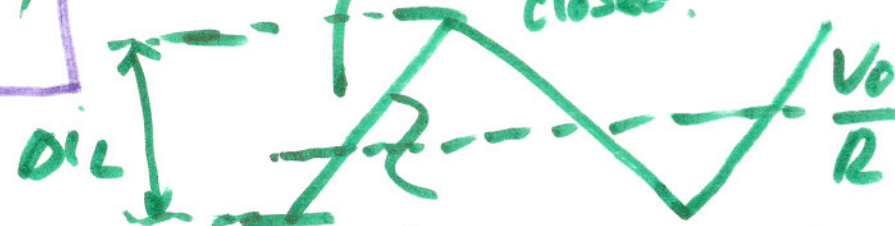


$$\frac{V_s}{L} = \frac{V_L}{L} = \frac{di_L}{dt}$$

1)

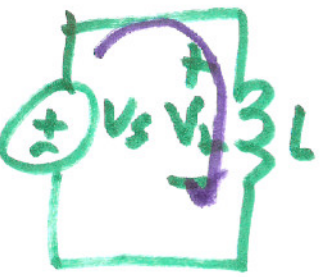

$$\frac{\Delta i_L}{DT} = \frac{V_s}{L}$$
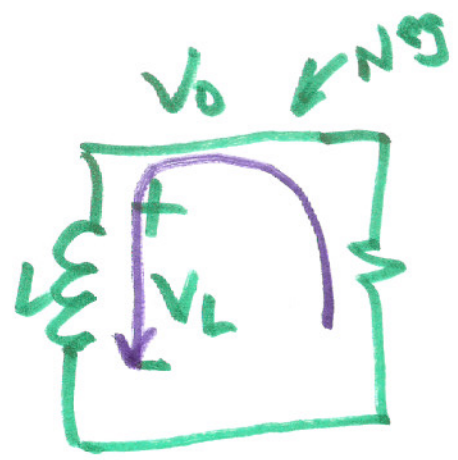
$$\Delta i_L = \frac{V_s \cdot DT}{L} = \frac{V_s \cdot D}{f \cdot L}$$



$$(1-D) \frac{\Delta i_L}{DT} = \frac{V_o}{L}$$


$$\Delta i_L = \frac{V_o(1-D)T}{L}$$

$$\frac{V_s \cdot DT}{L} = \frac{-V_o(1-D)T}{L}$$

$$\frac{V_o}{V_s} = \frac{D}{D-1}$$

$V_s = 10V$   
 $D = 0.5$   
 $V_o = \underline{\underline{-10V}}$

2)

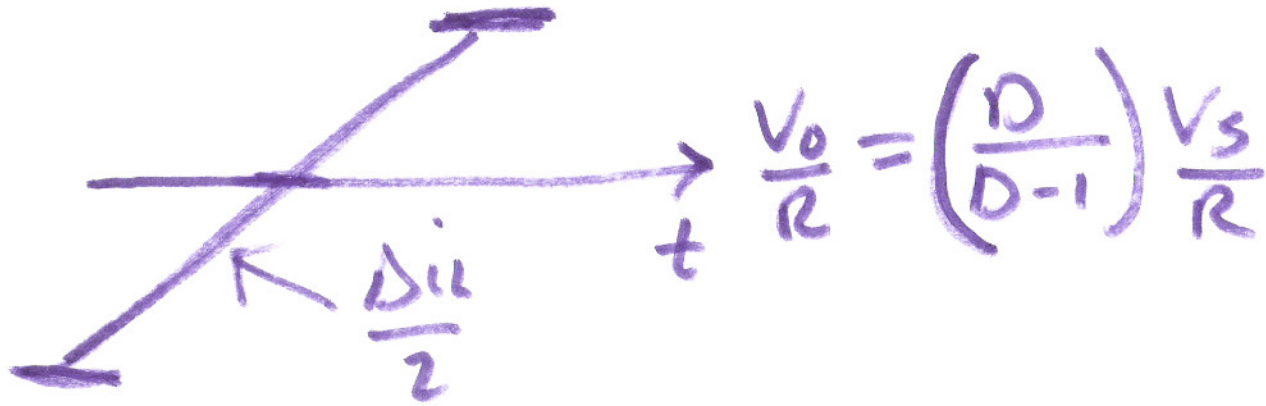

$$I = \frac{V_o}{R} = \left( \frac{D}{D-1} \right) \frac{V_s}{R}$$

$$\frac{V_s}{R} \left( \frac{D}{1-D} \right) + \frac{\Delta i_L}{2} = \frac{V_s \cdot DT}{2L_{min}} - \frac{V_s}{R} \left( \frac{D}{D-1} \right) = 0$$

$$\frac{1}{2fL_{min}} = \frac{DT}{2L_{min}} = \frac{1}{R} \frac{D}{D-1}$$


$$L_{min} = \frac{-R(D-1)^2}{2f}$$

$\frac{5 \cdot .36}{2 \cdot 10^5}$   
 $94 \mu H \uparrow$   
 $= \frac{5(.6)^2}{2 \cdot 10^5}$   
 $\frac{3 \cdot 10^{-5}}{2}$   
 $15 \mu H$

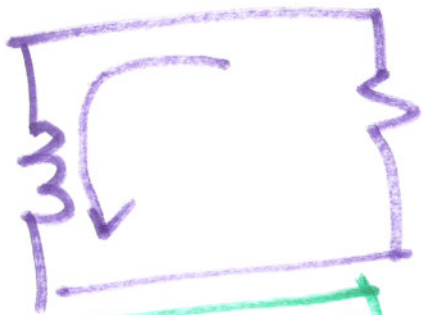3)

$$I_L = \frac{V_o}{R} = \frac{V_o^2}{V_s \cdot R D} = \frac{V_o \cdot V_s D}{V_s \cdot R \cdot D (D-1)}$$

$$\frac{V_s \cdot D}{R (D-1)^2} \neq \frac{V_s \cdot D}{L \cdot \frac{D}{2}} V_o = -V_s \cdot \frac{D}{1-D} = \frac{V_s D}{D-1}$$



$$\Delta i_L = \frac{V_o (1-D) T}{L}$$

$$L_{min} = \frac{R (D-1)^2}{2f} \quad \frac{V_o (1-D) T}{2 L_{min}} = \frac{D}{D-1} \frac{V_s}{R}$$

4)


$$\frac{\Delta i_L}{2} = \frac{V_s \cdot DT}{2L}$$

$$I_L = \frac{V_o}{R}$$

---

$$I_s \cdot V_s = I_o R_o$$

5)

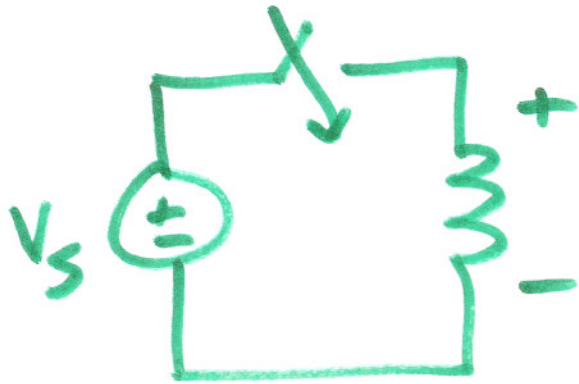

$$\frac{\Delta i_L}{2} = DT \cdot \frac{V_s}{L} \cdot \frac{1}{2}$$

A small triangle diagram with a vertical double-headed arrow labeled  $\Delta i_L$ .

$$P_s = \frac{V_s^2 (DT)^2}{2L_{min}}$$

$$P_s = P_L$$

$$R_{min} = \frac{R(1-D)^2}{2 \cdot f}$$

$$V_o = V_s \cdot \frac{D}{1-D}$$

$$P_s = \frac{V_o^2 \cdot (1-D)^2}{2L_{min} D^2 f}$$

$$P_L = \frac{V_o^2}{R}$$

6)

$$\frac{V_0 \cdot DT}{R} = \Delta Q$$

Amp. sec

$\frac{\text{Coul. sec.}}{s}$

$$CV = Q$$

$$\Delta V_0 = \frac{\Delta Q}{C}$$

$$\Delta V_0 = \frac{V_0 \cdot DT}{CR}$$

$$\frac{\Delta V_0}{V_0} = \frac{DT}{RC}$$


1%  
.01

$$\frac{V_0}{\Delta V_0} = \frac{CR}{DT}$$

$$= \frac{80 \times 5}{.4 \cdot 10^4}$$

$$= \frac{400}{4} = 100$$

1)

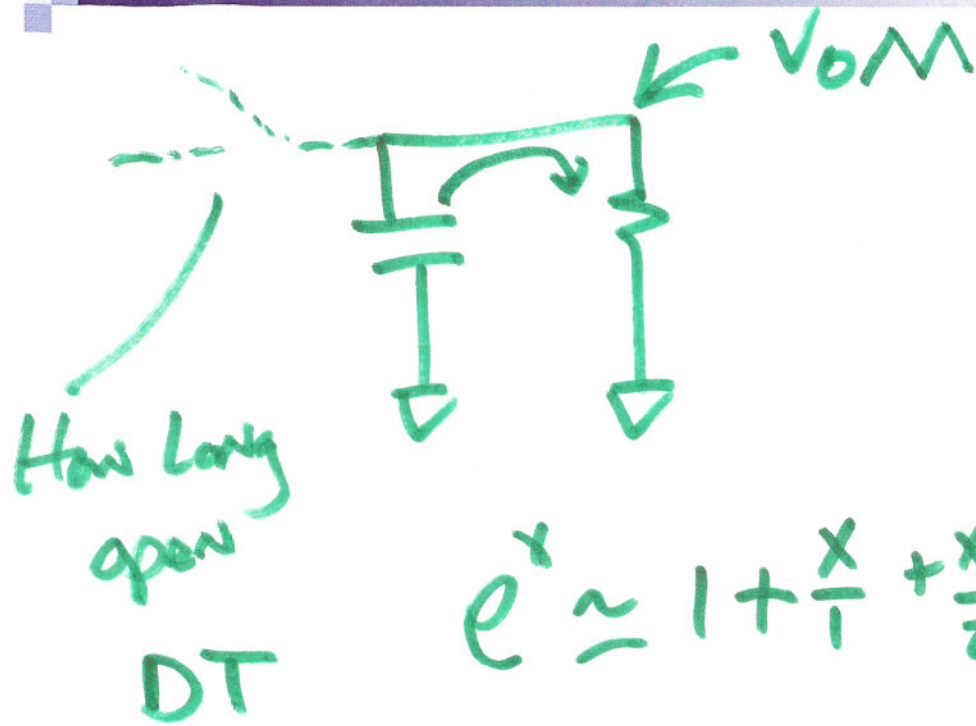

$$\frac{V_0}{R} \cdot DT = \Delta Q$$

$$CV = Q$$

$$\Delta V = \frac{\Delta Q}{C}$$

$$e^x \approx 1 + \frac{x}{1} + \frac{x^2}{2!} + \dots$$

$$\Delta V = \frac{V_0 DT}{RC}$$

$$10\% = .01 = \frac{\Delta V}{V} = \frac{DT}{RC}$$


if  $V = 16V$

$$\Delta V = \underline{\underline{160mV}}$$

8)




$L_{min}$

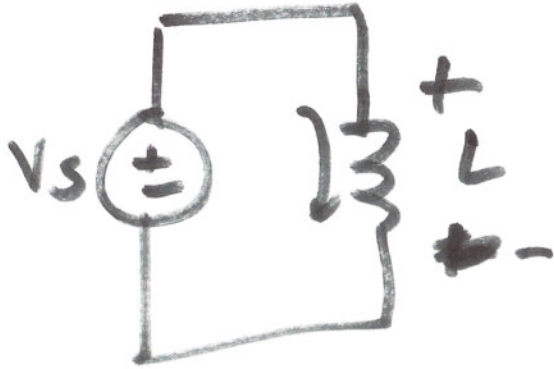

$$\frac{\Delta i_L}{2} = \frac{V_s}{2L} \cdot DT$$

$$P_s = \frac{V_s^2 \cdot DT}{2L}$$

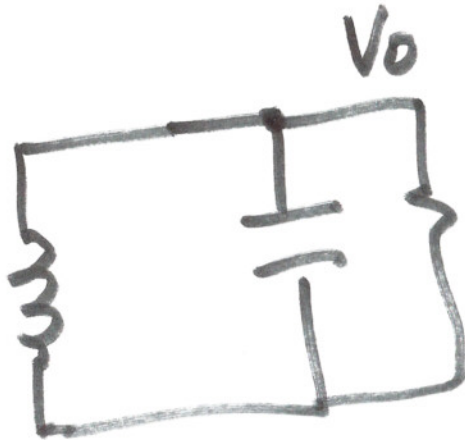

$$P_L = \frac{V_o^2 \cdot (1-D)T}{2L}$$

$$\frac{D}{(1-D)} V_s = V_o$$

$$V_s = \frac{1-D}{D} \cdot V_o$$

$$\frac{(1-D)^2 \cdot V_o^2 \cdot DT}{D^2 \cdot 2L}$$

9)

$$V_o = V_s \frac{D}{D-1}$$

$$I_s = D I_L$$

$$I_o = \frac{V_o}{R} \text{ (Average current)}$$