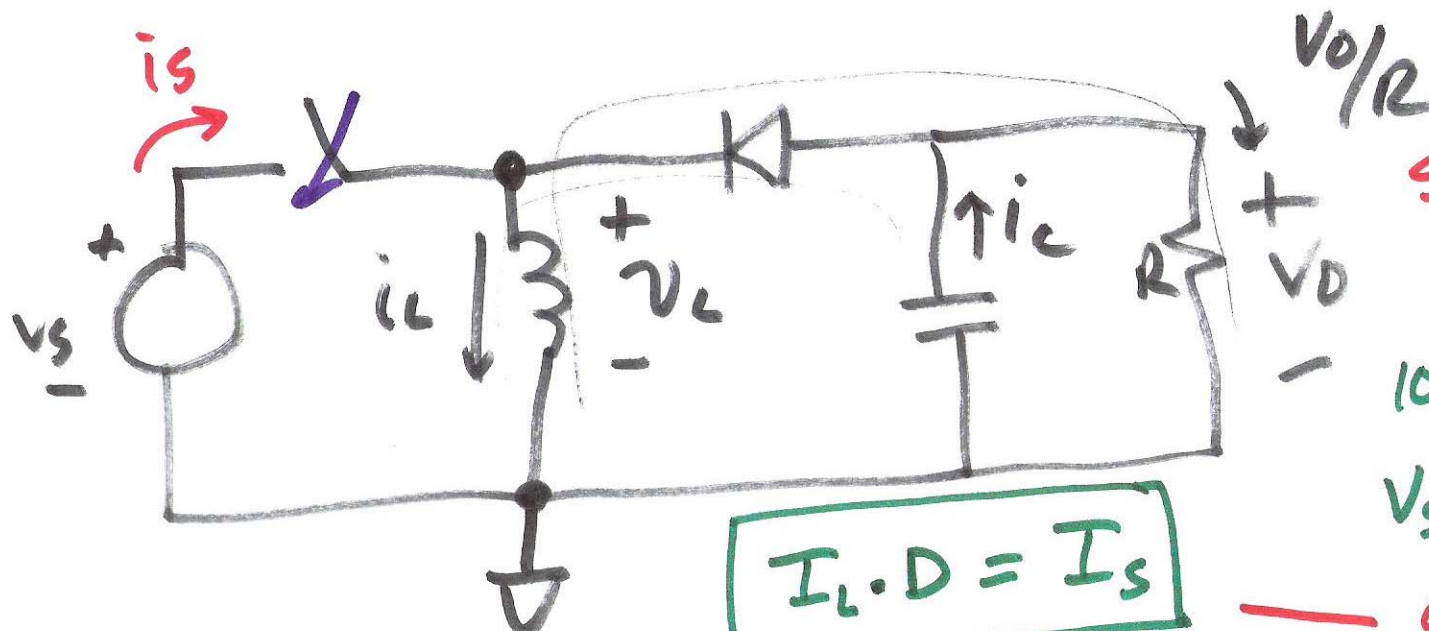


Lecture 7


Sept. 13, 2011



Switch closed
 $i_s = i_L$
 100% eff. conv.
 $V_s \cdot i_s = \frac{V_o^2}{R}$


$$I_L \cdot D = I_s$$

0 → 15 ~~104~~ 104
 3.34

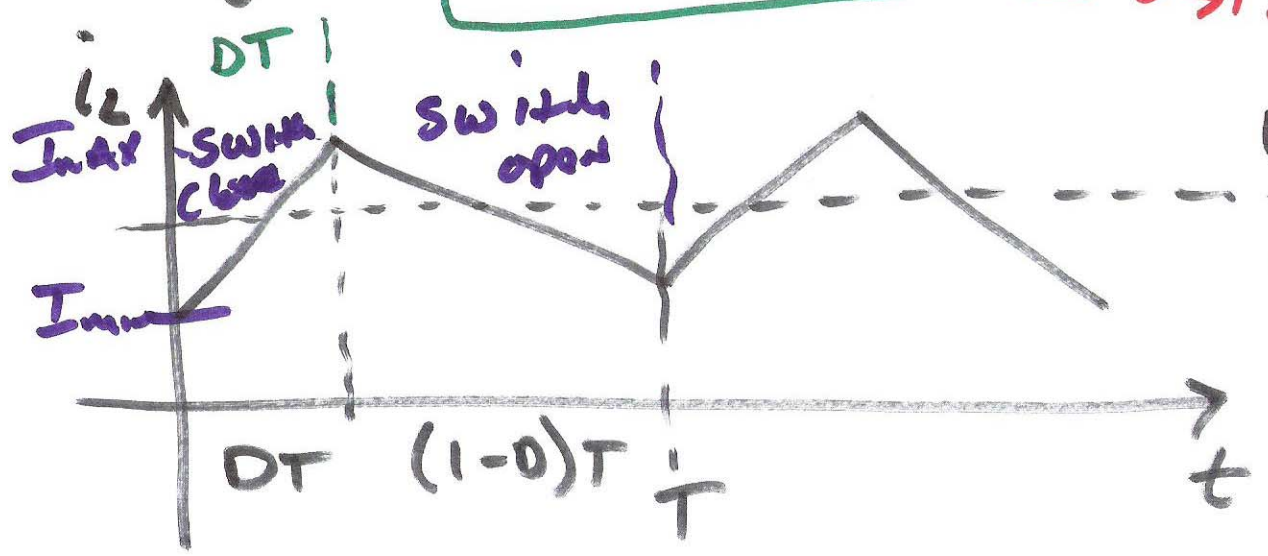

1)

Switch closed

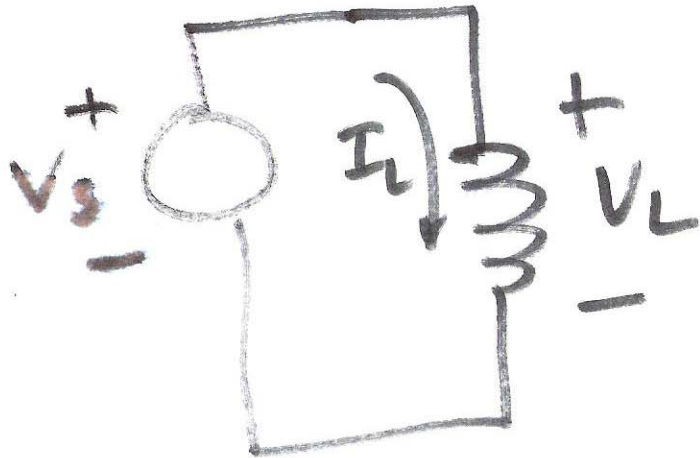

$$V = L \frac{di_L}{dt}$$

$$\frac{V_s}{L} = \frac{\Delta i_L}{D.T}$$

$$\Delta i_L = \frac{D.T \cdot V_s}{L} = \frac{D V_s}{f \cdot L}$$




$$D.T \cdot \frac{V_s}{L} = \frac{V_0(1-D)T}{L}$$

$$V_0 = \frac{D}{1-D} \cdot V_s$$

2)


Switch open

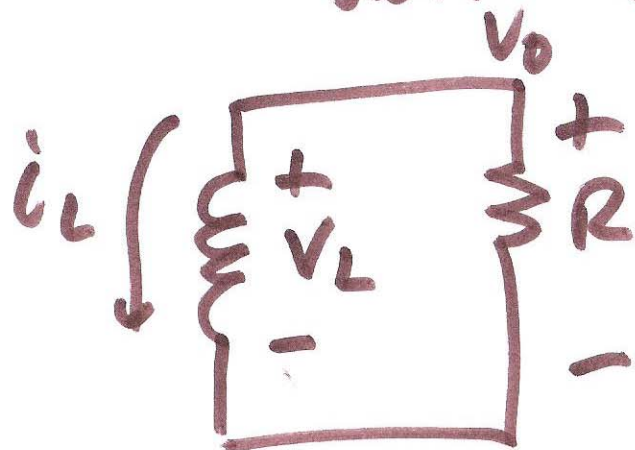

$$V = L \cdot \frac{di}{dt}$$

$$\frac{V_O}{L} = \frac{\Delta i_L}{(1-D)T}$$
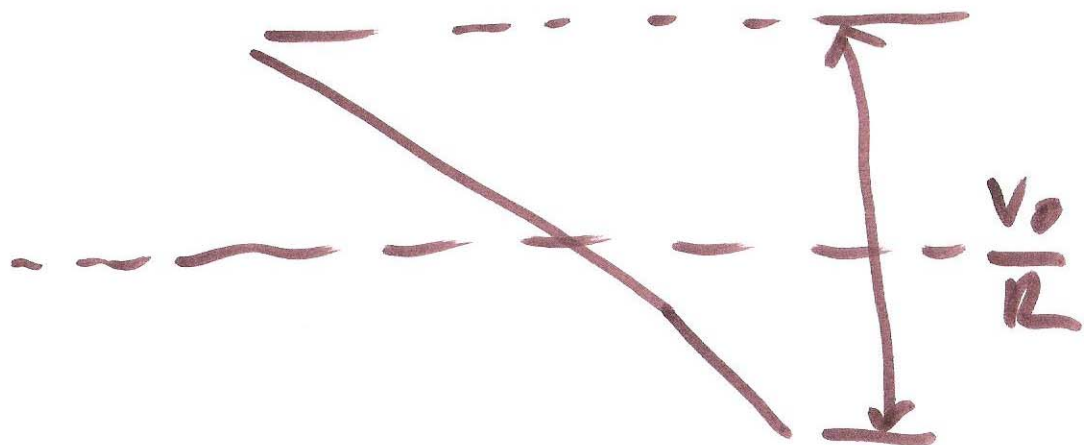
$$\Delta i_L = \frac{V_O \cdot (1-D)T}{L}$$



3)


$$5 = \frac{D}{1-D} \cdot 10 \frac{V_0^2}{R} = V_s \cdot I_s = V_s \cdot D \cdot I_L$$

$$\frac{D}{1-D} = \frac{1}{2}$$

$$D = \frac{1}{2} - \frac{1}{2}D \rightarrow \frac{3}{2}D = \frac{1}{2} \rightarrow D = \frac{1}{3}$$

$$V_s = 10$$

$$D = \frac{1}{3}$$

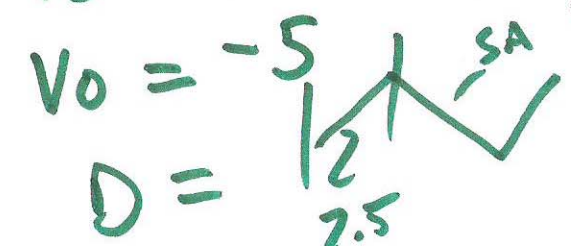

$$I_L = \frac{V_0^2}{R \cdot V_s \cdot D}$$

$$I_L = \frac{V_s \cdot D}{R(1-D)^2}$$

$$I_L = \frac{7.5 \cdot 3.3}{.67^2}$$

$$\frac{10 \cdot .33}{(1-.33)^2}$$

R=1

Minimum/Max

$$I_{max} = I_L + \frac{\Delta I_L}{2} = \frac{V_s \cdot D}{R(1-D)^2} + \frac{DTV_s}{2L}$$

$$I_{min} = I_L - \frac{\Delta I_L}{2} = \frac{V_s \cdot D}{R(1-D)^2} - \frac{DTV_s}{2L}$$

4)



Minimum inductor value

$$\frac{DV_s \cdot T}{2L_{min}} = \frac{V_s \cdot D}{R(1-D)^2}$$





$$L_{min} = \frac{R(1-D)^2}{2f}$$

$$L_{min} = \frac{1 (.67)^2}{200 \cdot 10^3} = 2.244$$

5)

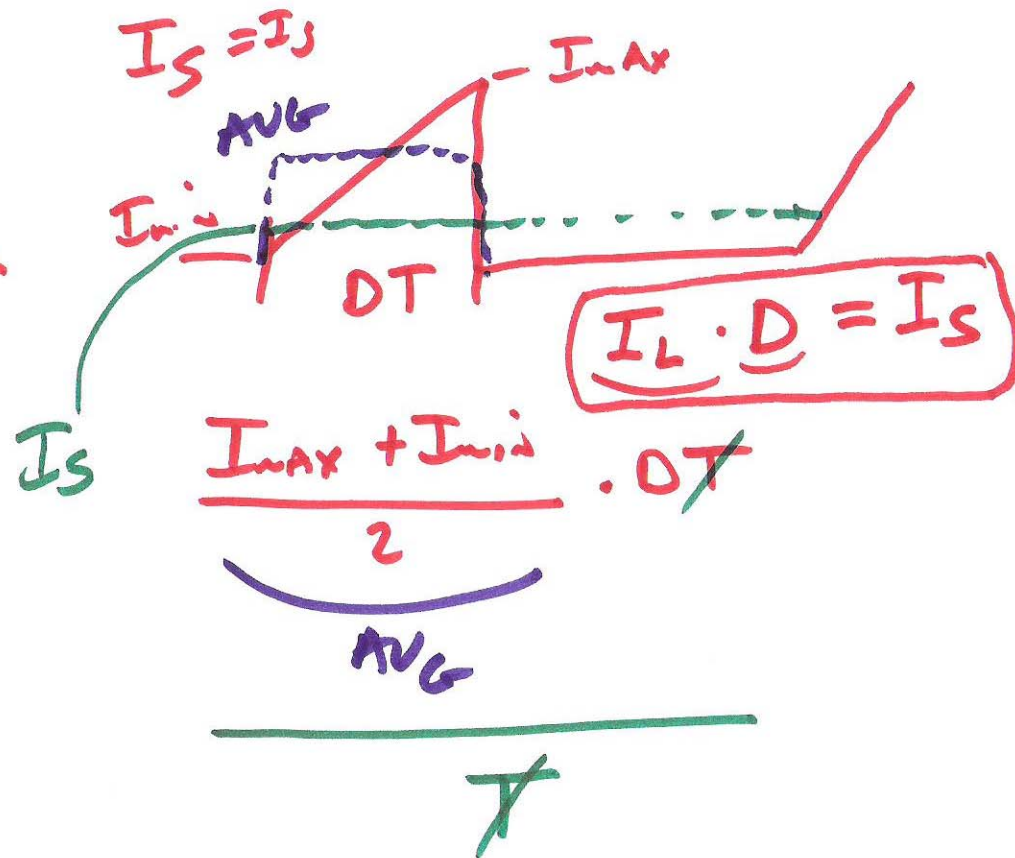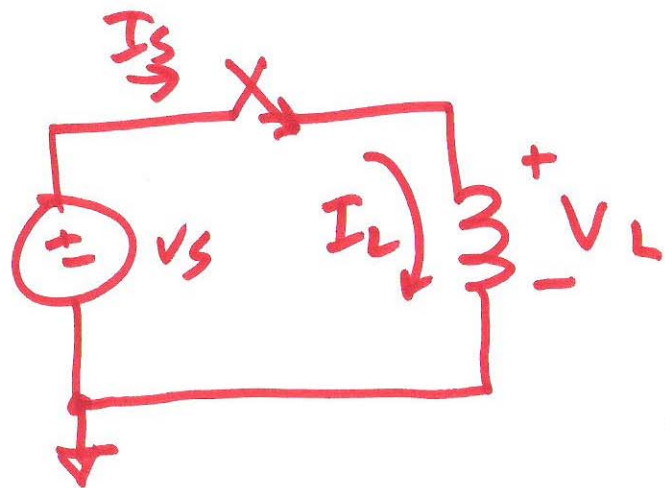


s)

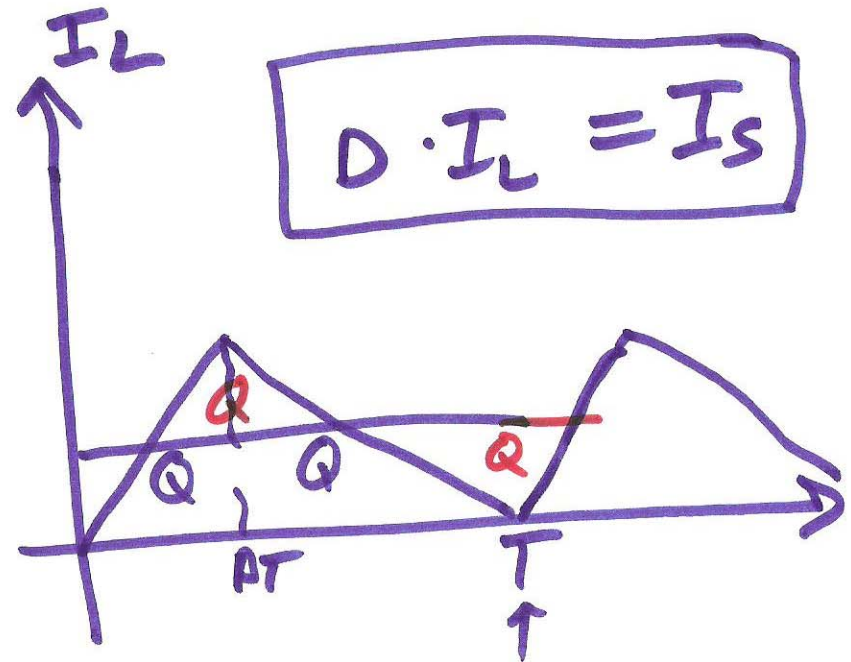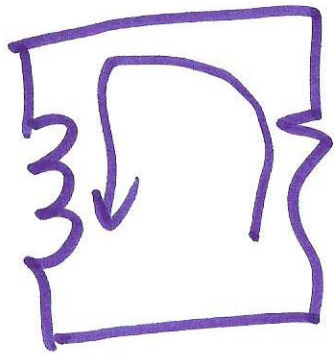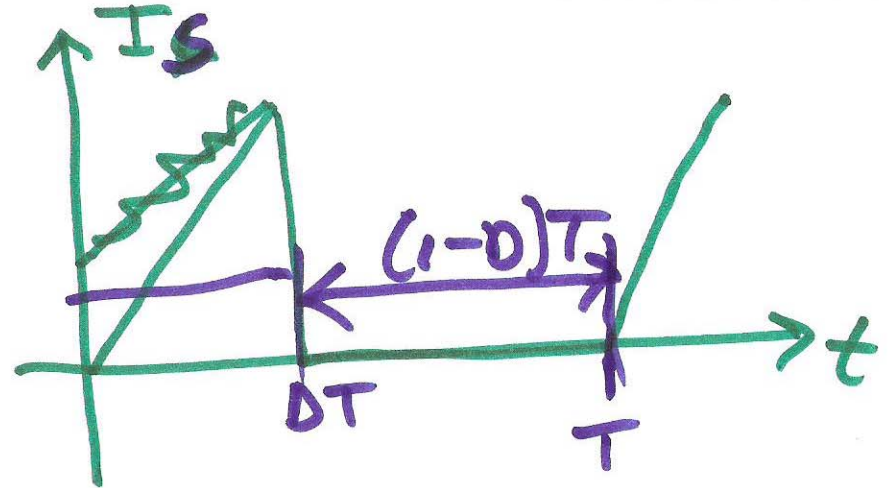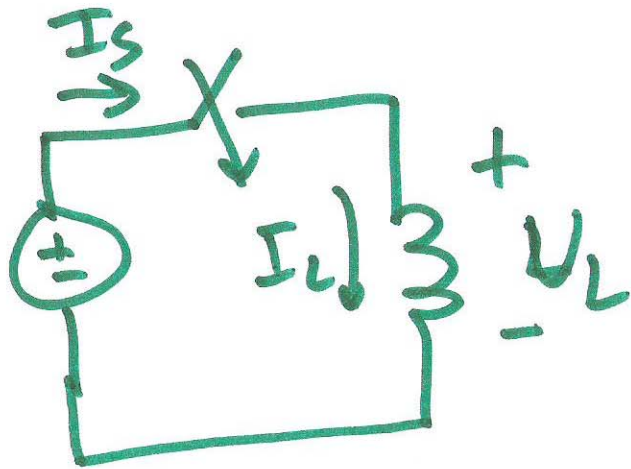

6)

Boost

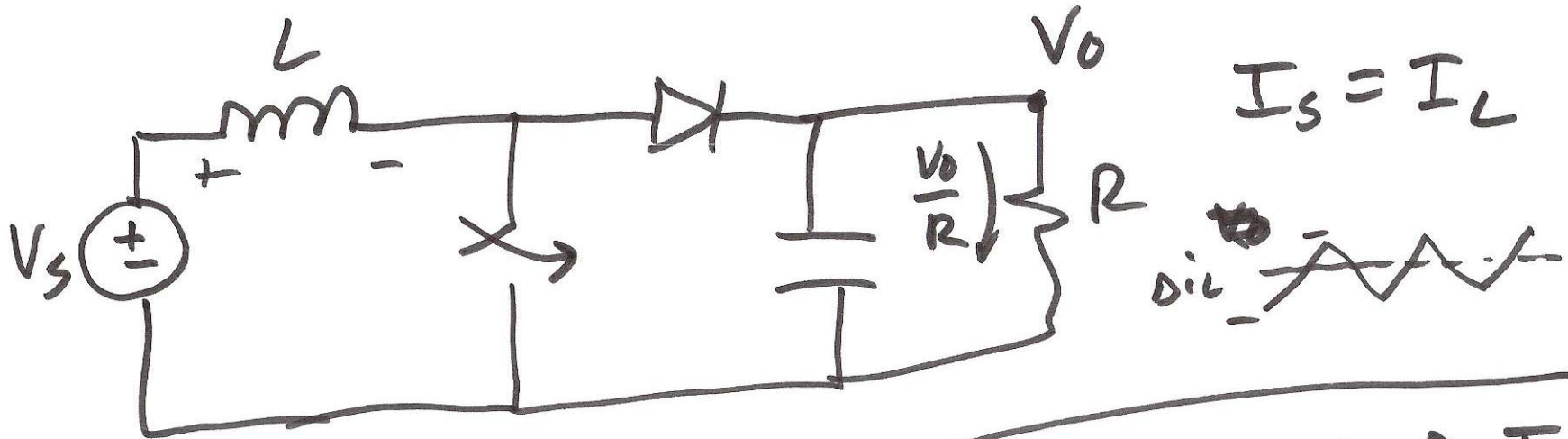

Switch closed

$$\frac{V_s}{L} = \frac{\Delta i_L}{D \cdot T}$$

$$\Delta i_L = \frac{V_s \cdot D \cdot T}{L}$$

Switch open

$$\frac{V_s - V_o}{L} = \frac{\Delta i_L}{(1-D)T}$$

$$\Delta i_L = \frac{(V_s - V_o)T(1-D)}{L}$$

$$D \cdot V_s = \frac{D \cdot V_s - D \cdot V_o}{-V_s + V_o} \cdot \frac{V_s \cdot D \cdot T}{L} = \frac{(V_s - V_o)T(D-1)}{L} \quad \left[\frac{V_s}{1-D} = V_o \right]$$

7)

$$\frac{V_o^2}{R} = V_s I_s, \quad V_o = \frac{V_s}{1-D}$$

$$I_o = \frac{V_o}{R} = V_o(1-D) \cdot I_s$$


$$V_s = V_o(1-D)$$

$$I_s = \frac{I_o}{1-D}, \quad V_o = \frac{V_s}{1-D}$$

$$V_o \cdot I_o = V_s \cdot I_s$$

8)

Cu'k "Chook" Converter

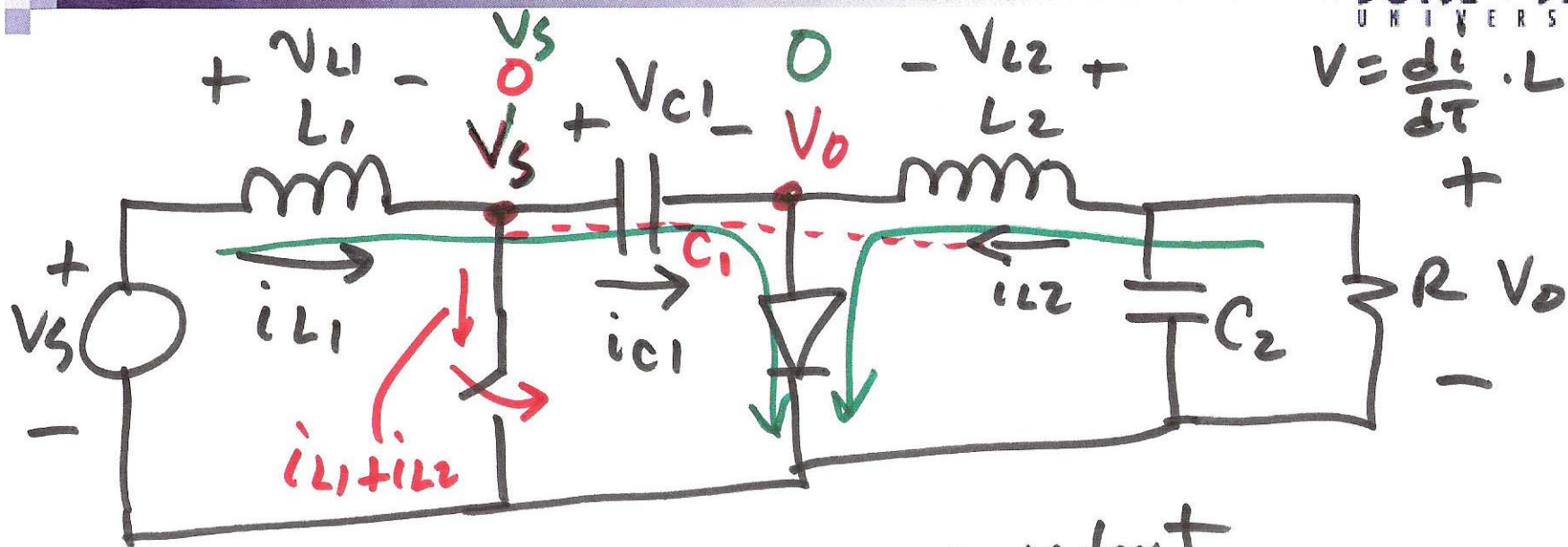

Currents are constant

$$-V_o \cdot I_{L2} = V_s \cdot I_{L1}$$

$$V_{c1} = V_s - V_o$$

Switch is closed

$$i_{c1} = C \frac{dV}{dt} = -i_{L2} = -C_1$$

Switch is open

$$i_{c1} = i_{L1}$$

$$+ I_{L2} D T = I_{L1} (1-D) T$$

$$\frac{I_{L1}}{I_{L2}} = \frac{D}{1-D}$$

$$P_s = P_o$$

$$V_s \cdot I_{L1} = -V_o \cdot I_{L2}$$

$$\frac{I_{L1}}{I_{L2}} = \frac{-V_o}{V_s}$$

$$V_o = -V_s \cdot \left(\frac{D}{1-D} \right)$$