

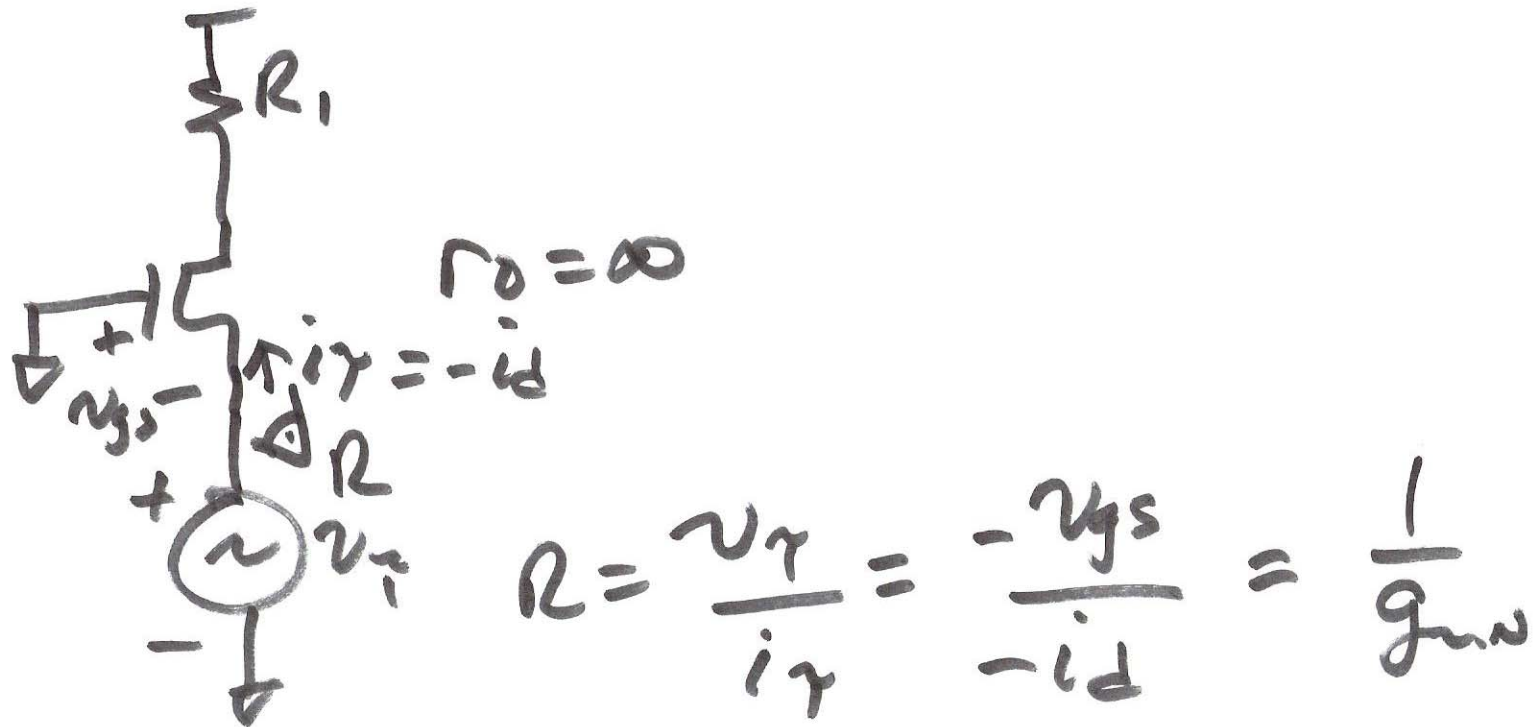


Sept. 2, 2011

SHUNT - SHUNT Amps

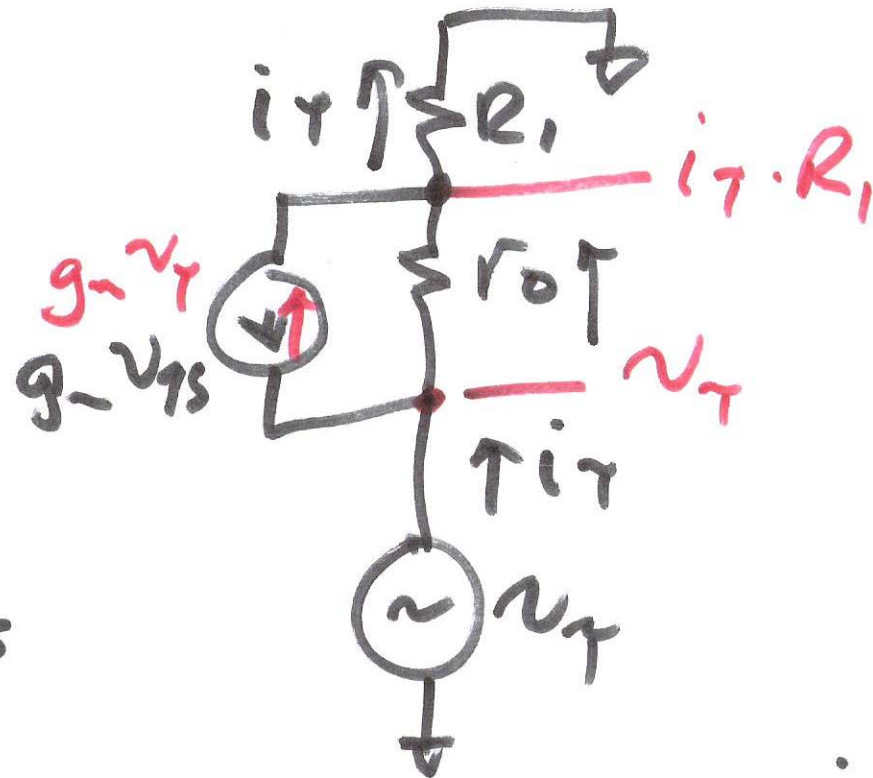

1)

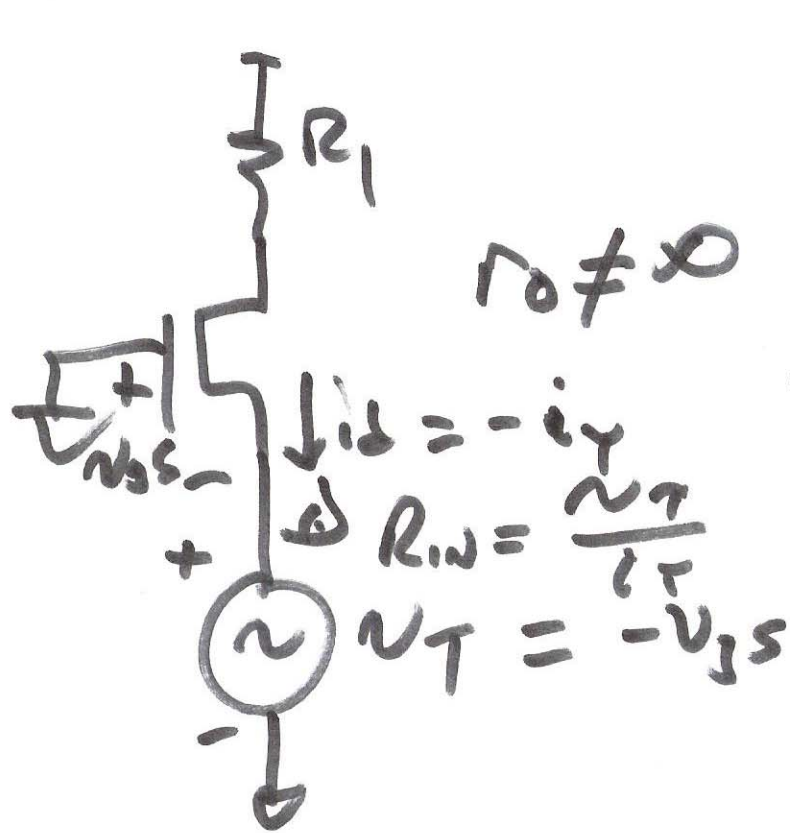


$$i_T = g_m v_T + \frac{v_T - i_T \cdot R_1}{r_o}$$

$$\frac{1 + \frac{R_1}{r_o}}{g_m + \frac{1}{r_o}} i_T \left(1 + \frac{R_1}{r_o} \right) = v_T \left(g_m + \frac{1}{r_o} \right)$$

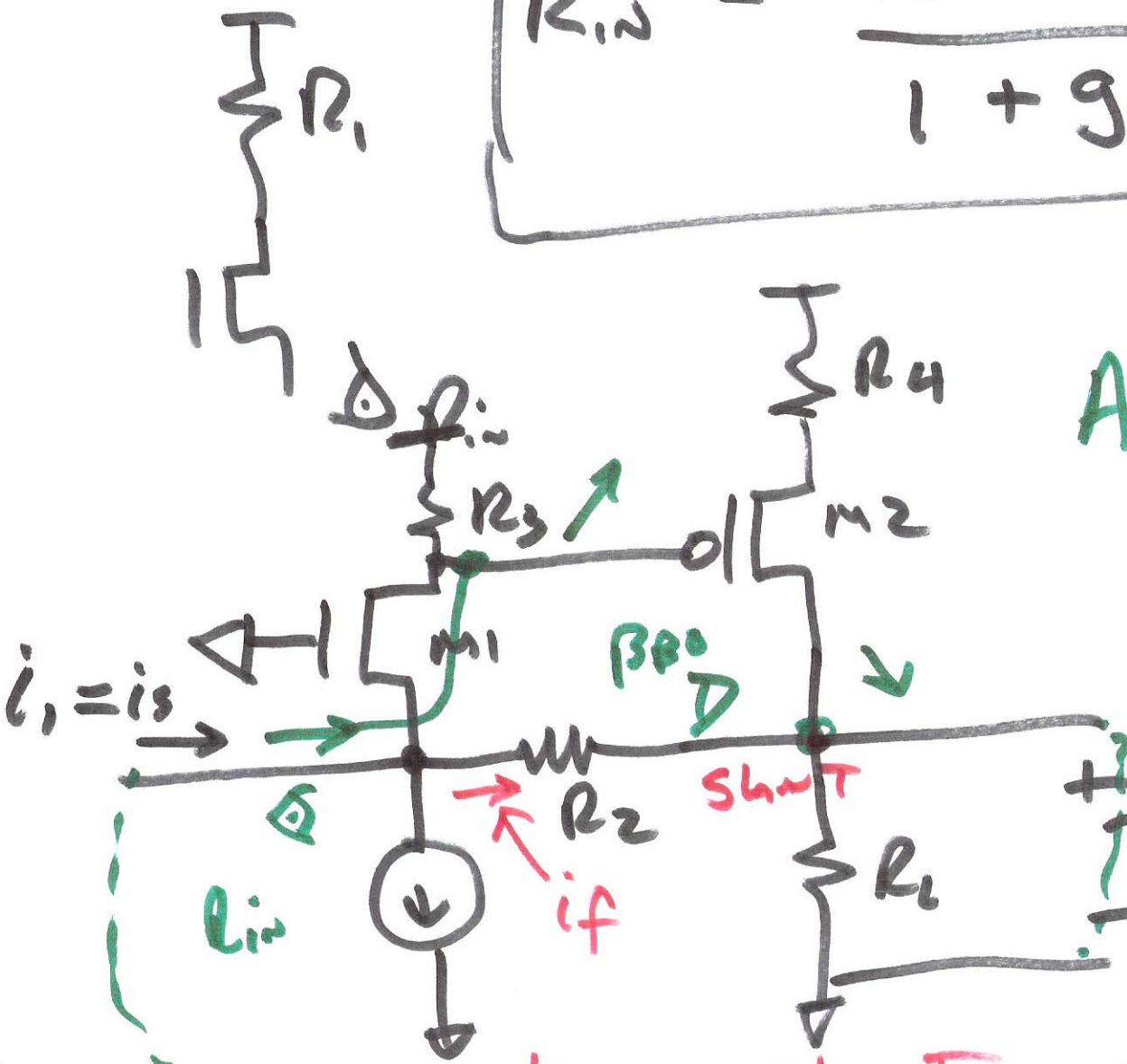2)

$$R_{in} = \frac{r_o + R_1}{1 + g_m r_o} = \frac{\frac{1}{g_m} \cdot (r_o + R_1)}{\frac{1}{g_m} + r_o}$$



$$A_{OL} = \frac{v_2}{i_1} \Rightarrow \text{NEG}$$

$$\beta = -R_2$$

$$R_{fi} = R_2 \quad 31.58$$

$$v_2 = v_o \quad R_I = R_2 || ()$$


$$R_{BO} = R_2 = R_2$$

$$R_{af} = \frac{R_o}{1 + A_{OL}\beta}$$

SHUNT-SHUNT TIA



3)

SERIES - SHUNT
CURRENT
BOOK

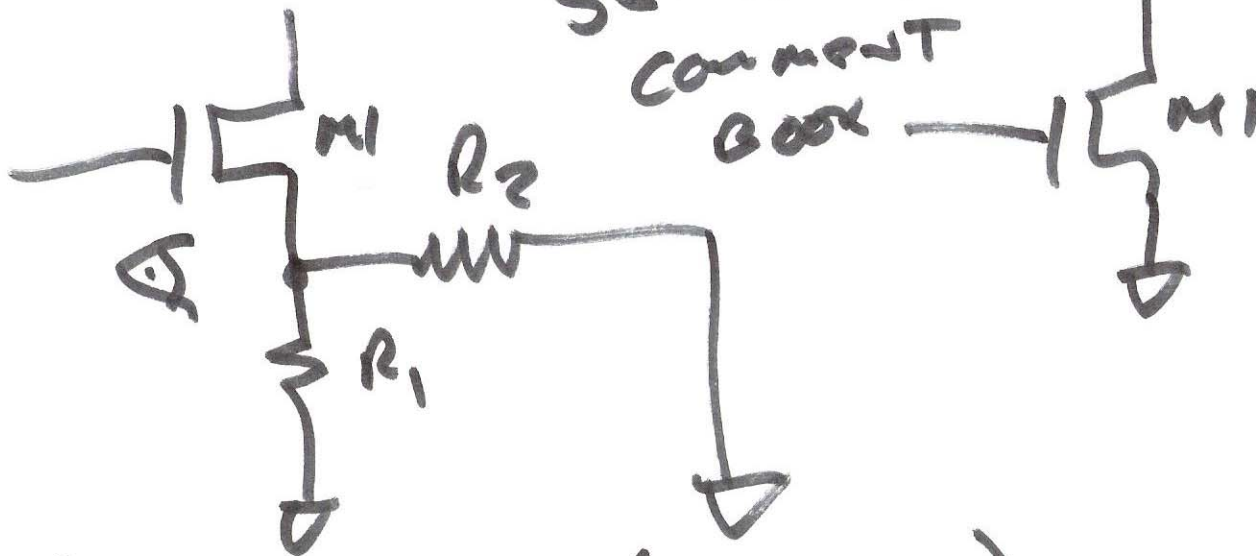

$R_{pi} = R_1 || R_2$ (Lecture)

$R_{pi} = R_2$

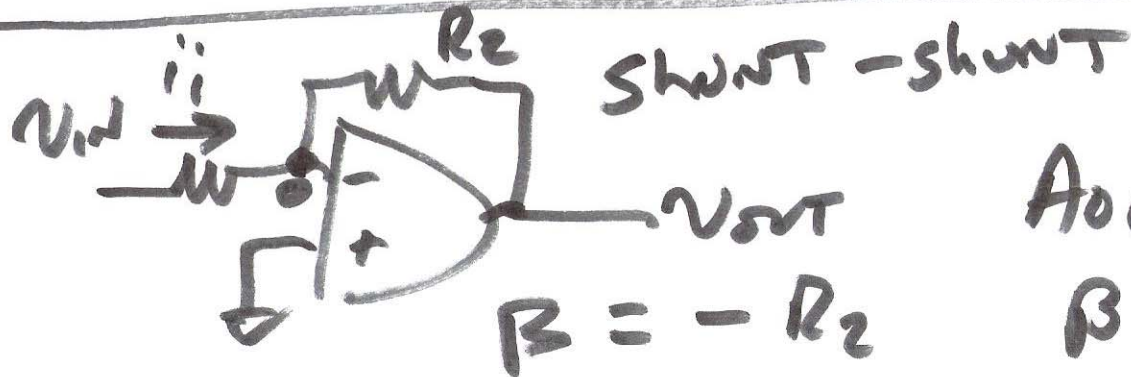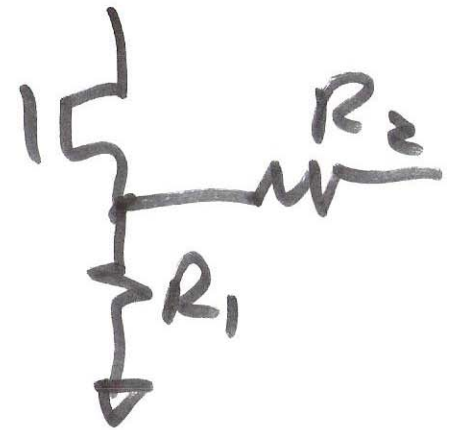


$A_{OL} \cdot B = POS.$

A_{OL} is NEG.

B NEG



4)

Calculate A_{OL}

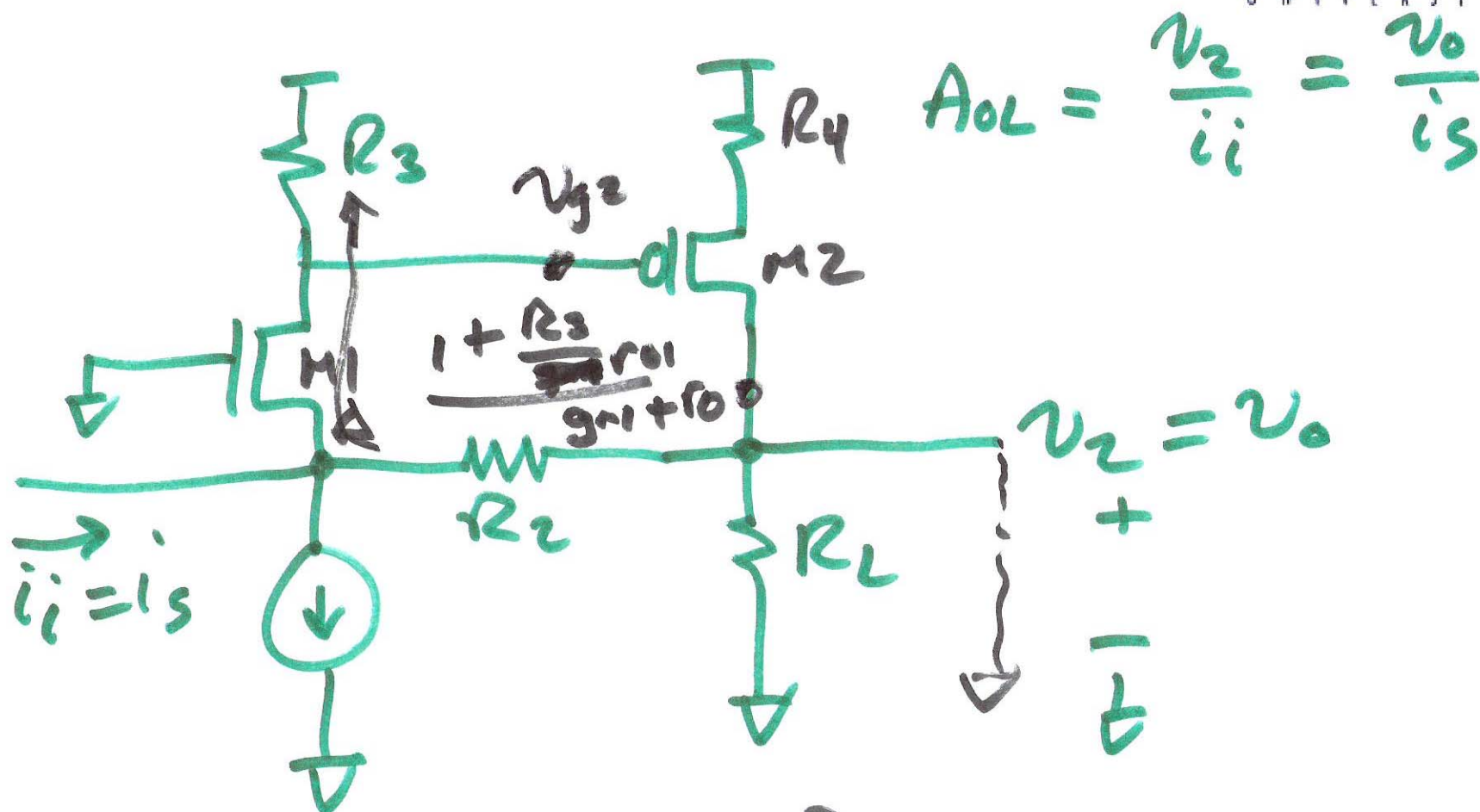

$$\frac{v_2}{v_{g2}} = \frac{-R_L \parallel R_2}{R_4 + \frac{1}{g_{m2}}}$$

5)

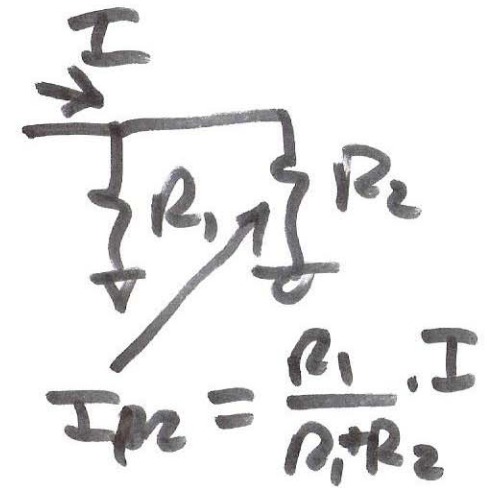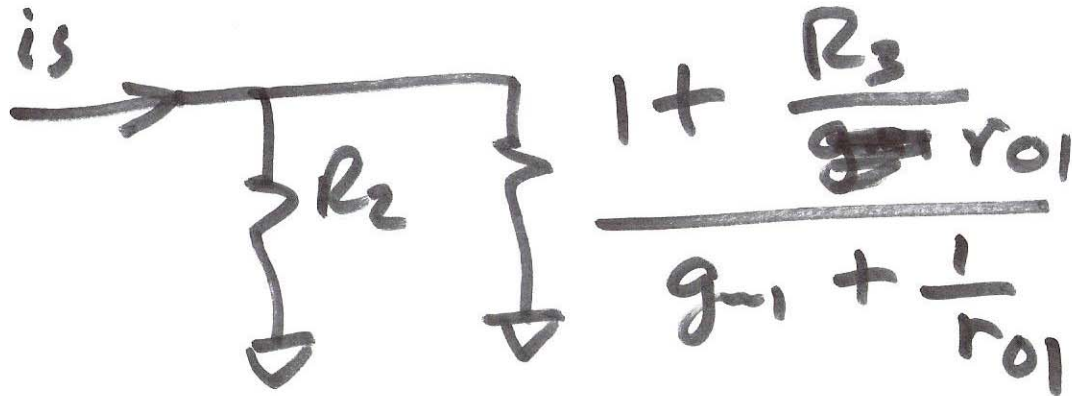

$$(R_3 \cdot i_d) = v_{g2} = i_s \cdot \frac{R_2 \cdot R_3}{R_2 + \frac{1 + \frac{R_3}{r_{o1}}}{g_{m1} + \frac{1}{r_{o1}}}}$$

6)


$$\frac{v_{g2}}{i_s} = \frac{R_2 \cdot R_3}{R_2 + 1 + \frac{R_3}{r_{o1}}}$$
$$g_{m1} + \frac{1}{r_{o1}}$$

$$\frac{v_2}{v_{g2}} = \frac{-R_L \parallel R_2}{R_4 + \frac{1}{g_{m2}}}$$

$$A_{vL} = \frac{v_2}{i_s} = \frac{v_o}{i_i} = \frac{-R_L \parallel R_2}{R_4 + \frac{1}{g_{m2}}} \cdot \frac{R_2 R_3}{R_2 + 1 + \frac{R_3}{r_{o1}}}$$
$$g_{m1} + \frac{1}{r_{o1}}$$

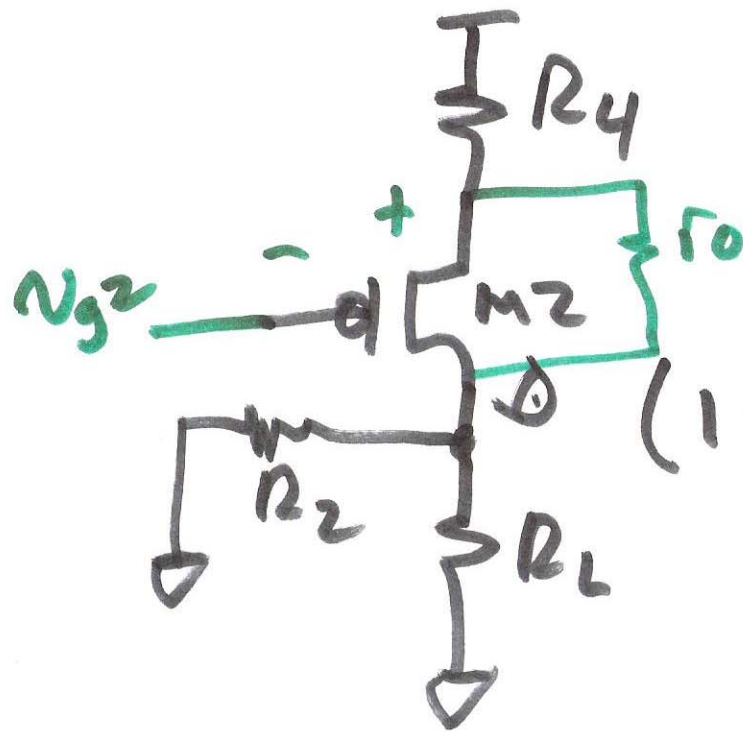7)

$$A_{OL} = \frac{v_2}{v_{g2}} \cdot \frac{v_{g2}}{v_1} \cdot \frac{v_1}{i_s}$$




$$\frac{v_2}{v_{g2}} = \frac{-R_L \parallel R_2 \parallel [(1 + g_{m2} R_4) \cdot r_o + R_4]}{\frac{R_4}{g_{m2} r_o} + \frac{1}{g_{m2}} + R_4}$$

$$(1 + g_{m2} R_4) \cdot r_o + R_4 \quad \text{EQ (20.53)}$$


$$\frac{v_{g2}}{v_1}$$

8)

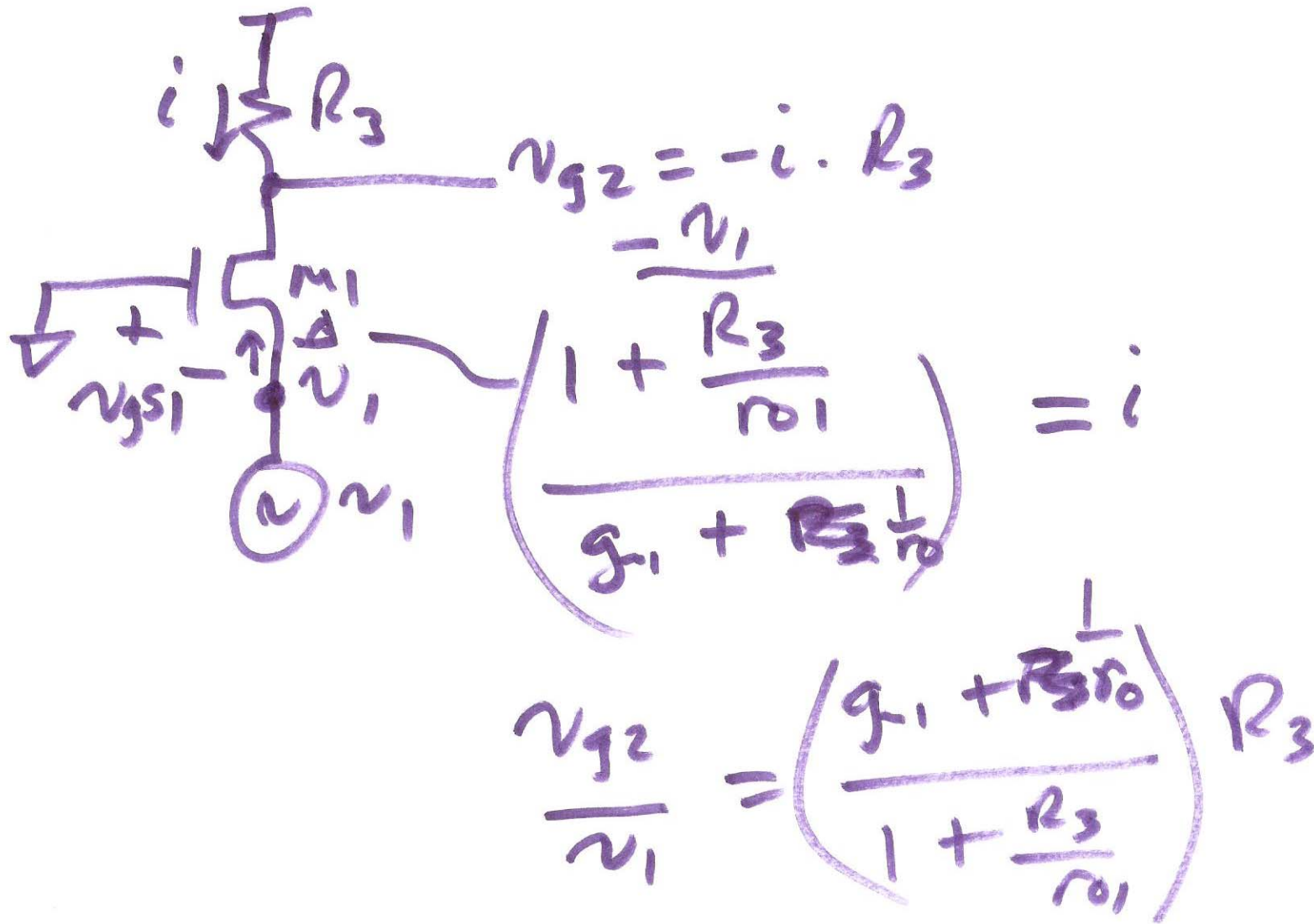

9)


$$\frac{v_1}{i_s}$$

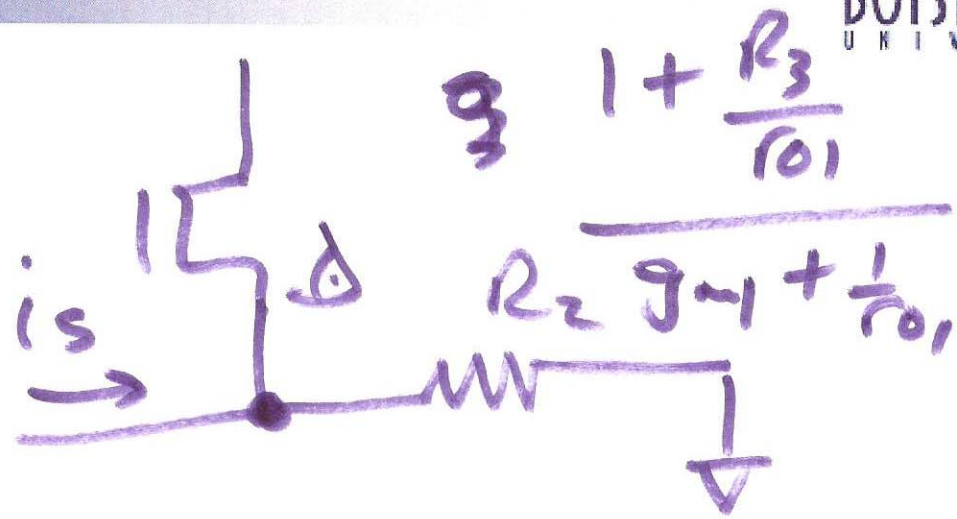


$$\frac{v_1}{i_s} = R_2 \parallel \left(\frac{1 + \frac{R_3}{r_{o1}}}{g_{m1} + \frac{1}{r_{o1}}} \right)$$

~~R_s~~ $\beta = -\frac{1}{R_2}$

Shunt-shunt f.b.

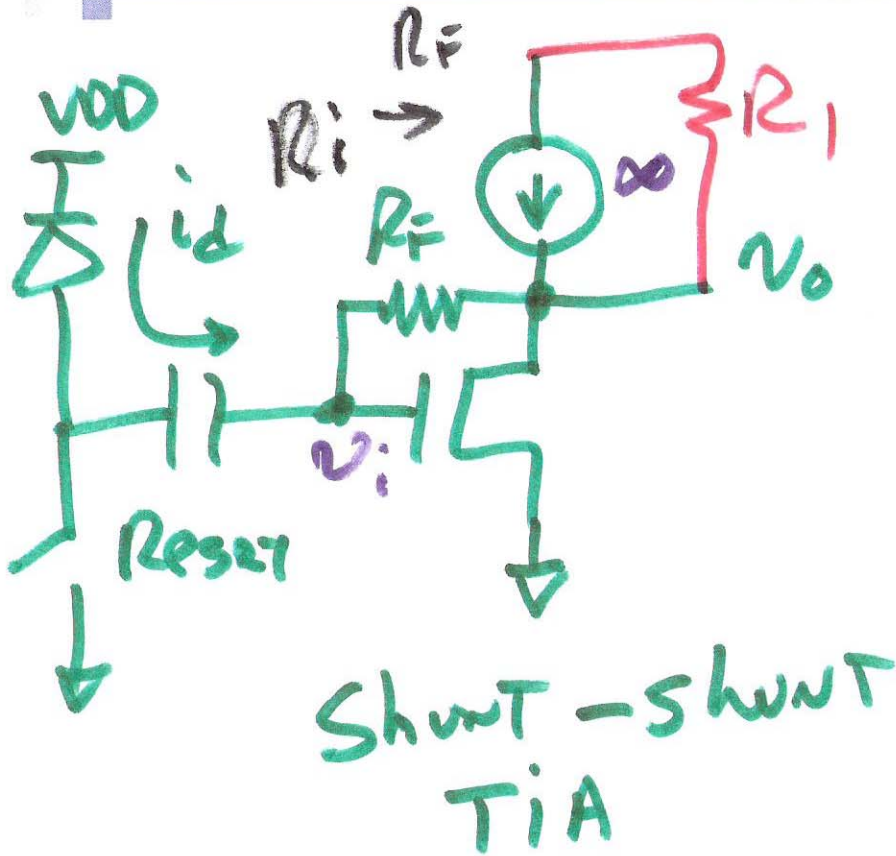


$$A_{OL} = \frac{v_o}{i_d}$$

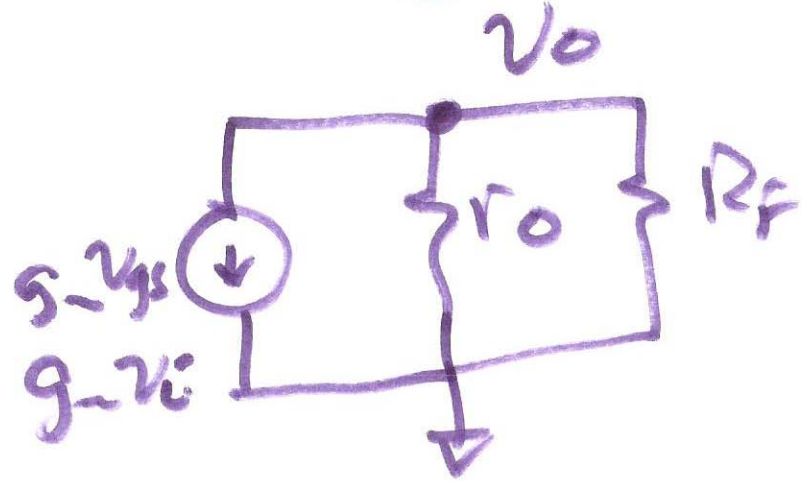

$$v_o = -g_m v_i \cdot (r_o \parallel R_f)$$
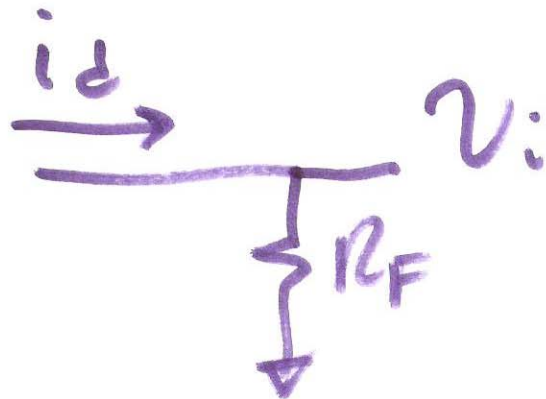
$$A_{OL} = -g_m R_f (r_o \parallel R_f \parallel R_i)$$




$$v_i = i_d \cdot R_f$$

$$A_{OL} = \frac{v_o}{i_d} = -g_m R_f (r_o \parallel R_f)$$

ii)

$r_o = \infty$

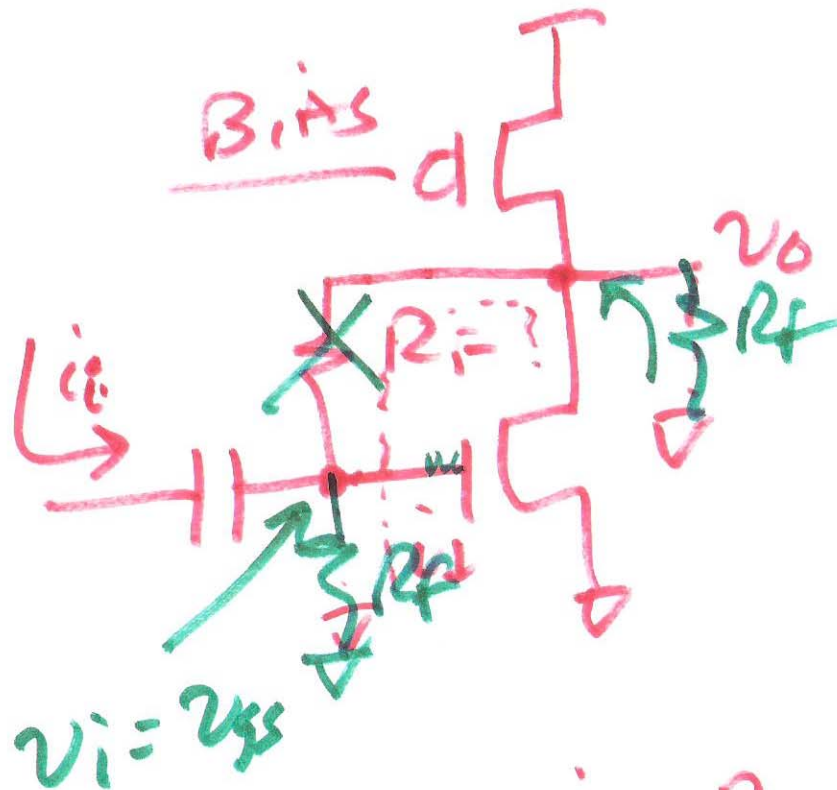$A_{OL} = \frac{v_o}{v_i} = \frac{-i_i R_F}{i_i}$




$A_{OL} = \frac{v_o}{v_i} \cdot \frac{v_i}{i_i} = \frac{-i_i R_F}{i_i R_F} = -\frac{g_m v_{gs} R_F}{v_i}$



$v_{gs} = i_i \cdot R_F$
 $i_d = i_i$
 $i_d = g_m \cdot v_{gs}$

$v_{gs} = g_m v_{gs} \cdot R_F$
 $1 = g_m \cdot R_F$

12)

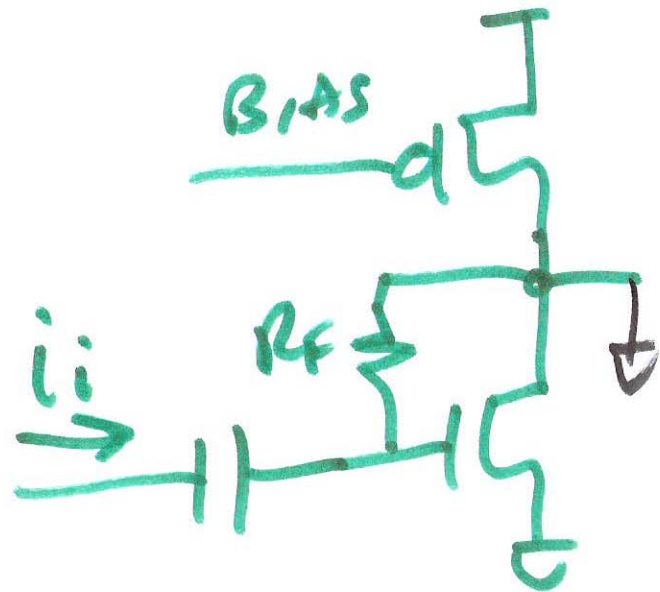

$R_D = \infty$ open loop

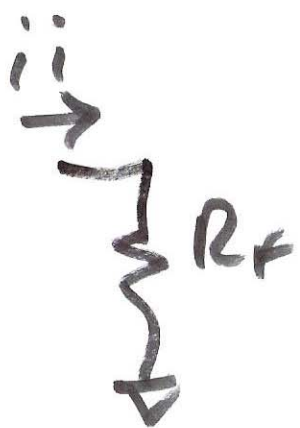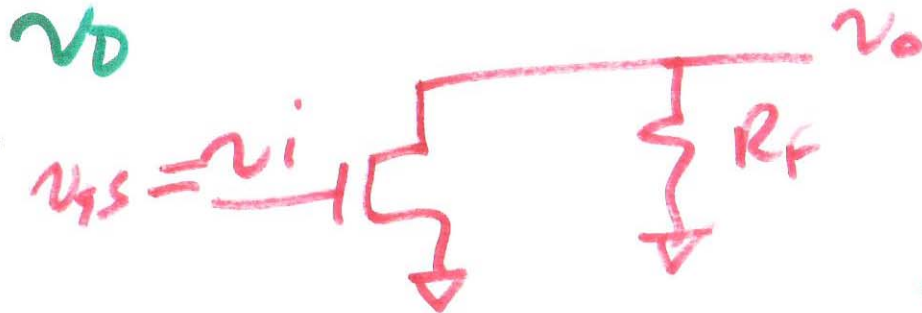

$$v_{gs} = i_i \cdot R_f = v_i$$

$$\frac{v_i}{i_i} = R_f$$

$$\beta = -\frac{1}{R_f}$$

$$\frac{v_o}{v_i} = \frac{-i_d \cdot R_f}{v_i}$$

$$= \frac{-g_m v_{gs} R_f}{v_{gs}}$$

$$\boxed{\frac{v_o}{v_i} = -g_m R_f}$$

$$A_{OL} = -g_m R_f^2 = \frac{v_o}{i_i}$$


13)

$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL} - g_m R_F^2}$$
$$= \frac{1}{1 + \left(-\frac{1}{R_F}\right) \left(-g_m R_F^2\right)}$$

$$A_{CL} \approx \frac{1}{\beta} = \frac{-g_m R_F^2}{1 + g_m R_F}$$

$$g_m R_F \gg 1 \quad \boxed{A_{CL} \approx -R_F}$$

14)

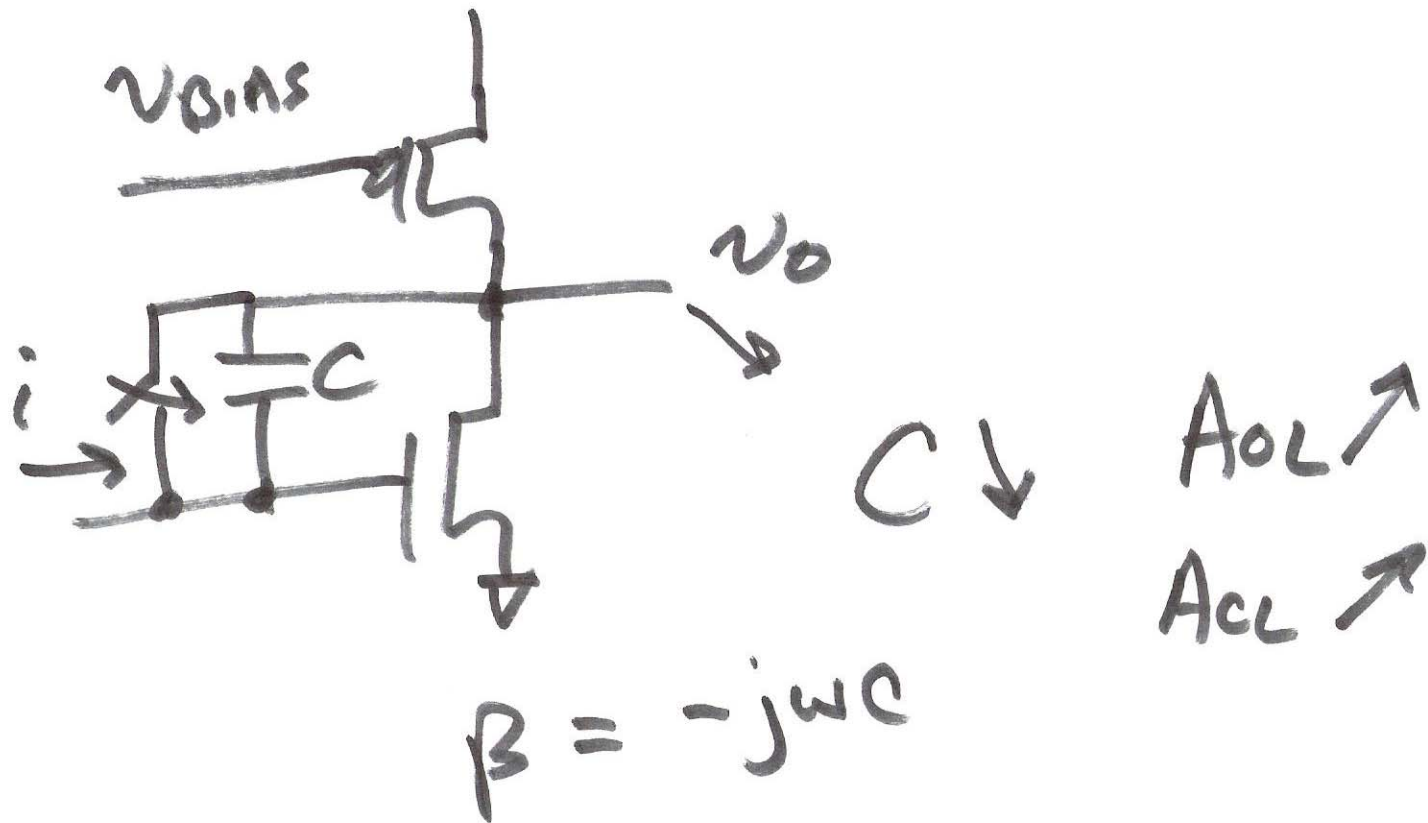

Series - series
 → Voltage - current ←

15)