

Sept. 6, 2011

Lecture 6

TRANSCONDUCTANCE

$$A_{OL} = \frac{i_o}{v_s} \text{ n.f.b.}$$

r_o is big comp. to 10K

$$\beta_{io} = v_f$$


series

$$\frac{167K}{4}$$


$$\beta = -10K \Omega = -\frac{r_o}{4} \parallel 10K$$

$$R_{pi} \approx 10K$$

$$R_{so} \approx 10K$$

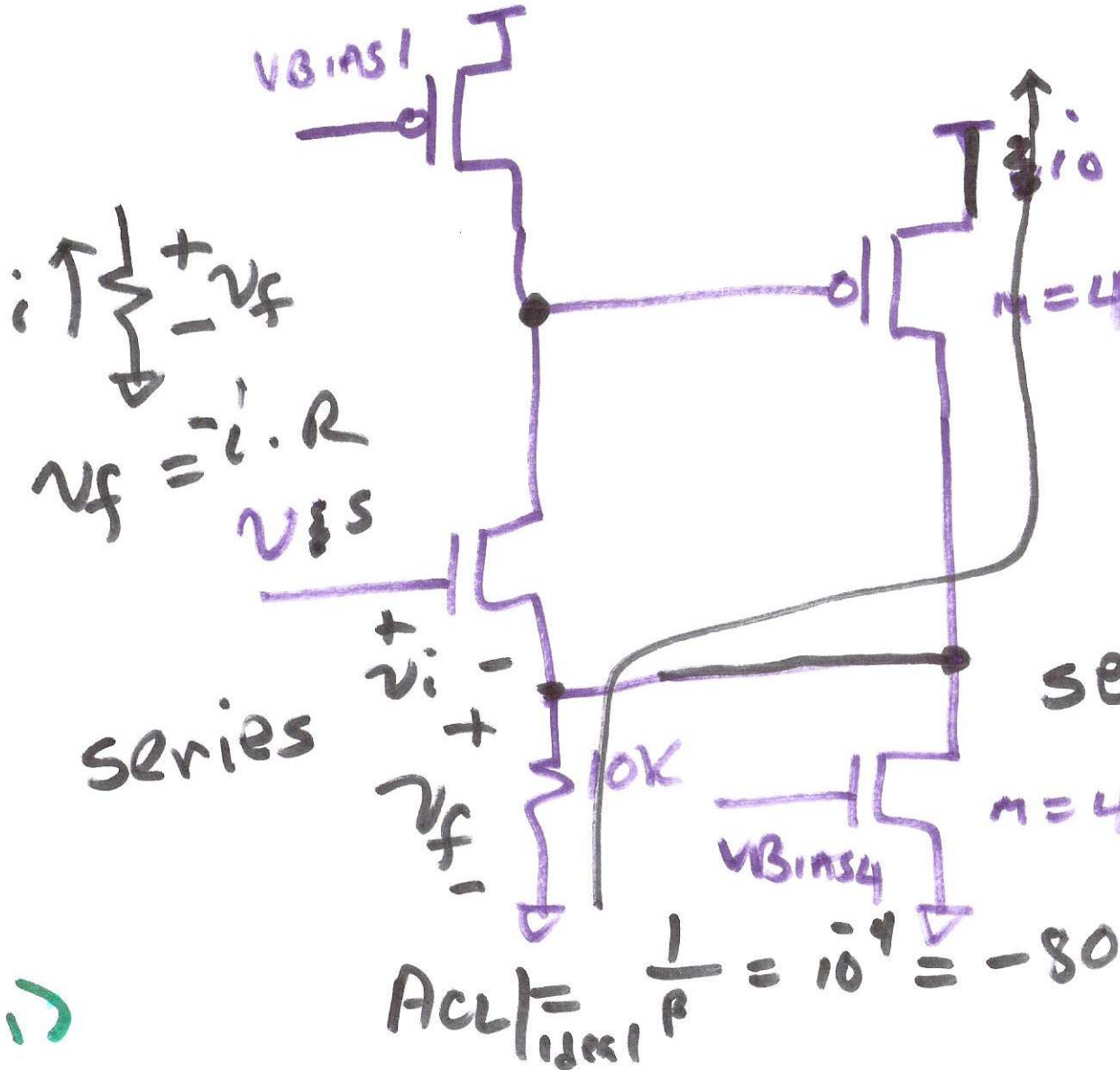

→

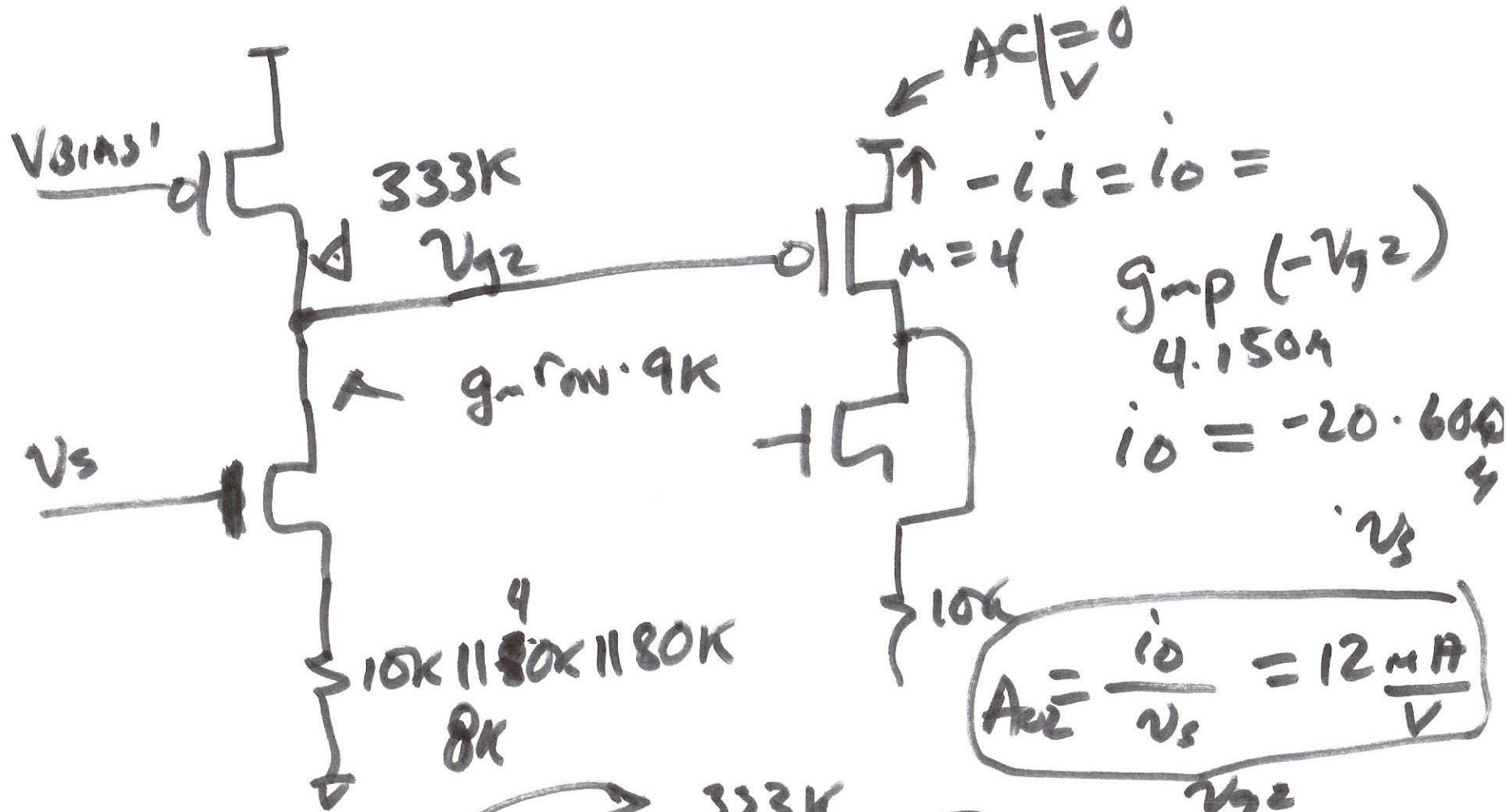


$$\frac{v_{g2}}{v_s} = \frac{-333K}{8K + 65K} \cdot \frac{400}{500} \approx -20 = \frac{v_{g2}}{v_s}$$

2)

$$\beta = -10K \quad A_{OL} = 12mA/V$$


$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}}$$
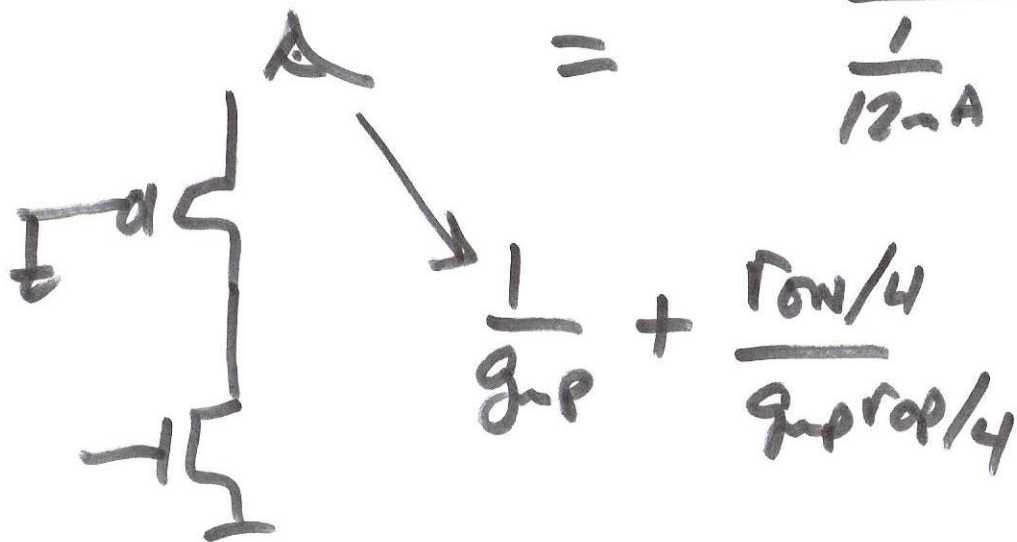
$$= \frac{1}{\frac{1}{12mA} - 10K} \approx -\frac{1}{10K} = -$$



80dB $\angle 180^\circ$

3)

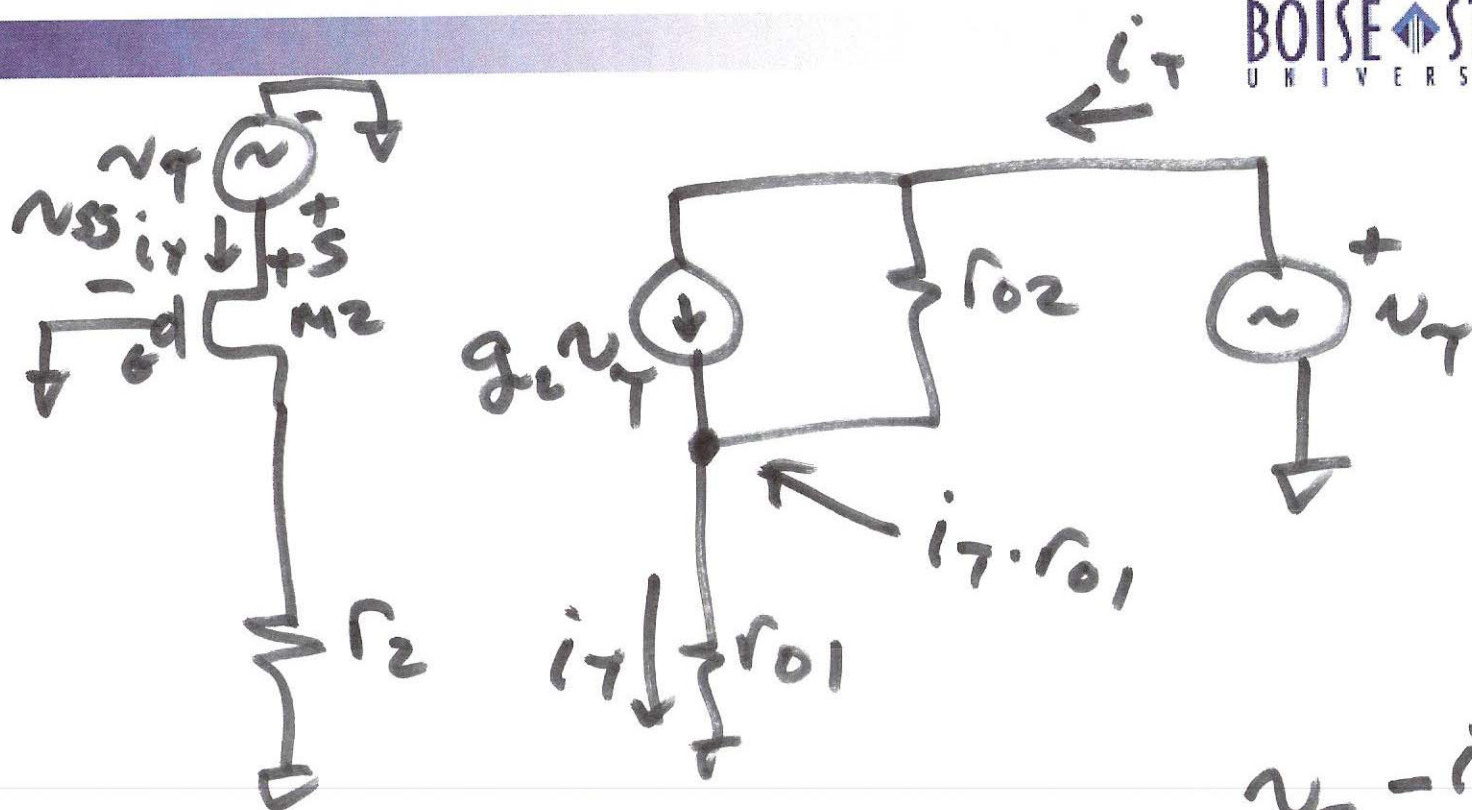


$$v_T = v_{sg}$$

$$i_T = g_{m2} v_T + \frac{v_T - i_T r_{o1}}{r_{o2}}$$

$$i_T \left(1 + \frac{r_{o1}}{r_{o2}} \right) = v_T \left(g_{m2} + \frac{1}{r_{o2}} \right)$$
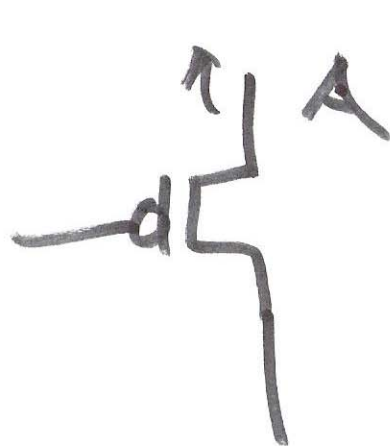
$$4) \quad \frac{v_T}{i_T} = \frac{1 + \frac{r_{o1}}{r_{o2}}}{g_{m2} + \frac{1}{r_{o2}}} \approx \frac{2}{g_{m2}}$$



$$\frac{2}{g_{m2}} = R_o$$

$$g_{m2} = \frac{1}{150\mu \cdot 4} \approx 1.2k$$

$$R_o \approx 2.5k$$

$$R_{of} = (1 + \beta A_{ol}) \cdot 2.5k$$

$$R_{of} = 2.5k \cdot 121$$


$$\approx 300k$$

$$\beta \cdot A_{ol} = \frac{12\mu A \cdot 10k}{1\mu A}$$

$$\beta A_{ol} \approx 1.2 \cdot 10^6$$

$$1 + \beta A_{ol} = 121$$

5)

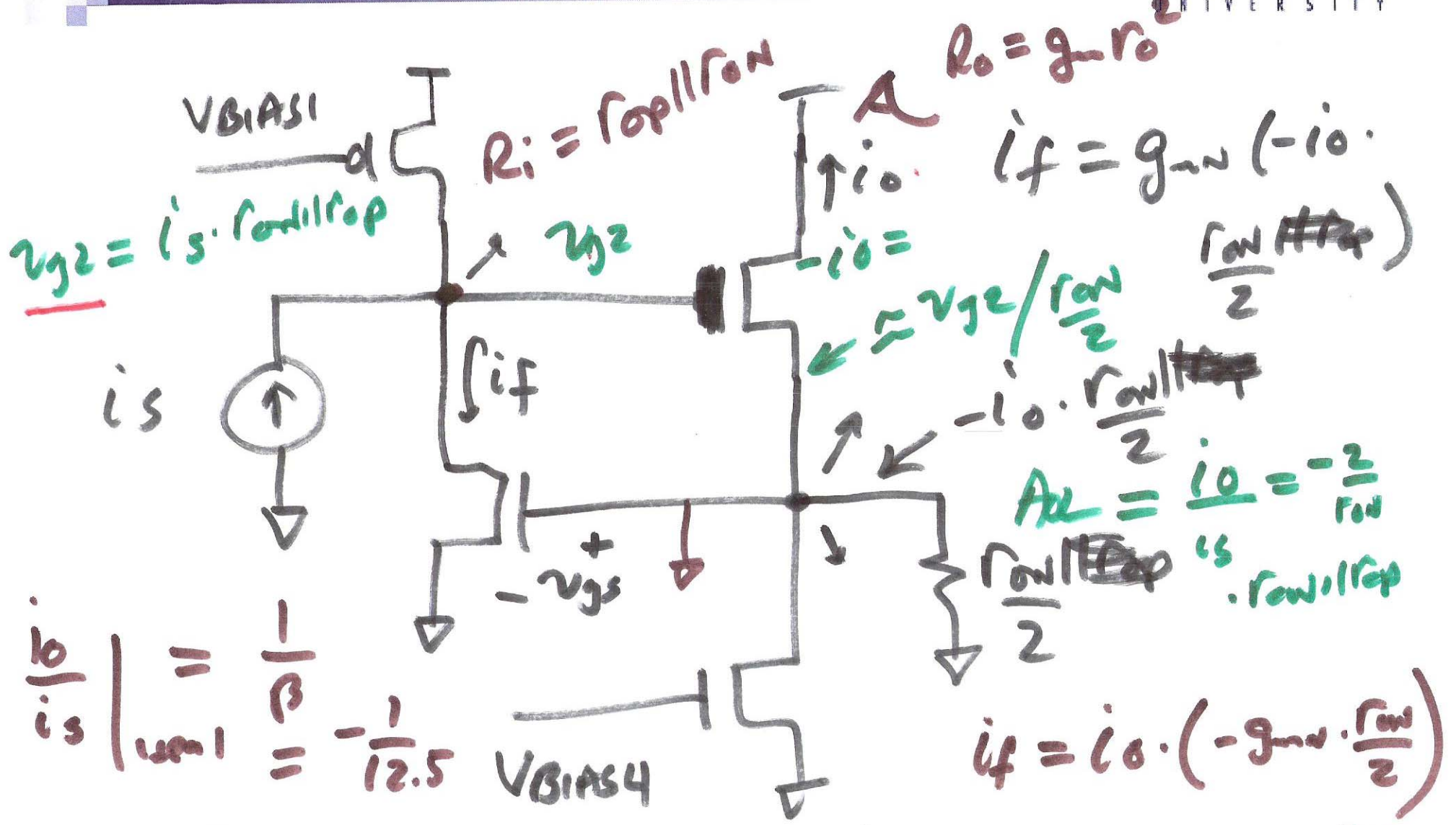

$\frac{i_o}{i_s} \Big|_{v_{gs}=0} = \frac{1}{\beta} = -\frac{1}{12.5}$

$A_{cl} = \underline{\underline{-0.08}}$ SHUNT CURRENT

SERIES CURRENT

$\beta = -g_m \cdot \frac{r_{on}}{2}$
 $\beta = -12.5$

6)

$$A_{OL} = -\frac{2}{r_{on}} \cdot r_{on} \parallel r_{op}$$

$$= -\frac{2}{167k} \cdot 167k \parallel 333k$$

$A_{OL} = \underline{\underline{g_{mp} \cdot r_{on} \parallel r_{op}}}$

$$\approx 1.5 \frac{A}{A}$$

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL} \cdot B} = \frac{1}{\frac{1}{1.5} + \frac{1}{12.5}}$$

$$R_i = \frac{R_{op} \parallel r_{on}}{1 + \frac{1}{12.5} \cdot 1.5} = \frac{20k}{10k} \approx \frac{1}{12.5} = -0.08$$

$$R_o = \underline{\underline{g_{ro}^2 (1 + B A_{OL})}} = \underline{\underline{1 \mu S}}$$

→