

Design and Operation of Delta-Sigma ADCs


ECE614 Advanced Analog IC Design


Joshua Nekl

May 5, 2008


What is a Delta-Sigma ADC

 - AKA Sigma-Delta ADC, over-sampling ADC, noise-shaping ADC, 1-bit ADC
- Integrates (Sigma) the difference (Delta) between the quantized output and the input



 

$\Delta\Sigma$ ADC

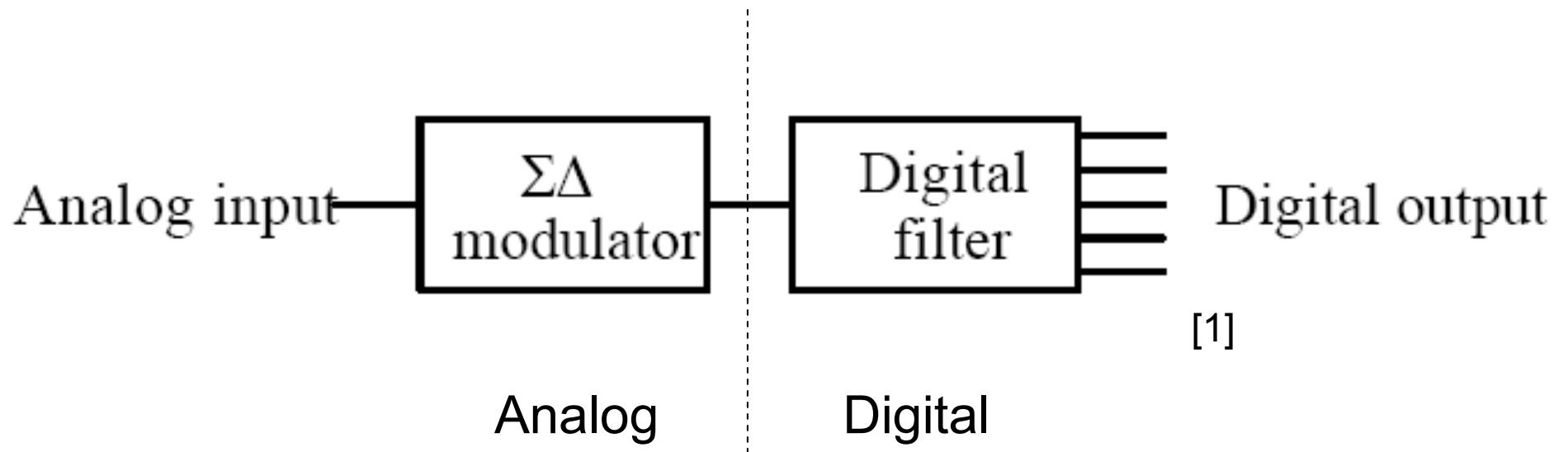


Benefits


- No precision matched analog components
- High achievable accuracy
- Low-pass filtering

Drawbacks


- Slower conversion time
- DC input current / resistive input impedance

Simple Modulator

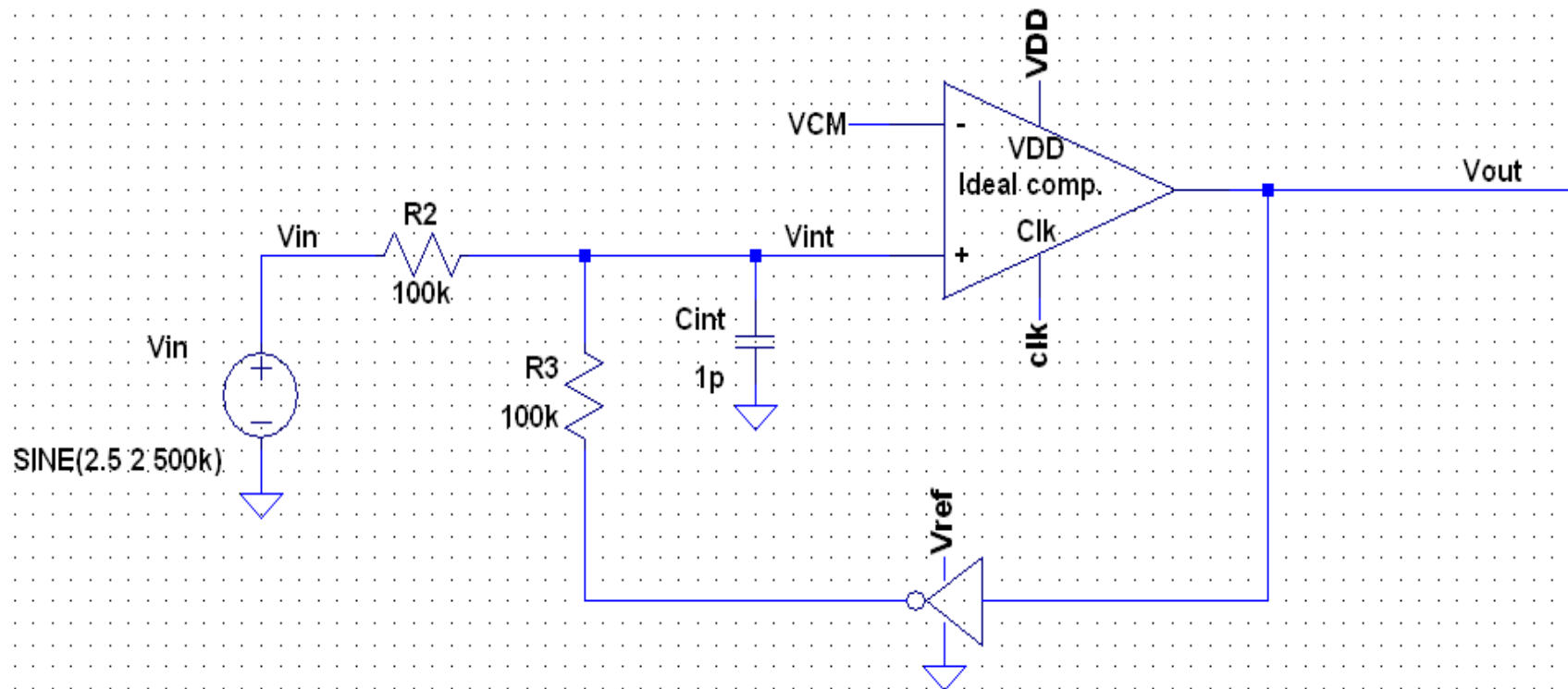

 

Modulator Output

 

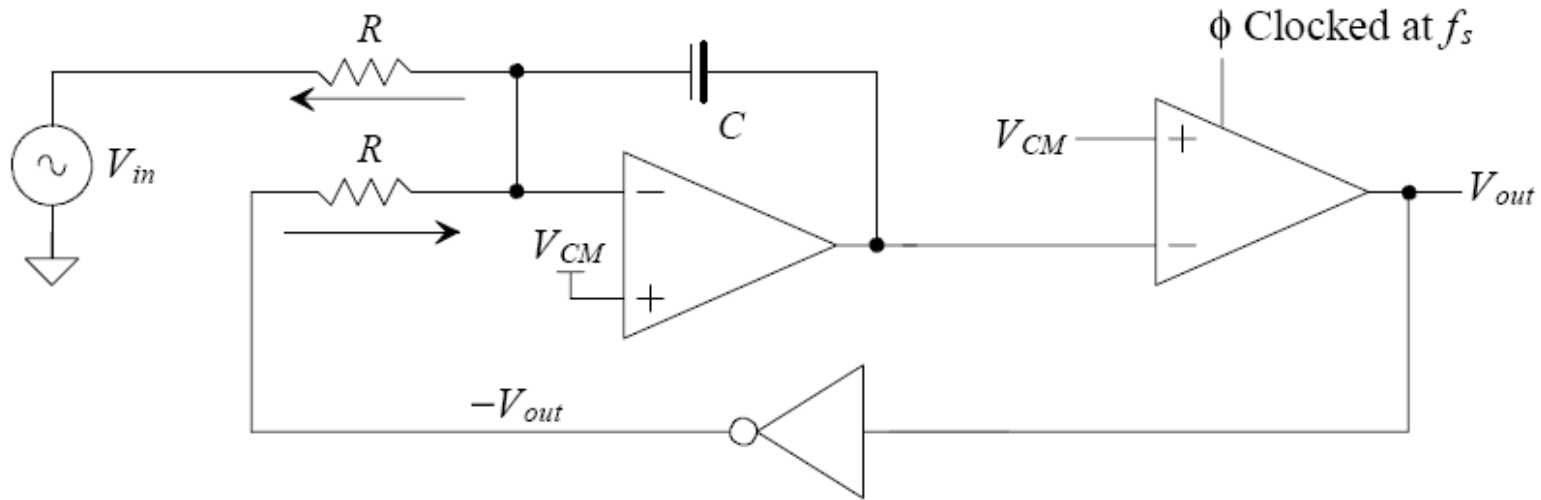


Figure 32.24 Analog circuit implementation of a first-order NS modulator. [2]


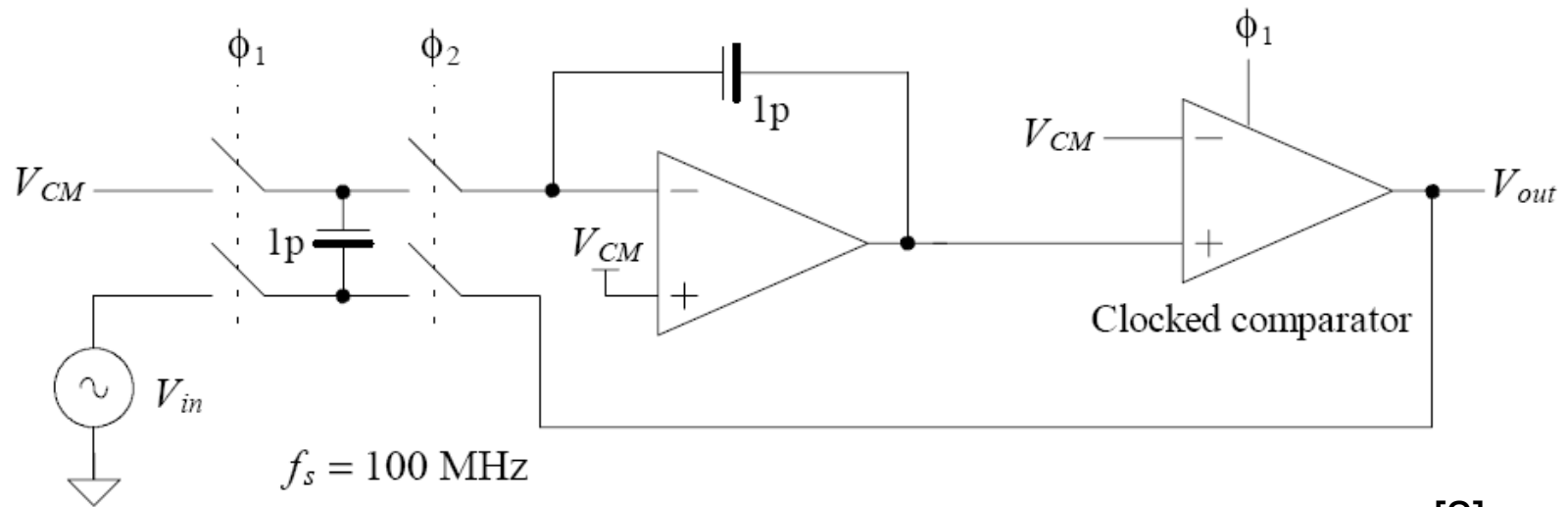


Figure 32.7 Circuit implementation of a first-order NS modulator. [2]

 

Feedback DAC Transfer Curve


 
 
 



Figure 32.25 Comparator output pulse shapes, input to the integrator.

[2]

 

Quantizer


Comparator

 


1-bit ADC


[1]

Offset Cancellation

 


 

Comparator Decision Errors

 


Noise Shaping

 

$$OUT = IN \frac{1}{1 + \frac{s}{A}} + Q_e \frac{s/A}{1 + \frac{s}{A}}$$


STF
NTF

 


$$OUT = IN \frac{1}{1 + \frac{s}{A}} + Q_e \frac{s/A}{1 + \frac{s}{A}}$$

STF *NTF*

Low Pass Filter

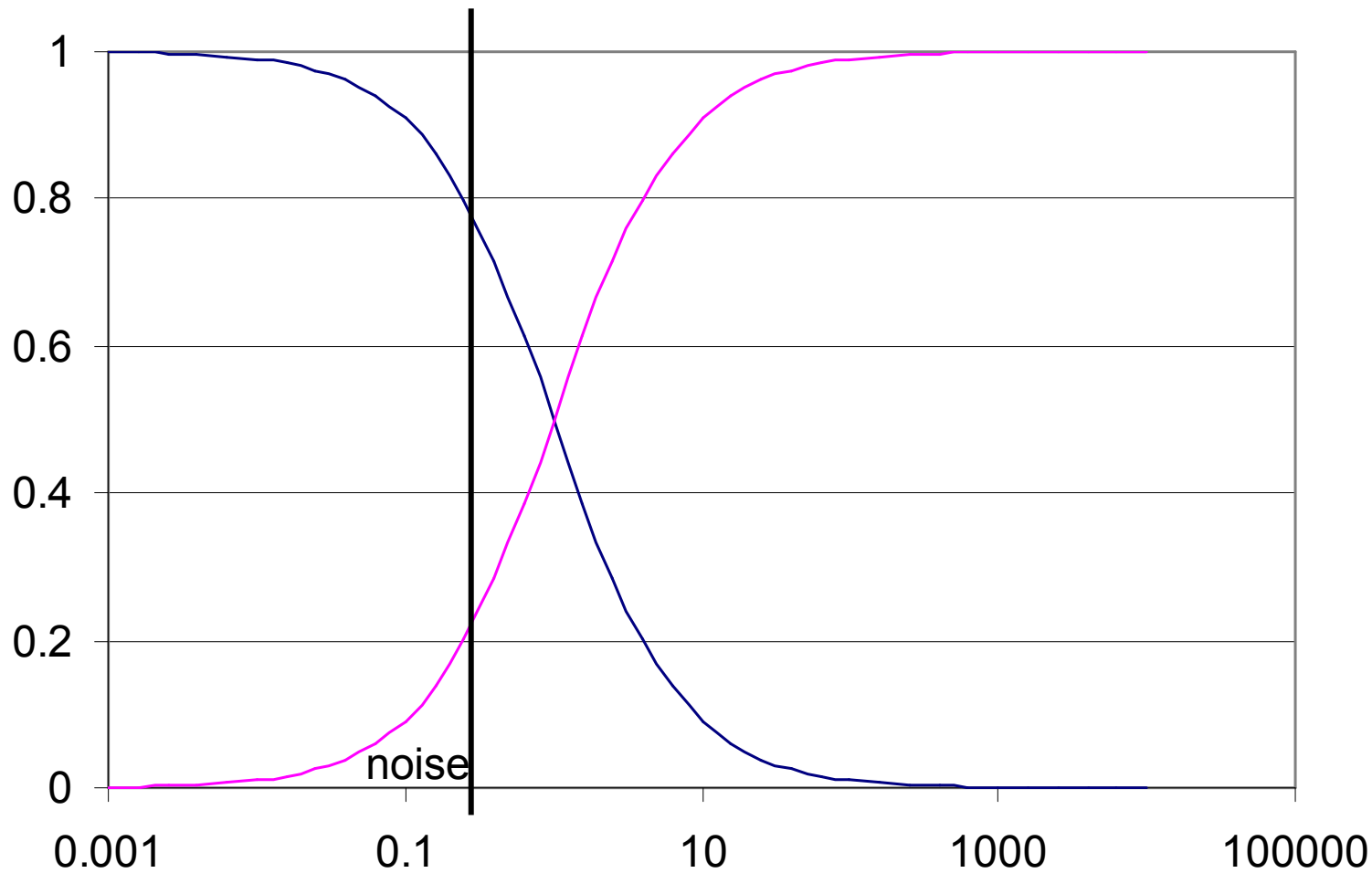

2nd order Modulator

 


$$OUT = IN \frac{1}{1 + \frac{s^2}{A_1 A_2} + \frac{s}{A_1} + 1} + Q_e \frac{s^2 / A_1 A_2}{1 + \frac{s^2}{A_1 A_2} + \frac{s}{A_1} + 1}$$

STF
NTF



Comparison of 1st & 2nd order modulator

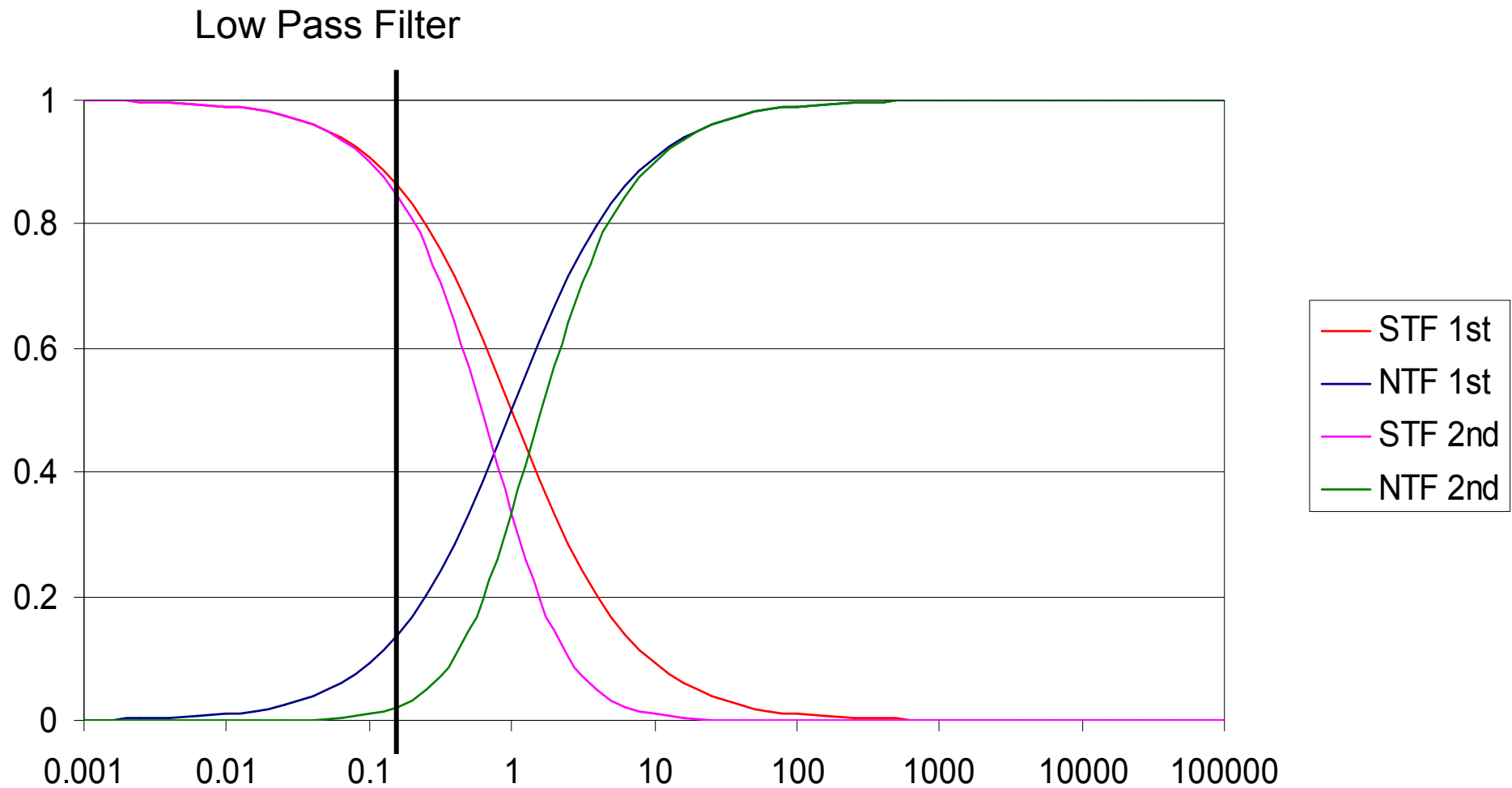


Speed vs Resolution

Analog Devices - AD7732


Table 5. Typical Effective Resolution in Bits vs. Conversion Time and Input Range with Chopping Enabled

FW	Conversion Time Register	Conversion Time (μ s)	Output Data Rate (Hz)	-3 dB Frequency (Hz)	Input Range/Effective Resolution (Bits)			
					± 10 V	0 V to +10 V	± 5 V	0 V to +5 V
127	FFh	2686	372	200	21.0	20.0	20.0	19.0
46	A Eh	999	1001	520	20.3	19.3	19.3	18.3
22	96h	499	2005	1040	19.7	18.7	18.7	17.7
17	91h	395	2534	1300	19.5	18.5	18.5	17.5
8	88h	207	4826	2500	19.0	18.0	18.0	17.0
6	86h	166	6041	3100	18.7	17.7	17.7	16.7
2	82h	82	12166	6300	17.3	16.3	16.3	15.3

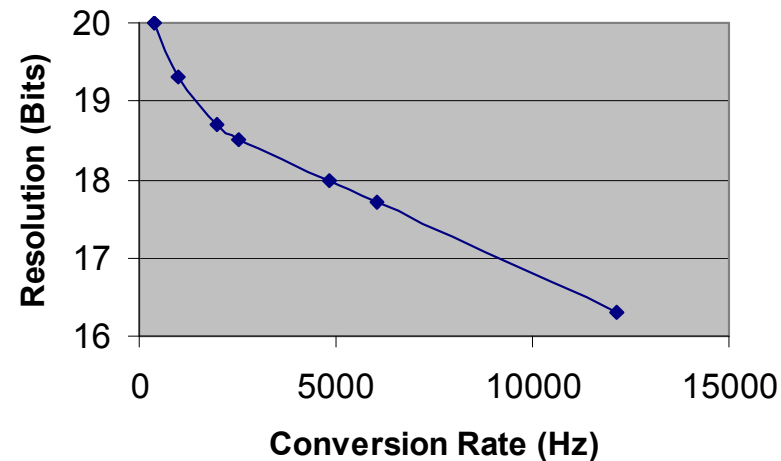

Low Pass Digital Filter

Simple Counter

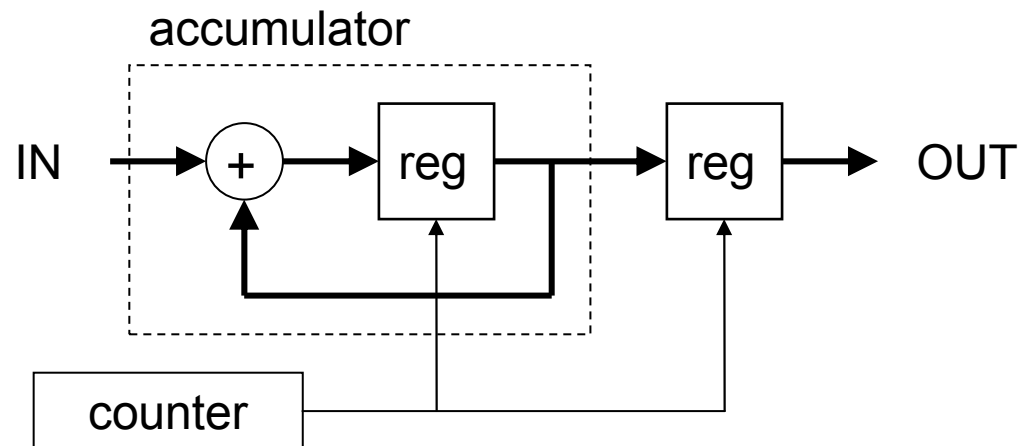


z-Transform

$$z = e^{j2\pi f T_s} = e^{j2\pi \frac{f}{f_s}}$$

$$y[n] = x[n] + x[n-1] + x[n-2] + \dots + x[n-(K-1)]$$


$$Y(z) = X(z) \cdot (1 + z^{-1} + z^{-2} + \dots + z^{-(K-1)}) \cdot \frac{1 - z^{-1}}{1 - z^{-1}}$$
 
$$H(z) = \frac{Y(z)}{X(z)} = \frac{1 - z^{-K}}{1 - z^{-1}}$$




[2]

Figure 31.40 Frequency response of the accumulate-and-dump for various values of K .

 

Types of Digital Filters

 - Higher Order Sinc Filters
- FIR filters
- BiQuad Filters




References

- [1] Baker, R. Jacob, CMOS: Circuit Design, Layout, and Simulation
- [2] Baker, R. Jacob, CMOS: Mixed-Signal Circuit Design
- [3] Analog Devices AD7732 Datasheet



Questions?

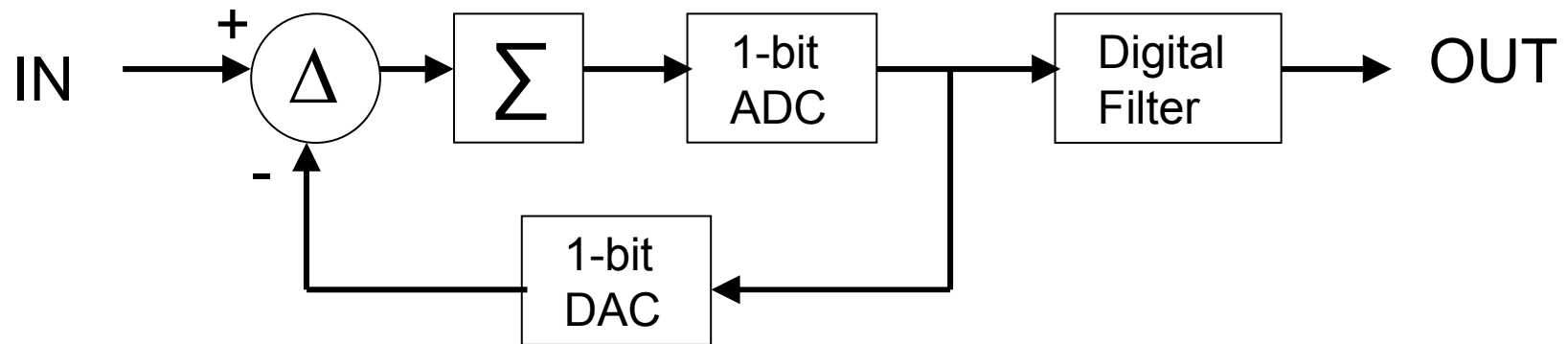


Design and operation of folding ADCs

ECE 614 Student Presentation
By Kaijun Li
May 5, 2008

Outline

 - Miscellaneous ADC
- Interpolating ADC
- Folding ADC
- Folding & Interpolation
- Simulation
- Conclusion



Miscellaneous ADC


 


Fig. from ref.[2]

Various FOMs


 
$$\text{FOM} = \frac{2^N 2\text{BW}}{P}$$



Miscellaneous ADC

- Trade-offs between high conversion rate and high resolution
- Latency concerns
- Complexity of the CMOS circuitry


Flash ADC

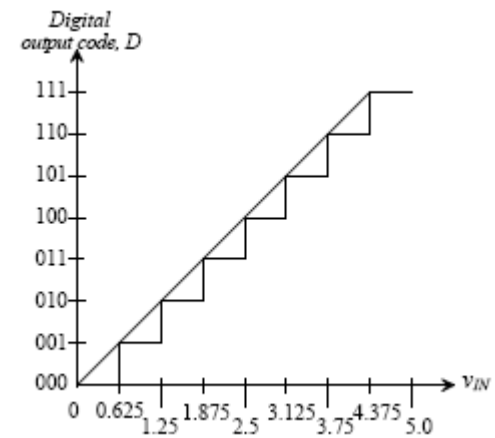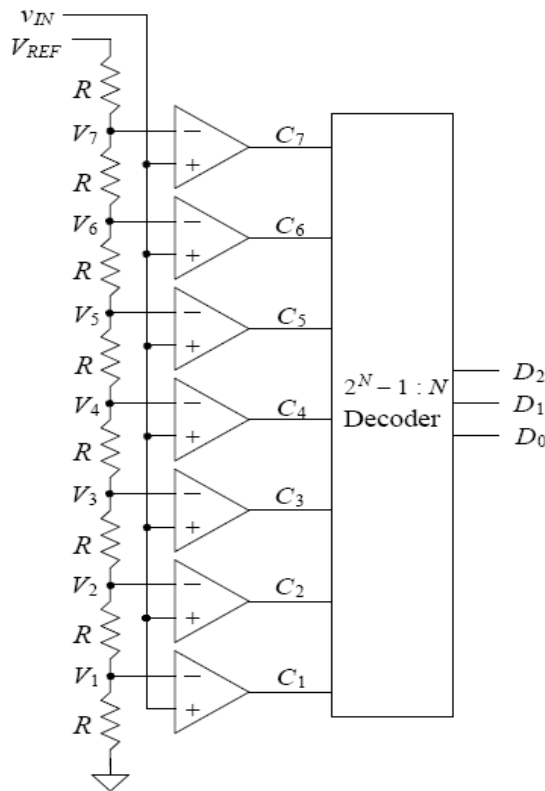

Undoubtedly the simplest ADC
 Fastest conversion
 Largest amount of Preamps and comparators

Figure from [1]

Subranging (or Two-step) ADC

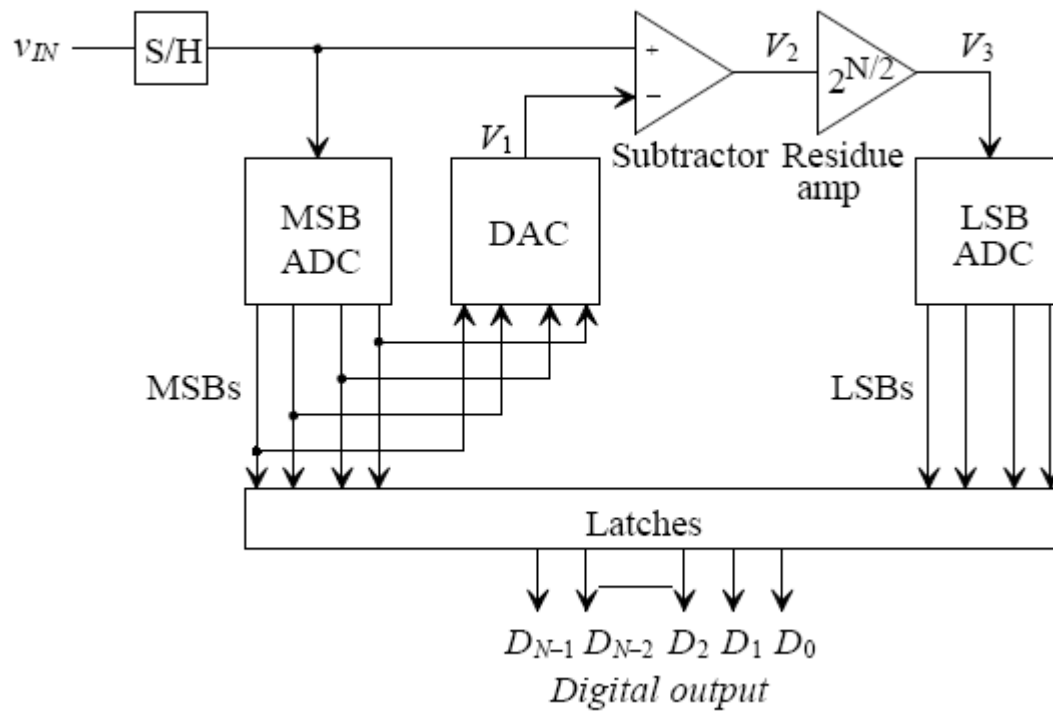

Less Comparators
 $2^N \rightarrow 2 \cdot 2^{N/2}$

Figure from [1]

Interpolating ADC



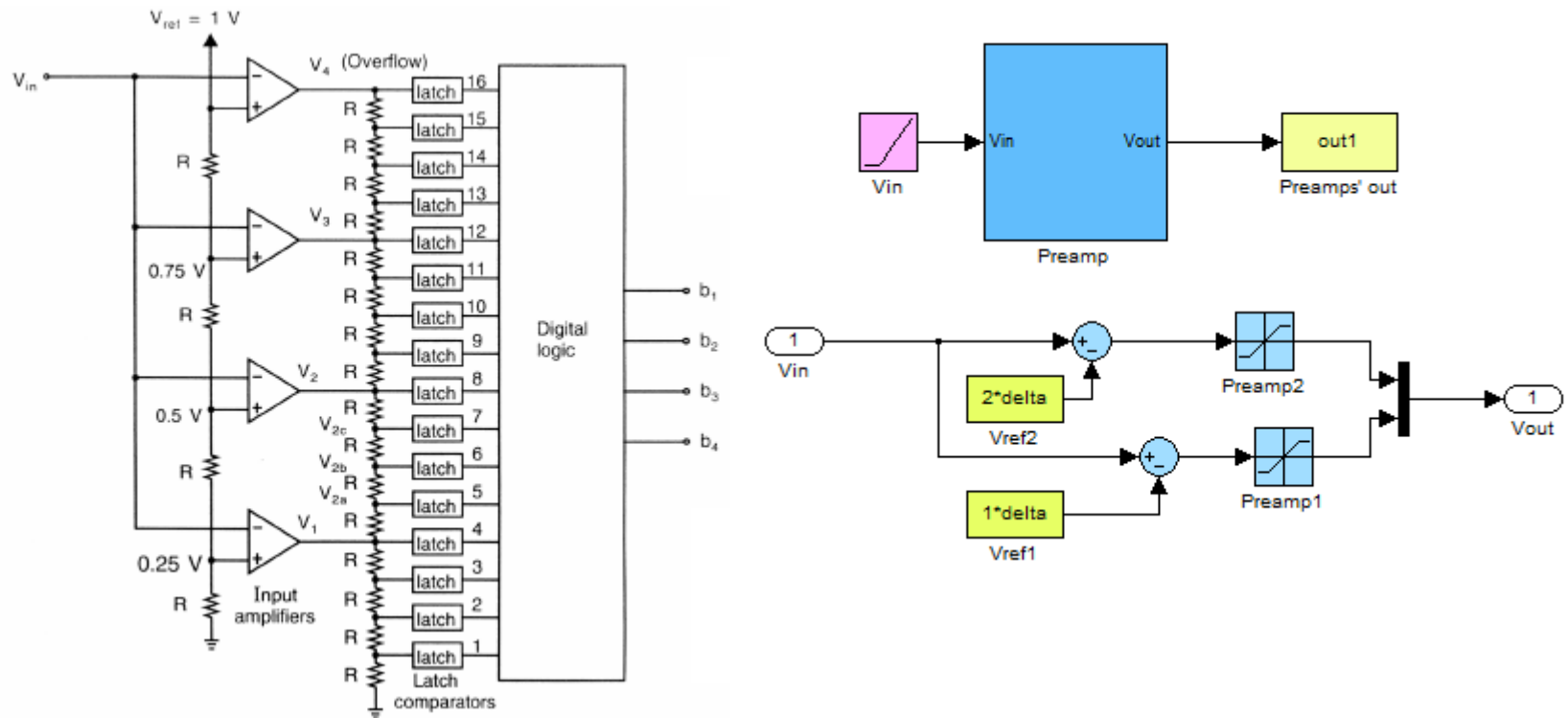
 
 


Figure from [4]

 

Interpolating ADC

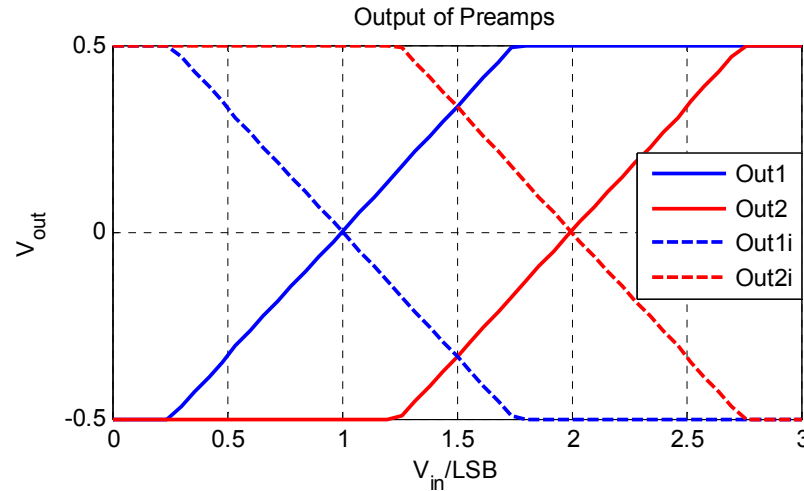

Less Comparators
Same amount of Latches

Figure from [2]

Higher order resistive interpolation




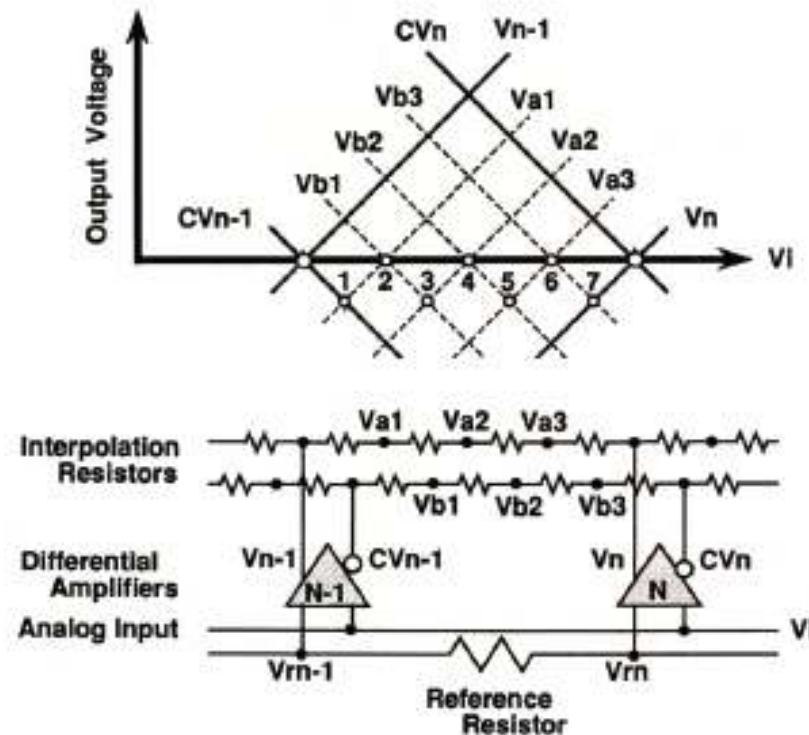
 


Figure from [5]

 

Transfer curves

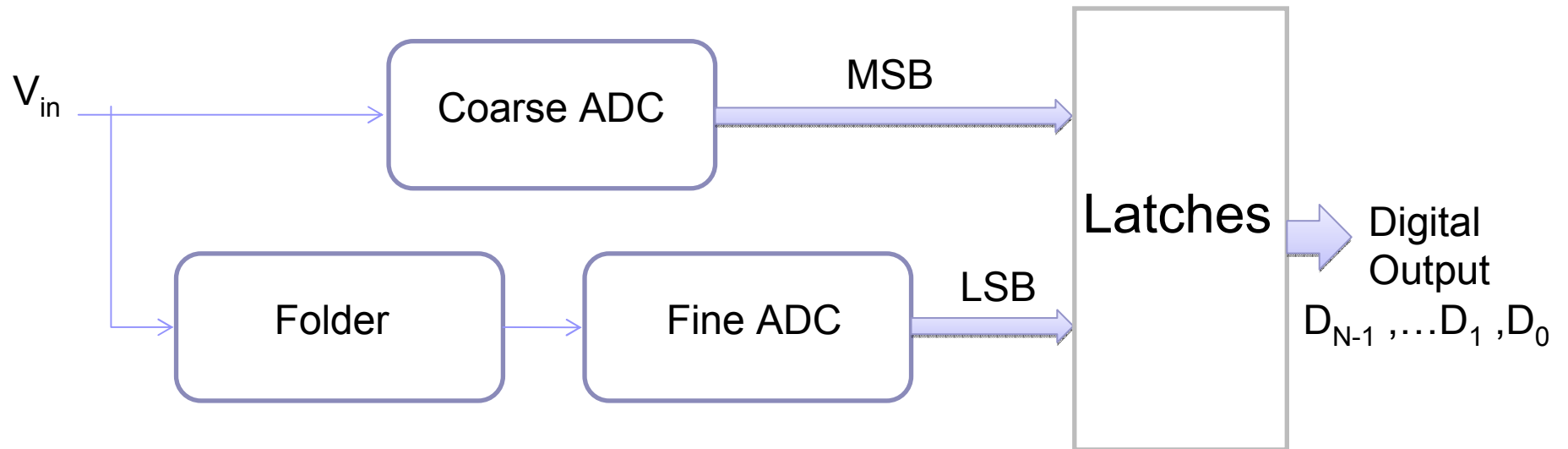

 

Realization of Folds via Source-Couple Pairs


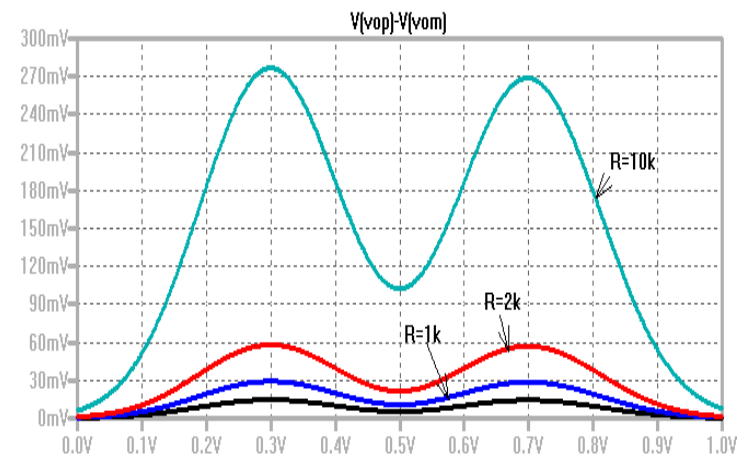
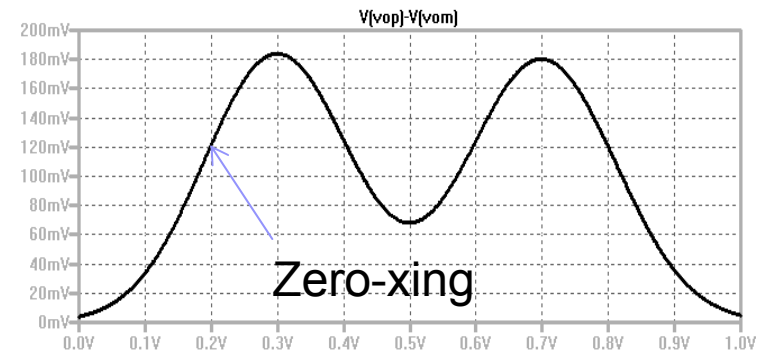
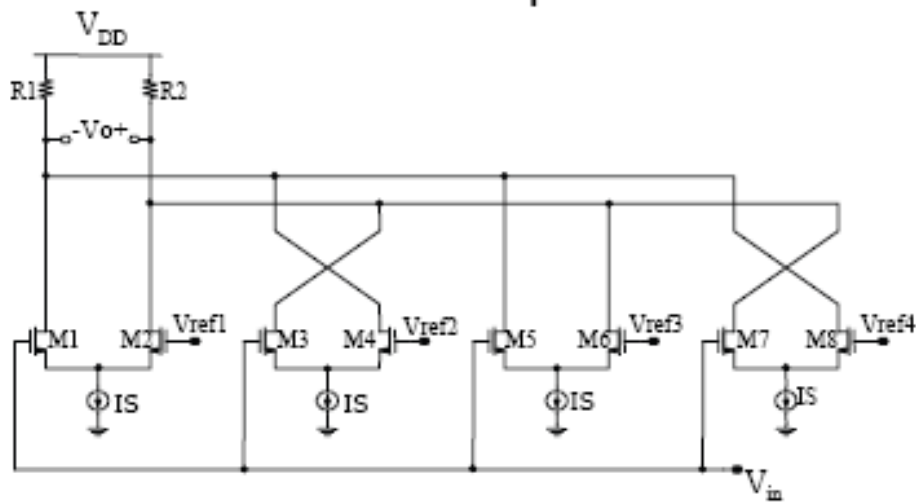


Figure from [2]

Folding & Interpolation

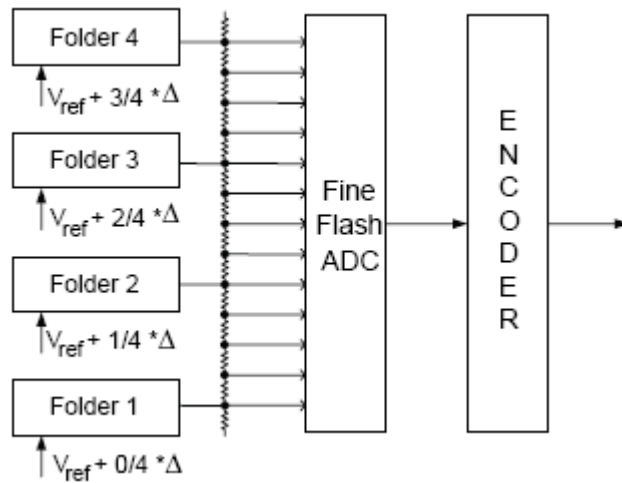

More practical, they are combined for application


 
 


Figure from [2]

LTSpice Simulation

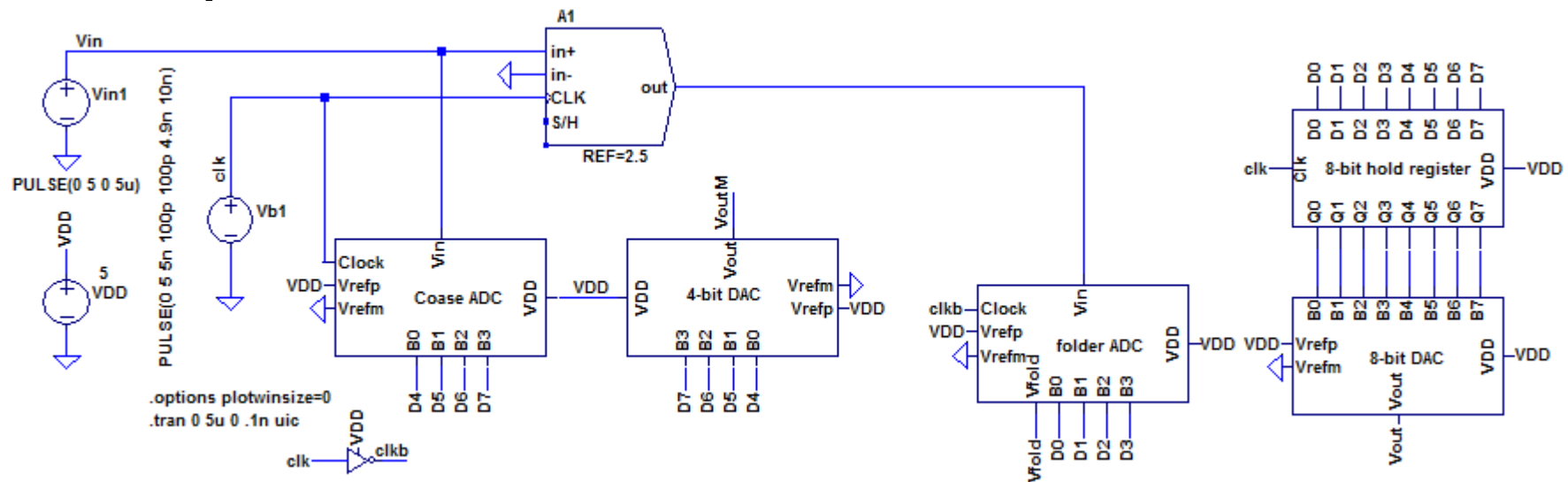


Conclusion

- Flash ADC, subranging (or two-step) ADC
- Interpolating and folding techniques
- Interpolating and folding ADC
- Simulation for illustration

References

 - [1] R. J. Baker, CMOS Circuit Design, Layout, and Simulation, Revised Second Edition, Wiley-IEEE, 2008
- [2] [http://webcast.berkeley.edu/EE 247](http://webcast.berkeley.edu/EE_247)
- [3] <http://www.analog.com>
- [4] Willy M.C. Sansen, Analog Design Essentials, Springer, 2006
- [5] H. Kimura et al, "A 10-b 300-MHz Interpolated-Parallel A/D Converter," JSSC April 1993, pp.438-446



Questions

