

# Design and Operation of Integrating ADCs

ECE614 - Advanced Analog IC Design  
Presented by Antonio Oblea  
May 7, 2008

## Integrating ADC Overview

- AKA ramp and slope ADC
  - Different flavors, e.g. single-slope and dual-slope
- Strengths<sup>[1],[2]</sup>
  - High resolution
  - High linearity
  - Relatively simple circuitry
  - Low-cost
- Weaknesses
  - Slow!
- Applications
  - Sensors, voltmeters, ammeters

# Single-slope ADC Operation


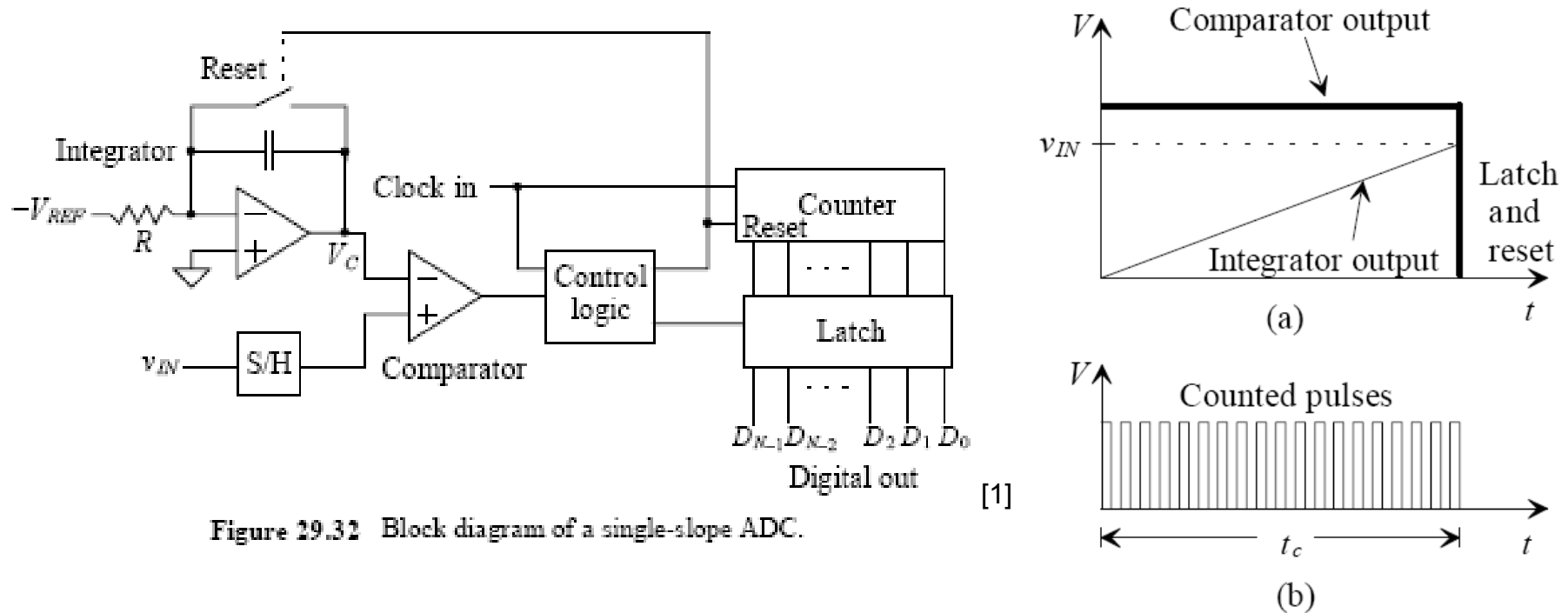


Figure 29.32 Block diagram of a single-slope ADC.

[1]


$$\frac{0 - (-V_{ref})}{R} = C \frac{dV_c}{dt} \rightarrow V_c = \frac{1}{RC} \int_0^t V_{ref} \cdot dt = \frac{V_{ref} \cdot t}{RC}$$

# Single-slope ADC Analysis

 


$$t_c = \frac{v_{IN}}{LSB} \cdot T_{CLK} = \frac{v_{IN}}{V_{REF}} 2^N \cdot T_{CLK}$$

(see why it's slow?)

 

$$V_C = \frac{V_{REF} \cdot t}{RC} = \frac{v_{IN}}{RC \cdot f_{CLK}} 2^N$$

# Single-slope ADC Implementation

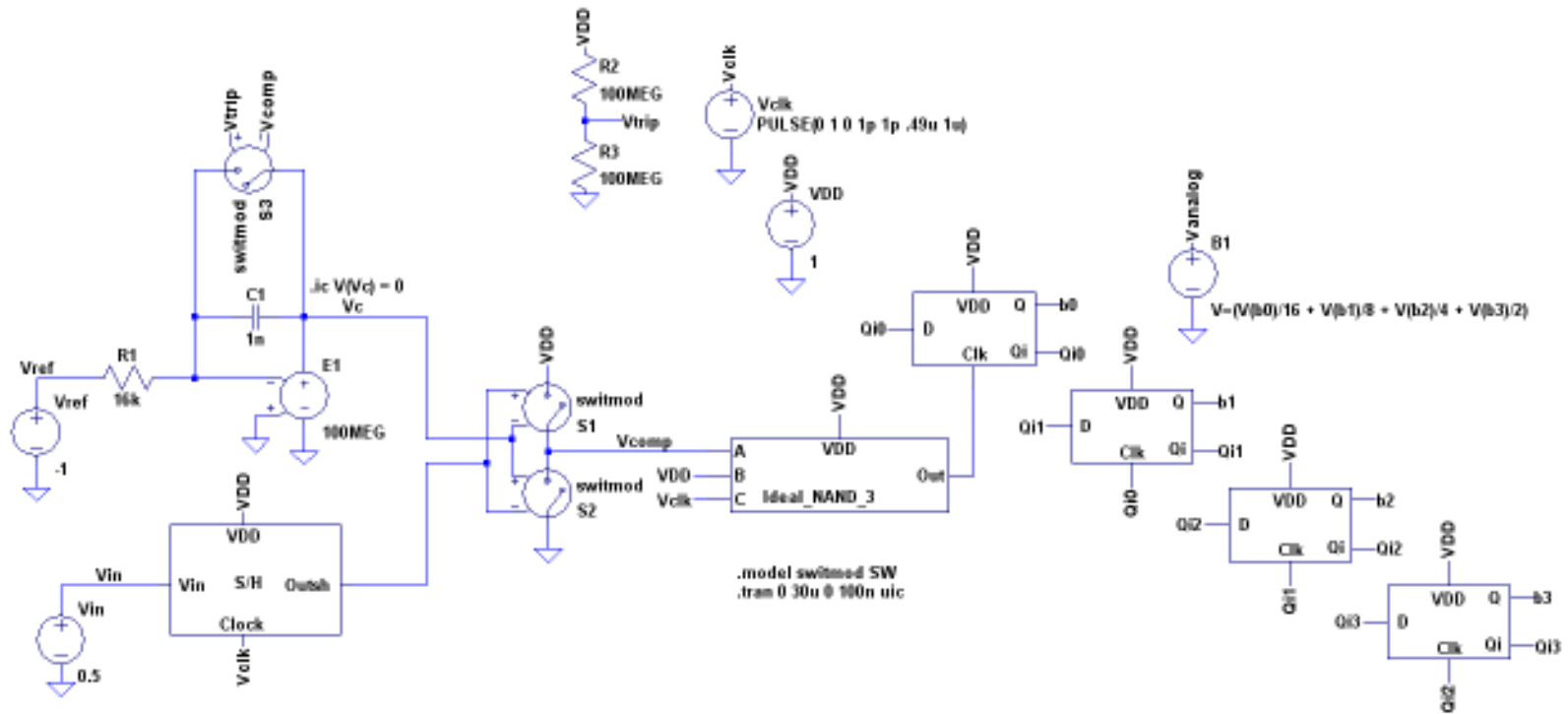

$$V_C = \frac{V_{REF} \cdot t}{RC} = \frac{v_{IN}}{RC \cdot f_{CLK}} 2^N$$

With  $v_{IN} = V_C$


$$N = 4$$

$$RC = 16/10^6 = 16\mu s$$

$$f_{CLK} = 1MHz$$

$$t_c = \frac{v_{IN}}{V_{REF}} 2^N \cdot T_{CLK} = \frac{0.5}{1} \cdot 16 \cdot T_{CLK} = 8T_{CLK}$$

## Single-slope ADC Simulations


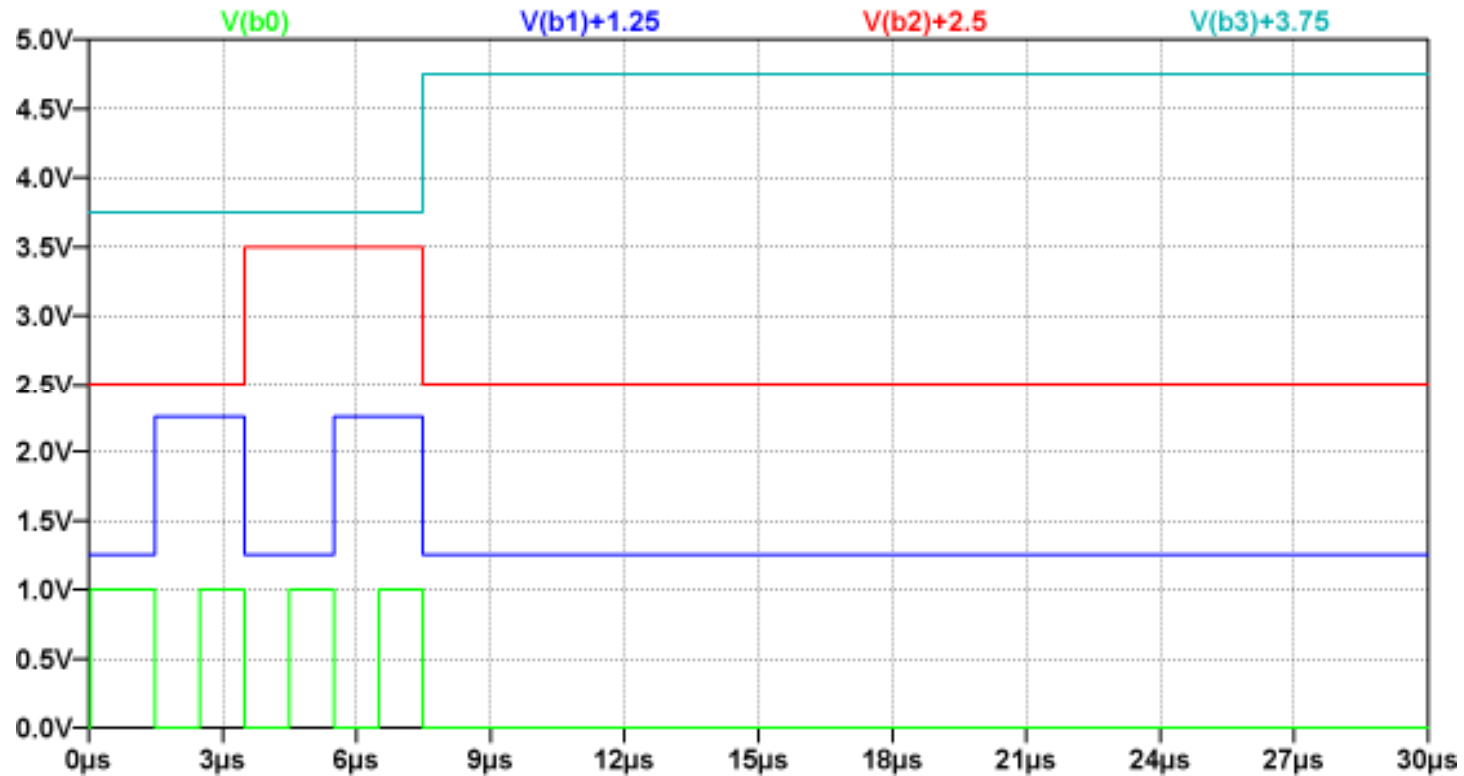


$$t_c = \frac{v_{IN}}{V_{REF}} 2^N \cdot T_{CLK} = \frac{0.5}{1} \cdot 16 \cdot T_{CLK} = 8T_{CLK} \checkmark$$

## Single-slope ADC Errors

- Errors from measurement of  $V_c$ 
  - Depends on CLK – jitter
  - Depends on RC – voltage coefficient, parasitic capacitances, poor processing
  
- Other errors
  - Offset voltage comparator, op-amp, etc.
  - Delays from non-ideal devices


# Dual-slope ADC Operation

 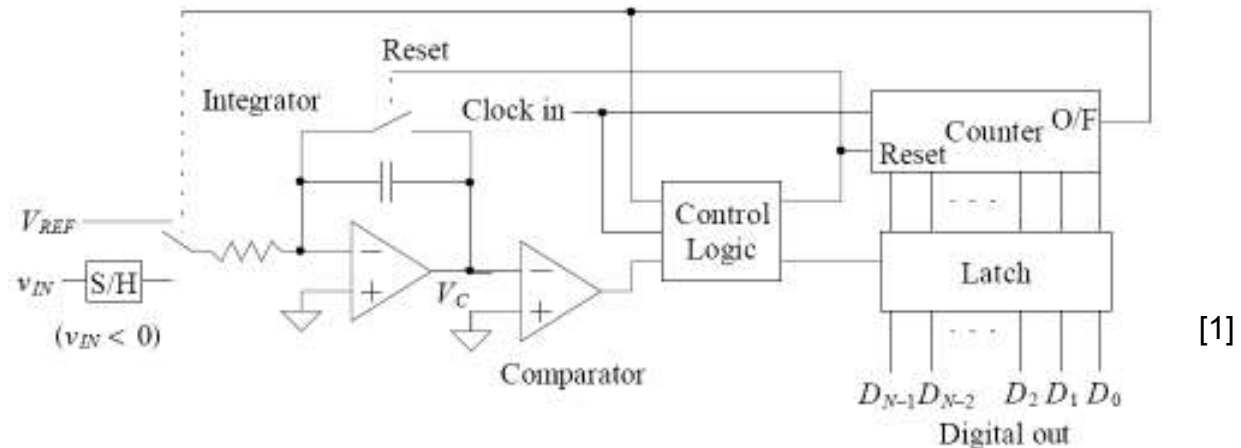

$$T_1 = 2^N \cdot T_{CLK}$$




# Dual-slope ADC Operation

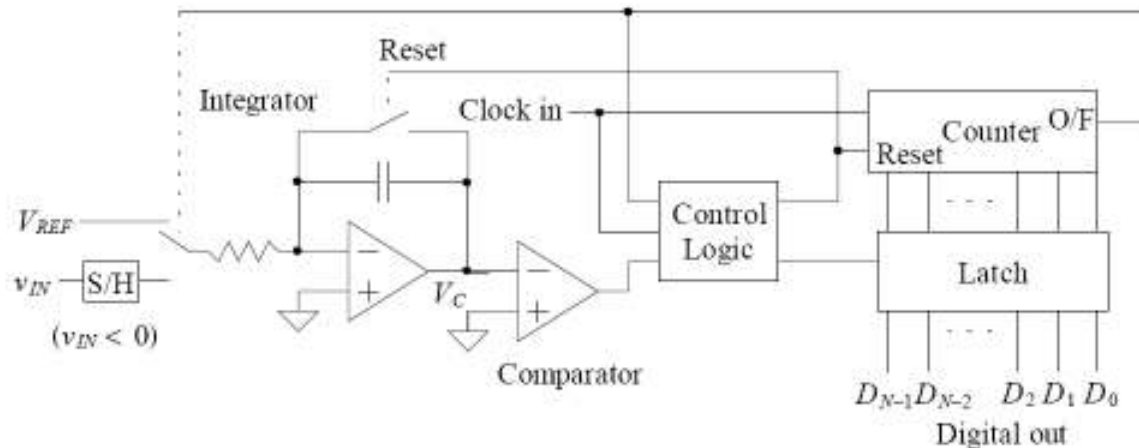


$$V_{C1} = \frac{-1}{C} \int_0^{T_1} \frac{v_{IN}}{R} dt = \frac{v_{IN} \cdot T_1}{RC}$$
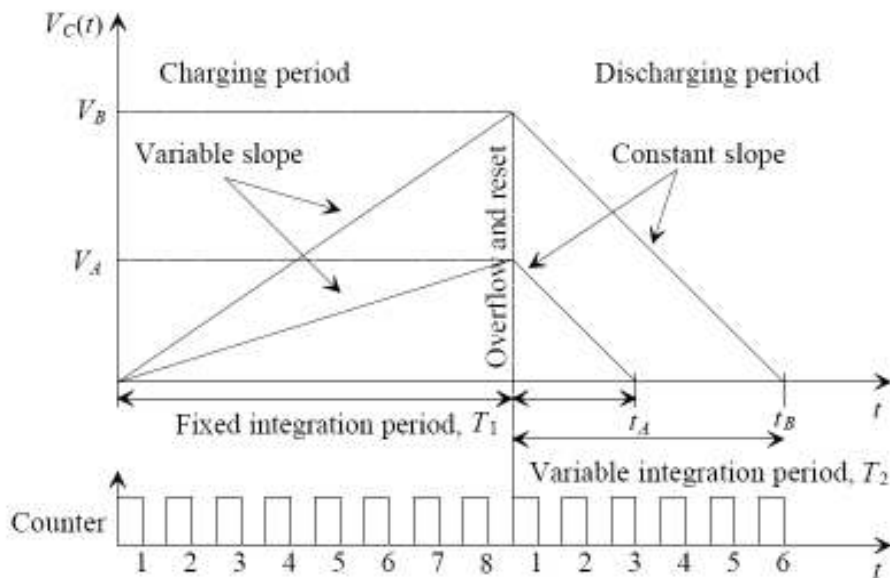
$$V_{C2} = \frac{1}{C} \int_0^{T_2} \frac{V_{REF}}{R} dt = \frac{V_{REF} \cdot T_2}{RC}$$



# Dual-slope ADC Analysis

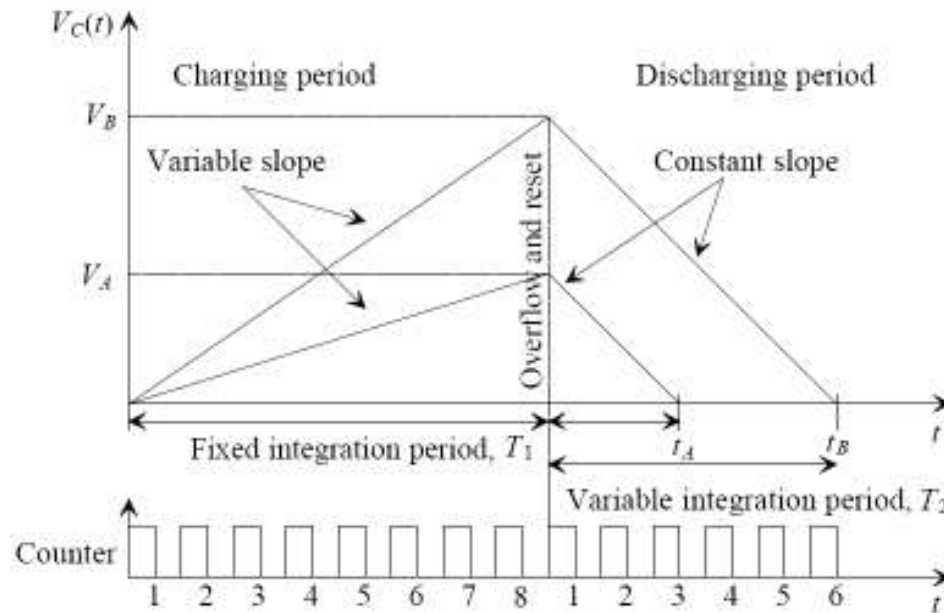

$$V_{C1} = \frac{-1}{C} \int_0^{T_1} \frac{v_{IN}}{R} dt = \frac{v_{IN} \cdot T_1}{RC}$$

$$V_{C2} = \frac{1}{C} \int_0^{T_2} \frac{V_{REF}}{R} dt = \frac{V_{REF} \cdot T_2}{RC}$$


$$V_C = V_{C1} - V_{C2} = (v_{IN} T_1 - V_{REF} T_2) / RC$$

$$\text{If } V_C = 0 \rightarrow v_{IN} T_1 = V_{REF} T_2$$


→

$$\frac{v_{IN}}{V_{REF}} = \frac{T_2}{T_1}$$

# Dual-slope ADC Implementation

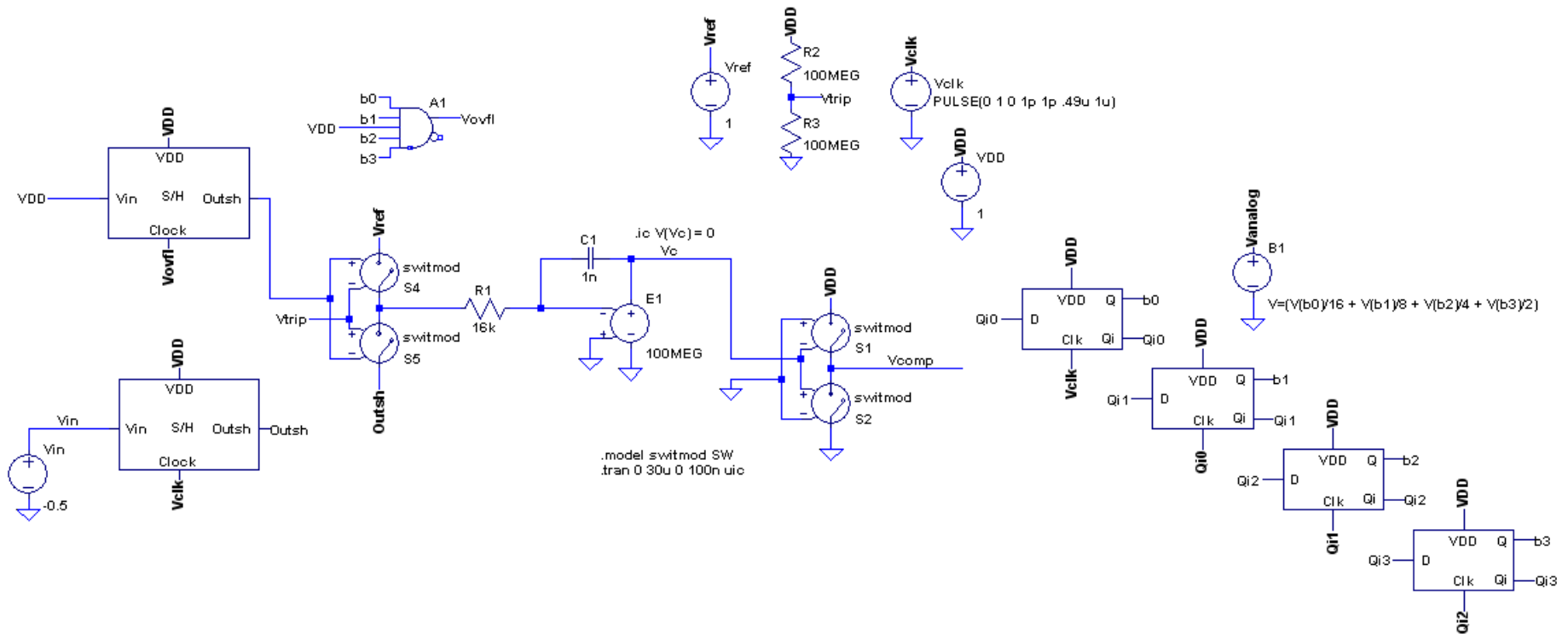

# Dual-slope ADC Simulation

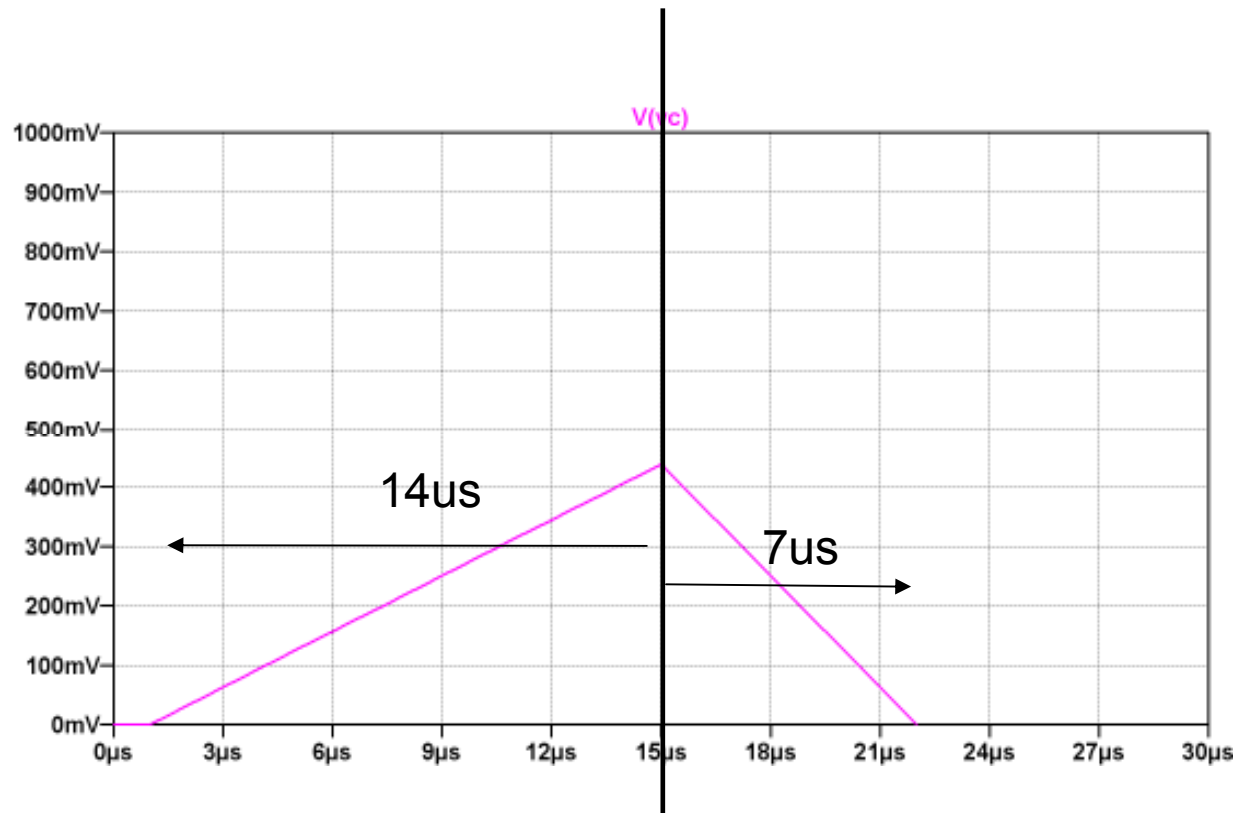

$$\frac{v_{IN}}{V_{REF}} = \frac{T_2}{T_1} = \frac{7\mu s}{14\mu s}$$

## Summary

- Integrating ADC
  - High precision
  - Slow speed
- Single-slope
  - $2^N$  clock cycles (worst-case)
  - Output depends on RC and clock (more error sources)
- Dual-slope
  - $2^{N+1}$  clock cycles (worst-case)
  - Output only depends on ratio  $T2/T1$
  - Same integrator clock produce  $T2$  and  $T1$ , so less error possible

## References

- [1] R.J. Baker, *CMOS: Circuit Design, Layout, and Simulation, 2nd ed.*, Wiley-IEEE Press, 2005
- [2] W. M. C. Sansen, *Analog Design Essentials*, Springer, 2006
- [3] D. A. Johns and K. Martin, *Analog Integrated Circuit Design*, John Wiley and Sons, 1997

Questions?

# Charge-Scaling DACs

Geng Zheng


May 7, 2008

# Agenda


- Operation
- Mismatch
- INL/DNL
- Topologies
- Simulation
- Summary



# Charge-Scaling Basics

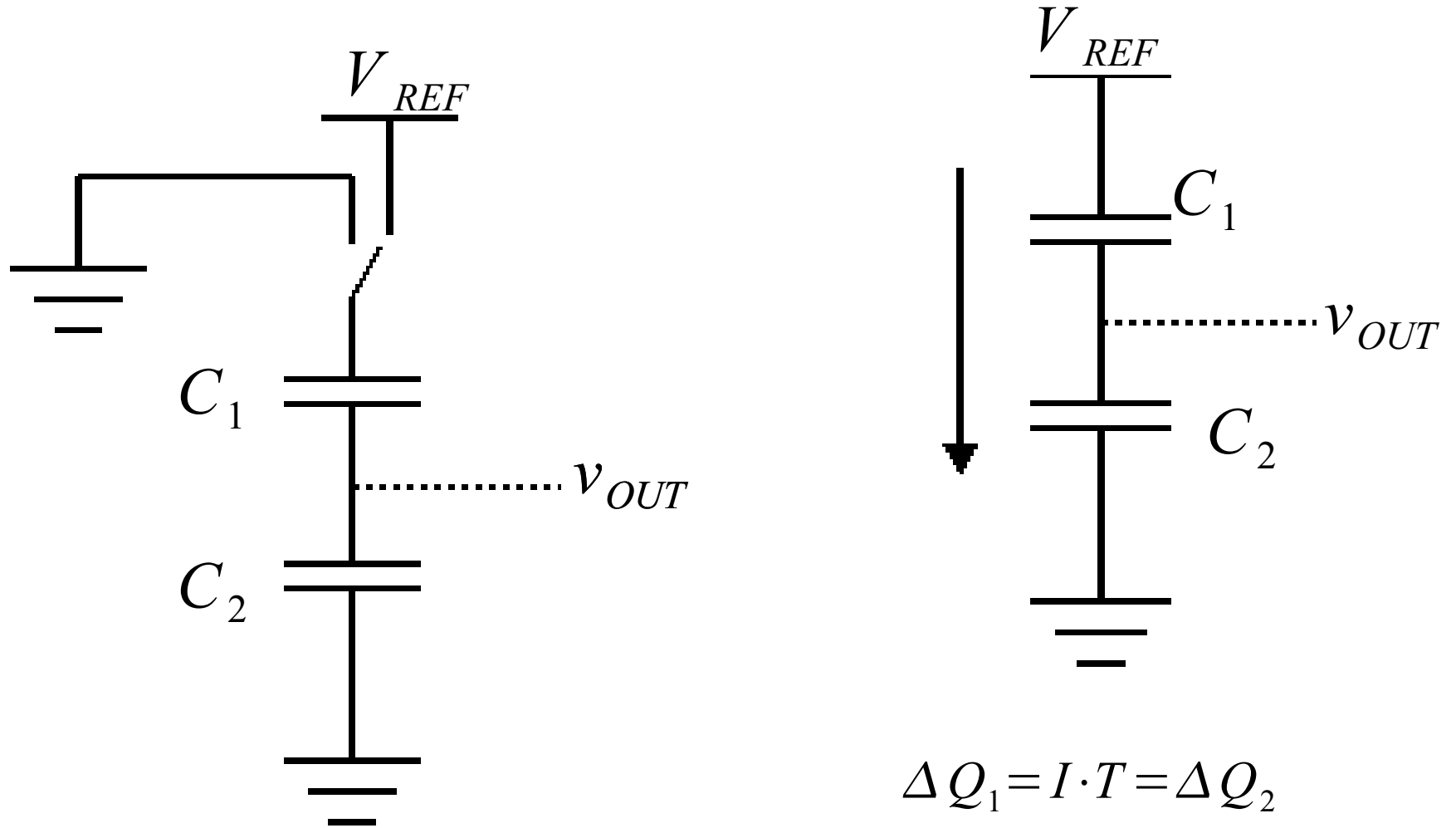

# Charge-Scaling Basics

 


$$\Delta Q_1 = (V_{REF} - v_{OUT}) \cdot C_1 - 0$$

$$\Delta Q_2 = v_{OUT} \cdot C_2 - 0$$

$$\Delta Q_1 = \Delta Q_2$$


$$\rightarrow v_{OUT} = \frac{C_1}{C_1 + C_2} \cdot V_{REF}$$

# Charge-Scaling Basics

 


$$v_{OUT} = V_{REF} \frac{C_1}{C_{total}}$$

# Charge-Scaling Basics

 

# Charge-Scaling Basics

 


$$\Delta Q_1 = (V_{REF} - v_{OUT}) \cdot C_1 - (0 - V_x) \cdot C_1$$

$$\Delta Q_2 = v_{OUT} \cdot C_2 - V_x \cdot C_2$$

$$\Delta Q_1 = \Delta Q_2$$



$$\rightarrow v_{OUT} = \frac{C_1}{C_1 + C_2} \cdot V_{REF} + V_x$$

# A N-bit Charge-Scaling DAC

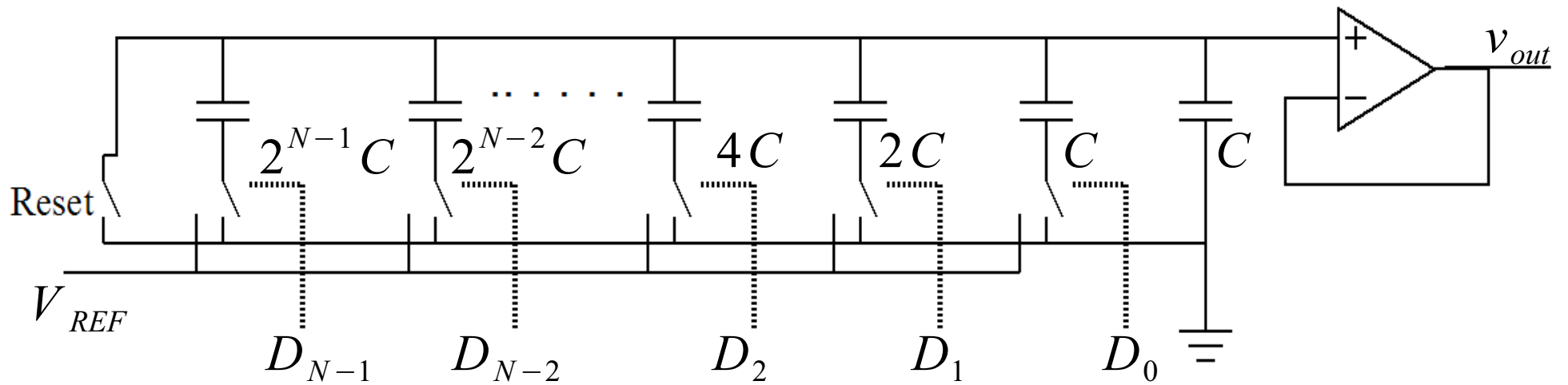


$$\sum \text{all capacitors} = 2^N C$$

# A N-bit Charge-Scaling DAC

  

$$\begin{aligned}
 v_{out} &= \sum_{k=0}^{N-1} D_k v_{out,k} \\
 &= \sum_{k=0}^{N-1} D_k 2^{k-N} V_{REF}
 \end{aligned}$$


# Capacitor Mismatch

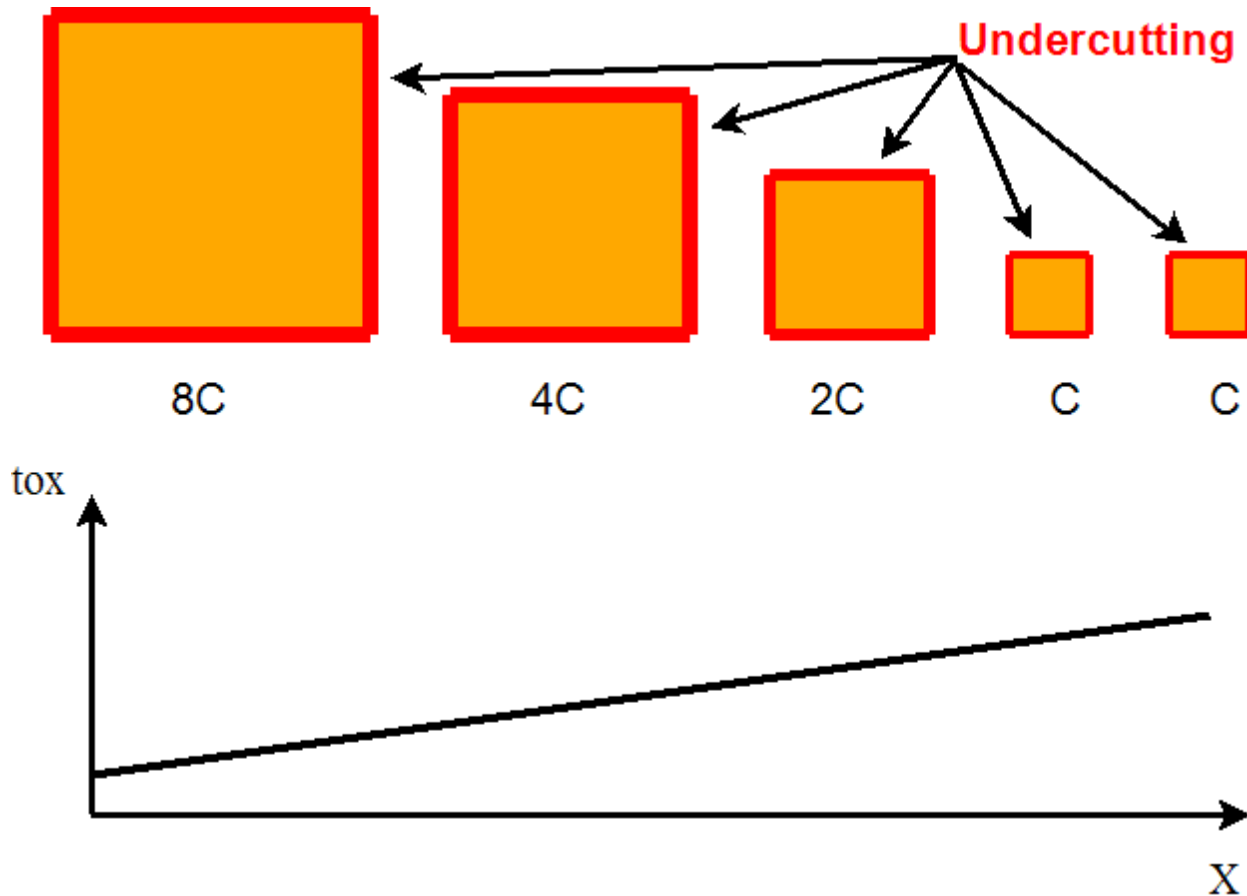

See Ref[2] for details




# Capacitor Mismatch

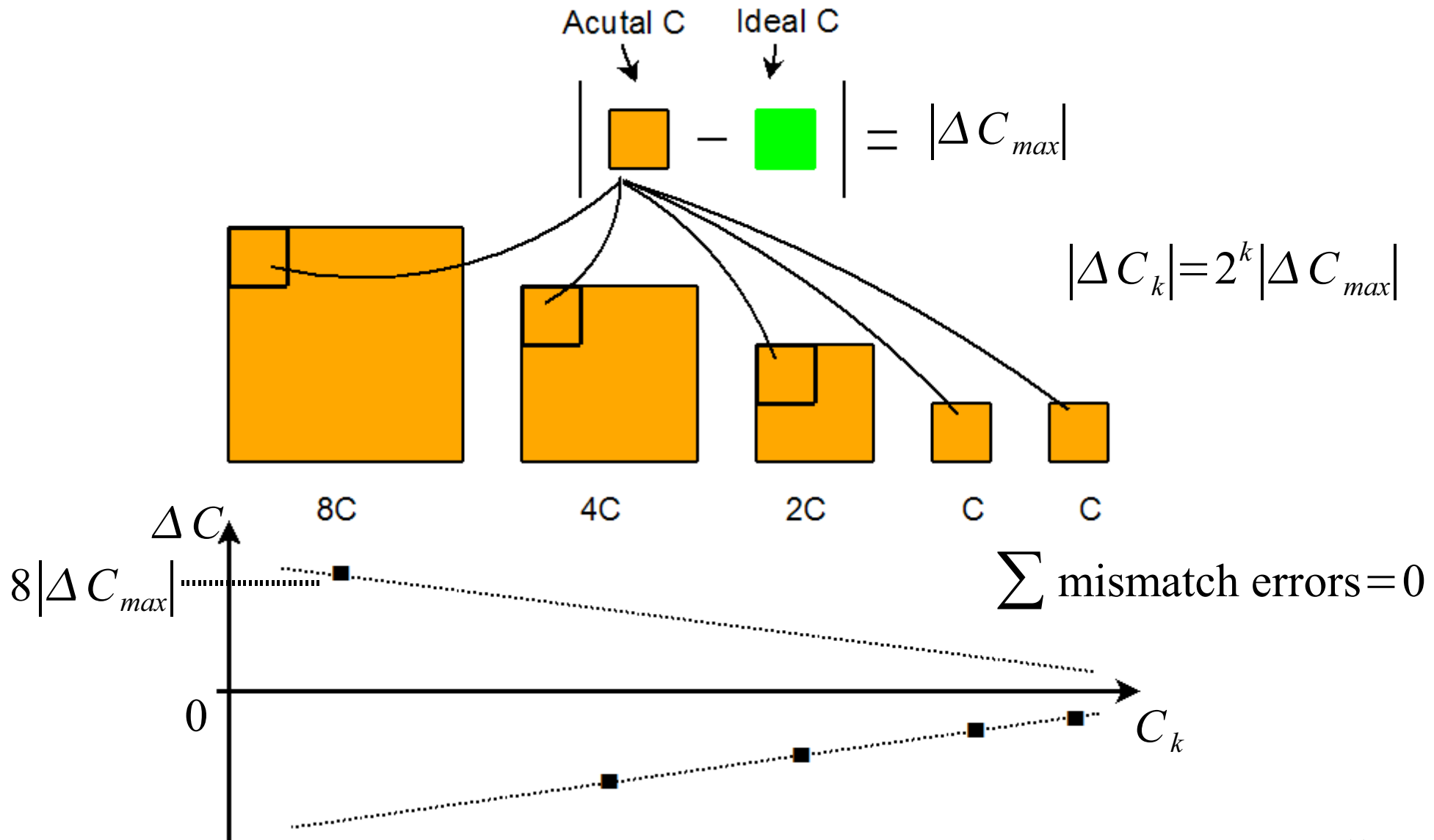

# INL

$$\begin{aligned}V_{out,k} &= \frac{C_k}{C_{total}} \cdot V_{REF} = \frac{2^k (C \pm \Delta C_{max})}{2^N C} \cdot V_{REF} \\ &= \frac{2^k C}{2^N C} V_{REF} \pm \frac{2^k}{2^N C} V_{REF} \frac{|\Delta C_{max}|}{C}\end{aligned}$$

 


$$|INL|_k = 2^k \frac{|\Delta C_{max}|}{C} LSB$$

The worst-case occur at midpoint ( $k = N-1$ ):

$$|INL|_{max} = 2^{N-1} \frac{|\Delta C_{max}|}{C} LSB \xrightarrow{|INL|_{max} \leq 0.5 LSB} \frac{|\Delta C_{max}|}{C} \leq \frac{1}{2^N}$$
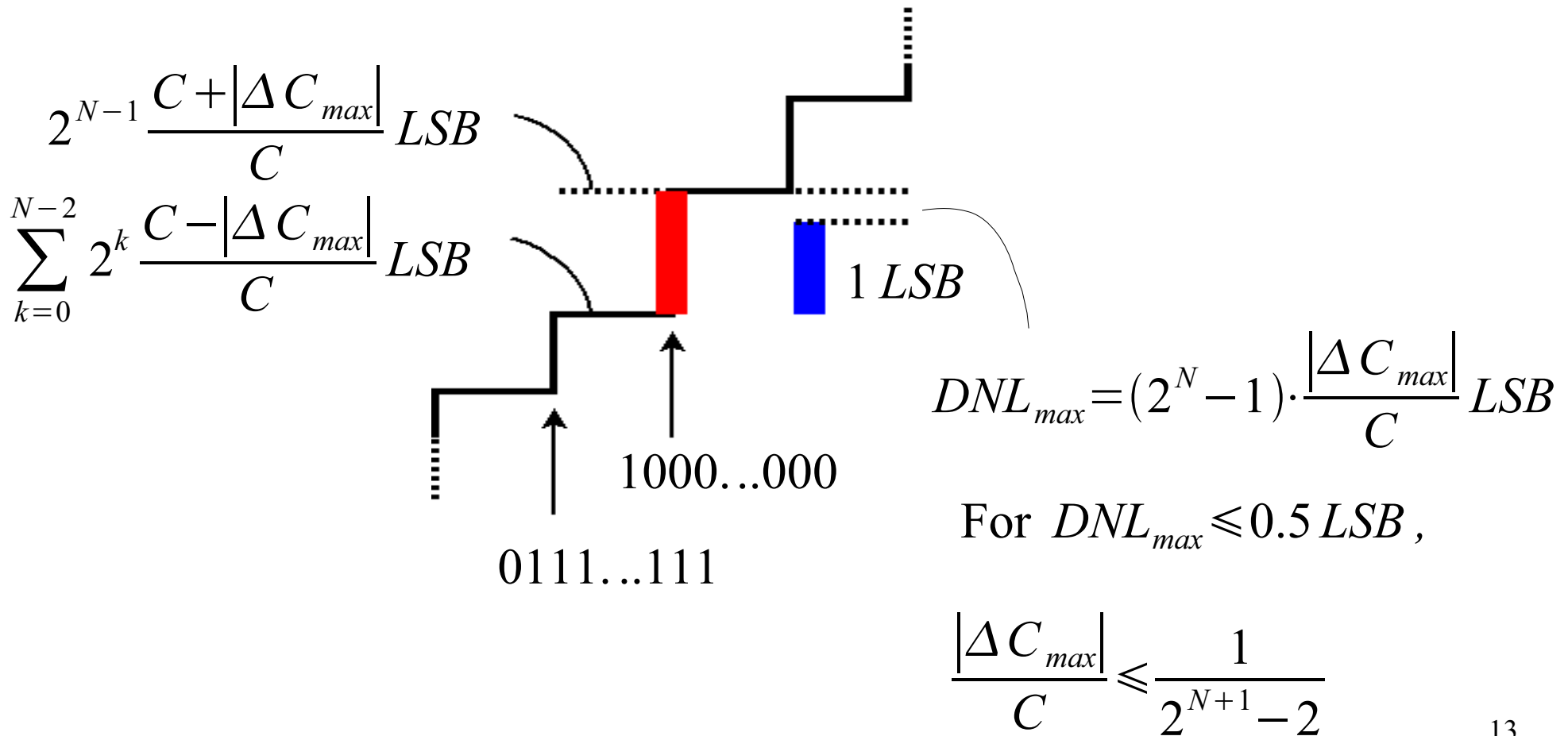
# DNL

The worst-case: 0111...111  $\rightarrow$  1000...000



# The Split Array

A 12-bit DAC with  $C = 100 \text{ fF}$ :

$$C_{MSB} = 2^{11} \cdot 100 \text{ fF} = 204.8 \text{ pF}$$


AMI's C5 (500 nm) process:

$$C_{p1-p2} \approx 900 \text{ aF} / \mu\text{m}^2$$

$$\rightarrow \text{Area}_{C_{MSB}} \approx 477 \times 477 \mu\text{m}^2 !!!$$


# The Split Array

## Subranging Topology

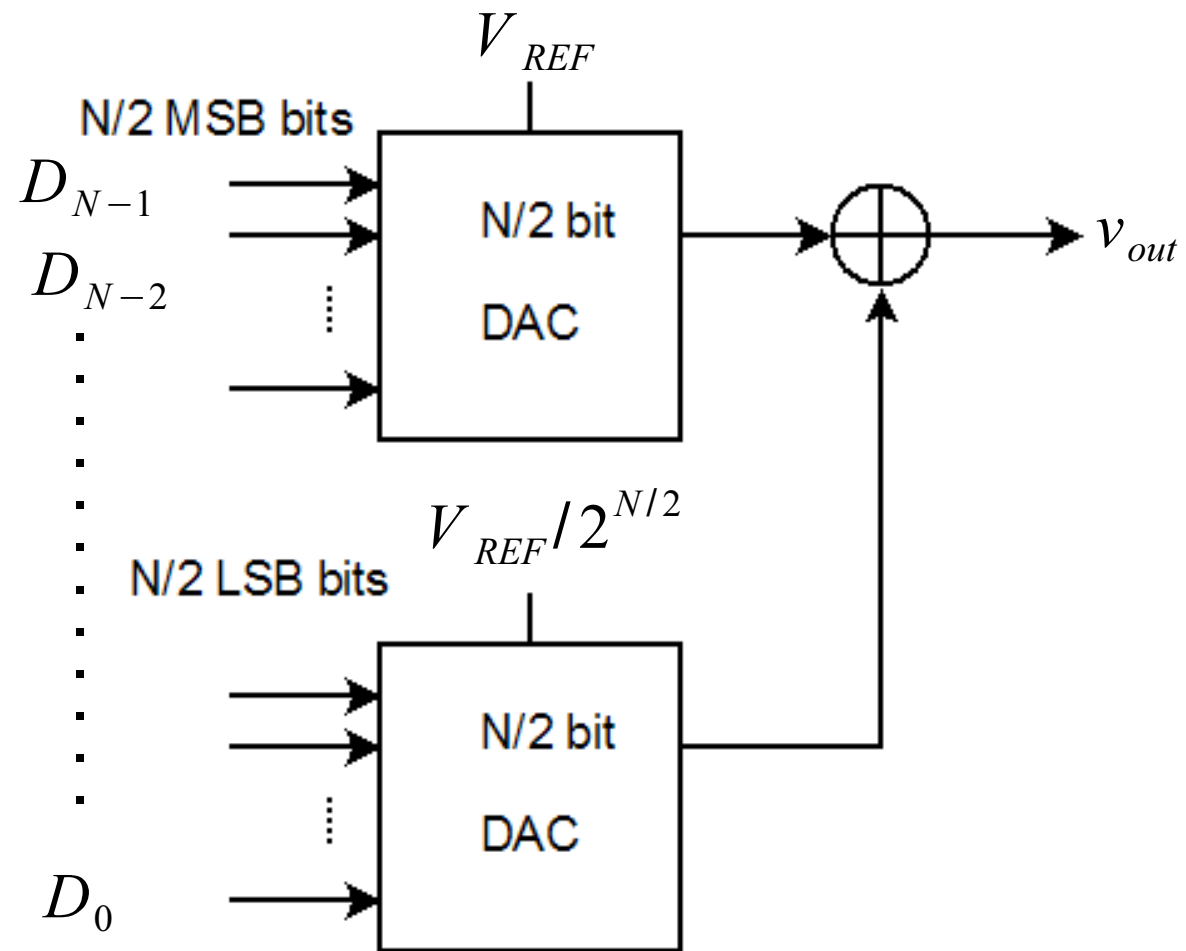

# The Split Array

A 6-bit split array charge-scaling DAC

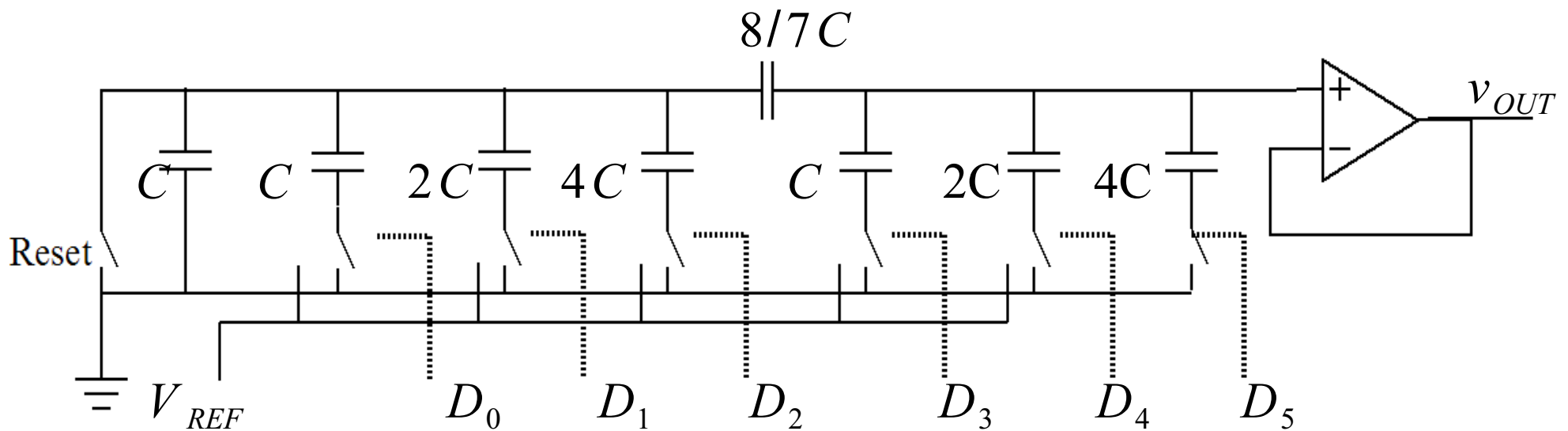


$$C_{atten} = \frac{\sum \text{LSB array capacitors}}{\sum \text{MSB array capacitors}} = \frac{C + C + 2C + 4C}{C + 2C + 4C} = \frac{8}{7}C$$
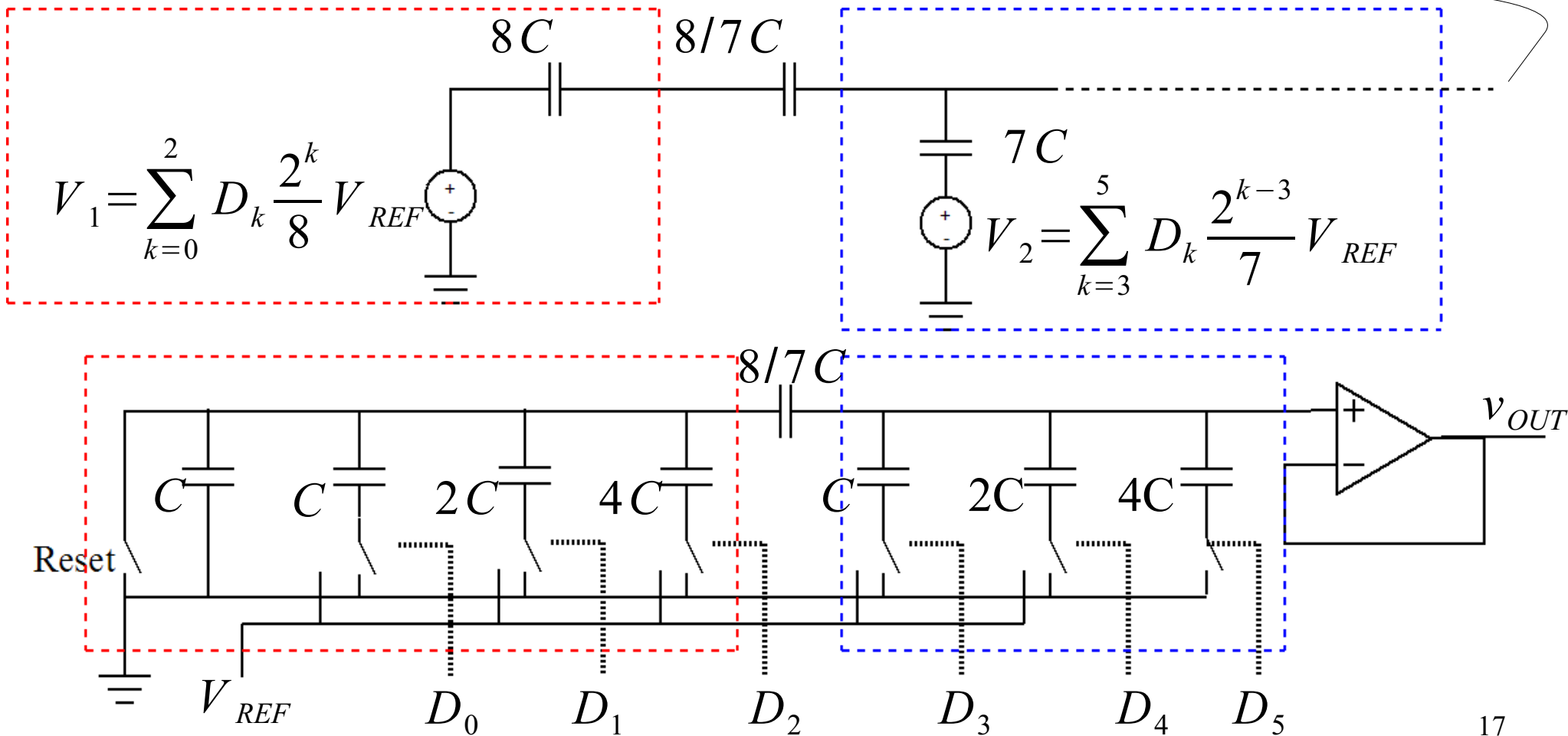
# The Split Array

Thevenin equivalent circuit


$$v_{OUT} = \frac{1}{8} V_1 + \frac{7}{8} V_2$$


 
# Issue and Other Topologies

- Parasitic Capacitance

$$v_{OUT} = \sum_{k=0}^{N-1} D_k \frac{2^k C}{2^N C + C_p} V_{REF}$$






# Issue and Other Topologies

- Parasitic Capacitance

$$v_{OUT} = \sum_{k=0}^{N-1} D_k \frac{2^k C}{C_F} V_{REF}$$


$C_F = 2^N C$
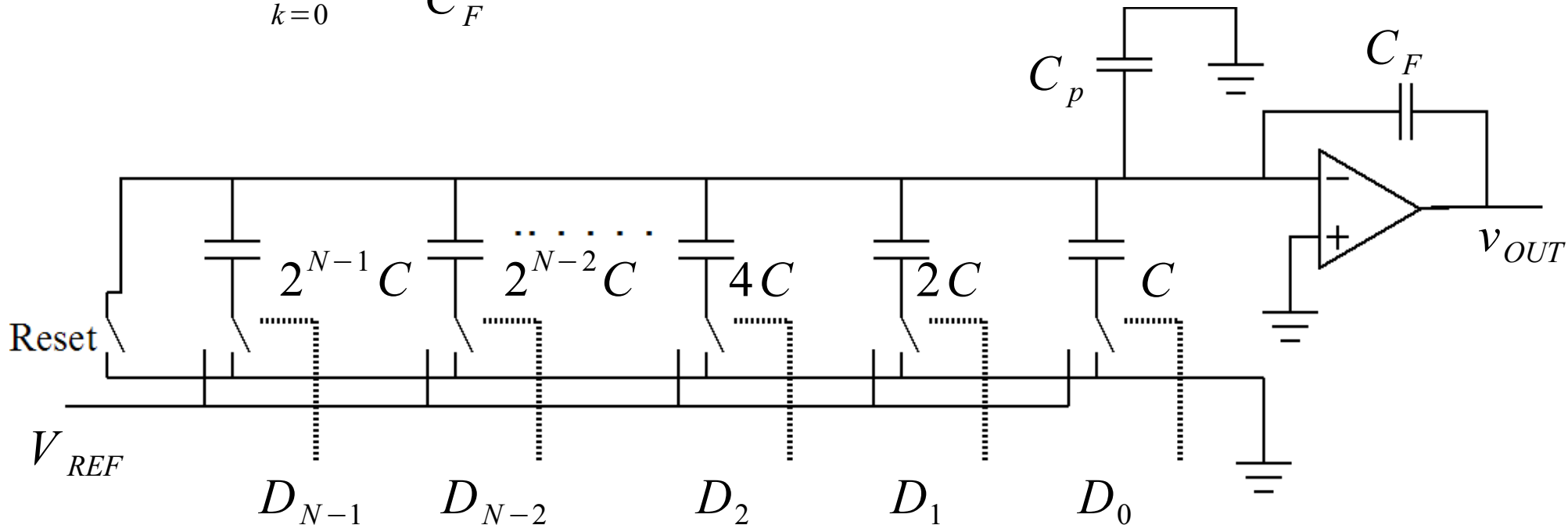
$$v_{OUT} = \sum_{k=0}^{N-1} D_k \frac{2^k C}{2^N C} V_{REF}$$




# Issue and Other Topologies

- SPICE Simulation

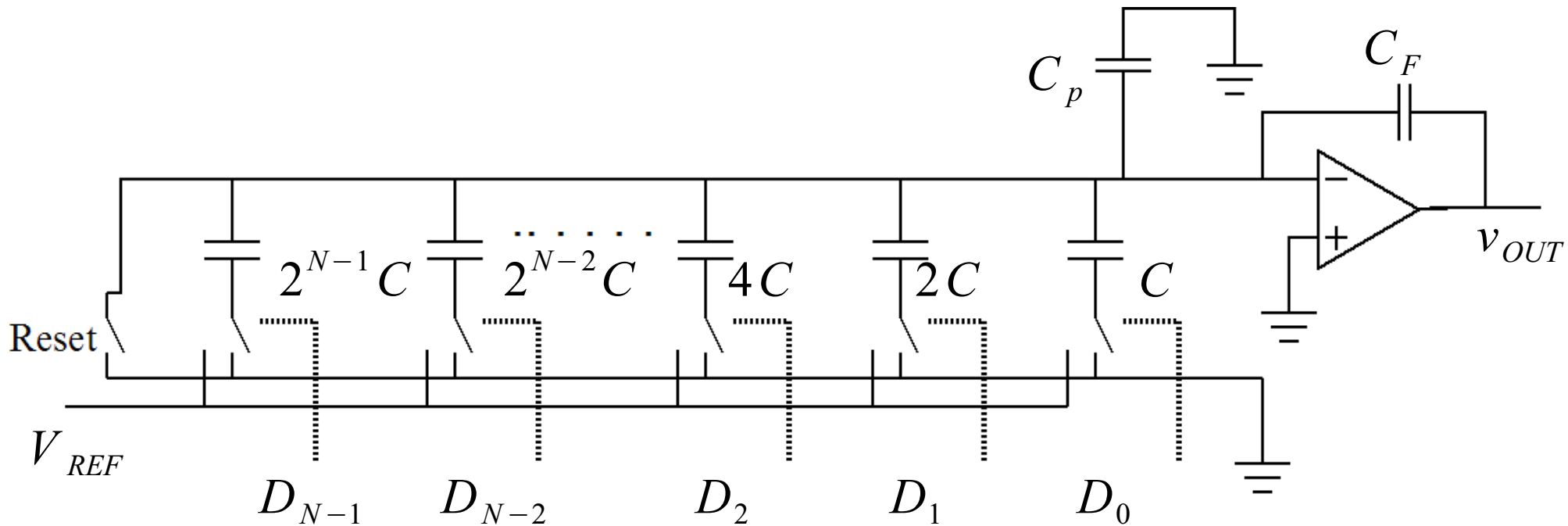

# Issue and Other Topologies

- Offset Compensation

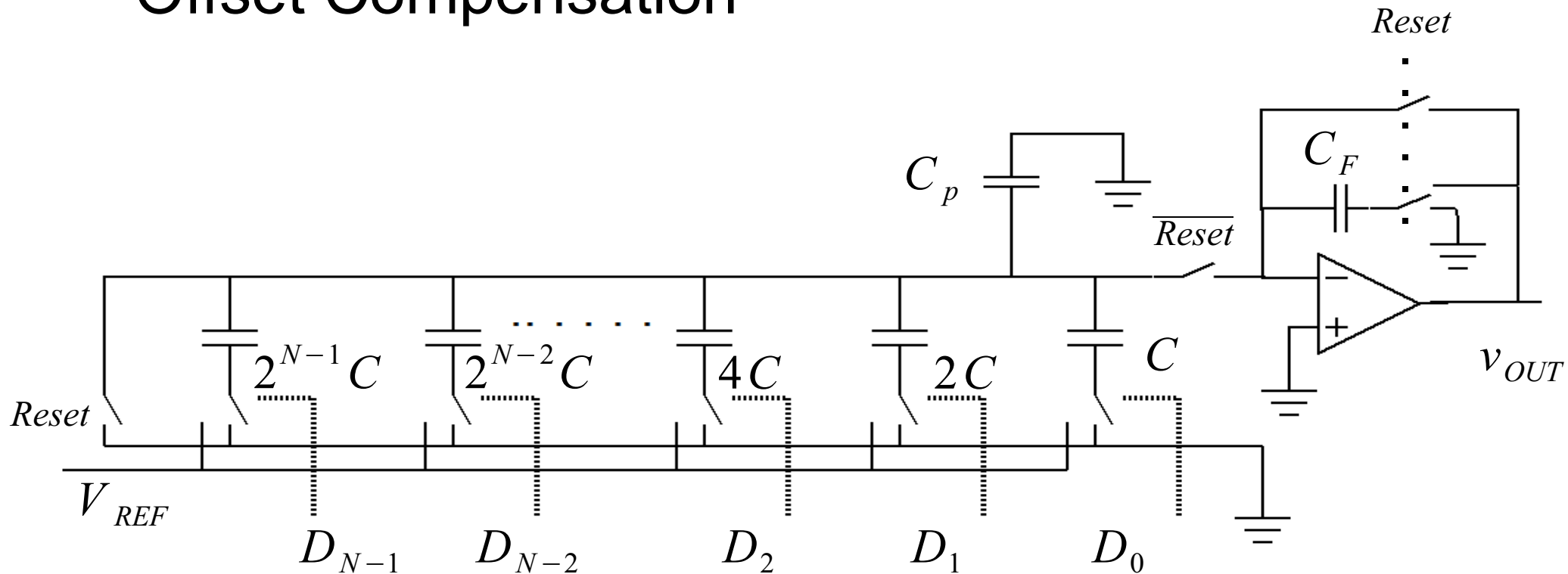

# Summary

- Large area for high resolution
- Large capacitor ratios; matching issue
- The simple topology sensitive to parasitic caps
- Offset is easy to compensate

# References

1. R. J. Baker, “CMOS Circuit Design, Layout, and Simulation”, 2nd ed, Wiley-IEEE, 2005.
2. J. L. McCreary and P. R. Gray, “All-MOS Charge Redistribution Analog-to-Digital Conversion Techniques – Part I”, IEEE Journal of Solid State Circuits, vol. 10, no. 6, pp. 371-379, Dec. 1975
3. <http://www.mosis.com/cgi-bin/cgiwrap/umosis/swp/params/ami-c5/t68z-params.txt>
4. [http://www.aicdesign.org/SCNOTES/2006notes/Chap10\(12\\_8\\_06\).pdf](http://www.aicdesign.org/SCNOTES/2006notes/Chap10(12_8_06).pdf)

# Question?