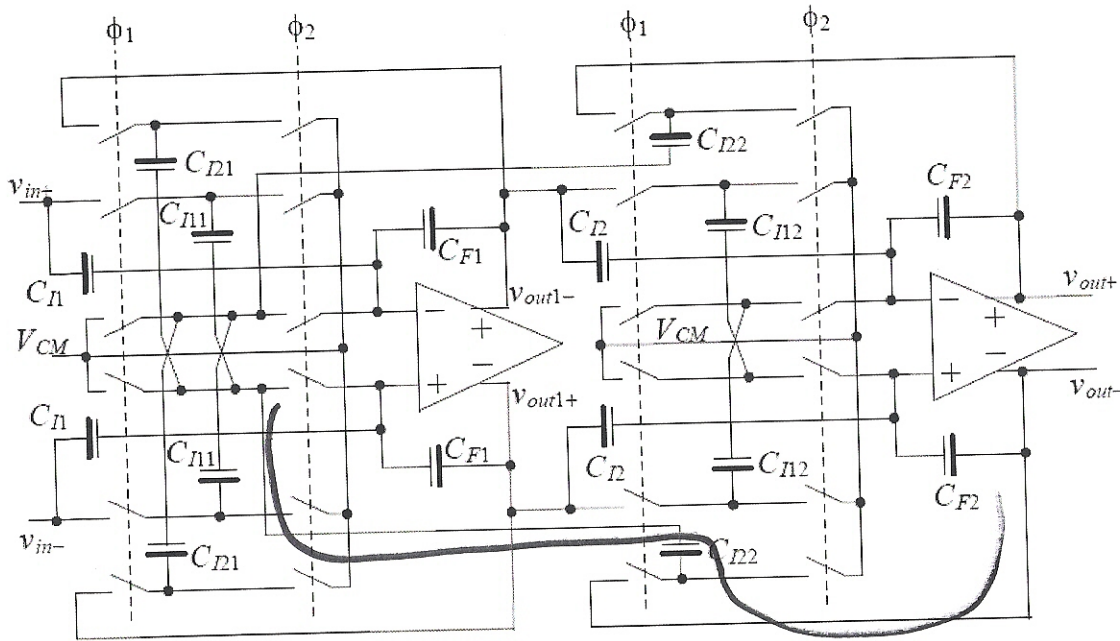



ECE 615 CMOS mixed-signal circuit design

Lecture 10
sept. 27, 2010



$$G_1 = \frac{C_{N1}}{C_{F1}} \cdot f_s \quad G_2 = \frac{C_{D1}}{C_{N1}} \quad G_3 = \frac{C_N}{C_{N1} \cdot f_s} \quad G_4 = \frac{C_{N2}}{C_{F2}} \cdot f_s \quad G_5 = \frac{C_{D2}}{C_{N1}} \quad G_6 = \frac{C_D}{C_{N2} \cdot f_s}$$

Figure 3.43 Implementing a biquad filter using switched capacitors.

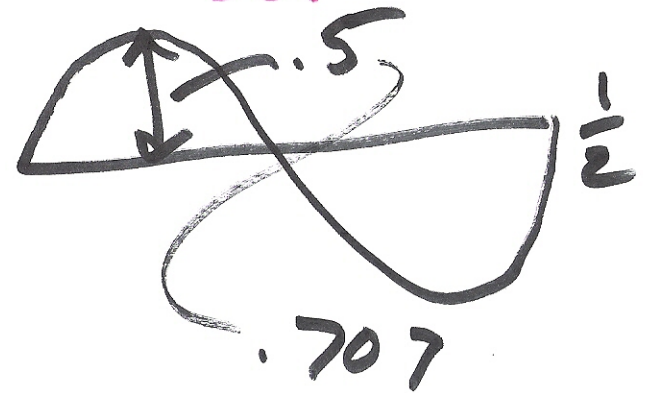

.707

.35


.85V

transconductor - C

fully-diff.

folded cascode

$$f_{uv} = \frac{g_m}{2\pi C_L}$$

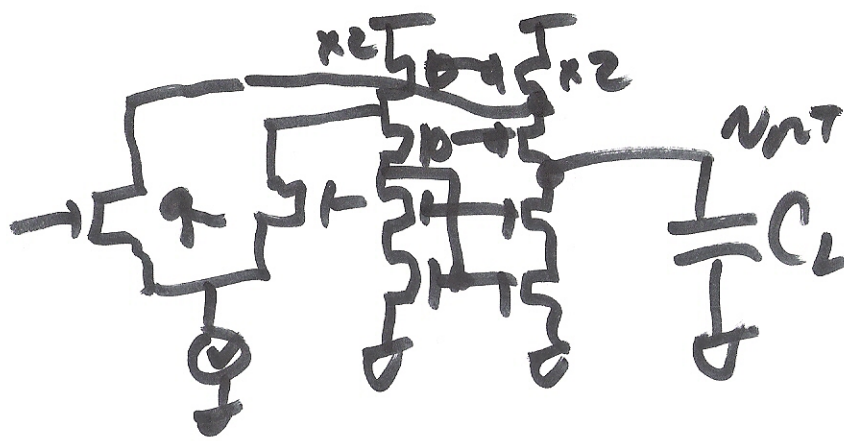

11)

EX. 3.12

Active-RC , $Q = 20$

$f_0 = 1.59 \text{ MHz}$

Bandpass

$$\frac{v_{out}}{v_{in}} = \frac{a \cdot s}{s^2 + \left(\frac{2\pi f_0}{Q}\right)s + (2\pi f_0)^2}$$

$$= \frac{s^2 G_1 G_3 G_4 G_6 + s(G_1 G_3 G_4 + G_1 G_4 G_6)}{s^2 G_1 G_3 G_4 G_6 + s(G_1 G_3 G_4 + G_1 G_4 G_6) + G_1 G_4}$$

$$s^2 + s(G_1 G_2 + G_1 G_4 G_5 G_6) + G_1 G_4 G_3$$

$G_2 = 0$

2)

Ex. 3.12 cont'd

$$\frac{v_{out}}{v_{in}} = \frac{a \cdot s}{s^2 + \left(\frac{2\pi f_0}{Q}\right)s + (2\pi f_0)^2} =$$

$$\frac{s \cdot G_1 G_3 G_4 + \cancel{G_1 G_4}^0}{s^2 + s G_1 G_2 + G_1 G_4 G_5}$$

$$G_1 = \frac{1}{R_{I1} C_{F1}} \quad G_3 = R_{I1} \cdot C_{I1}$$

$$G_4 G_1 G_3 = \frac{C_{I1}}{C_{F1}} \cdot \frac{1}{R_{I2} C_{F2}}$$

$$G_4 = \frac{1}{R_{I2} C_{F2}}$$

3)

3.12 → Active RC

$$C_{F1} = C_{F2} = 10\mu\text{F}$$

$$R_{I2} = R_{F2} = 10\text{k}$$

$$R_{F1} = 200\text{k}$$

to get $Q = 20$

$$\frac{2\pi f_0}{Q} = \frac{1}{R_{F1} \cdot C_{F1}} = G_{1,62}$$

$$f_0 = \text{CONST}$$

$$\boxed{Q \uparrow \rightarrow \frac{R_{F1} \uparrow}{C_{F1} \uparrow}}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{C_{F1} R_{I2} C_{F2} R_{F2}}}$$

$$G_2 = \frac{R_{I1}}{R_{F1}}$$

4)

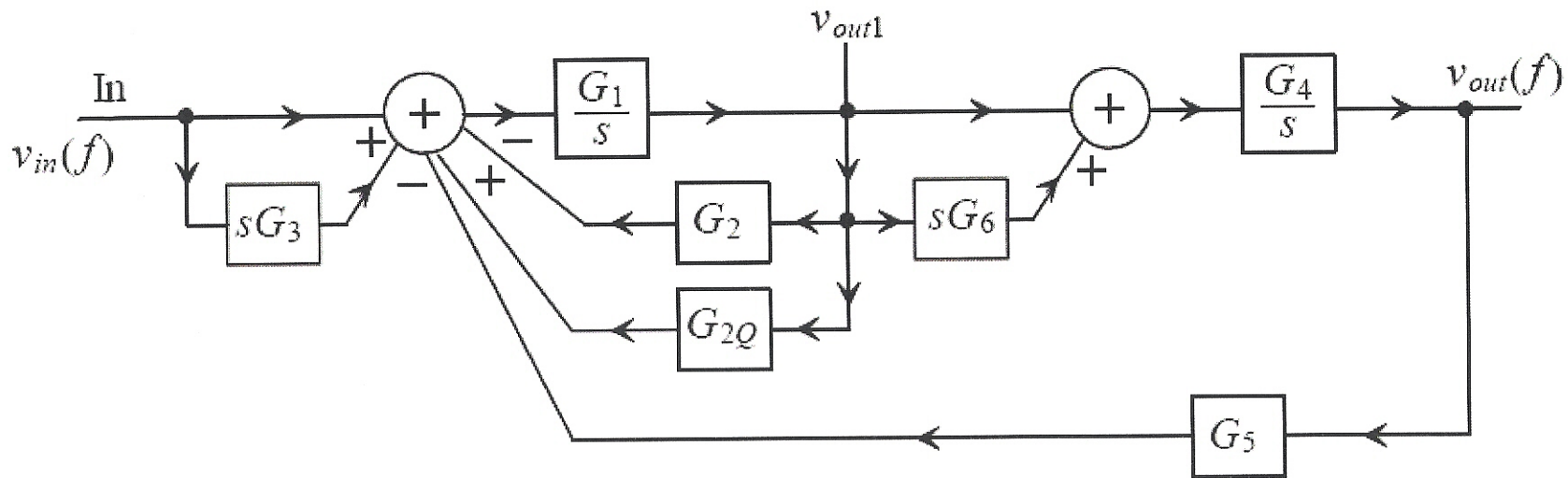


Figure 3.44 Implementation of a "high-Q" biquadratic transfer function.


(3.79)


$$\frac{\pi f_0}{Q} = G_1(G_2 - G_{2Q})$$

$$G_2 > G_{2Q}$$

Look at Ex 3.13

s)

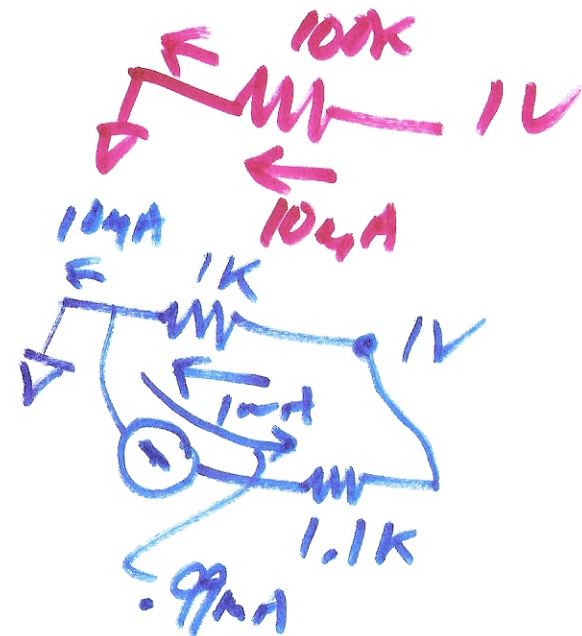

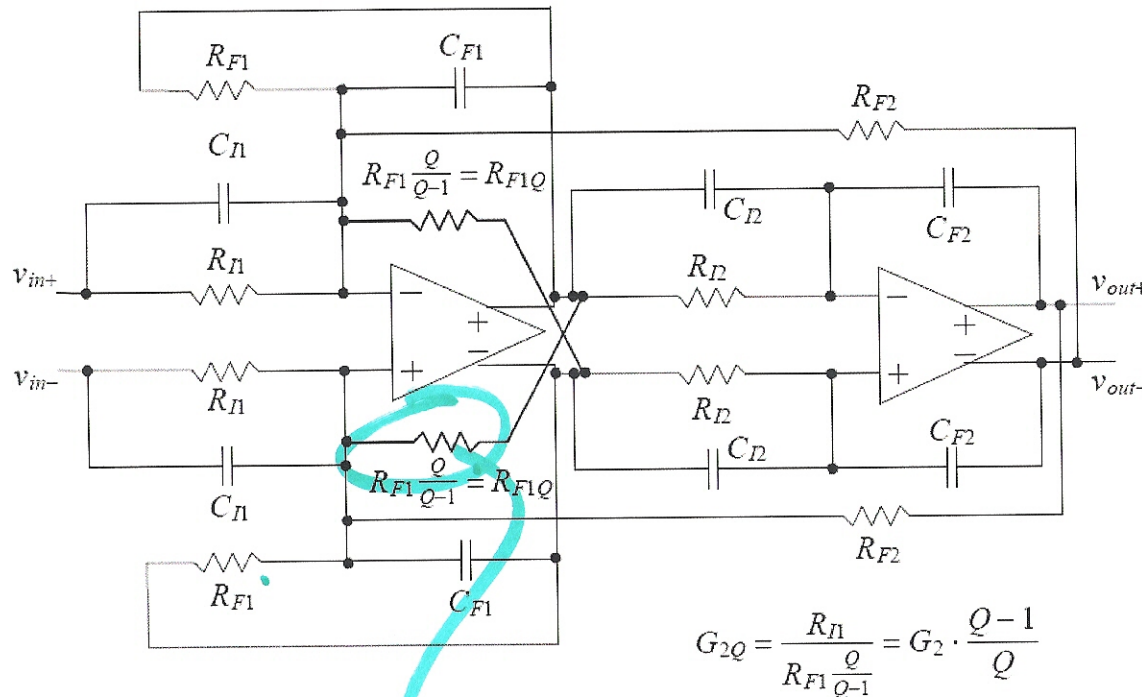


$$G_{2Q} = \frac{R_N}{R_{F1} \frac{Q}{Q-1}} = G_2 \cdot \frac{Q-1}{Q}$$

Figure 3.45 Implementation of the "high-Q" active-RC biquadratic transfer function filter. The bold lines indicate the added components.

Implement Hi-Q!

6)

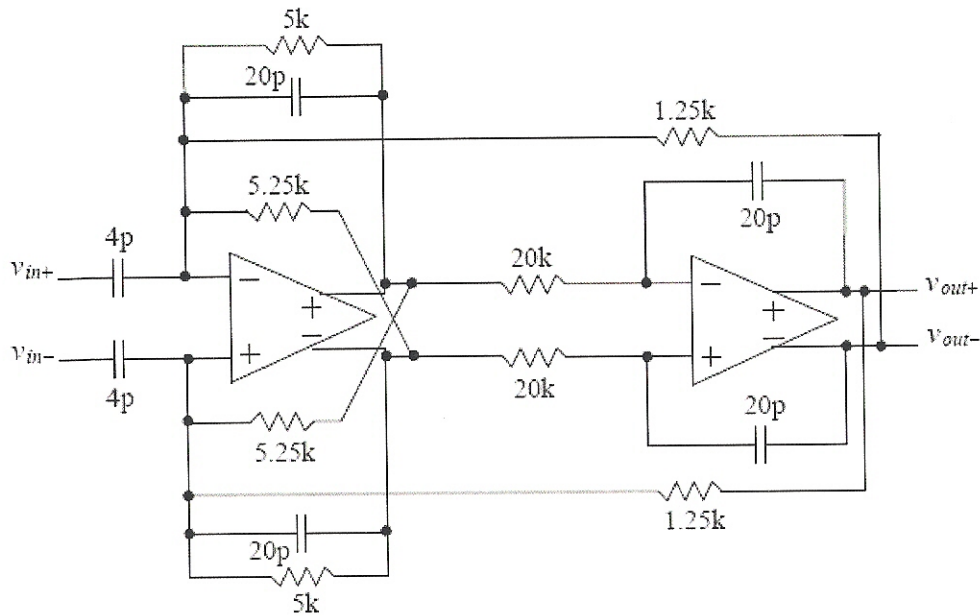

Sim Results
for Ex 3.13


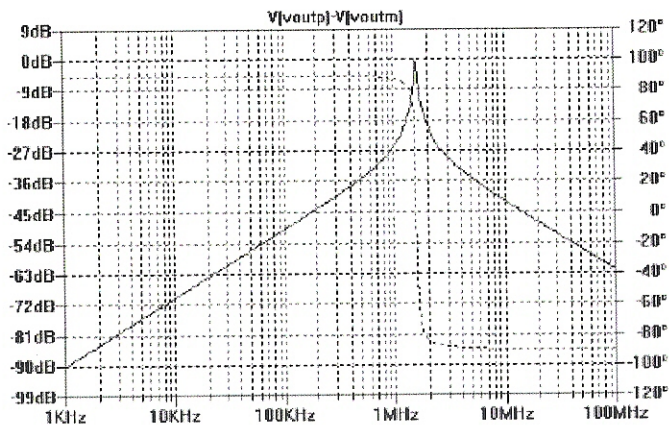


Figure 3.46 Bandpass filter discussed in Ex. 3.13.

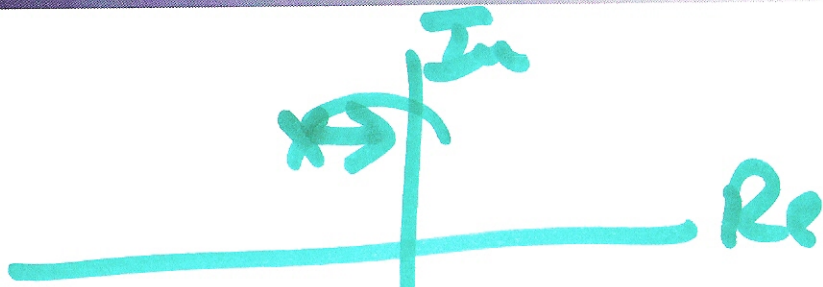

Hi-Q



Active-RC
↓
SC


$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$$

Q

$$R = \frac{1}{fC}$$

$$\sqrt{\frac{1}{z-1}} = \frac{z^{-1}}{1-z^{-1}} = \frac{1}{s}$$
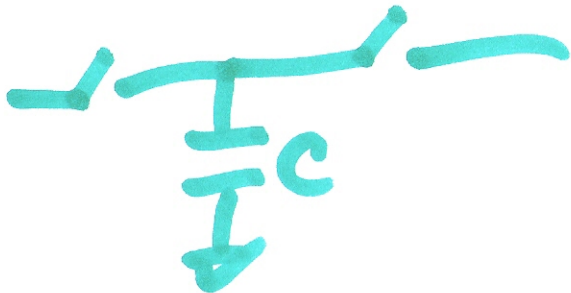
$$z \approx 1 + j\frac{4}{5} \cdot 2\pi$$



$$z \approx 1 + s$$


↑ if varied

$$\frac{1}{s}$$

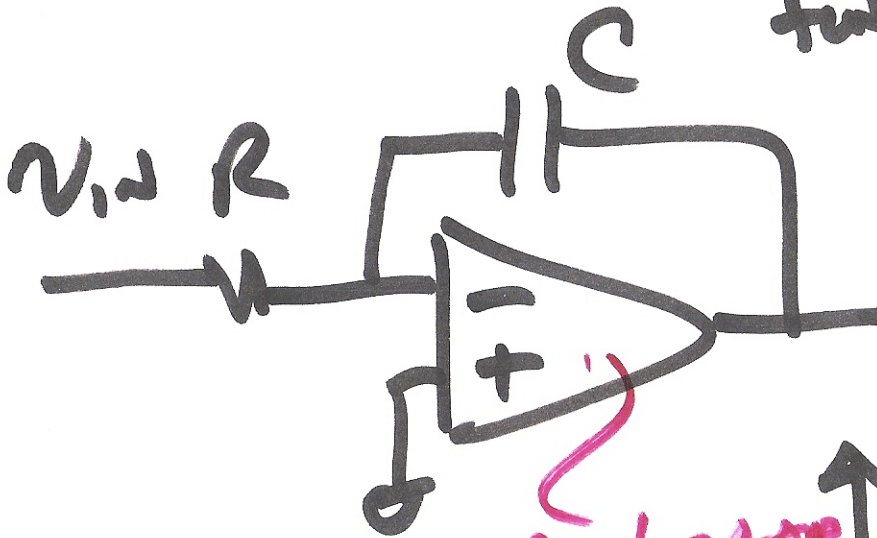8)

Q-peaking


$$A_{OL} \approx \frac{1}{j\omega f_{uL}}$$



$$\frac{1}{sRC}$$

$$\left| \frac{v_o}{v_i} \right| = \left| \frac{1}{R} \right| = \frac{1}{2\pi f RC}$$

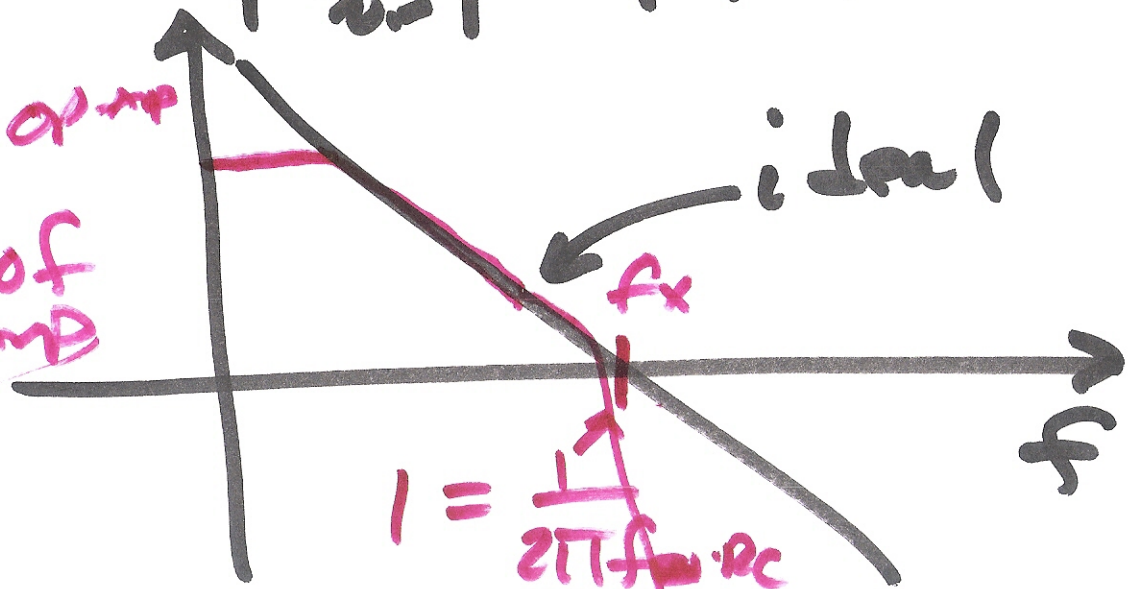$f_x \ll f_u$
 Real op-amp
 fun of op-amp



$$1 = \frac{1}{2\pi f_x RC}$$

$$f_x = \frac{1}{2\pi RC}$$

$$\frac{1}{s} \rightarrow$$

$$\frac{1}{s \left(1 + \frac{s}{2\pi f_w} \right)}$$


$$\frac{1}{s \left(1 + \frac{s}{2\pi f_w} \right) + p_1}$$

$$\cdot \frac{1}{s \left(1 + \frac{s}{2\pi f_w} \right) + p_2}$$

Eq. 3.85

$$s + p_1 -$$

$$\frac{(2\pi f)^2}{2\pi f_w}$$
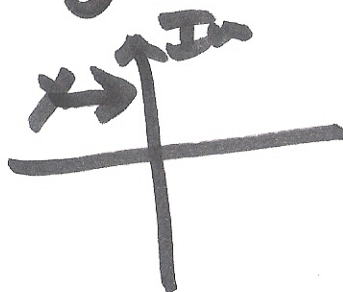
$$s = -p_1 + \frac{(2\pi f)^2}{2\pi f_w}$$


10)

Op-Amp

$$A_{OL} = \frac{A_{OLC}}{1 + j \frac{f}{f_{3dB}}}$$

$$= \frac{1}{\frac{1}{A_{OLC}} + j \frac{f}{f_w}}$$


$$\frac{1}{1 + \frac{s}{2\pi f_w}}$$

Shift in Q

$$Q_{\text{shift}} = \frac{Q}{1 - Q \cdot \frac{2f_0}{f_{\text{in}}}}$$

$$\frac{Q \cdot 2f_0}{f_{\text{in}}} \ll 1$$

11)

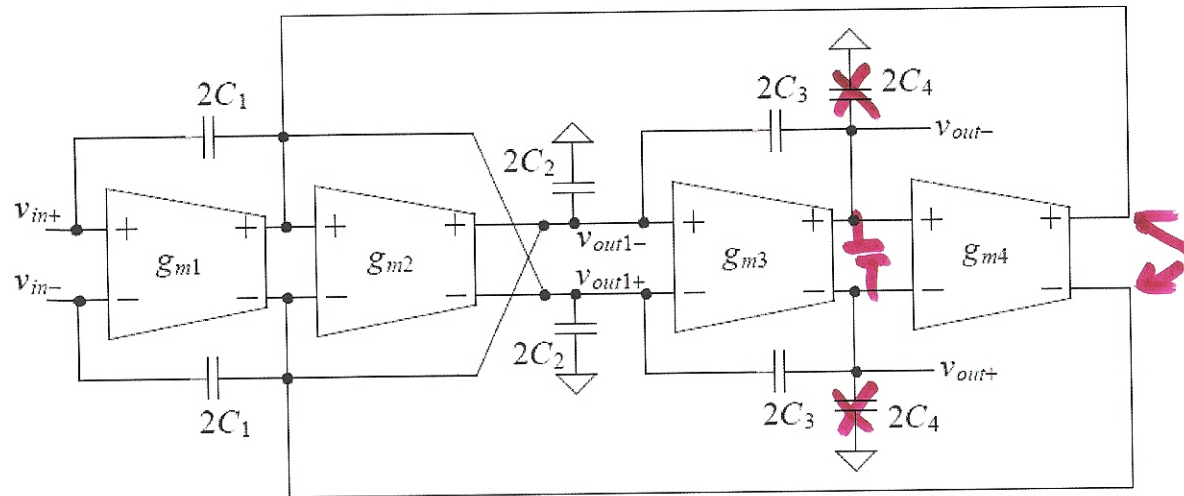

$$G_1 = g_{m1}/(C_1 + C_2) \quad G_2 = \frac{g_{m2}}{g_{m1}} \quad G_3 = \frac{C_1}{g_{m1}} \quad G_4 = g_{m3}/(C_3 + C_4) \quad G_5 = \frac{g_{m4}}{g_{m1}} \quad G_6 = \frac{C_3}{g_{m3}}$$

Figure 3.53 Implementing a biquadratic filter using transconductors.