
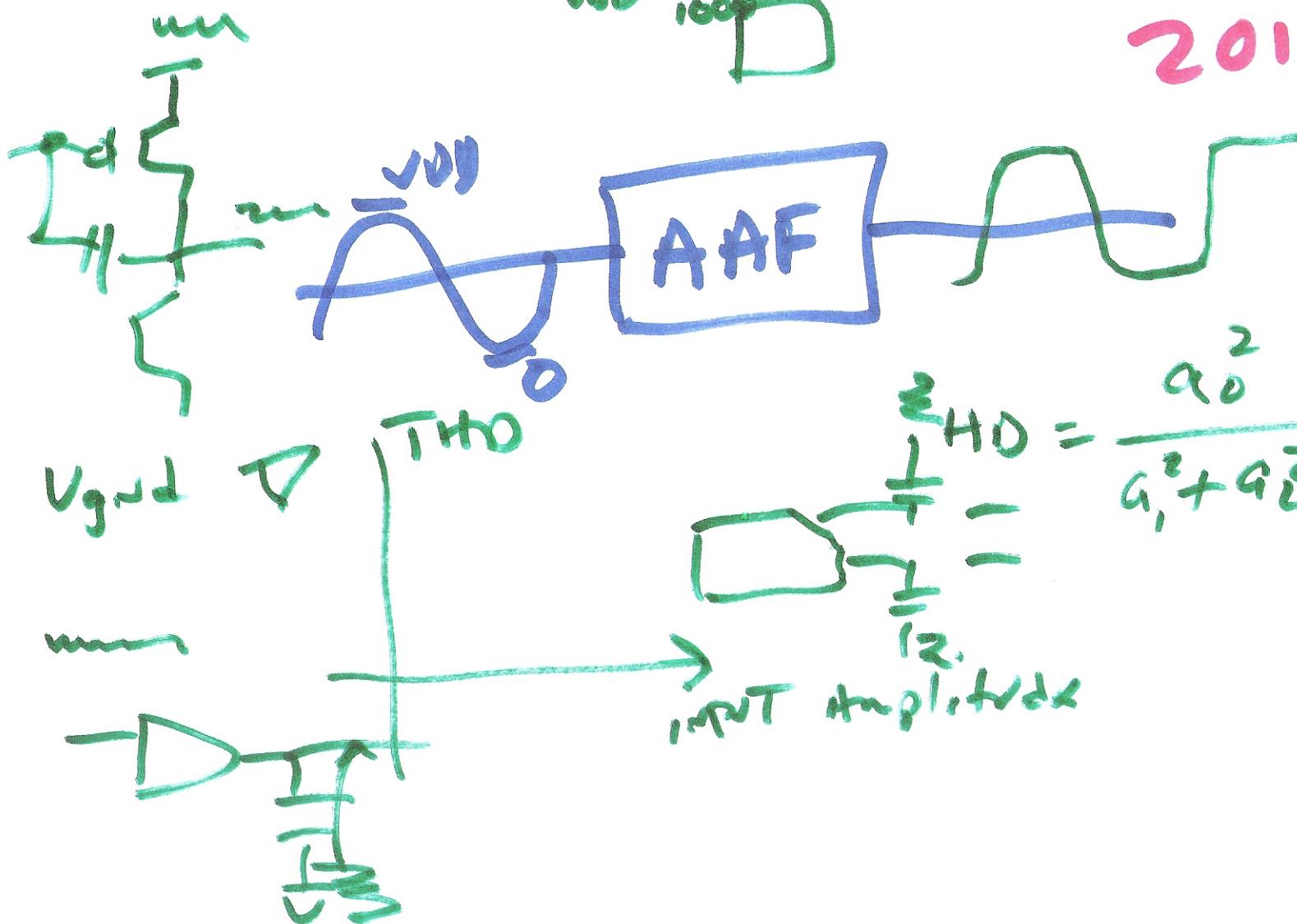



circuit Design

Lecture 13 Oct. 13, 2010

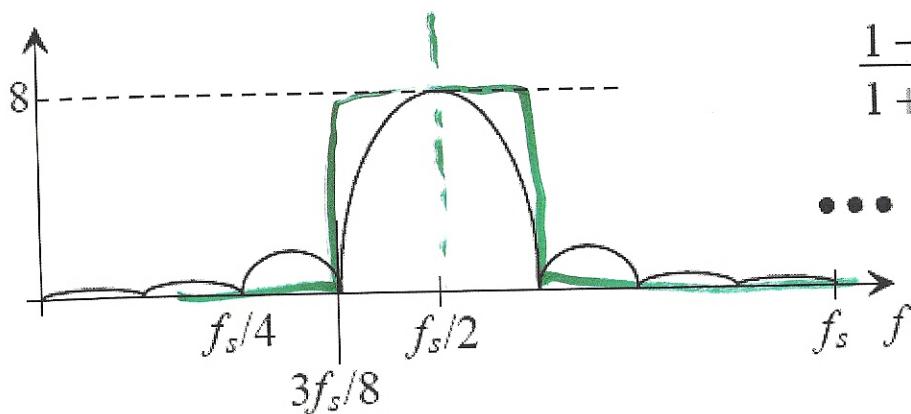


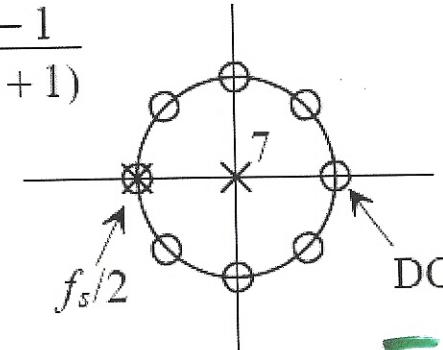
$$\frac{1 - z^{-8}}{1 + z^{-1}} = \frac{z^8 - 1}{z^7(z+1)}$$



.99532

Integers!

Figure 4.19 A highpass filter implementation using a comb filter.

comb filter followed
by a resonator

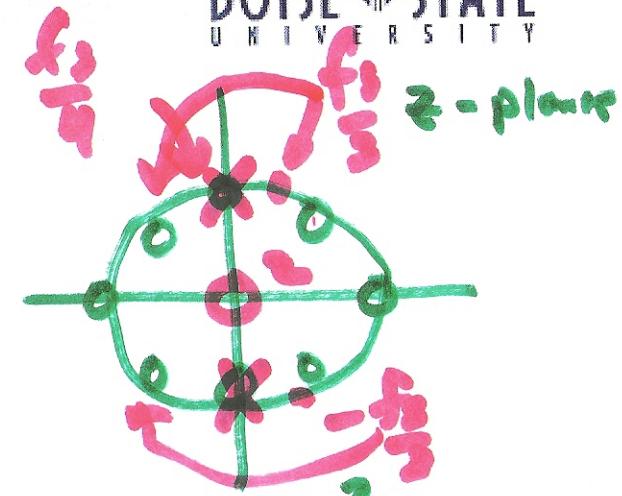
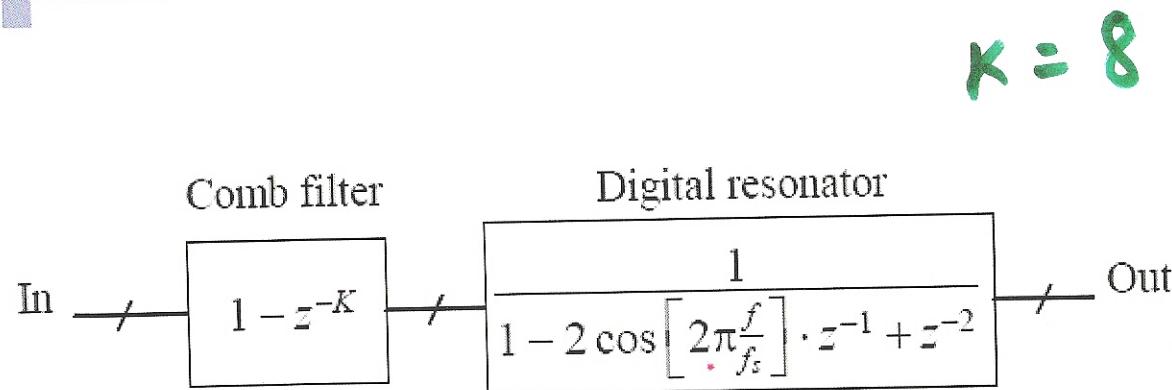


Figure 4.20 Implementing a sinc-shaped bandpass filter.

$$\frac{1}{1 + z^{-2}} = \frac{z^2}{z^2 + 1} = \frac{z^2}{(z + j)(z - j)}$$

$$\frac{1}{1 - z^{-1} + z^{-2}} = \frac{z^2}{z^2 + z + 1} \quad \text{change sign}$$

$$\frac{-1 \pm \sqrt{1 - 4}}{z^2} = \frac{-1 \pm \sqrt{5}}{z^2}$$

3) $= -\frac{1}{2} \pm \frac{\sqrt{5}}{2}j \quad K=12 \quad (z + \frac{1-\sqrt{5}}{2}j)(z + \frac{1+\sqrt{5}}{2}j)$

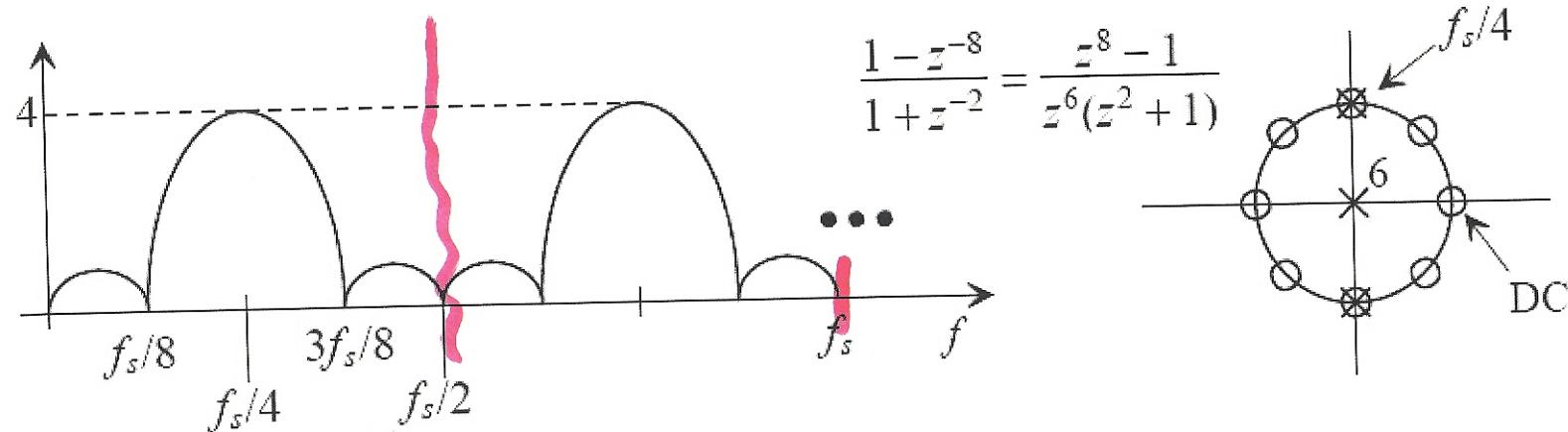


Figure 4.21 A bandpass filter implementation using a comb filter and digital resonator.


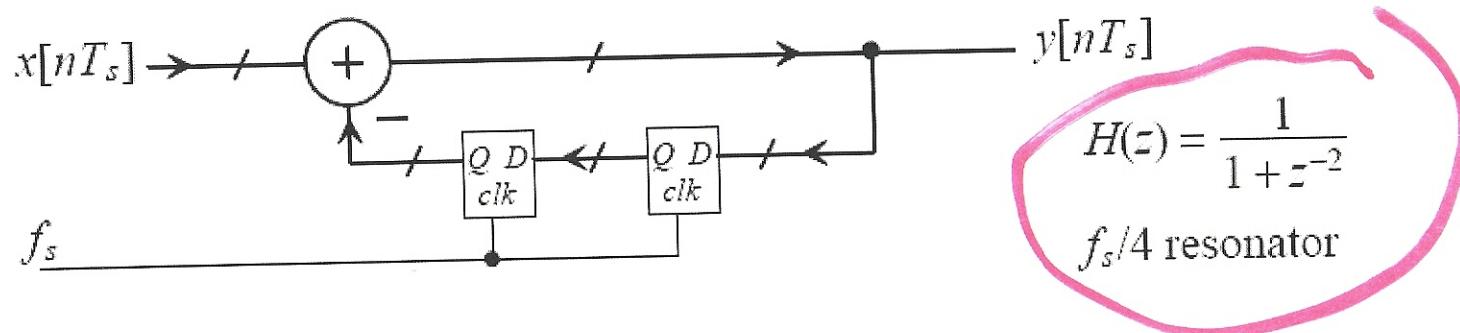


Figure 4.23 Implementation of a digital resonator.

$$\frac{1}{1 - z^{-1} + z^{-2}}$$

$$x + yz^{-1} - yz^{-2} = y$$
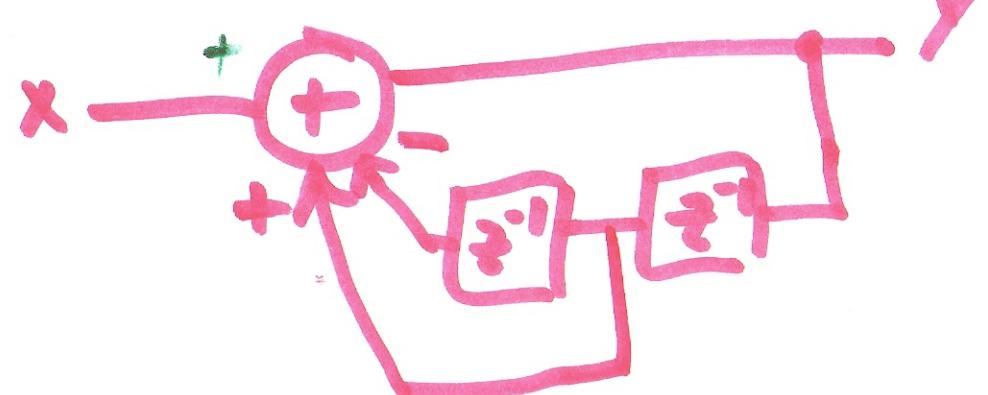
$$\frac{y}{x} = \frac{1}{1 - z^{-1} + z^{-2}}$$



5)

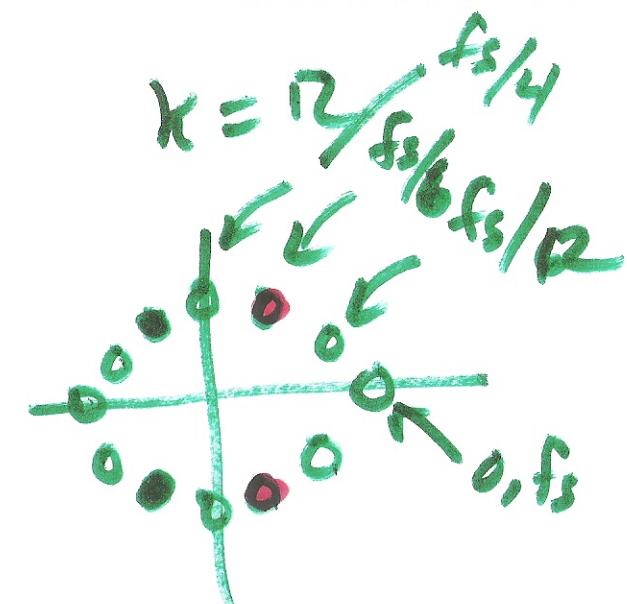
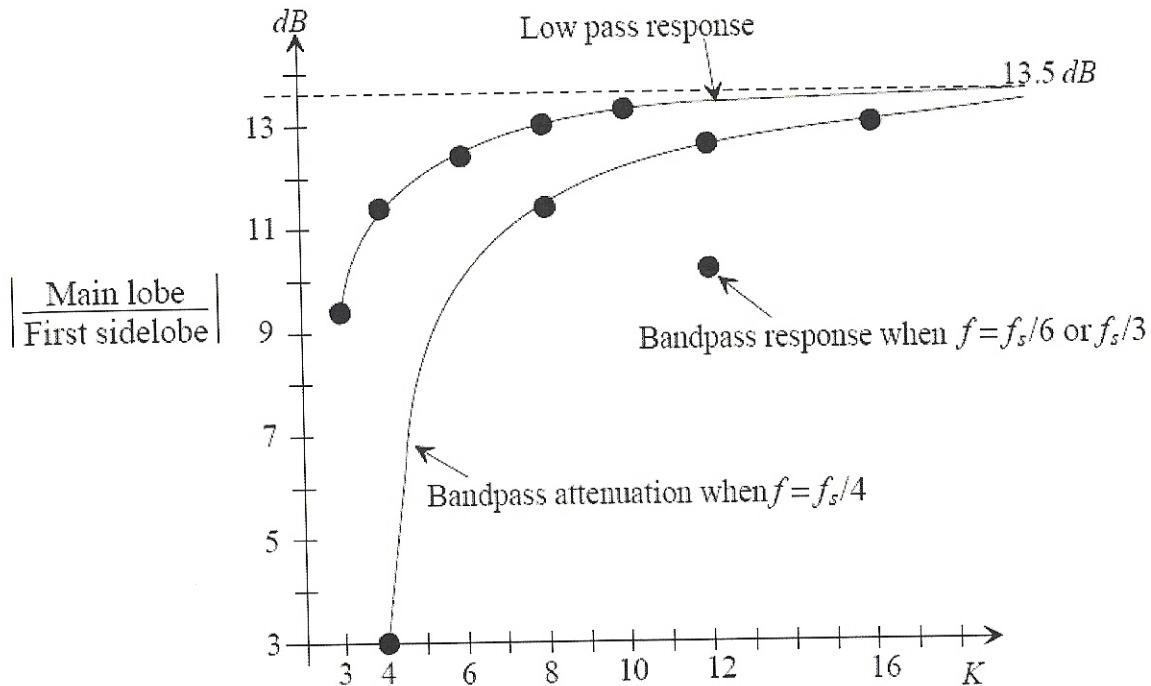


Figure 4.22 Lowpass and bandpass filter attenuation versus number of comb filter zeroes, K.


for $\frac{f_s}{3}$ \rightarrow $\frac{1 - z^{-1}}{1 + z^{-1} + z^2}$ Comb filter - $\frac{1}{1 + z^{-1} + z^2}$ $\stackrel{\text{DT}}{\Rightarrow}$ BP @ $f_s/3$

$$z = -\frac{1}{2} \pm \frac{\sqrt{3}}{2}j$$

for $\frac{f_s}{6}$ $\frac{1 - z^{-1}}{1 + z^{-1} + z^2}$ $\frac{1}{1 - z^{-1} - z^2}$ $z = \frac{1}{2} \pm \sqrt{\frac{3}{2}}j$


$$\frac{1}{1 - 2z^{-1} + z^{-2}} = \frac{z^2}{z^2 - 2z + 1}$$

IV

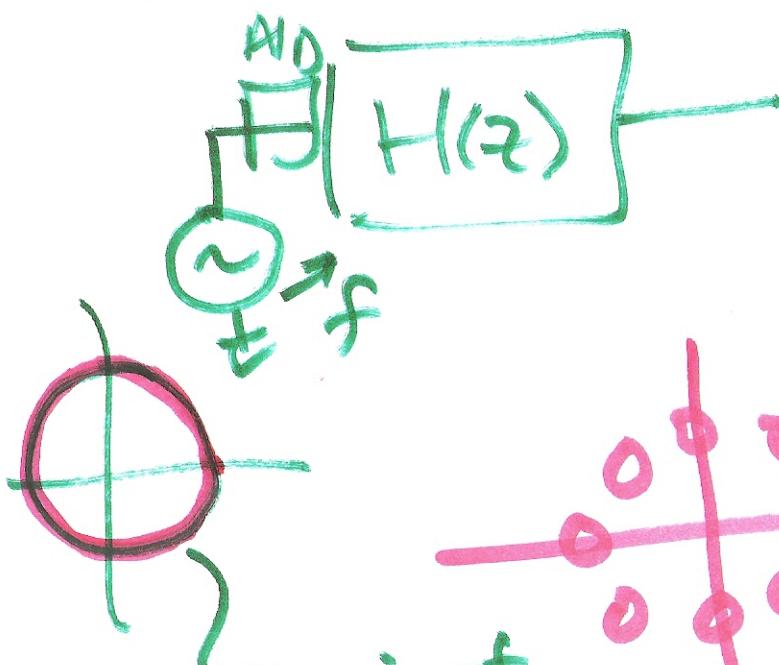

$$z = e^{j\frac{2\pi f}{f_s}}$$

$$= \frac{z^2}{(z-1)(z-1)}$$

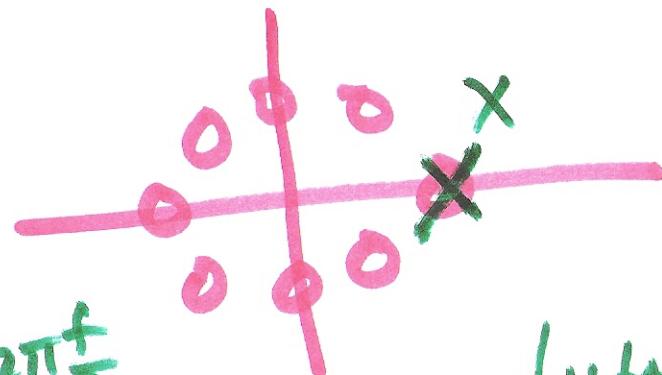

distance to zeros
distance to poles



7)

$$\frac{1}{1 - \frac{1}{2}z^{-1} + z^{-2}} = \frac{z^2}{z^2 - \frac{1}{2}z + 1}$$

$$z = \frac{\frac{1}{2} \pm \sqrt{\frac{1}{4} - 4}}{2}$$

$$= \frac{1}{4} \pm j \cdot \sqrt{\frac{1}{8} - 1}$$
$$= \frac{1}{4} \pm j \sqrt{\frac{15}{8}}$$

a)


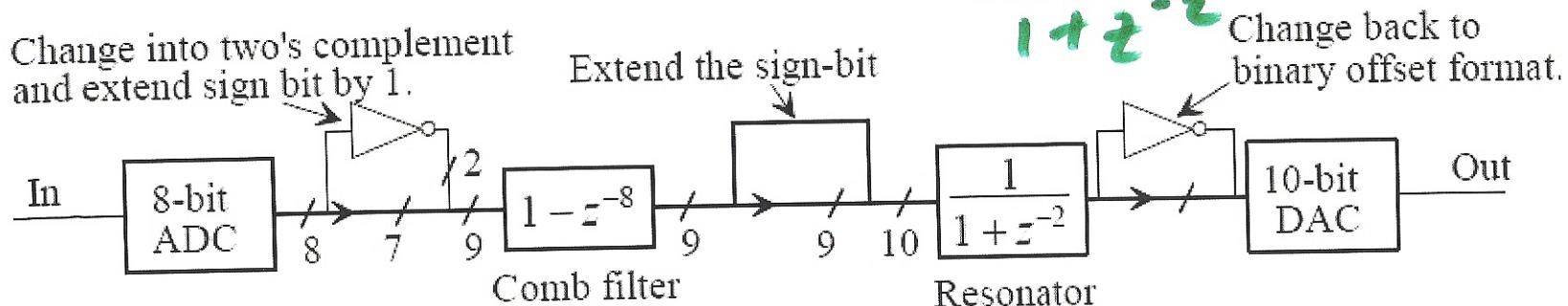


Figure 4.24 Digital filter sketch for Ex. 4.7.

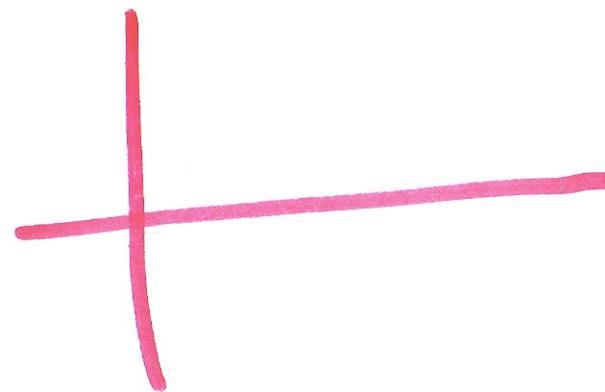

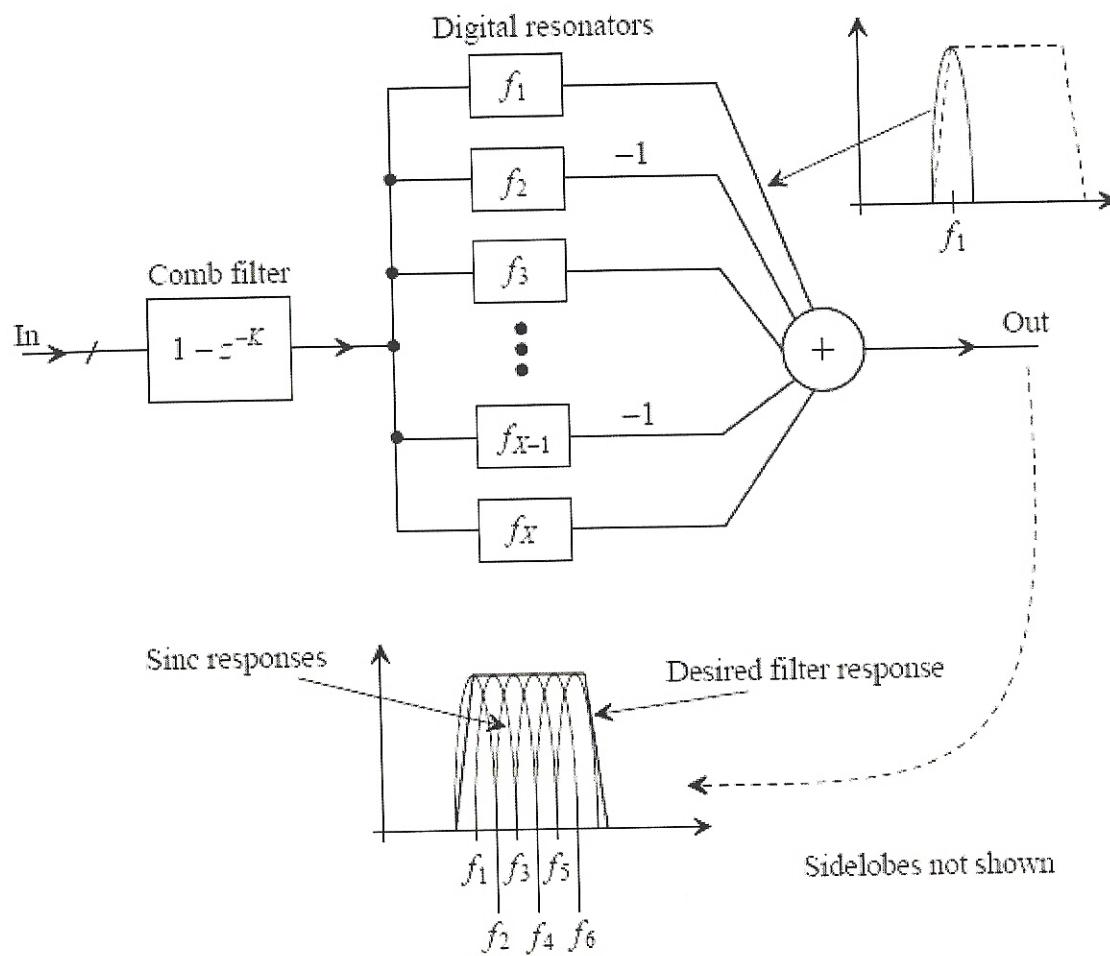


Figure 4.26 A frequency sampling filter.



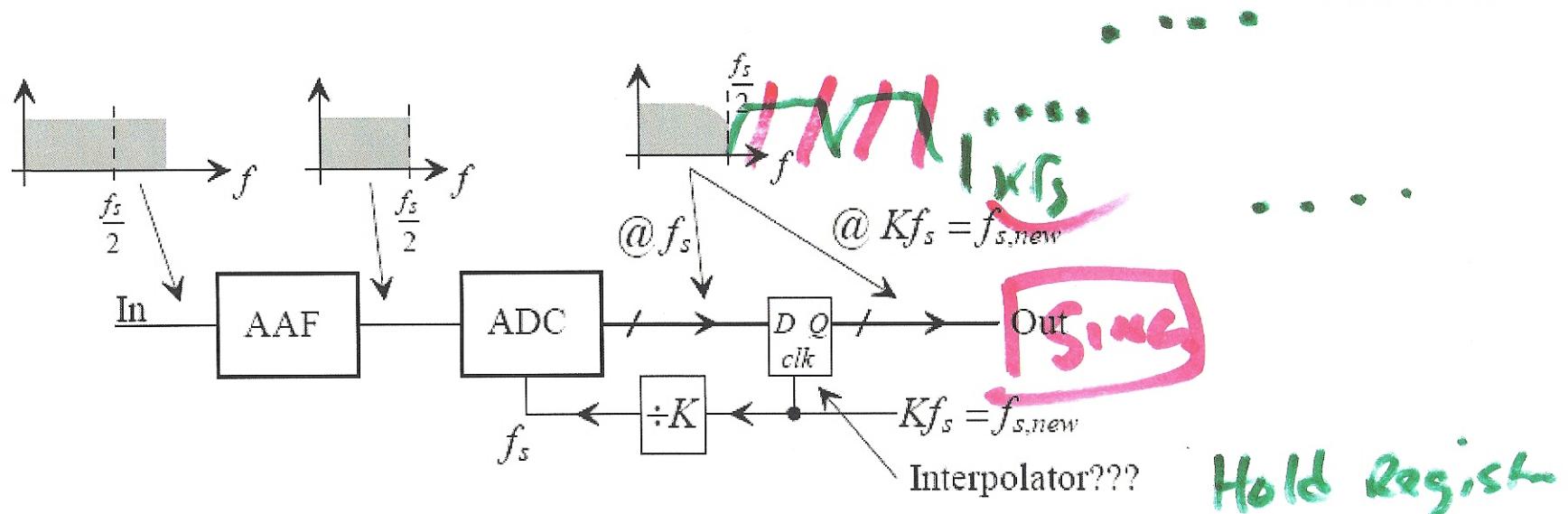


Figure 4.27 Interpolation using a hold register (see Sec. 2.1.5).

Sinc filter




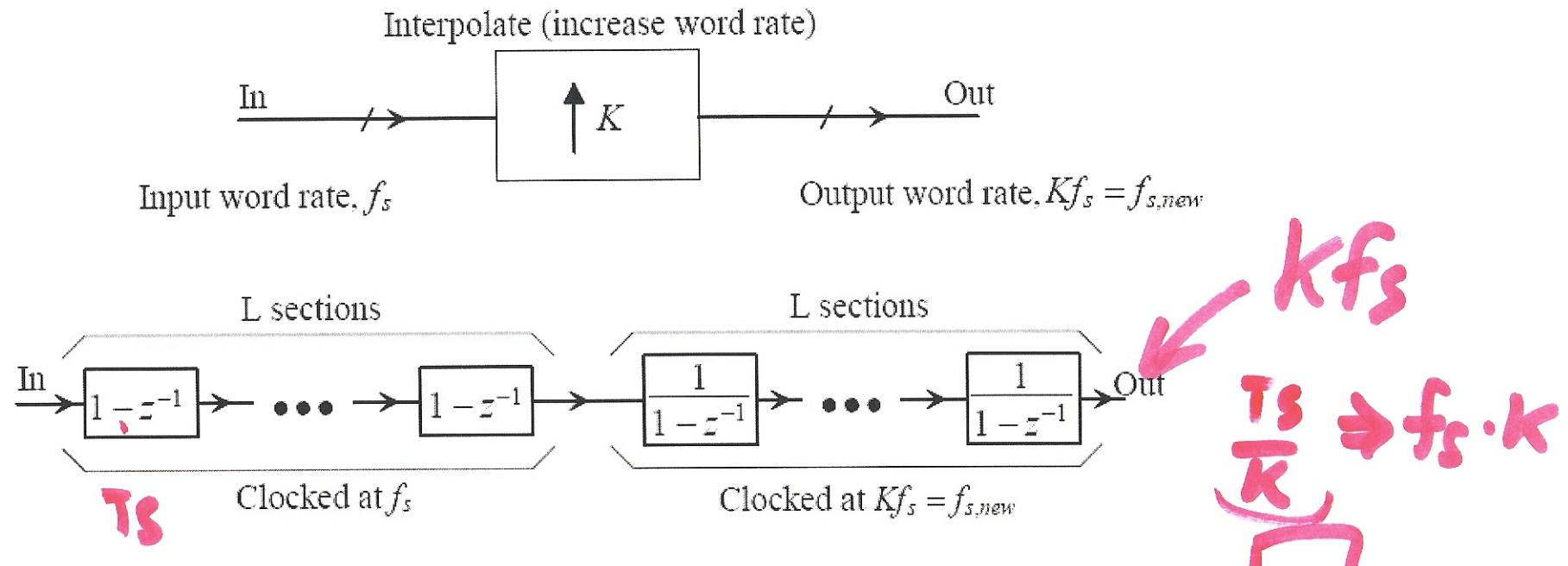


Figure 4.28 Interpolating using Sinc filters for image removal.

$$\left(\frac{1-z^{-K}}{1-z^{-1}} \right)^L$$

↑ c_{f_s}

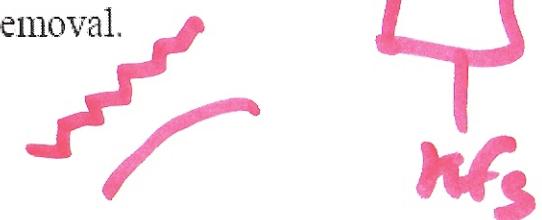


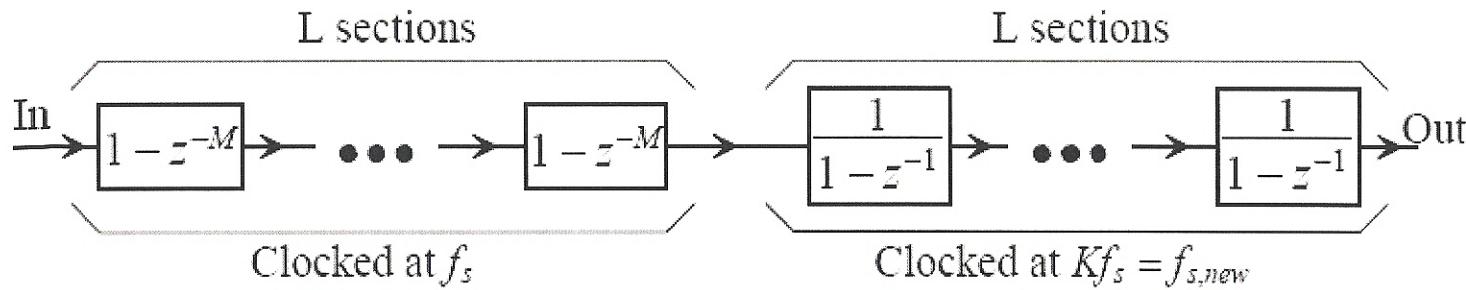


Figure 4.30 General interpolation using Sinc filters.
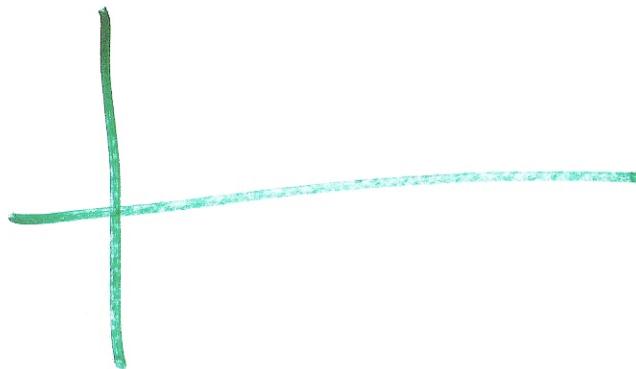
$$\left(\frac{1 - z^{-Km}}{1 - z^{-1}} \right)$$



13)

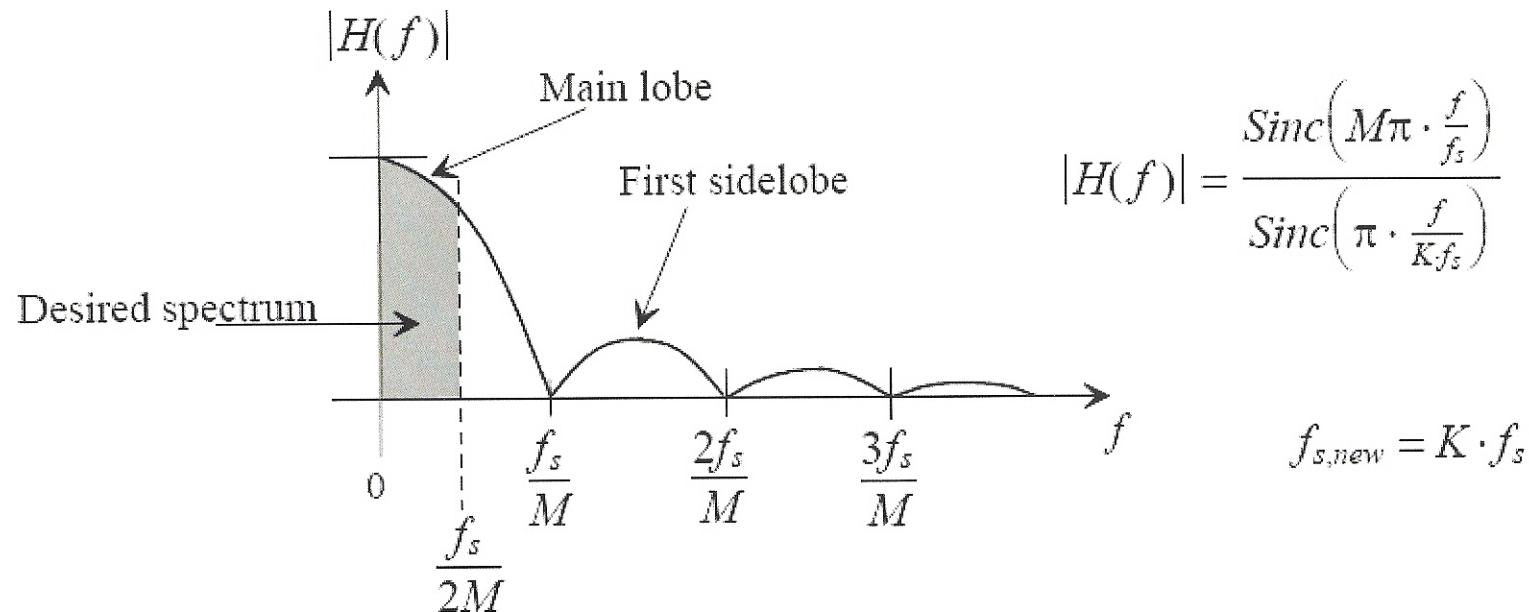


Figure 4.31 Frequency response image removal filter using a Sinc interpolator, Fig. 4.30.