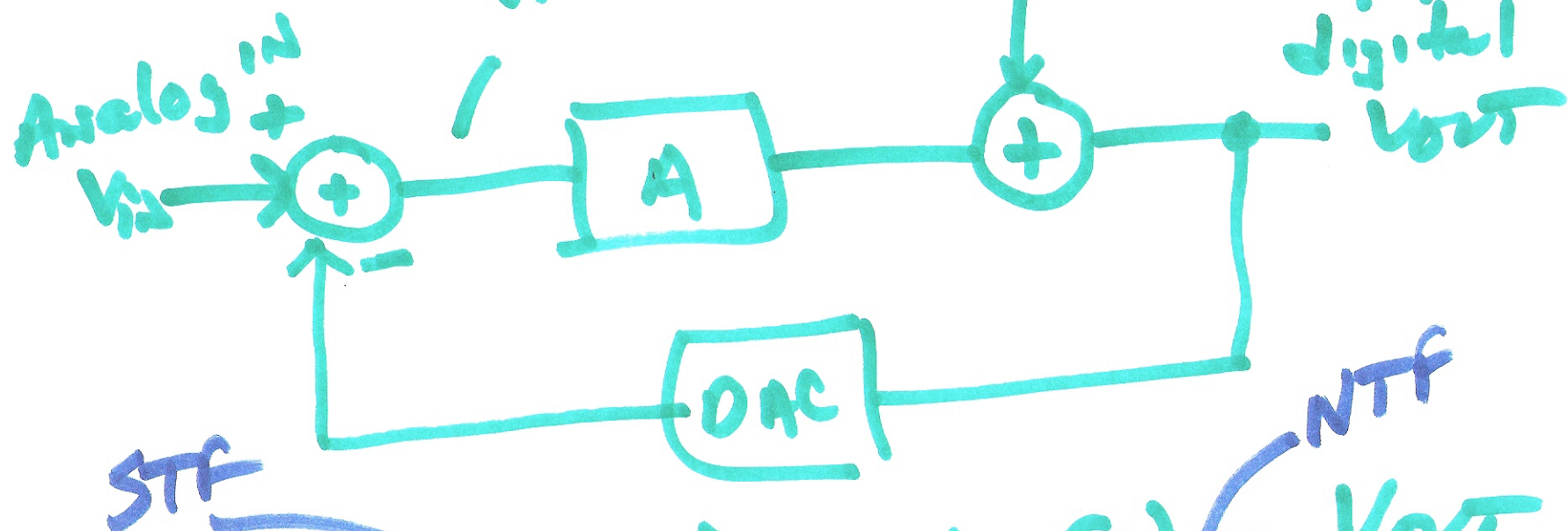


Lecture 19

OCT. 27,
Vae(f) 2010



Noise-shaping
 $V_{in} - V_{out}$



$$A(V_{in} - V_{out}) + V_{ae}(f) = V_{out}$$

$$V_{in} \left(\frac{A}{1+A} \right) + V_{ae} \cdot \left(\frac{1}{1+A} \right) = V_{out}$$

1)

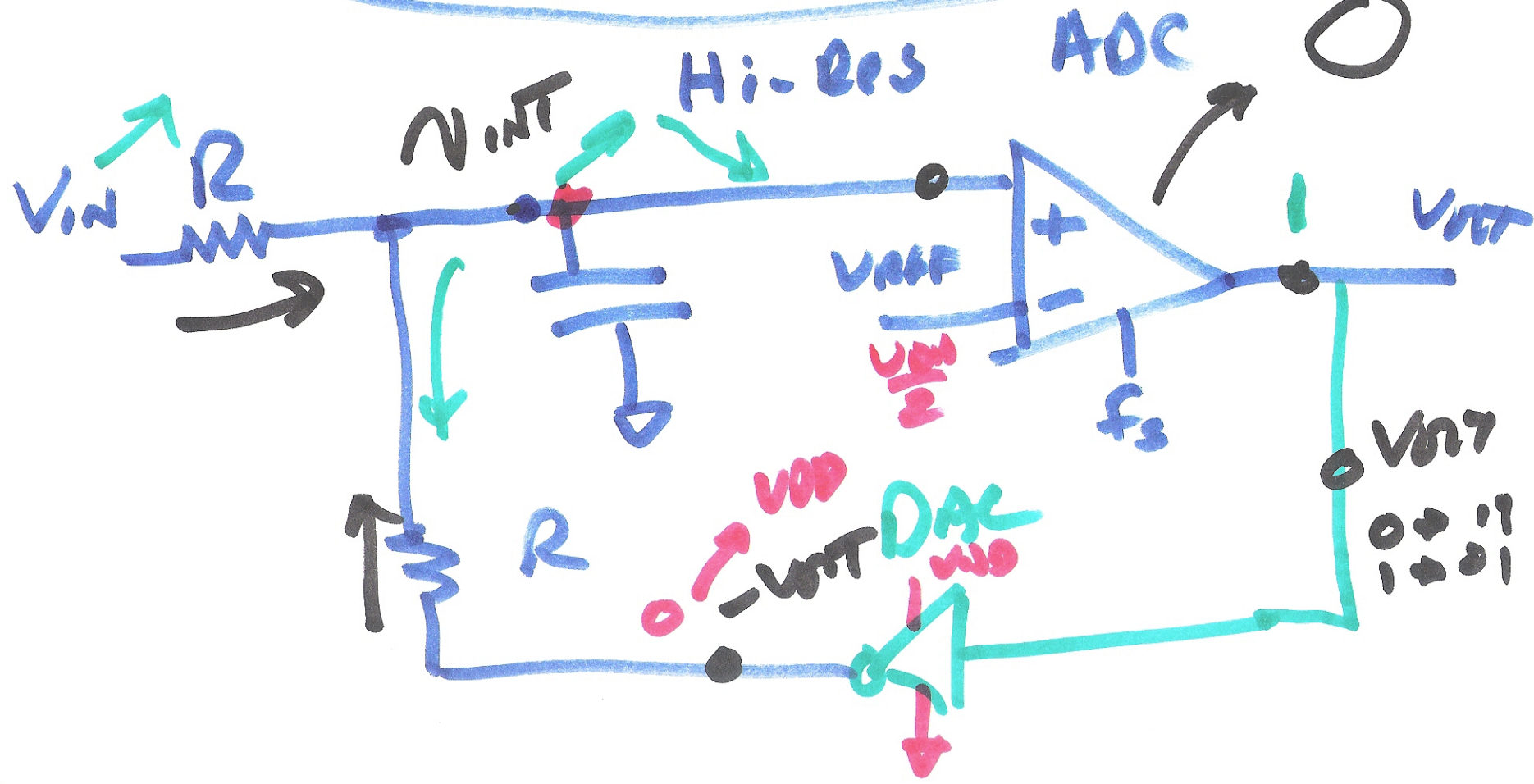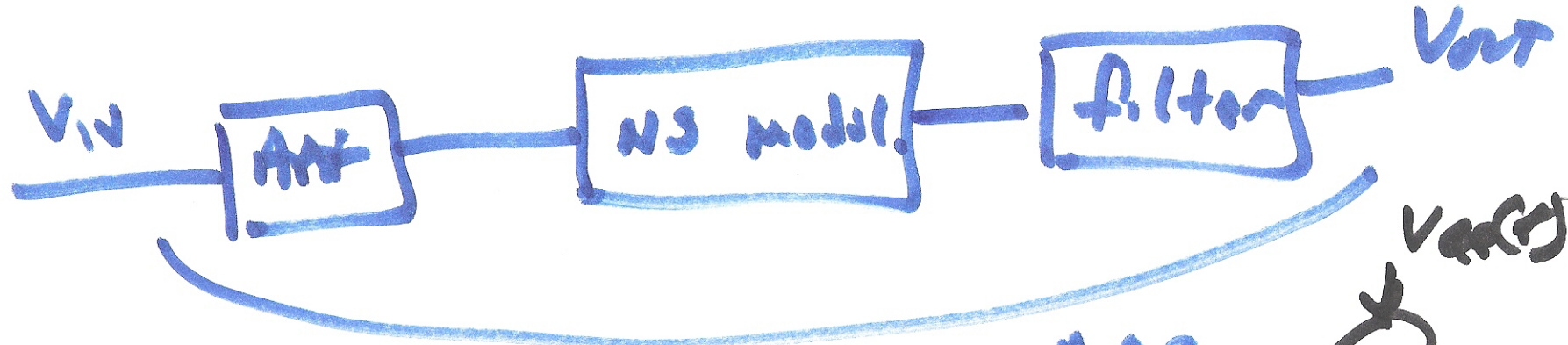

2)

$V_{out} + V_{oe} = V_{in}$

$$V_{in} + V_{oe} = V_{out}$$

$$\frac{V_{in} - V_{out}}{R} + \frac{-V_{out} - V_{out}}{R} = \frac{V_{out}}{j\omega C}$$

$$j\omega RC V_{out} = V_{in} - 2V_{out}$$

$$V_{in} - 2V_{out} + V_{oe} \cdot j\omega RC = 0$$

$$V_{out} (1 + j\omega RC) = V_{in} + V_{oe} \cdot j\omega RC$$


$$V_{out} = \frac{1}{1 + j\omega RC} \cdot V_{in} + \frac{j\omega RC \cdot V_{oe}}{1 + j\omega RC}$$

unwanted

$$+ \frac{-2V_{out}}{1 + j\omega RC}$$

→


$$V_{NT} \rightarrow 0$$

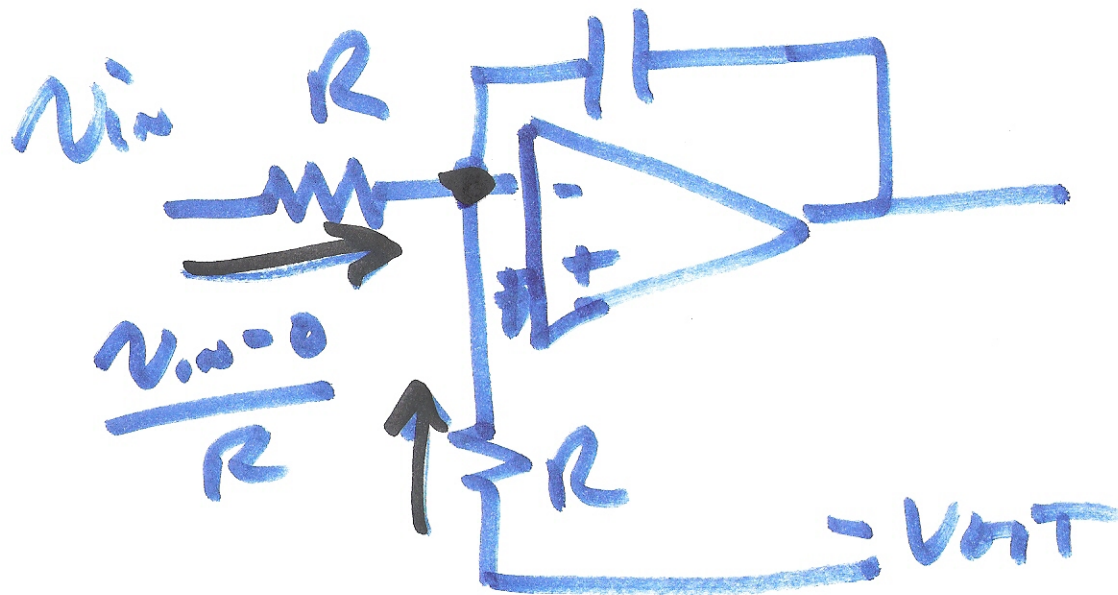


$$\frac{-V_{NT} = 0}{R}$$

NTF
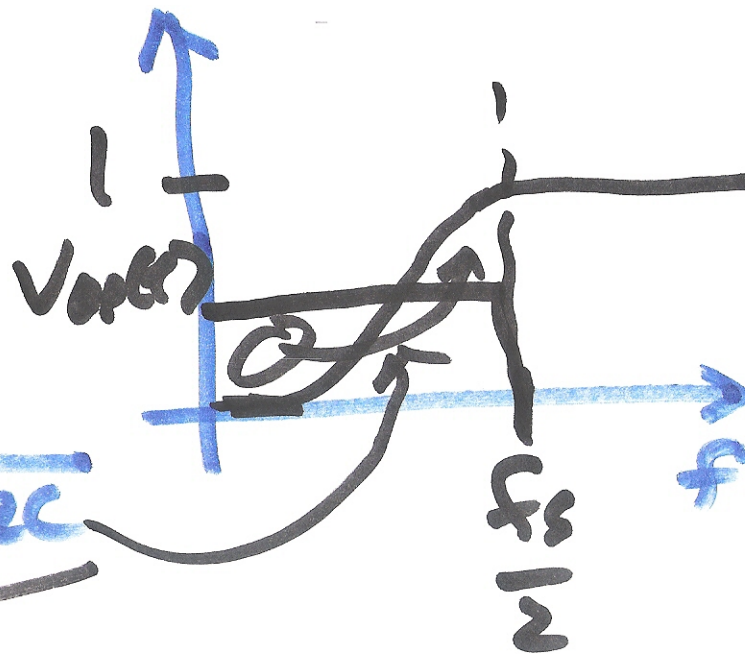
$$V_{oe} \cdot \frac{j\omega RC}{1 + j\omega RC}$$




4)

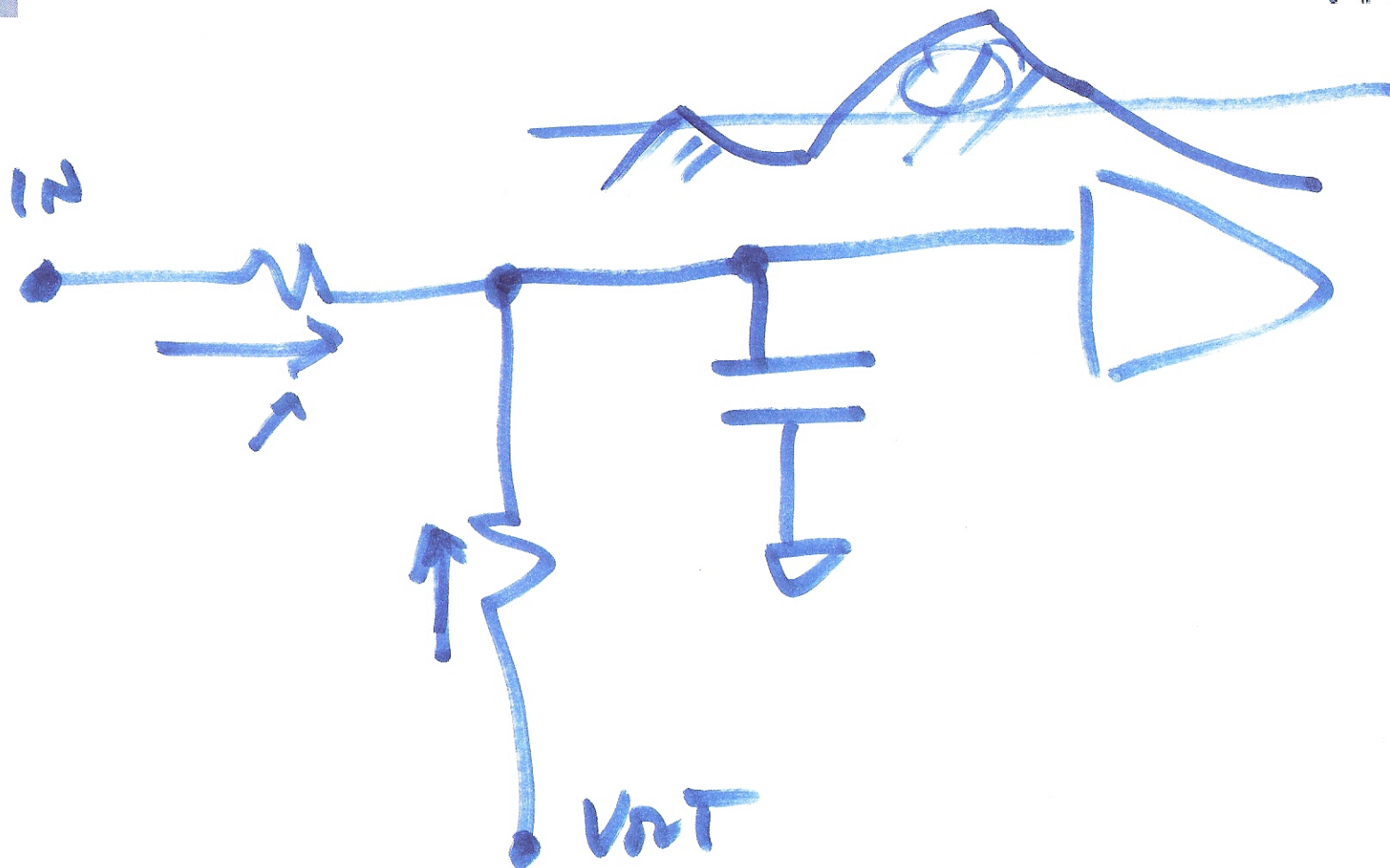

5)

$|V_{out}|^2 \cdot |NTF|^2 = \text{modulation noise}$

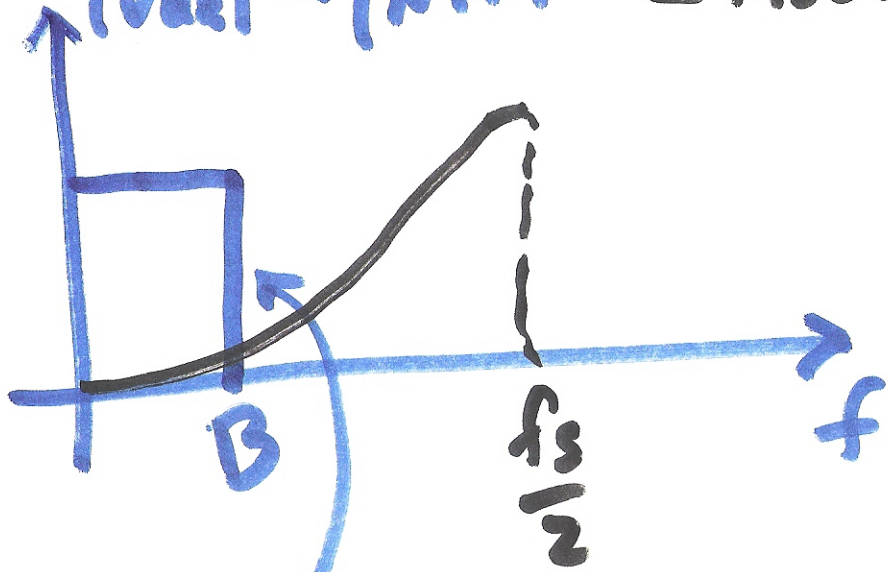

low freq
 $\frac{j\omega RC}{1+j\omega RC} \approx j\omega RC$

$|j\omega RC|^2 = \omega^2 R^2 C^2$

ideal lowpass response


$$V_{noise, rms}^2 = \int_0^B \frac{V_{LSS}^2}{12f_s} \cdot (\omega RC)^2 \cdot df = 2 \cdot \frac{V_{LSS}^2}{12f_s} \cdot \frac{B^3}{3}$$

6)

$$B = \frac{f_s}{2k}$$

$$V_{noise, rms}^2 = \frac{V_{LSB}^2}{12} (2\pi ac)^2$$

$$\frac{f_s^2}{12k^3}$$

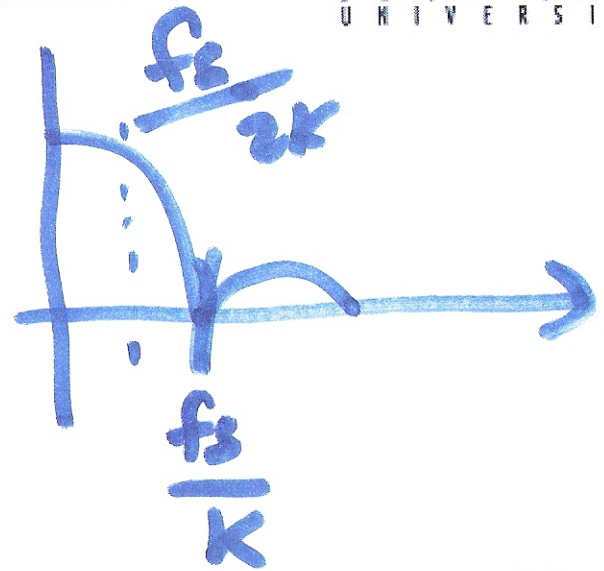

0.5 bits
1.5 bits

$$SNR = 20 \log \frac{V_P/\sqrt{2}}{V_{noise, rms}}$$

$$= 6.02N + 1.76 +$$

$$- 20 \log \frac{2\pi ac \cdot f_s}{\sqrt{12}}$$

$$+ \underbrace{20 \log k^{3/2}}_{30 \log k}$$

$$30 \log k$$

18.06

36 bits

7)

$$\log_2 k \geq \frac{30 \log_2 k - 18.06}{6.02}$$

Nine


$$\log_2 2^3 = .9$$

$$k = 8$$

$$\log_2 2^3 \geq \frac{27 - 18.06}{6.02} \approx 1.5$$

$$\underline{\underline{3 \geq 1.5}}$$


$$k \leq 256 \quad L = 1$$

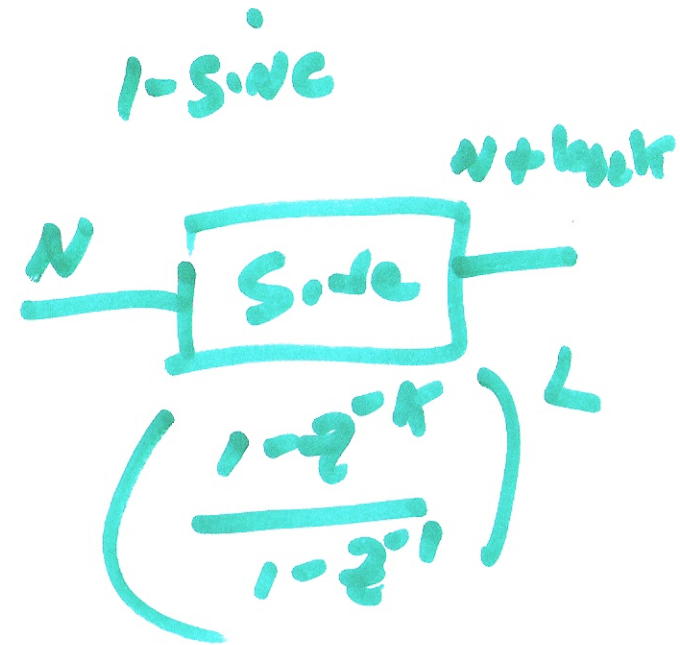


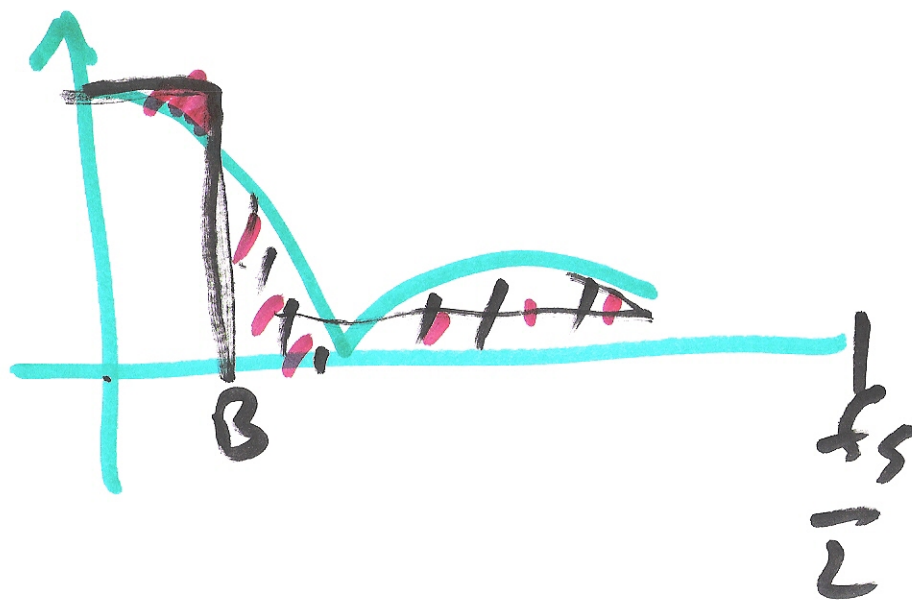
8)

Using a sinc filter

$$V_{be,rms}^2 = \frac{V_{LSS}^2}{12} (2\pi RC)^2 \cdot \frac{f_s^2}{2\pi^2 K^3}$$



a)

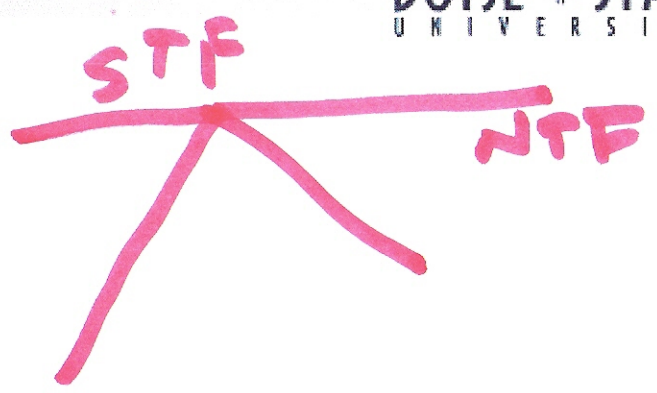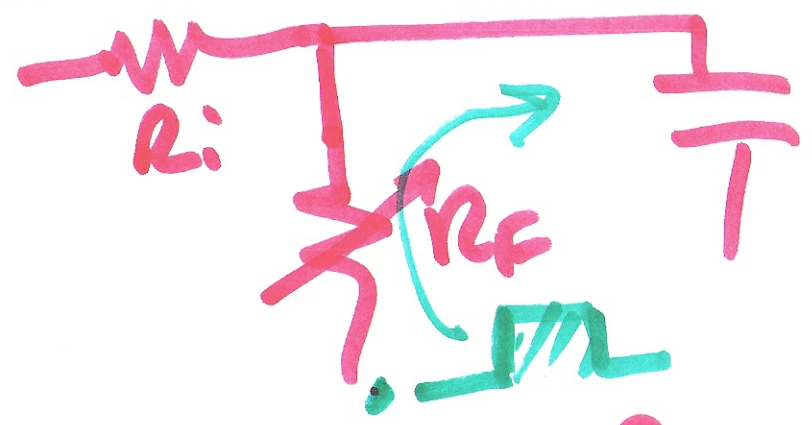


$$\frac{\frac{R_f}{R_i} \cdot V_{in}}{1 + j\omega C R_f}$$


STF

$$\frac{V_{op} + j\omega R_f}{1 + j\omega R_f C}$$

NTF

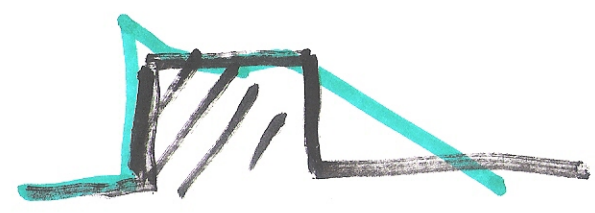

10)

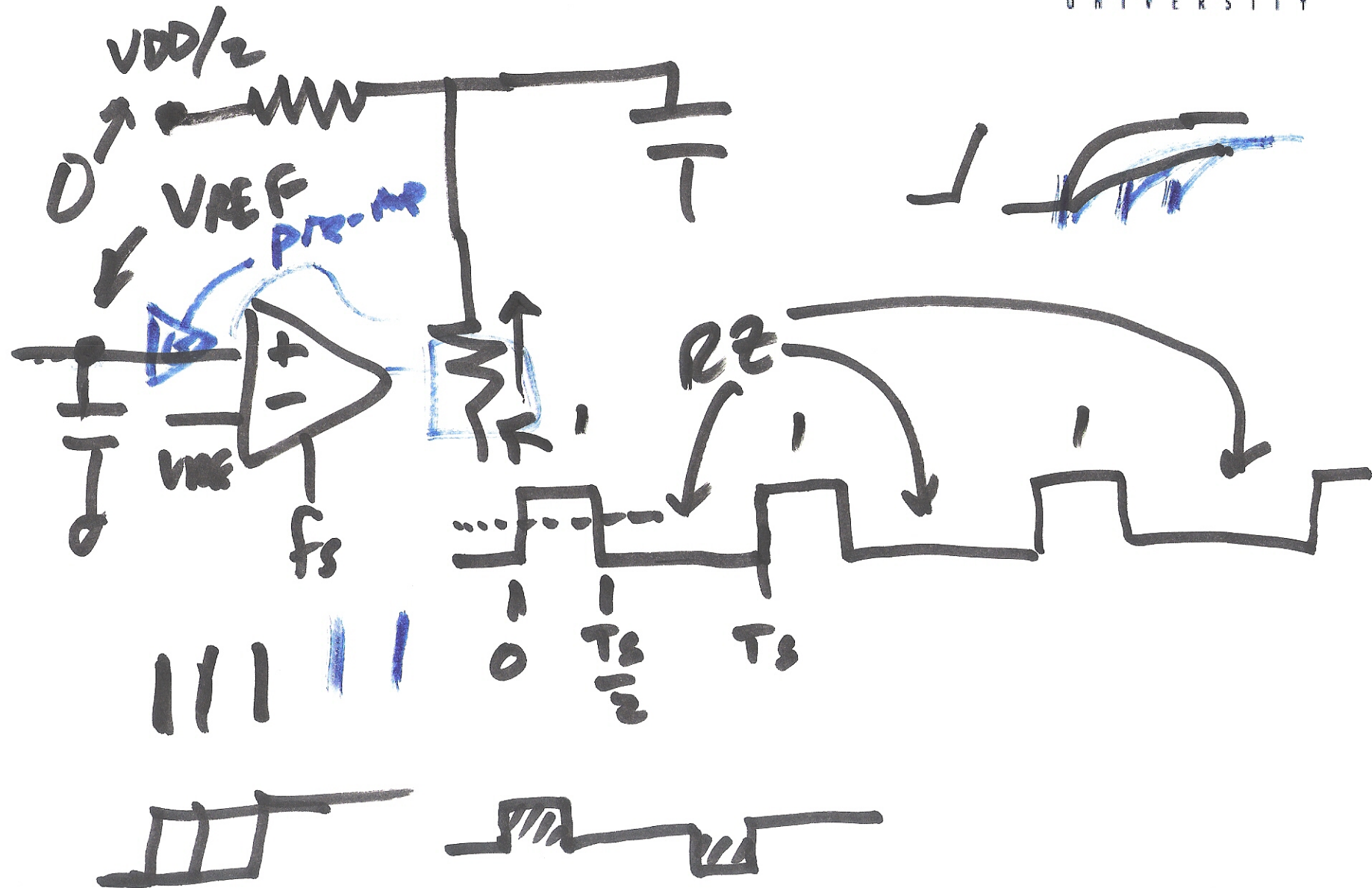

ii)