


# ECE 615 CMOS Mixed-Signal



## Circuit Design

Lecture 23,

Nov. 10, 2010

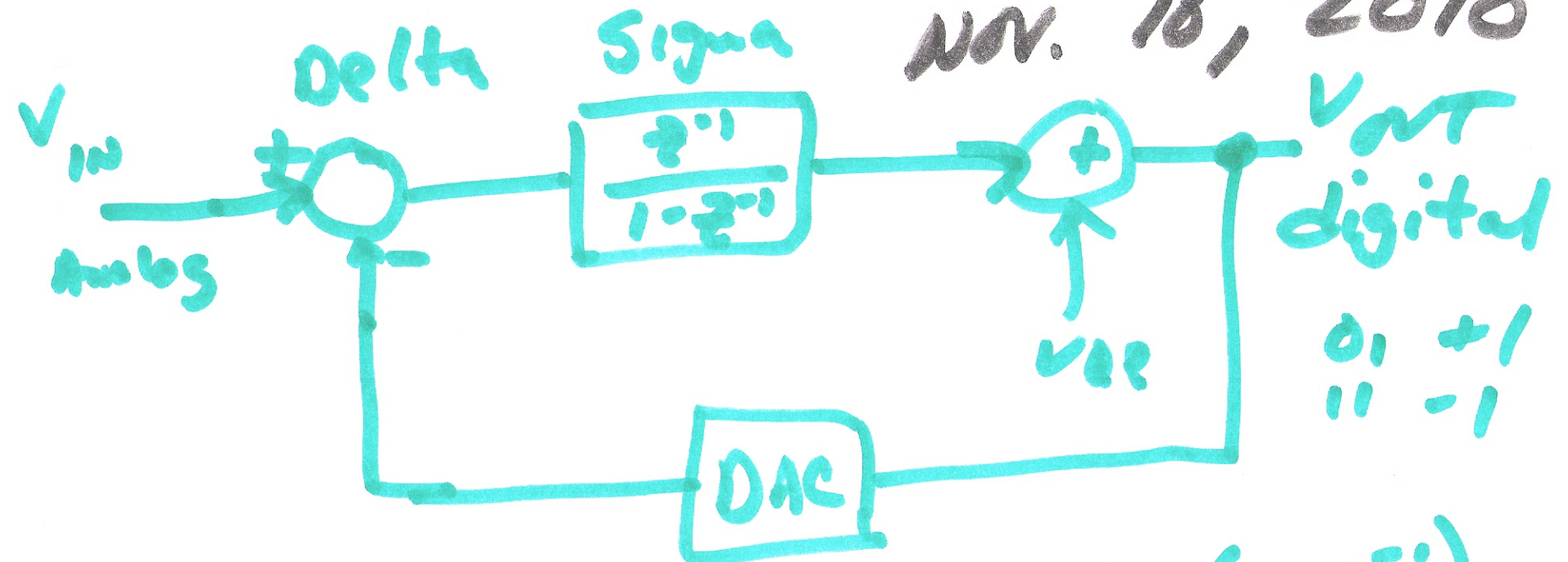

$$V_{OUT} = z^{-1} \cdot V_{IN} + V_{DAC}(1 - z^{-1})$$

$$V_{OUT}[NTS] = V_{IN}[(N-1)TS] + V_{DAC}[NTS] - V_{DAC}[(N-1)TS]$$

1)

$$2 \sin \pi f / f_s$$

$$NTF \cdot V_{oe} = (1 - e^{-j2\pi f \cdot T_s}) \cdot \frac{V_{LSB}}{\sqrt{12f_s}}$$

$$V_{LSB} = \frac{V_{REF} - V_{REF}}{2N}$$

$$0 \leq f \leq \frac{f_s}{2}$$

$$|NTF \cdot V_{oe}|^2 = \frac{V_{LSB}^2}{12f_s} \cdot 4 \cdot \sin^2 \pi \frac{f}{f_s}$$

$$R_{ms} = 2 \int_0^B \frac{V_{LSB}^2}{12f_s} \cdot 4 \cdot \sin^2 \pi \frac{f}{f_s} \cdot df$$

$$B = \frac{f_s}{2K} \quad B < f_s \quad \sin x \approx x$$

2)

$$\approx 8 \frac{V_{LSB}^2}{12 f_s} \cdot \frac{\pi^2}{f_s} \int_0^B f^2 df$$

$$V_{OP,MS}^2 = \frac{8\pi^2}{12} \cdot \frac{V_{LSB}^2}{f_s^3} \cdot \frac{B^3}{3}, \quad B = \frac{f_s}{2k}$$

$$= \frac{8\pi}{12} \cdot \frac{V_{LSB}^2}{f_s^2} \cdot \frac{f_s^3}{8k^3}$$

$$V_{OP,MS} = \frac{V_{LSB}}{\sqrt{12}} \sqrt{\frac{\pi}{k^2}} \frac{\pi}{\sqrt{3}} \cdot \frac{1}{k^{3/2}}$$

3)

$$\text{SNR}_{\text{ideal}} = 6.02 \overset{1\text{-bit}}{N} + 1.76 - 5.17 + 30 \log K$$

first-order

$$= 6.02(N + N_{\text{ave}}) + 1.76$$

1-bit

5-bits


$$N_{\text{ave}} =$$

$$\frac{30 \log K - 5.17}{6.02}$$

$$K = 8$$

$$3.64 \text{ bits} \rightarrow 4 \text{ bits}$$
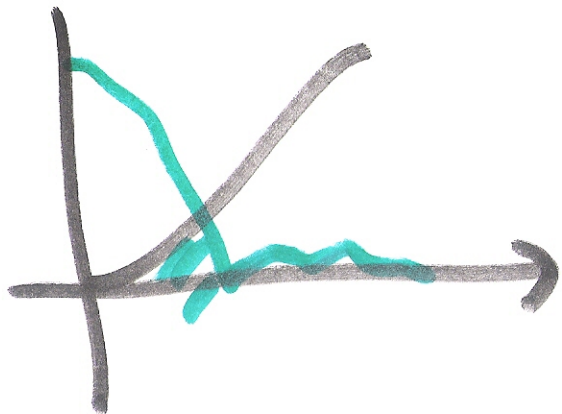
$$\frac{1 - 2^{-8}}{1 - 2^{-1}} \rightarrow \log_2 K = 3.6 \text{ bits}$$



4)

$L = \#$  Sinc filters we  
cascade

$$L \cdot \log_2 K \geq \frac{30 \log K - 5.17}{6.02}$$


$M =$  order of the modulation

$M = 1$  (first order)

$$L = M + 1$$

5)

# Filtering output of 1st-order

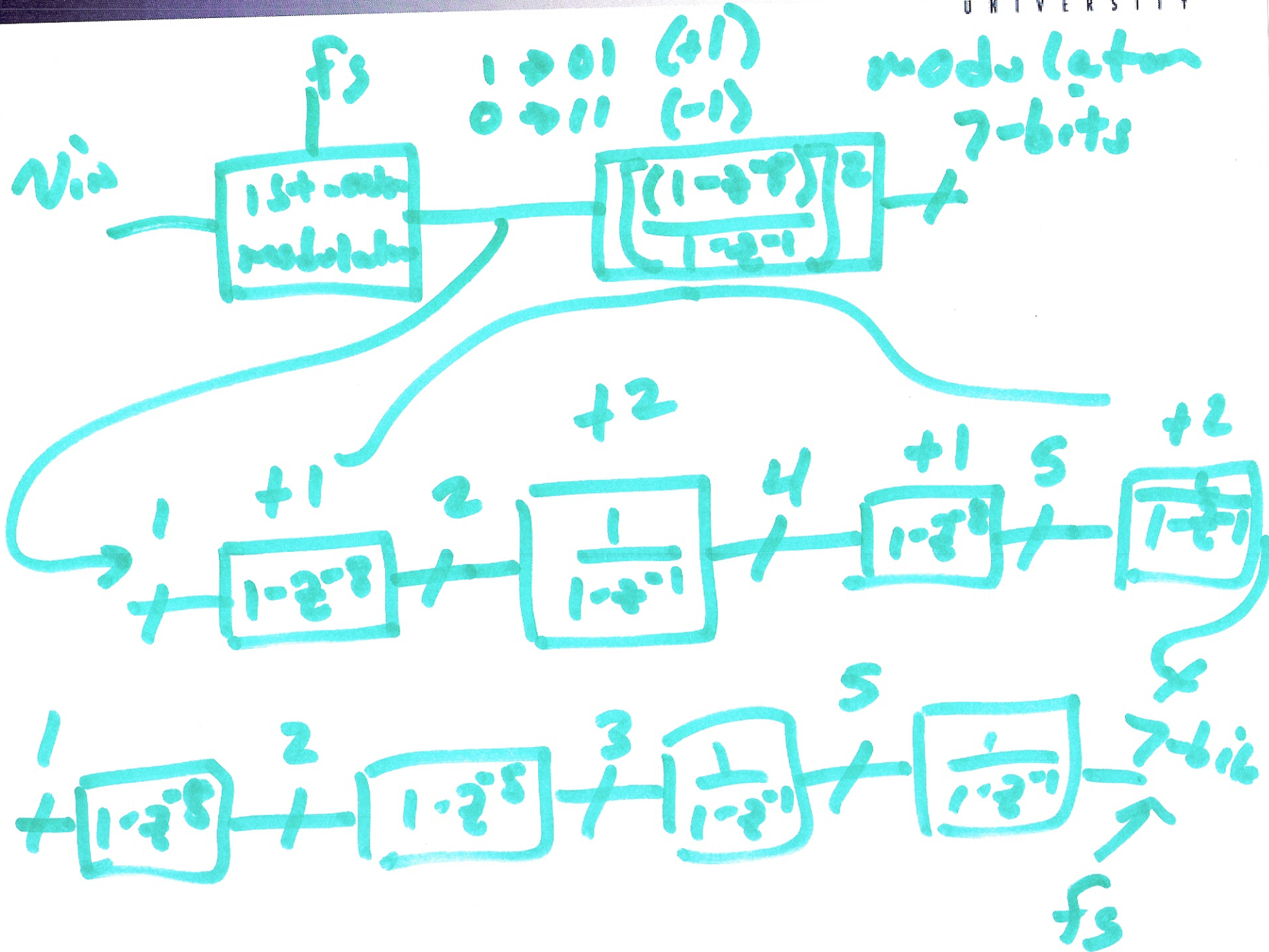

6)


# 1st-order Modulation $K=8$

$$\left[ \frac{1-z^{-8}}{1-z^{-1}} \right]^2$$

$$L=2$$



$$M=1$$

Mixing decimation & filtering

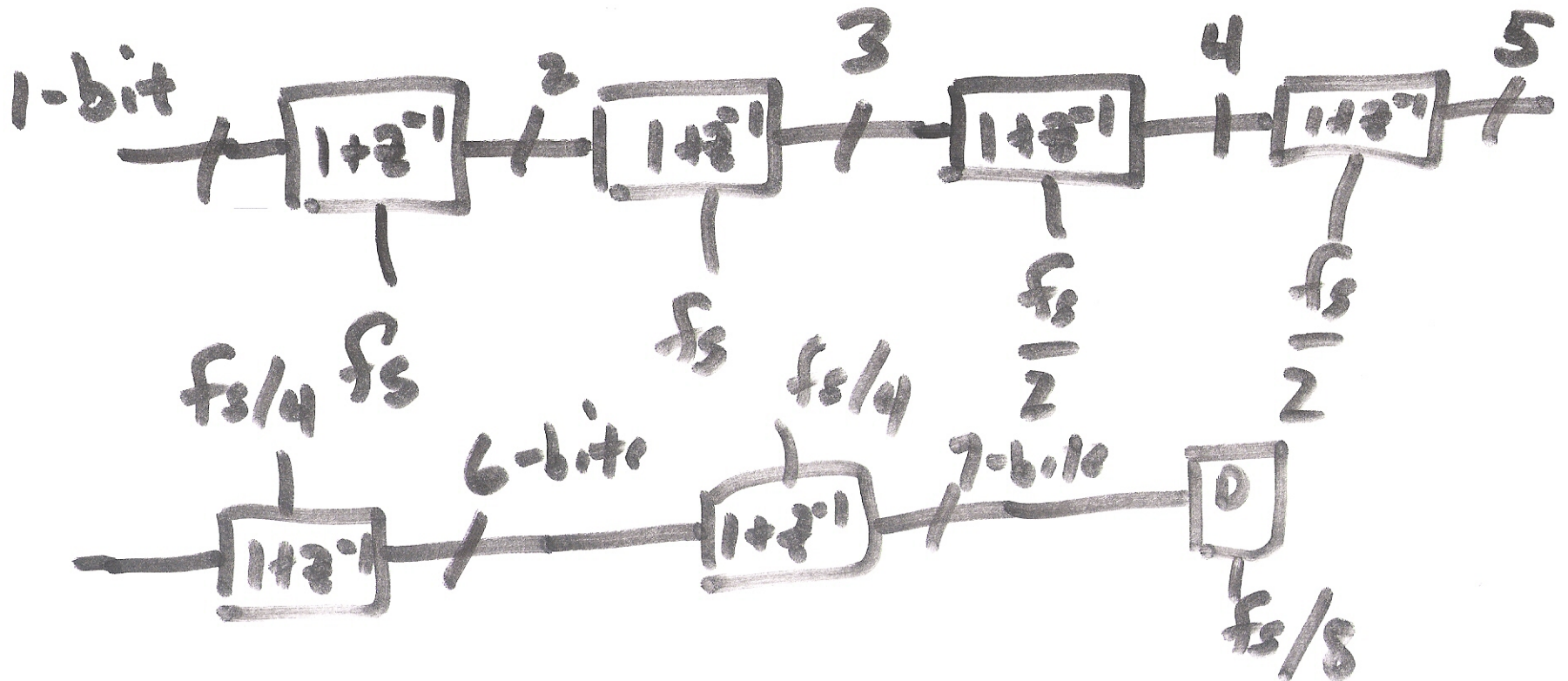

7)

# Limit cycle oscillations

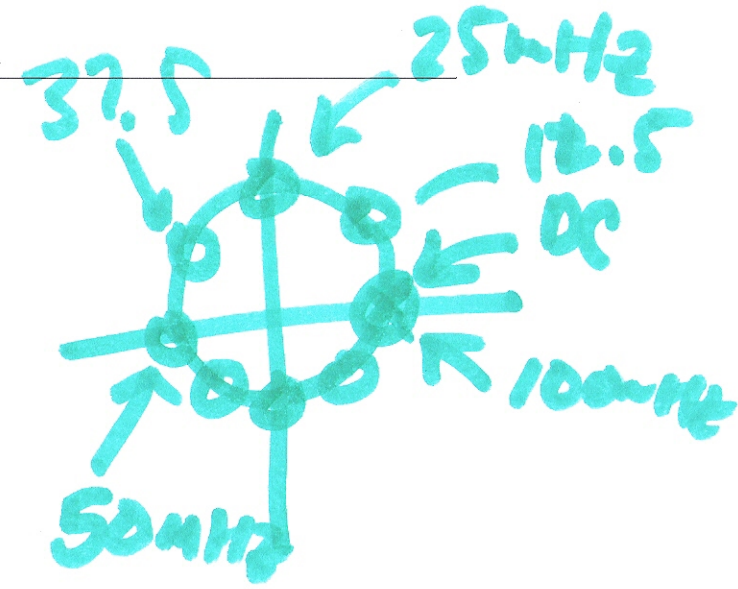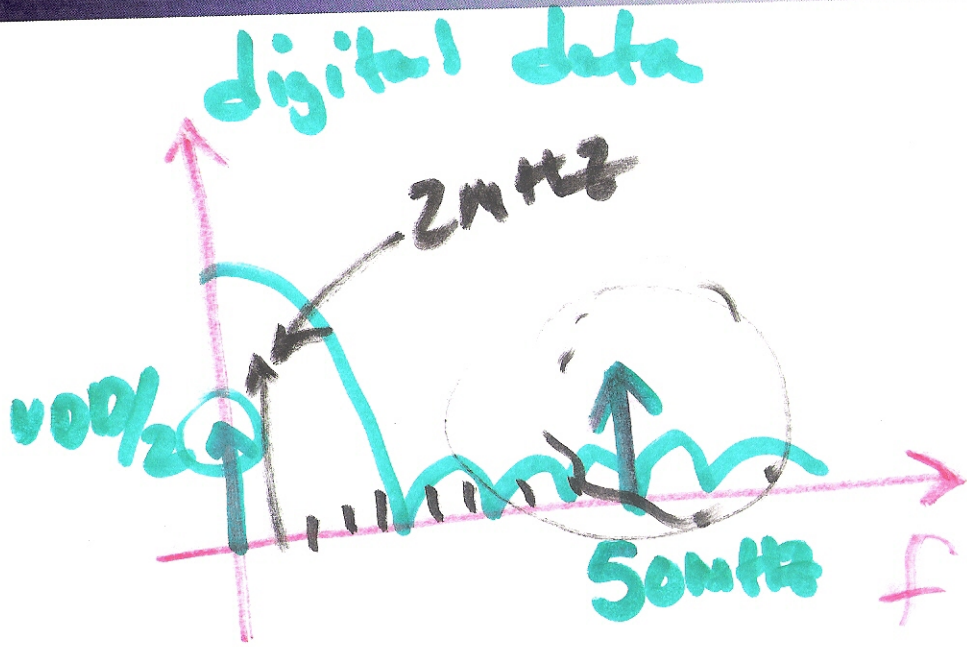

$k=8$

1101010101 11010101  $\rightarrow$  .51V

1101011100101011




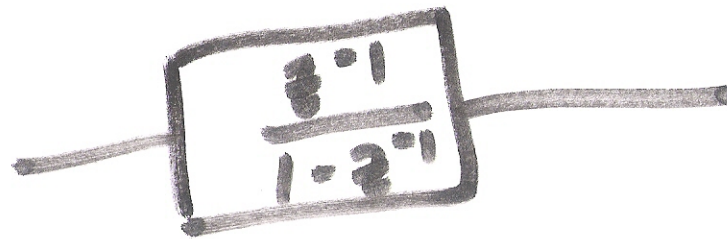8)




SAY you add a noise dither

$$V_{OUT} = (V_{in} + V_{dither})z^{-1} + (V_{acc} + V_{dither})(1 - z^{-1})$$



9)

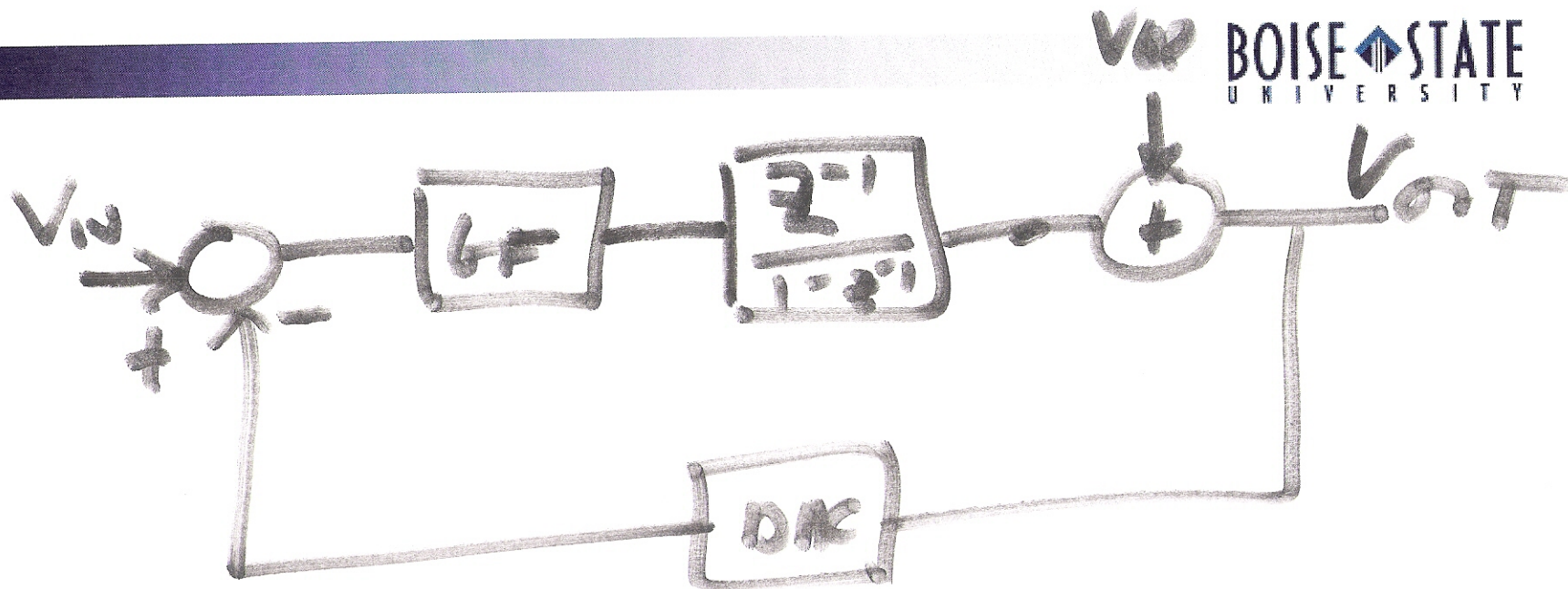


$$(V_{IN} - V_{OUT}) GF \cdot \frac{z^{-1}}{1-z^{-1}} + V_{DP} = V_{OUT}$$

$$V_{OUT} (1-z^{-1}) + V_{OUT} z^{-1} GF = V_{IN} \cdot GF z^{-1} + V_{DP} (1-z^{-1})$$

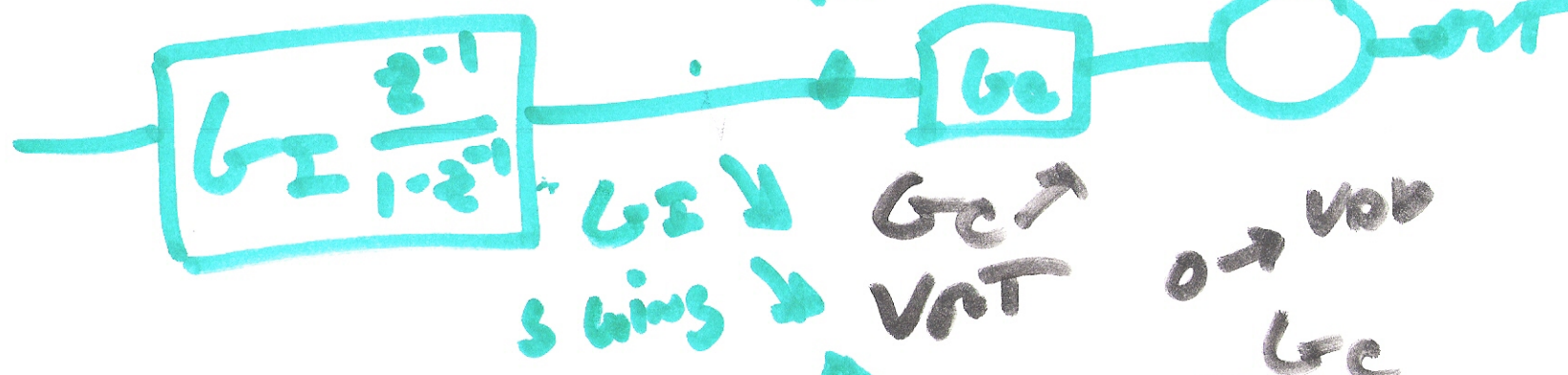
10)

$$V_{AT} = \frac{V_{in} G_F z^{-1}}{1 - z^{-1}(1 - G_F)} + \frac{V_{op}(1 - z^{-1})}{1 - z^{-1}(1 - G_F)}$$

$$1 = G_I \cdot G_o \quad \text{comp. in}$$




$$G_I = \frac{C_I}{C_F}$$

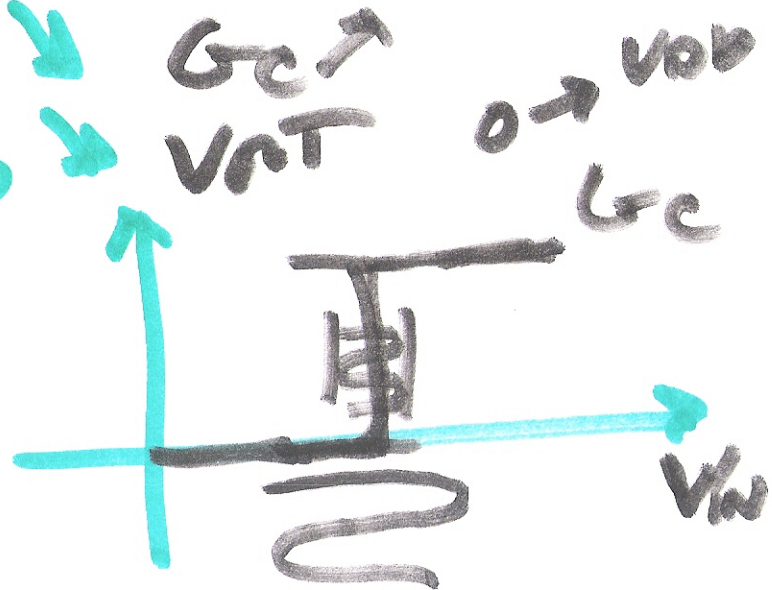

iii


# problems with multi-bit

## quantizers

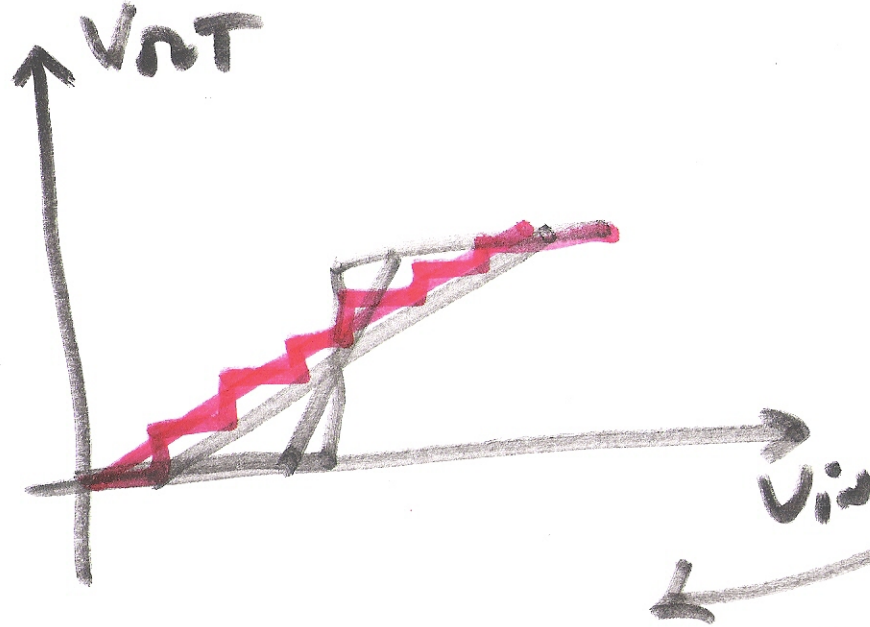

$$GF \neq 1 \quad GF = \frac{1}{2}$$


$$\frac{\frac{1}{2}}{z - \frac{1}{2}}$$

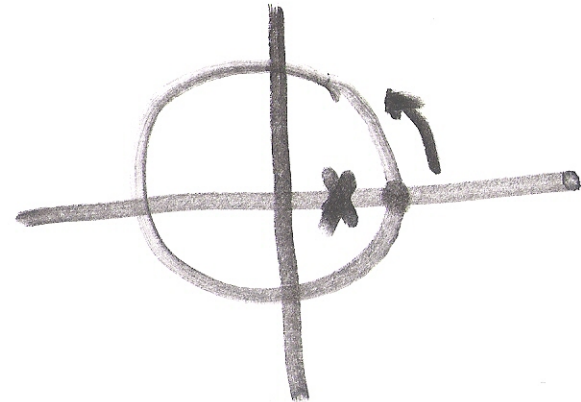

STF


12)

# Comparator gain, offset, hysteresis

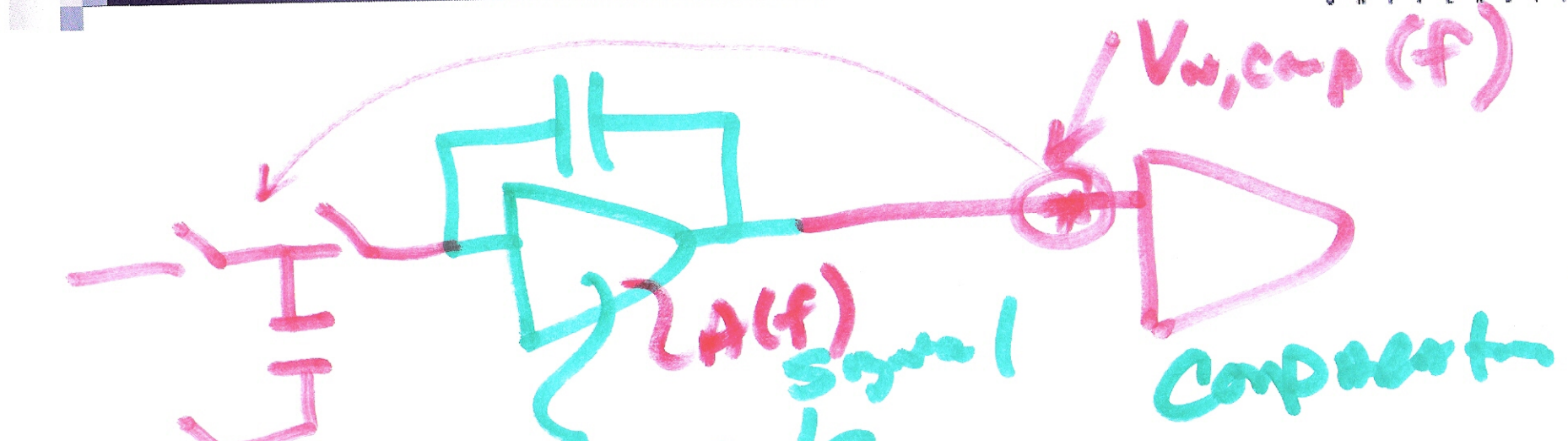


Gain High in 'fresque.

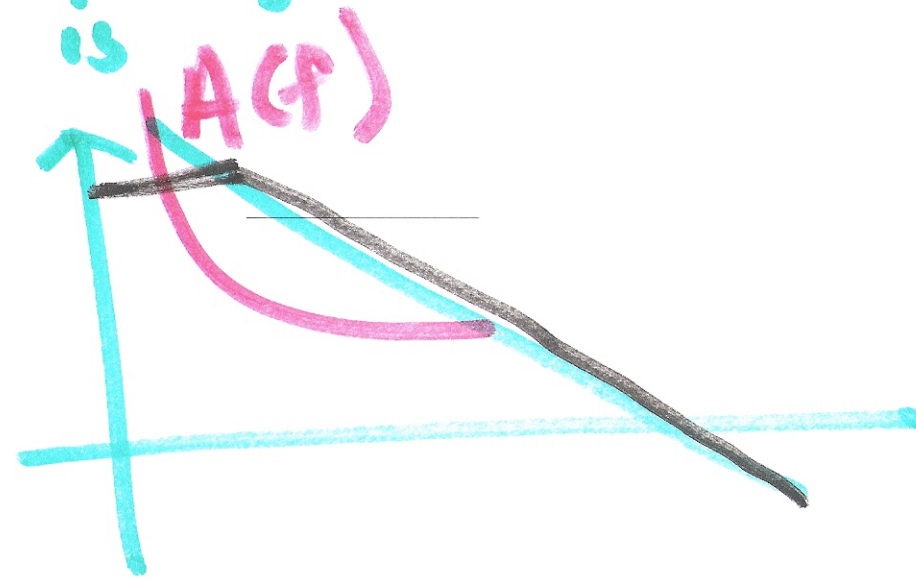$V_{in}$   
↓  
 $V_{out,comp}(f)$   
-----  
 $A(f)$



13)

# OP-Amp gain

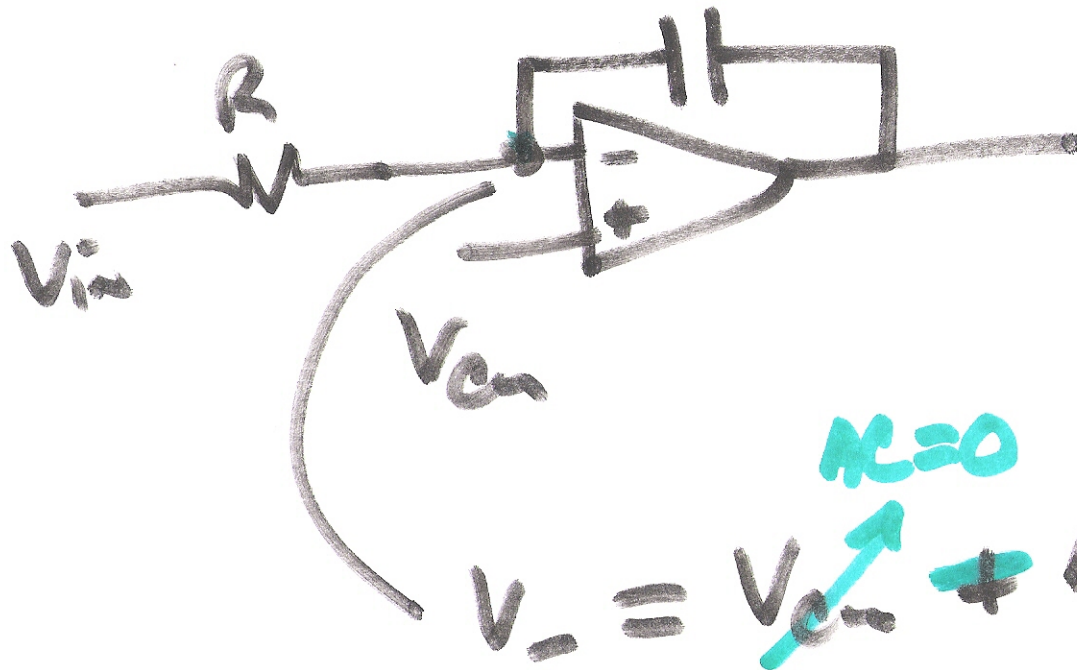


$$\Delta V_{NT} = A_{OL} \cdot$$

$$(V_+ - V_-)$$

$\Delta = 0$
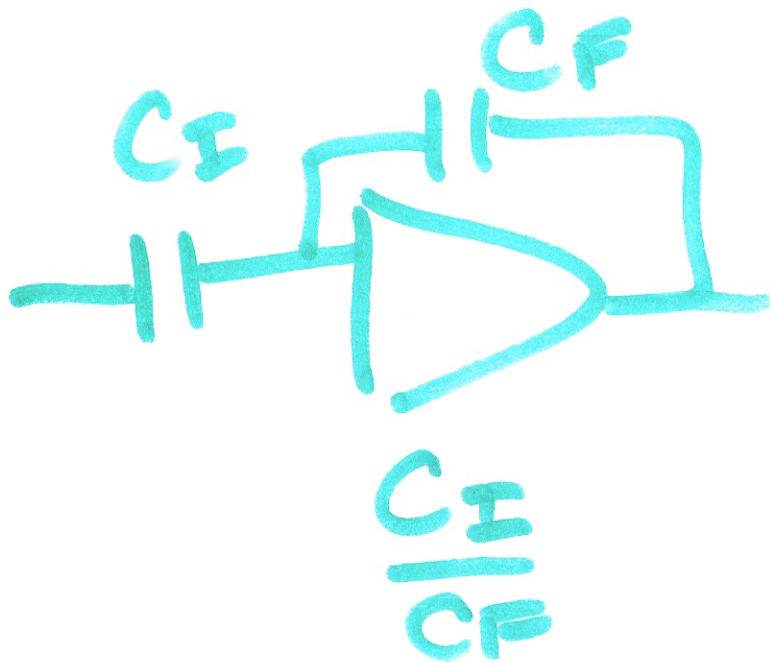
$$V_- = V_{cn} + \frac{\Delta V_{NT}}{A_{OL}}$$




$$\frac{z^{-1} \cdot V_{in}}{1 + \frac{C_E}{C_F} \cdot \frac{1}{A_{OL}}}$$

STF      Egain

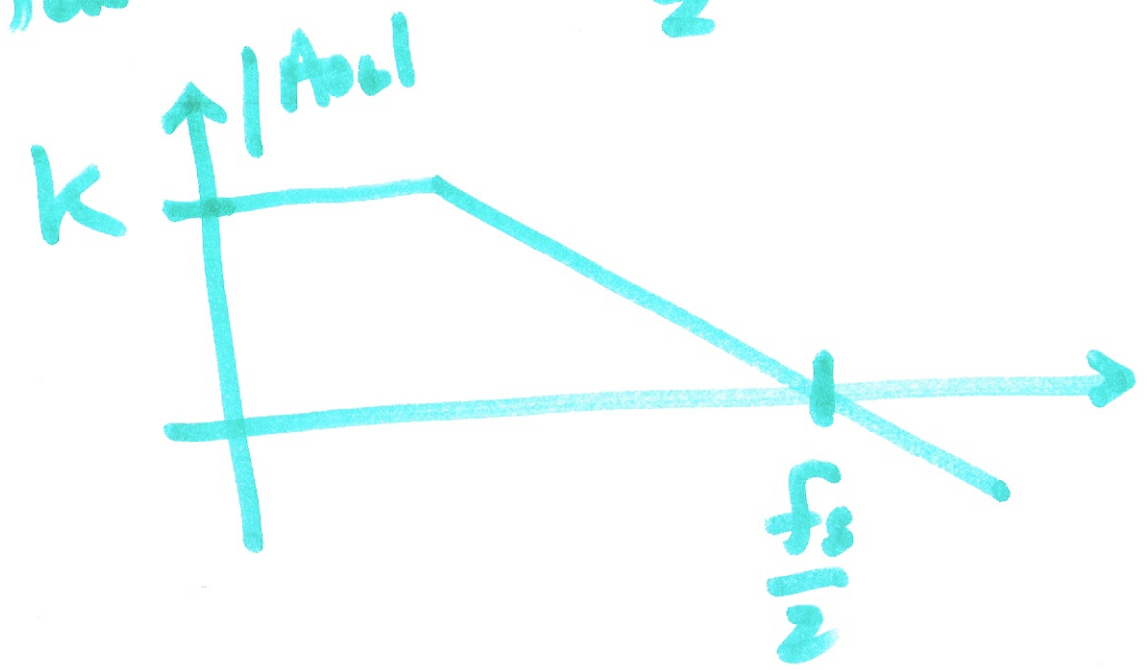14)

$A_{v(oc)} \approx K$  (over amplification)  
↑  
op-amp DC gain

$$f_{bw} \approx K \cdot B = \frac{f_u}{2}$$



15)