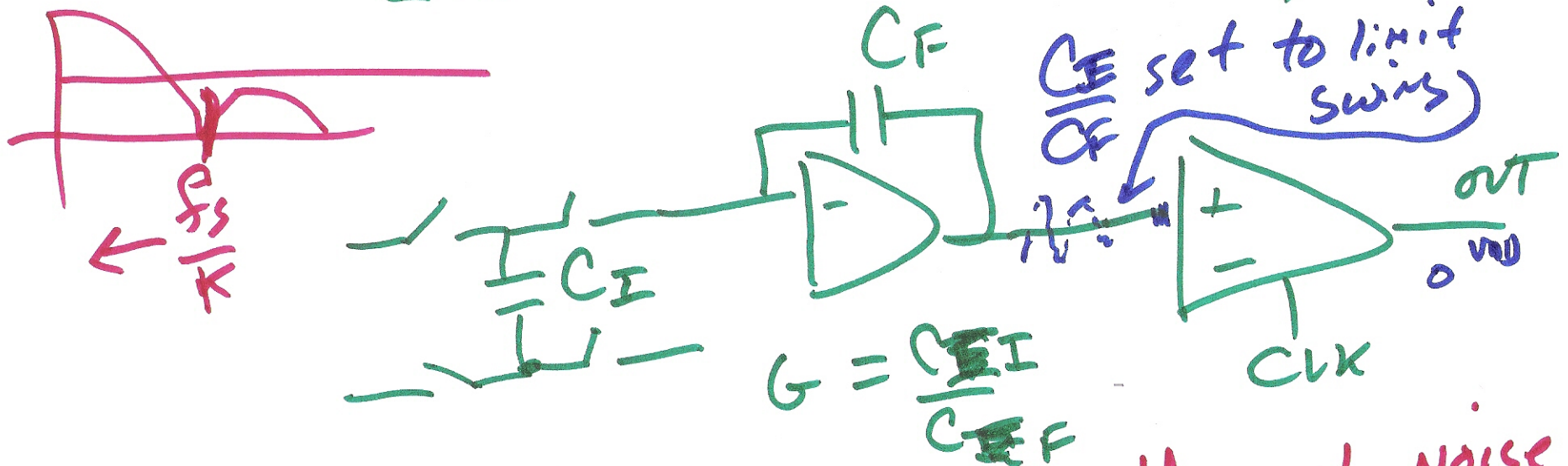


## Circuit Design

Lecture 24

NOV. 15, 2010



Select  $C_I$  based upon thermal noise considerations

$$V_N = \sqrt{\frac{kT}{C_I}}$$

$$V_N^2 = \frac{kT}{C_I}$$

Boltzmann's constant.

$$\text{eff noise} = \frac{V_N^2}{K}$$


OSR  $\rightarrow$

# Second-order NOISE-SHAPING

1st-order FIRST  
 $x(t) - x(t - T_s)$   
 $\lim_{T_s \rightarrow 0} \frac{1}{T_s} \rightarrow \frac{d}{dt}$


$$V_{NT} = V_{IN} \cdot z^{-1} + V_{OP} (1 - z^{-1})$$

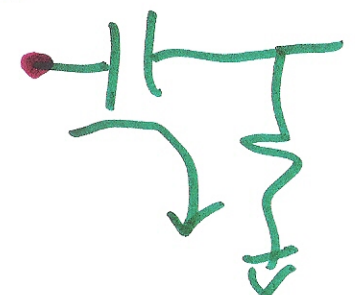$f \ll \frac{1}{2\pi RC}$   $\omega T_s \approx 1$   
 $V_{NT} = i \cdot R$



$$i = C \frac{dv}{dt} = C \frac{d(v_u - v_{NT})}{dt}$$

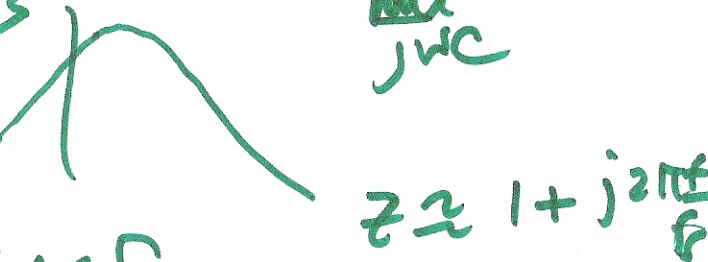$z = e^{j\omega \cdot T_s}$   
 $\frac{d}{dt} = \frac{d}{dt} e^{j\frac{\omega}{f_s} \cdot 2\pi}$




$$v_{NT} = \frac{v_u \cdot R}{R + \frac{1}{j\omega C}}$$

$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$$

$$\frac{v_{NT}}{v_u} = \frac{j\omega RC}{1 + j\omega RC}$$

$f \ll \frac{1}{2\pi RC}$   
 $\approx j\omega RC$
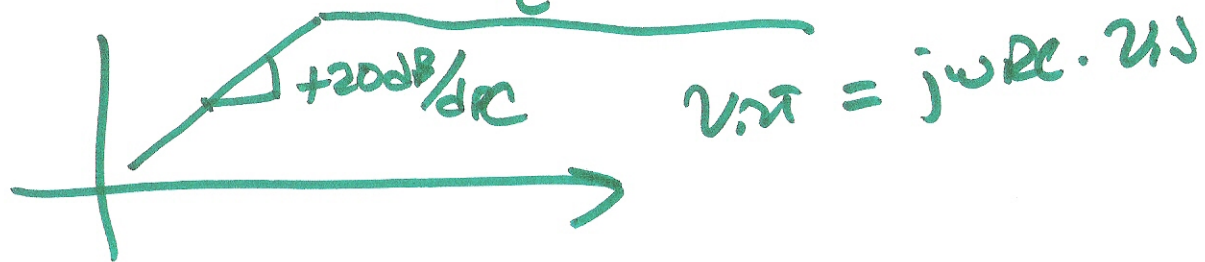
$$1 - z^{-1} = \frac{z - 1}{z} = j2\pi \frac{f}{f_s}$$




2)


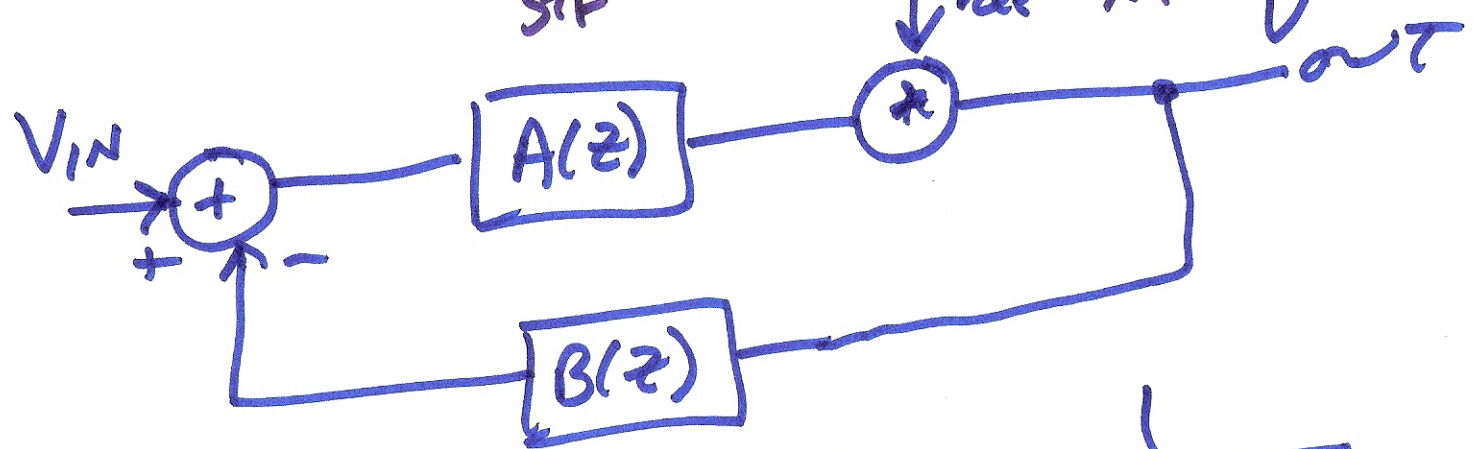
# second-order noise-shaping

$$V_{OUT} = \underbrace{V_{IN} \cdot z^{-1}}_{STF} + \underbrace{V_{QEP} (1 - z^{-1})^2}_{V_{QEP} NTF}$$




$$V_{OUT} = V_{IN} \cdot \underbrace{\frac{A}{1+AB}}_{\substack{STF \rightarrow 1 \\ A \rightarrow \infty}} + V_{QEP} \cdot \underbrace{\frac{1}{1+AB}}_{\substack{NTF \rightarrow 0 \\ A \rightarrow \infty}}$$


$$z^{-1} = \frac{A}{1+AB} \quad (1 - z^{-1})^2 = \frac{1}{1+AB}$$

$$A = \frac{z^{-1}}{(1-z^{-1})^2} = \frac{1}{1-z^{-1}} \frac{z^{-1}}{1-z^{-1}}$$
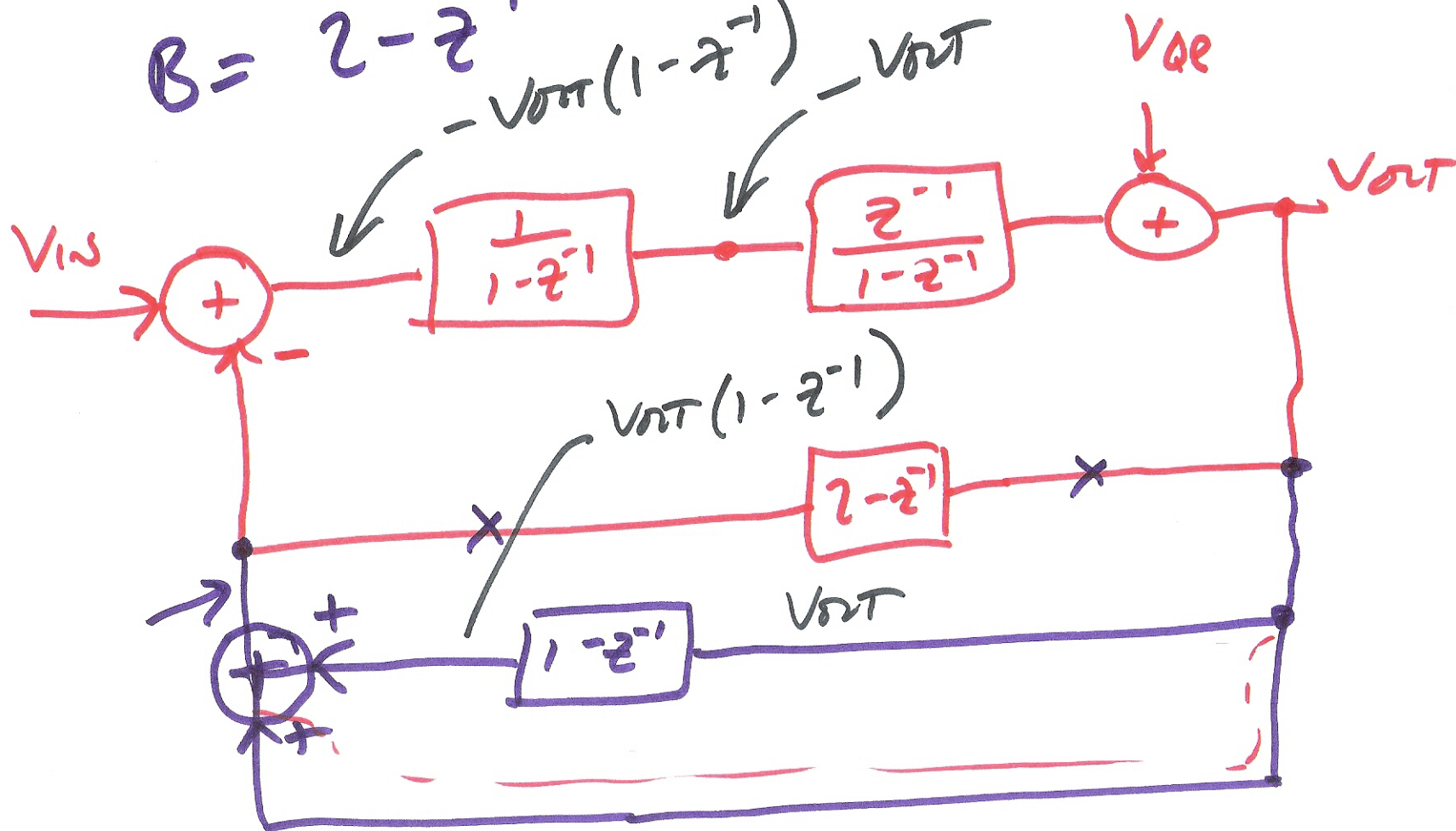
$$B = z - z^{-1} = z(1 - z^{-2}) = z(1 - z^{-1})(1 + z^{-1})$$



4)

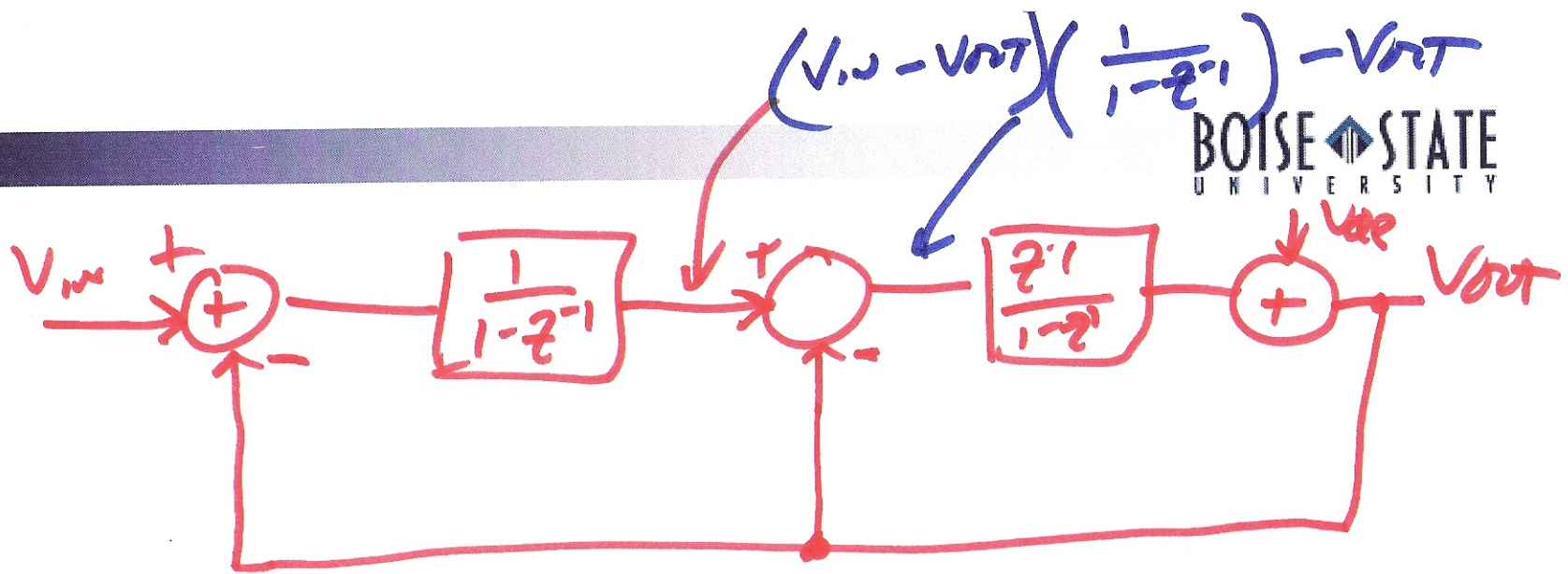

$$(1-z) \left( \frac{(V_{IN}-V_{OUT})z^{-1}}{(1-z^{-1})^2} - \frac{V_{OUT}z^{-1}}{1-z} \right) \frac{z}{1-z} + V_{QP} = V_{OUT}$$

$$z^{-1} V_{IN} (1-z) - V_{OUT} (1-z^{-1}) - V_{OUT} z^{-1} (1-z^{-1}) + V_{QP} (1-z^{-1})^2 = V_{OUT} (1-z^{-1})^2$$

5)



$$z^{-1} \cdot V_{in} - V_{out} \cdot z^{-1} - V_{out} z^{-1} (1 - z^{-1}) + V_{oe} (1 - z^{-1})^2 = V_{out} (1 - z^{-1})^2$$

$$z^{-1} V_{in} - \cancel{V_{out} z^{-1}} - \cancel{V_{out} z^{-1}} + \cancel{V_{out} z^{-2}} + V_{oe} (1 - z^{-1})^2 = V_{out} - \cancel{2z^{-1} V_{out}} + \cancel{V_{out} z^{-2}}$$

$$V_{out} = V_{in} \cdot z^{-1} + V_{oe} (1 - z^{-1})^2$$


for every doubling in OSR (=k)  
we get 2.5 bits  $\uparrow$  in  $N_{eff}$

b)


15dB

$$(1 - z^{-1}) V_{oe} \rightarrow$$

$$(1 - z^{-1})^2 V_{oe}$$

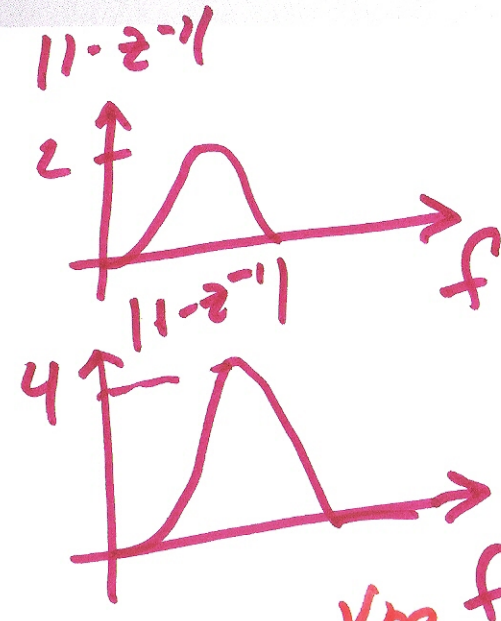

Stability in first-order

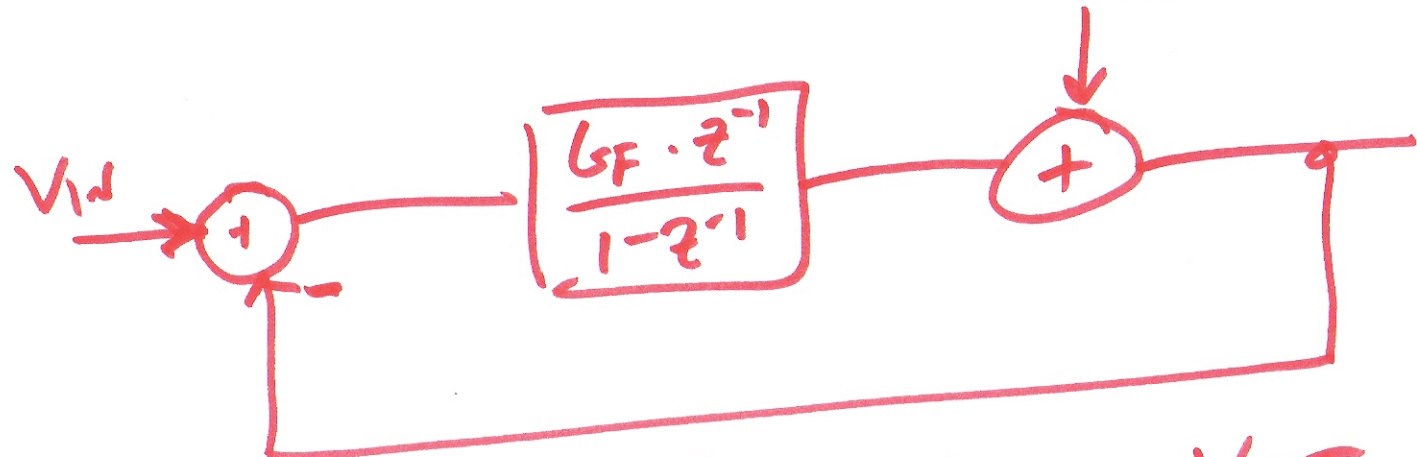

$$\frac{G_F \cdot z^{-1}}{1 - z^{-1}} (V_{in} - V_{out}) + V_{oe} = V_{out}$$


$$G_F \cdot z^{-1} V_{in} - V_{out} G_F z^{-1} + V_{oe} (1 - z^{-1}) = V_{out} (1 - z^{-1})$$

7)

$$G_F z^{-1} V_{IN} + V_{OP} (1 - z^{-1}) = V_{OUT} (1 - z^{-1} + G_F z^{-1})$$

$$V_{OUT} = \frac{G_F z^{-1} V_{IN}}{1 - z^{-1} (1 - G_F)} + \frac{V_{OP} (1 - z^{-1})}{1 - z^{-1} (1 - G_F)}$$

page 146-147  
Fig. 4.37

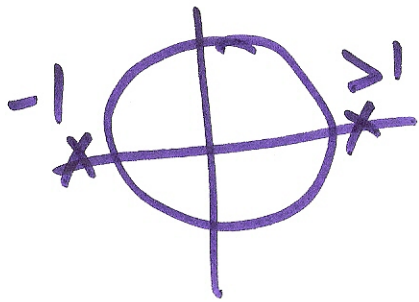

$$z_{p1,2} = 1 - G_F \text{ and } z_{p2} < -1$$

$$STF = \frac{V_{OUT}}{V_{IN}} = \frac{G_F}{z - (1 - G_F)}$$

$$NTF = \frac{V_{OUT}}{V_{OP}} = \frac{z - 1}{z - (1 - G_F)}$$

$$G_F > 2$$


$$G_F < 0$$

$$0 < G_F < 2$$

8)




# Second-order Modulator

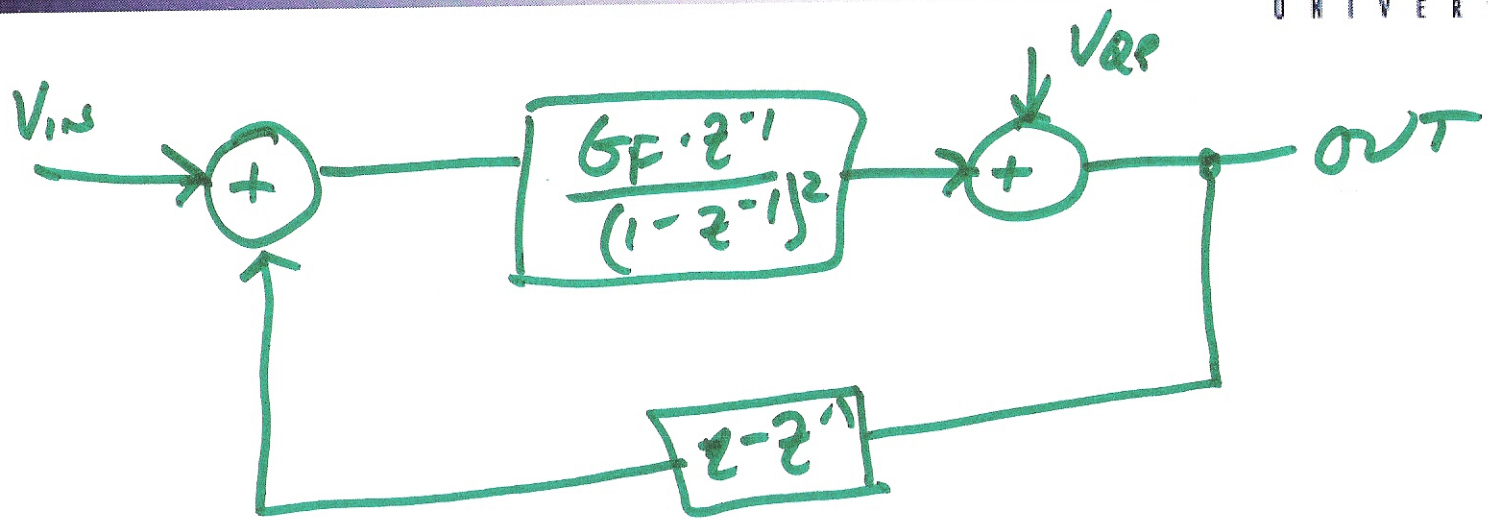

$$z^2 + z(2 \cdot (GF - 1)) + (1 - GF)$$

$$0 \leq GF \leq 1.33$$

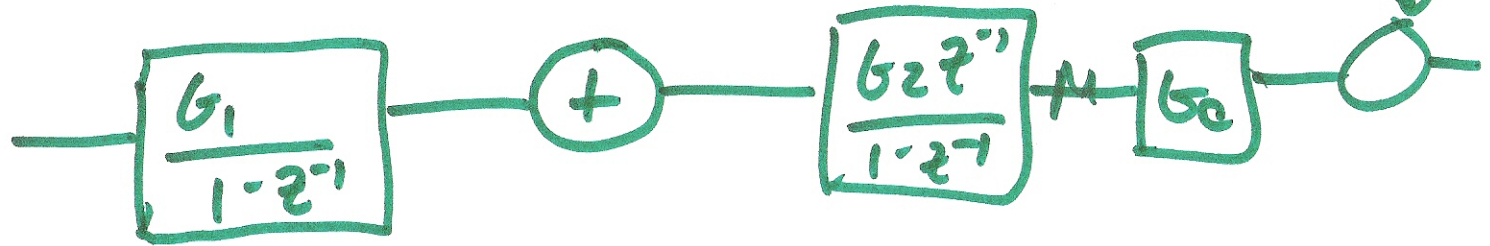

10)