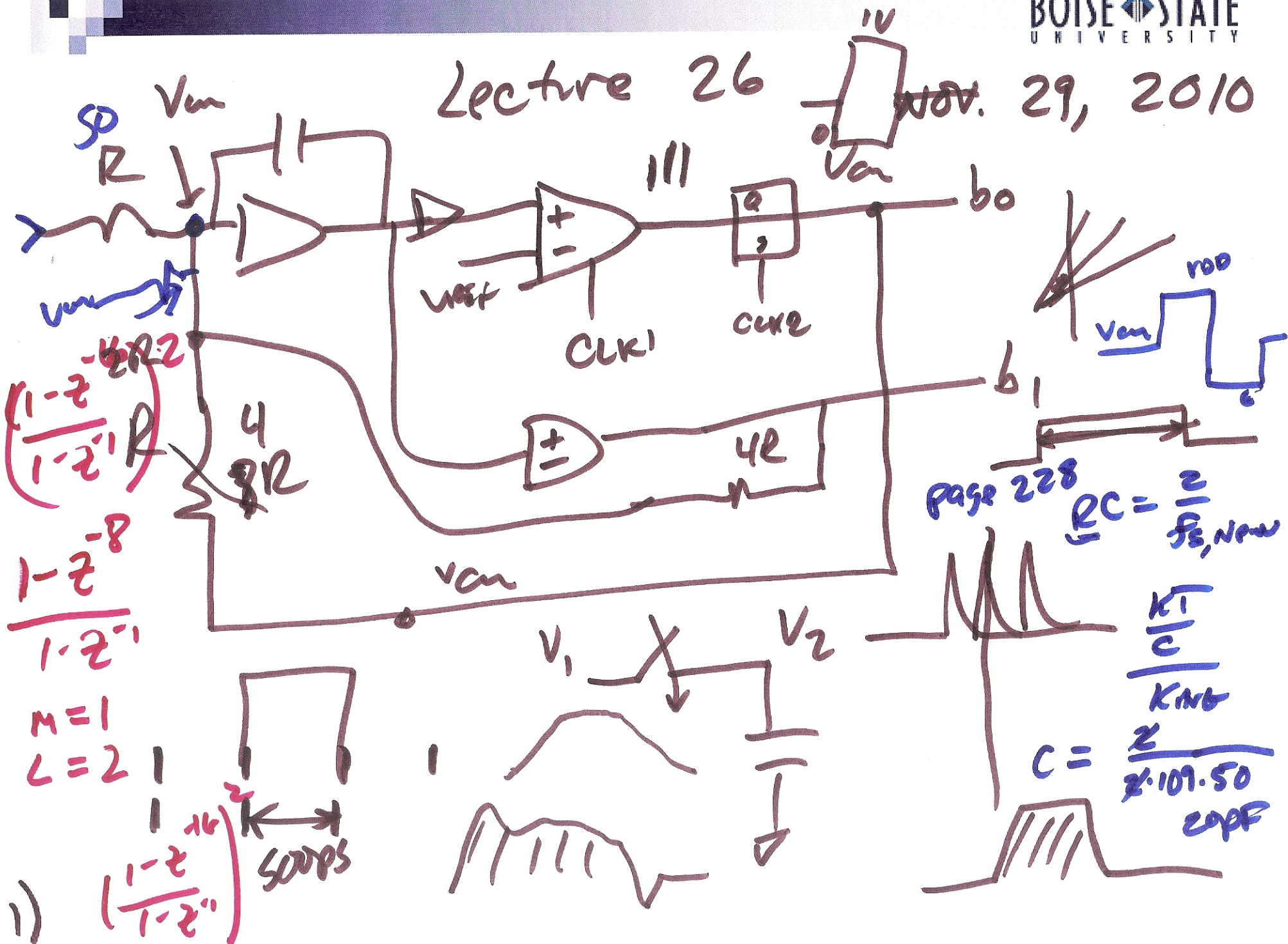


ECE 615 CMOS mixed-signal circuit Design

Lecture 26

Nov. 29, 2010



$$\left(\frac{1-z^{-1}}{1-z^{-1}} \right) R$$

$$\frac{1-z^{-1}}{1-z^{-1}}$$

$M=1$
 $L=2$


$\left(\frac{1-z^{-1}}{1-z^{-1}} \right) R$
 500PS



page 228
 $RC = \frac{2}{f_{S, New}}$

$C = \frac{KT}{K_{inb}}$
 $C = \frac{2}{2 \cdot 10^9 \cdot 50} \text{ 20PF}$

Second-order modulator gains

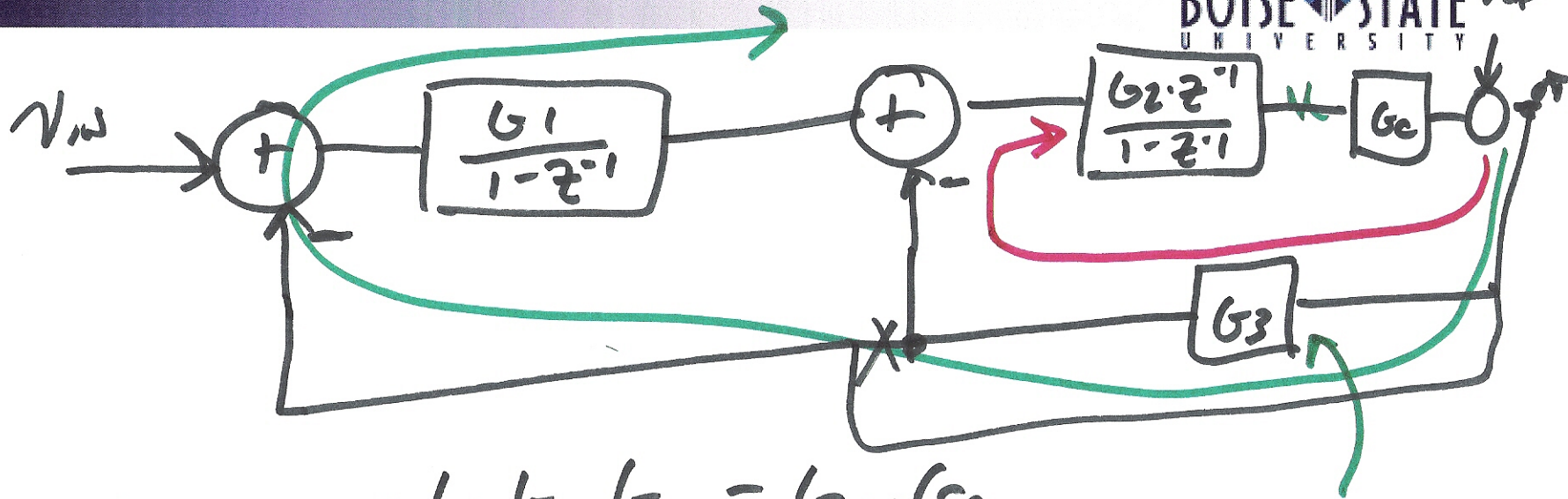

$$1 = G_F = \underbrace{G_1}_{G_I} \underbrace{G_2}_{G_C} G_C = G_I \cdot G_C$$

$$0 \leq G_F \leq 1.333$$

$$(7.59) \quad z_{p1,p2} = (1 - G_F) \pm \sqrt{(1 - G_F)^2 - (1 - G_F)}$$

$$\frac{1}{z} = z^{-1} \quad G_F = 1 \quad z_{p1,p2} = 0$$

2)

with G_3 Eq. (7.62)

$$z_{p1, p2} = \frac{2 - G_1 G_2 G_c}{2} - \frac{G_2 G_3 G_c}{2}$$

$$\pm \frac{\sqrt{(2 - G_1 G_2 G_c - G_2 G_3 G_c)^2 - 4(1 - G_2 G_3 G_c)}}{2}$$


$$\frac{G_1 G_2 G_c}{(z - z_{p1})(z - z_{p2})} = 1$$

$$(z - z_{p1})(z - z_{p2})$$

$$G_1 = G_2 = G_3 = 0.4$$


3)

Higher-order modulators

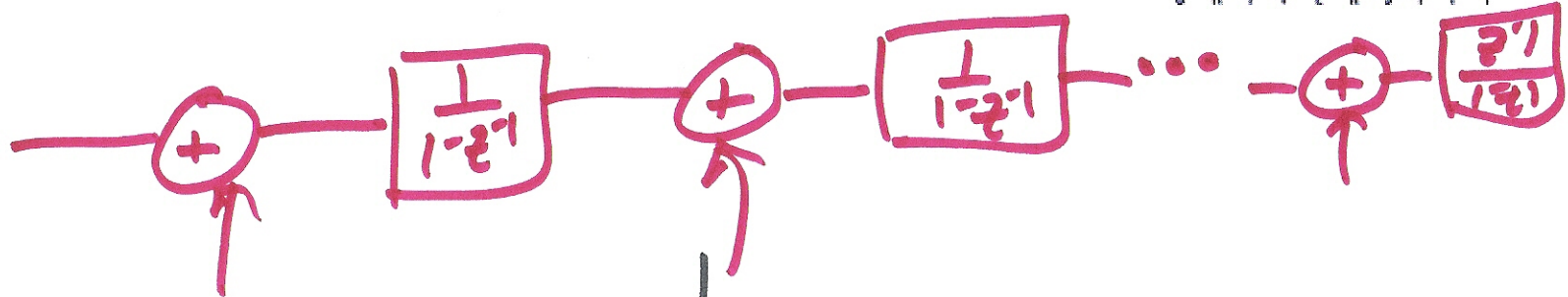


$$V_{out} = V_{in} \cdot z^{-1} + V_{op} (1 - z^{-1})^m$$

$m = \text{order of modulator}$

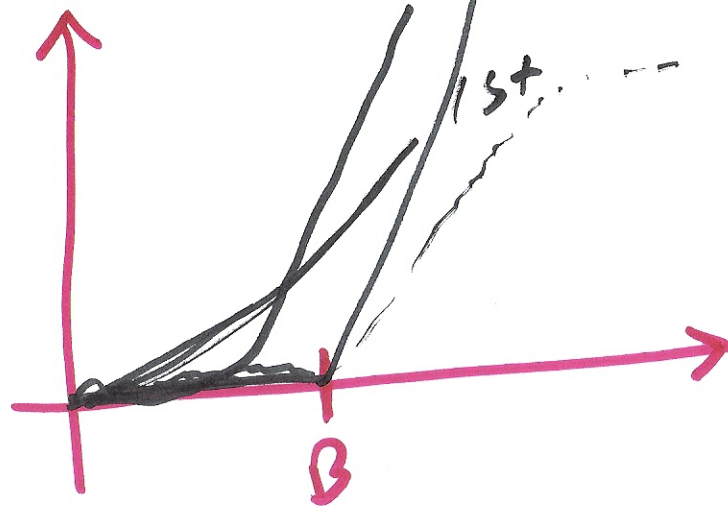

4)

Multi-bit modulators

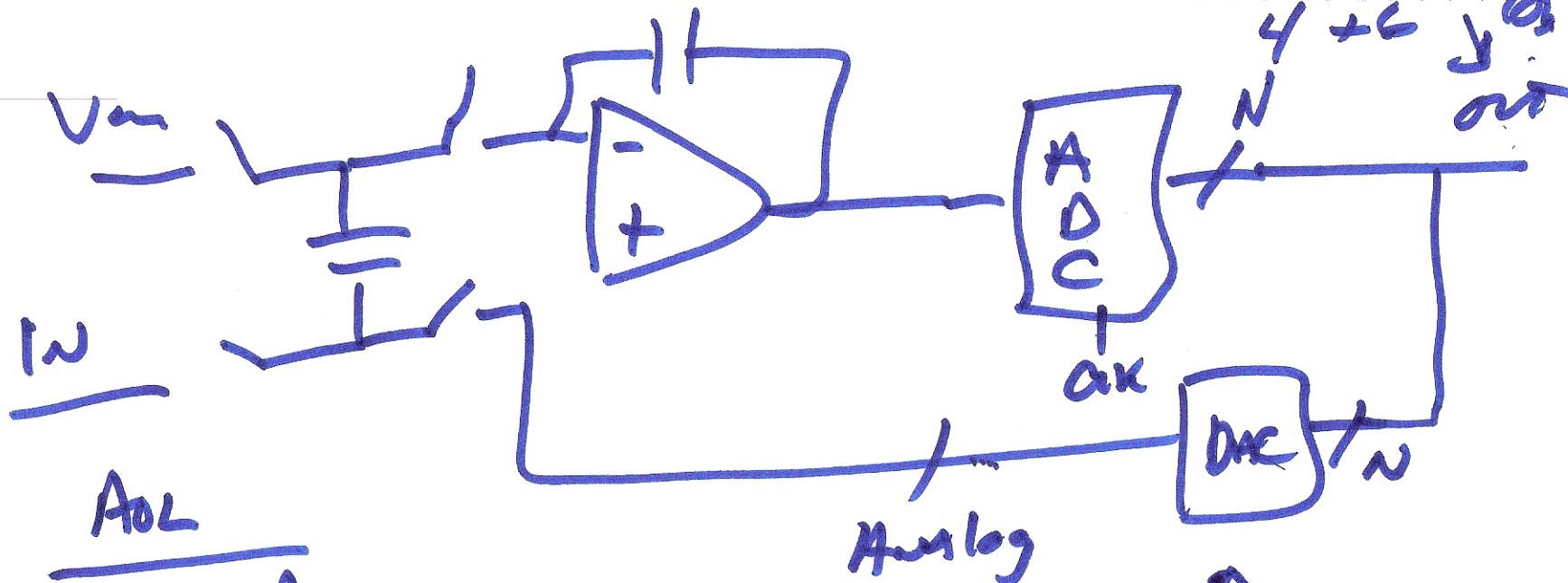


$$\frac{A_{OL}}{1 + \beta \cdot A_{OL}}$$


$$\frac{1}{\frac{1}{A_{OL}} + \beta}$$

$$2^4 = 16$$
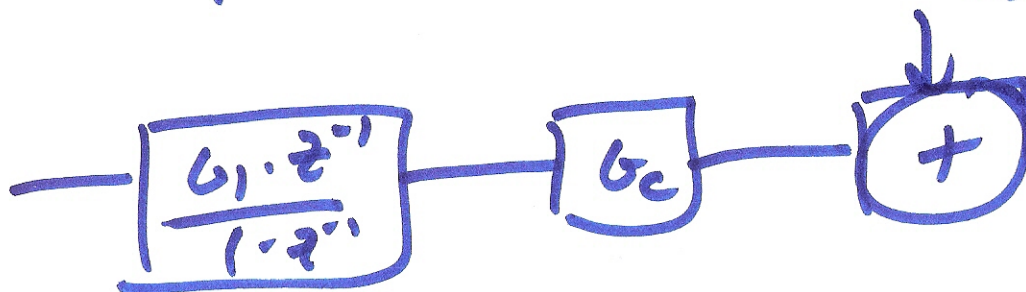
$$4 \cdot 1.5 \text{ bits} = 6 \text{ bits } V_{ref}$$



5)

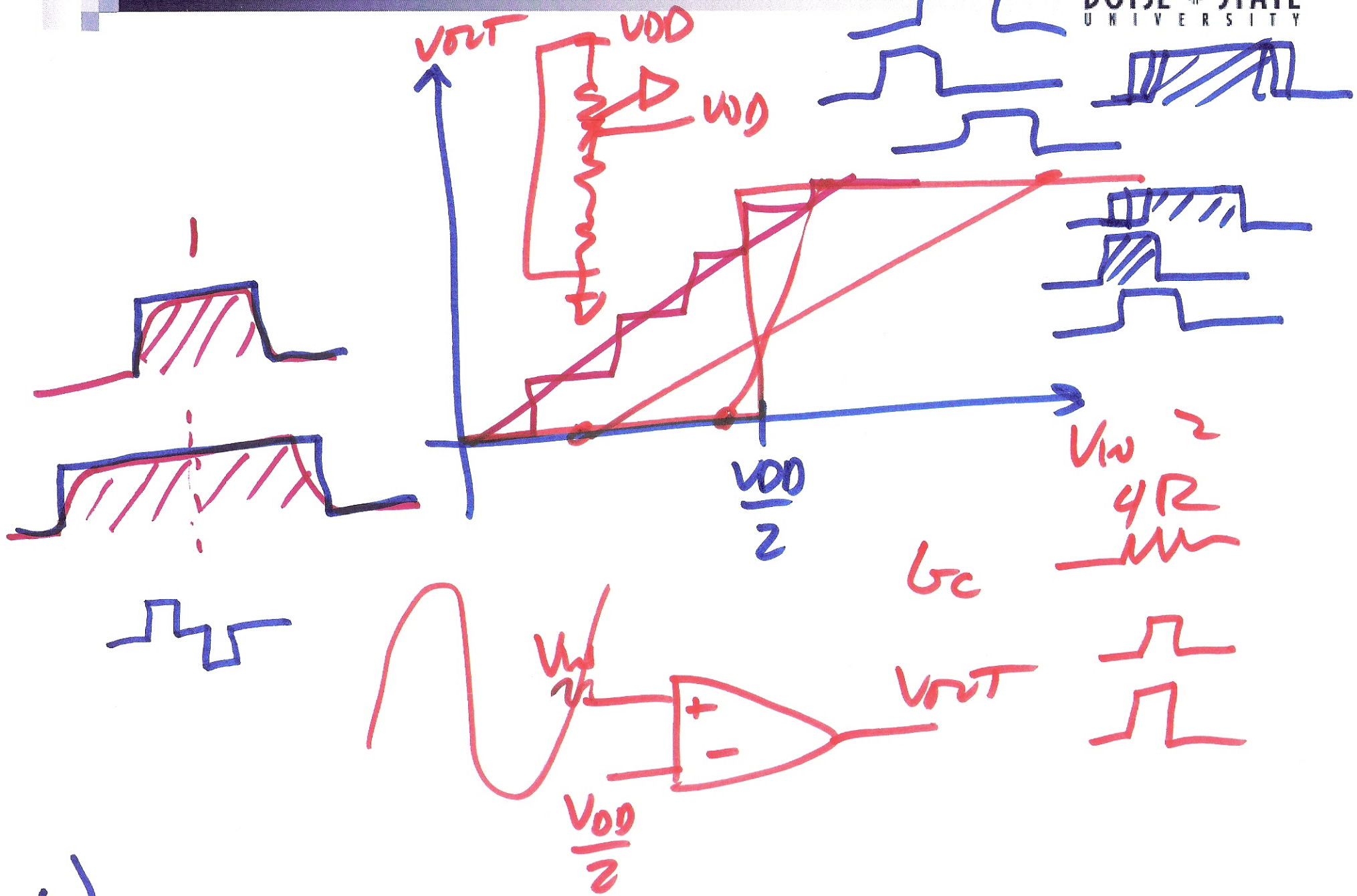

b)