

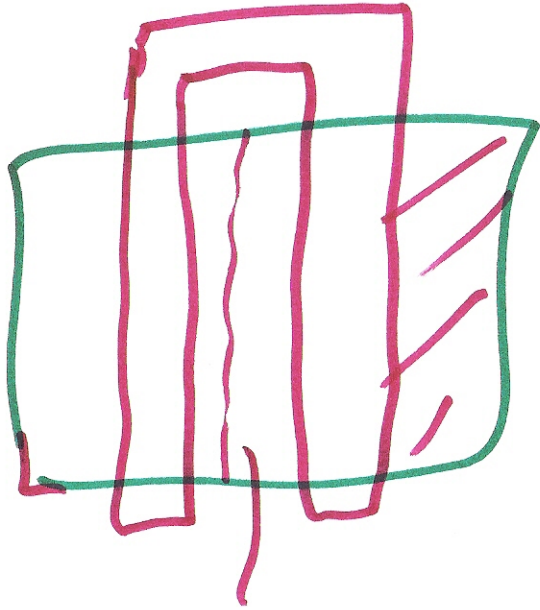


ECE 615 CMOS Mixed-Signal CKT

NF

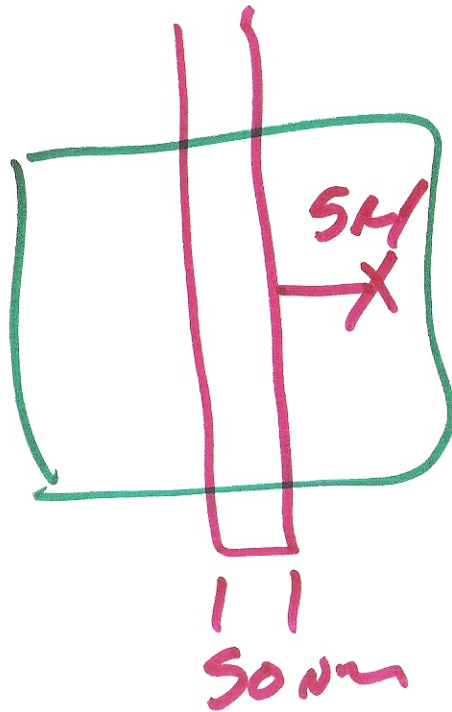


gradient


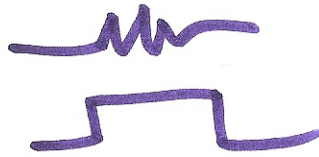


$$\frac{1}{2} \frac{5}{3} \cdot 1.51 = 200$$

BANDPASS

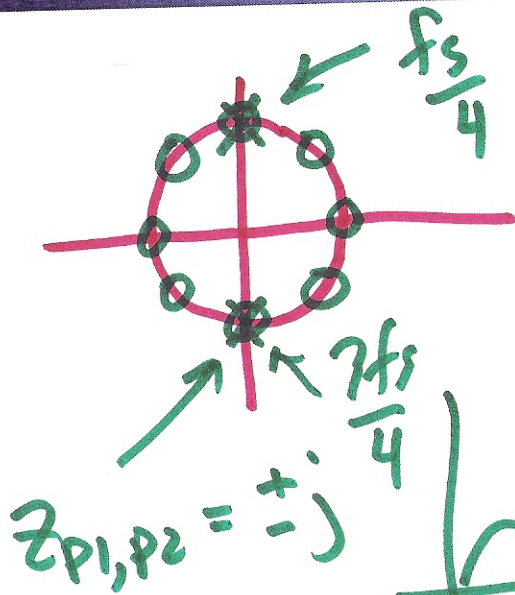

$$\frac{1 - z^{-8}}{1 + z^{-2}}$$

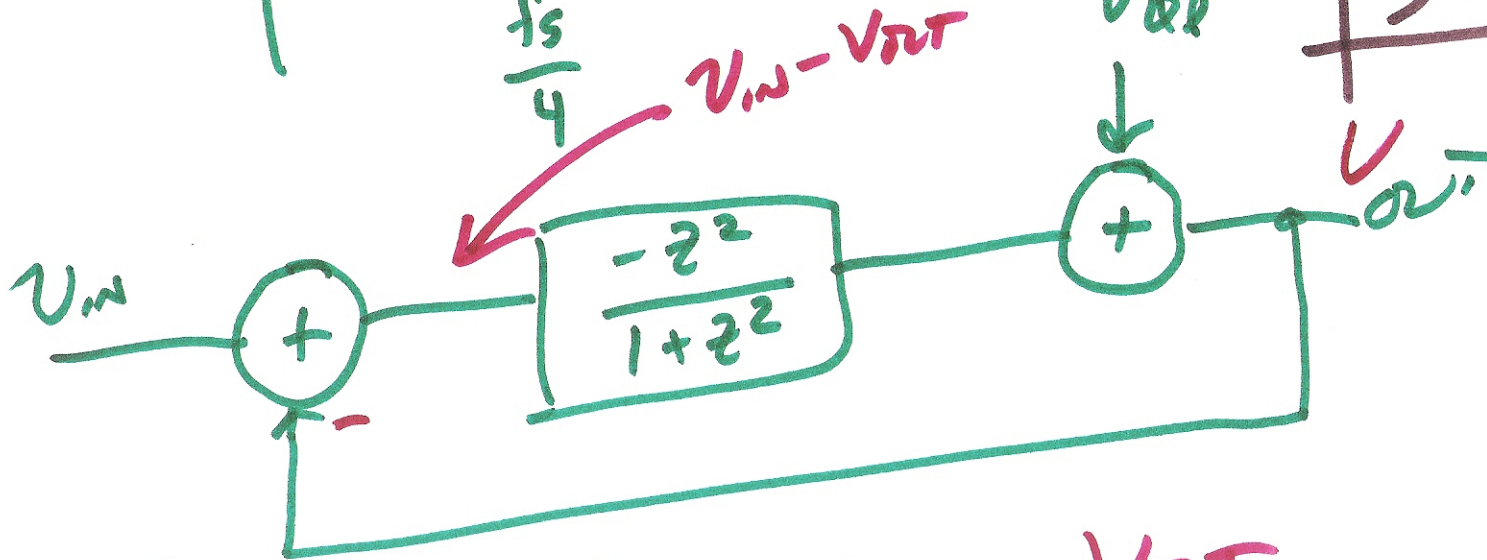
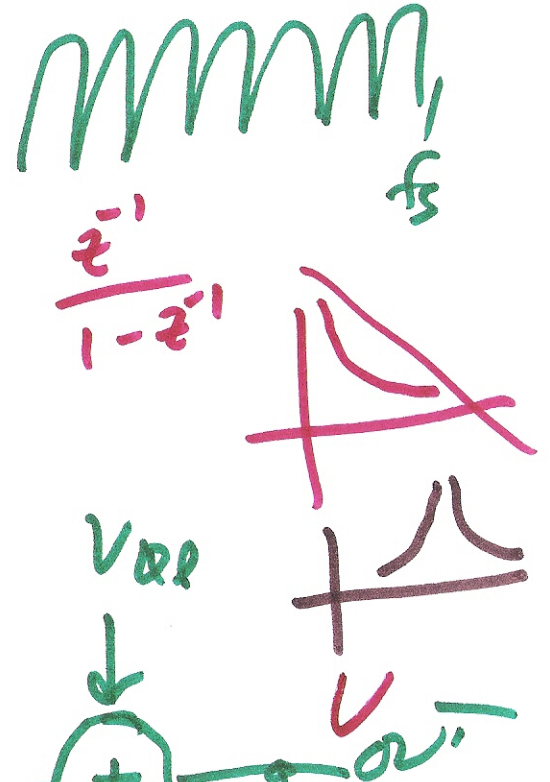


$$\frac{-z^2}{1+z^2} (V_{in} - V_{out}) + V_{out} = V_{out}$$

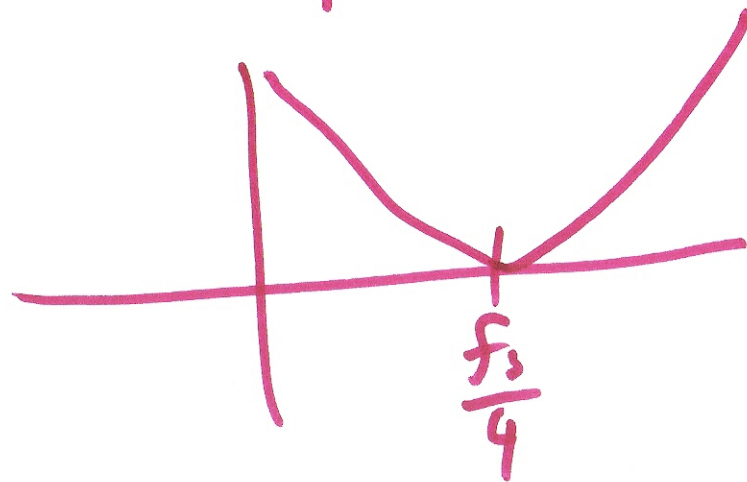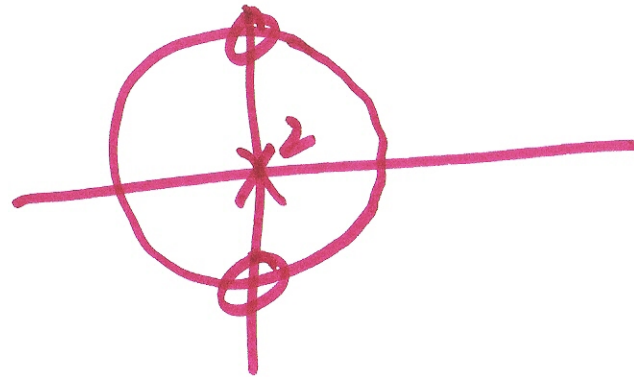2)

$$-\bar{z}^2 V_{in} + \bar{z}^2 V_{out} + V_{oe} = (1 + \bar{z}^2) V_{out}$$



$$V_{out} = \frac{-\bar{z}^2 V_{in} + V_{oe}(1 + \bar{z}^{-2})}{\bar{z}^2 + 1}$$



3)

$$\frac{z}{1+z}$$


f_s

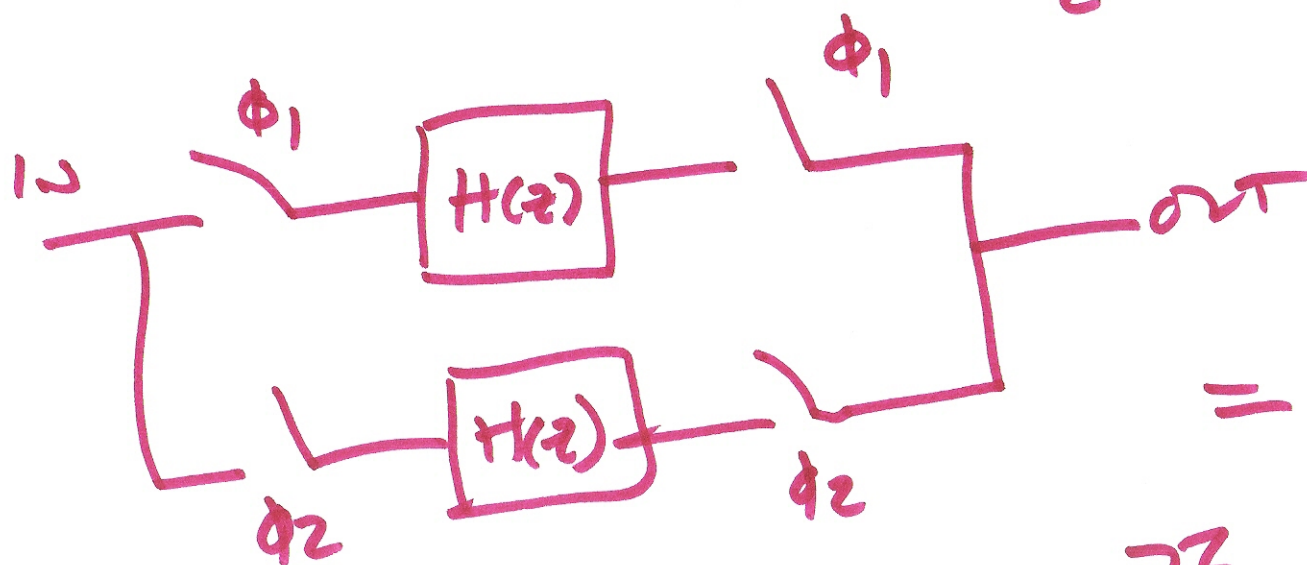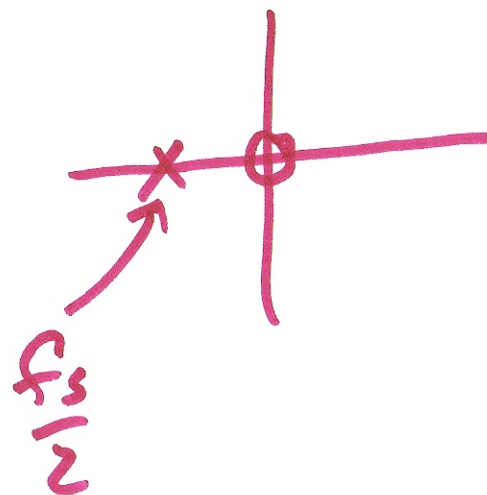


$$= H(z^2)$$

$$\frac{z^2}{1+z^2}$$


4)

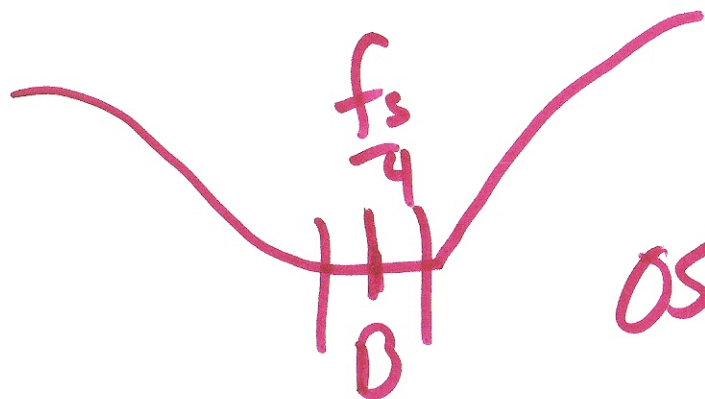

$$OSR = \frac{f_s}{2B}$$

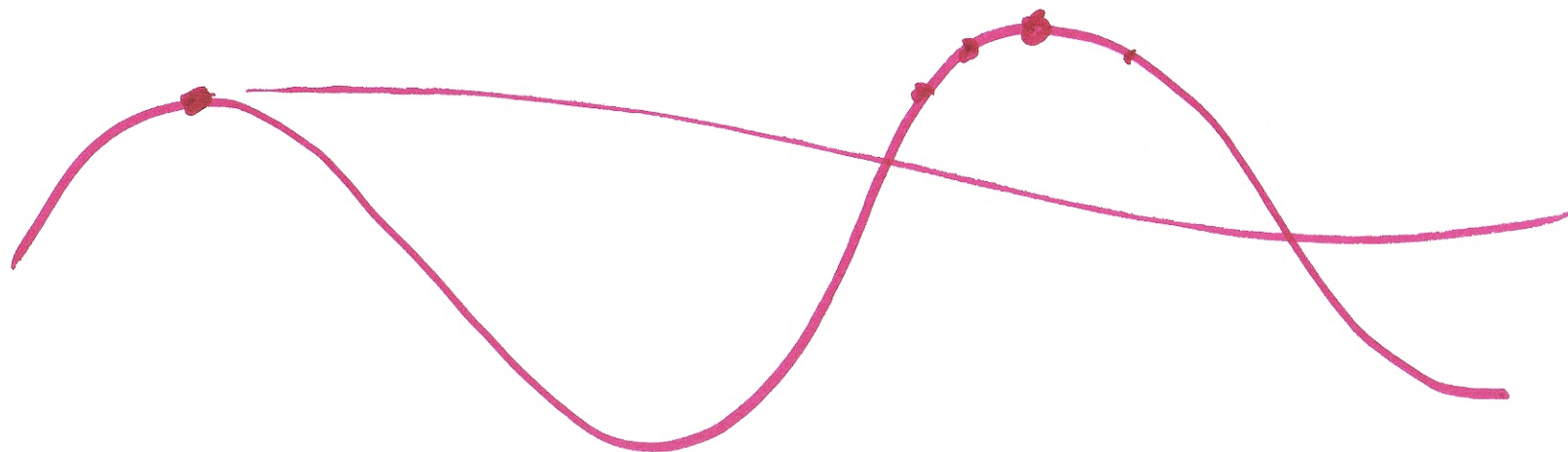

s)

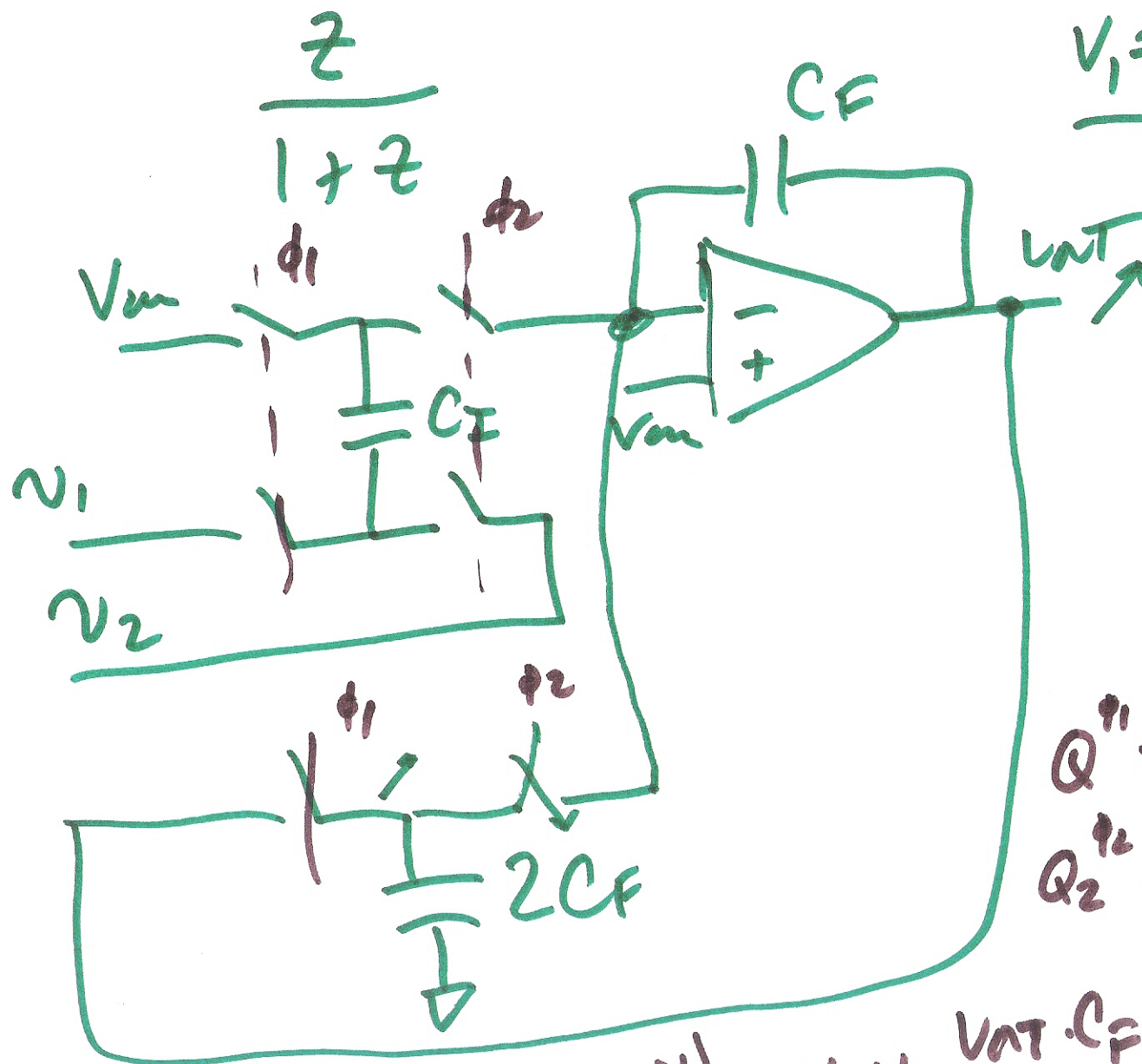

$$\frac{V_1 z^{-1/2} - V_2}{1 - z^{-1}} \frac{C_I}{C_F}$$

$$\frac{V_1 - V_2}{1 - z^{-1}} = V_{out}$$

$$\frac{z}{1+z}$$

$$Q_1^{phi_1} = V_1 C_I + V_{out} \cdot 2C_F$$

$$Q_2^{phi_2} = V_2 \cdot C_I + 2C_F V_{out}$$

$$V_{out} \cdot C_F = (V_1 - V_2) C_I + V_{out} (1 - 1) 2C_F$$

$$V_{out}(z) \cdot C_F (1 - z^{-1}) = V_1 - V_2 \cdot C_I$$

b)