

$$A_{OL}(f) = \frac{A_{OLDC}}{1 + j \frac{f}{f_{3dB}}}$$

1,000

$\sim A_{OLDC}$



$$\frac{A_{OLDC}}{j \frac{f}{f_{3dB}}}$$

$f_u = \text{unity-gain freq.}$

$f_u > f_{3dB}$


Gain-BW product

$$= f_{3dB} \cdot A_{OLDC} = f_u$$

$$\frac{1}{j \frac{f}{f_{3dB}}} A_{OLDC}$$

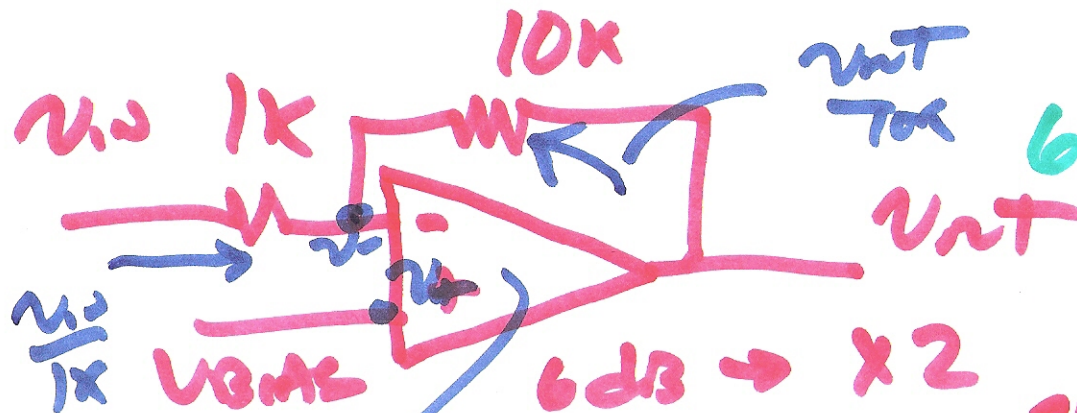
1)

$A_{OL} = 10^3$, $f_{3dB} = 50 \text{ MHz}$




10^3 open-loop op-amp

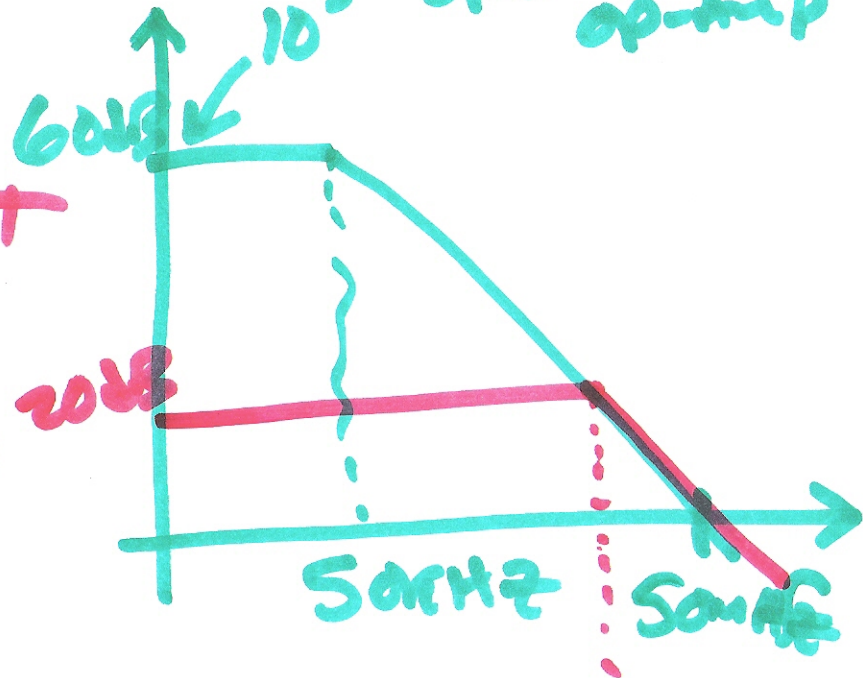- 6dB \rightarrow $\times 2$
- 20dB \rightarrow $\times 10$
- 14dB \rightarrow $\times 5$
- 6dB \rightarrow $\div 2$




$$A_{CL}(f) = \frac{v_{out}}{v_{in}} = \frac{A_{OL}}{1 + j \frac{f}{f_{3dB}}} = 5 \text{ MHz}$$
 Closed Amp = 5 MHz

2)

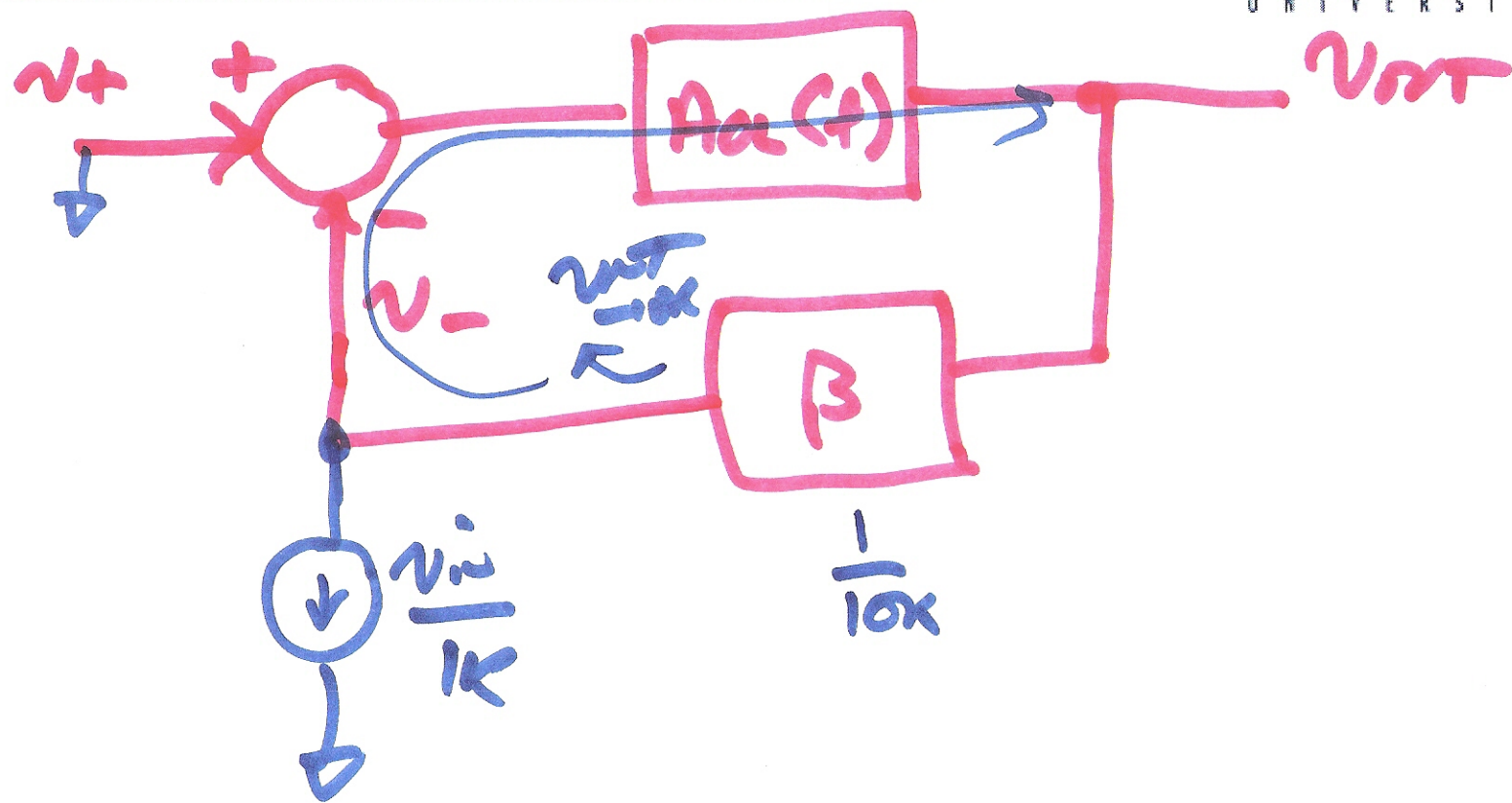


3)

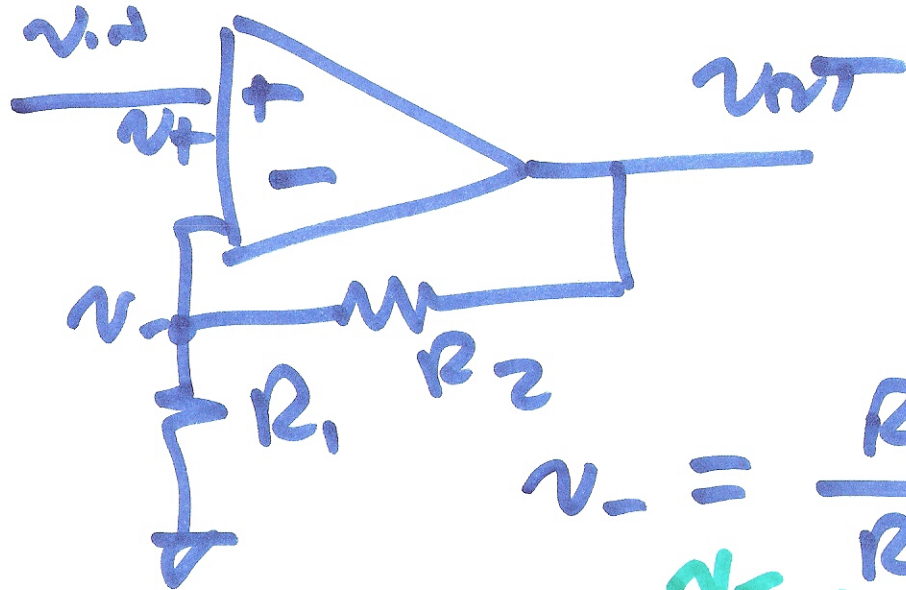

$$\frac{1}{\beta} = 1 + \frac{R_2}{R_1}$$

$$v_- = \frac{R_1}{R_1 + R_2} \cdot v_o$$

$$v_i - v_- = \frac{v_o}{\beta}$$

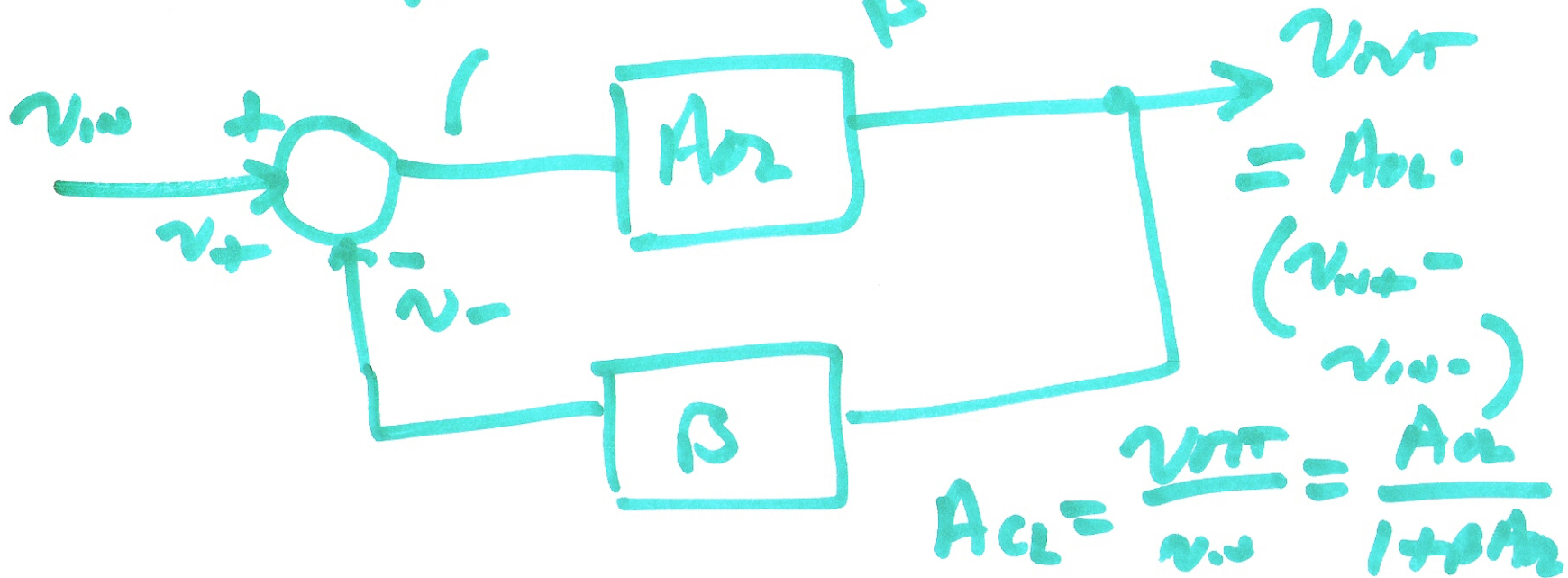

4)

$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}} \quad \text{if } A_{OL} \rightarrow \infty \quad A_{CL} = \frac{1}{\beta}$$

$$A_{CL} = \frac{A_{OLDC}}{1 + j f f_{3dB}}$$

$$= \frac{1 + \beta \cdot \frac{A_{OLDC}}{1 + j \frac{f}{f_{3dB}}}}{1 + j \frac{f}{f_{3dB}} + \beta A_{OLDC}}$$

5)

$$A_{cl}(f) = \frac{1}{\frac{1}{A_{olc}} + j \frac{f}{f_{3dB} \cdot A_{olc}} + \beta}$$


$\frac{1}{\beta} = A_{clc}$

$$f_{3dB_{cl}} = \frac{f_{3dB_{olc}}}{A_{clc}} \frac{1}{\frac{1}{A_{olc} \cdot \beta} + 1 + j \frac{f}{f_{3dB_{olc}} \cdot \beta}}$$

≈ 0

$$A_{clc} f_{3dB_{cl}} = \frac{f_{3dB_{olc}}}{1 + j \frac{f}{f_{3dB_{olc}} / \beta}}$$

v)

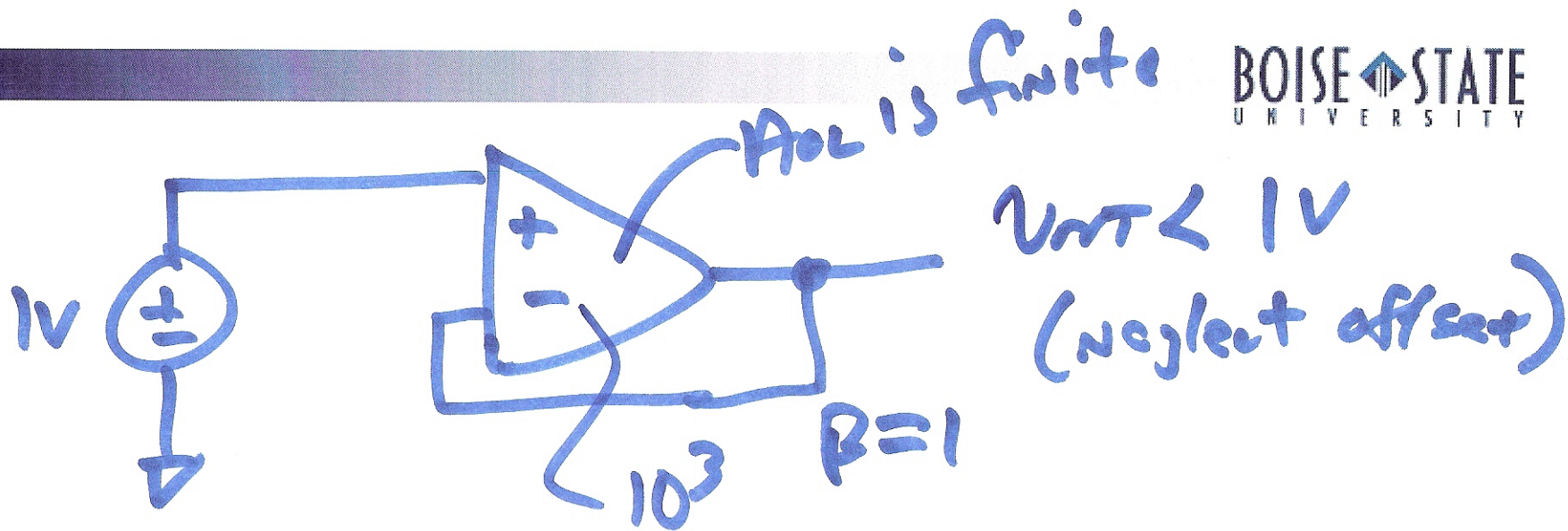

Resolution

1 LSB

$$\frac{V_{REF+} - V_{REF-}}{2^N}$$

$N = 10\text{-bits}$

$\frac{1}{2^{10}} \approx 1mV$

$$(1 - v_{out}) \cdot 10^3 = v_{out}$$

$$10^3 = v_{out} (1 + 10^3)$$

$$v_{out} = \frac{10^3}{1 + 10^3}$$

$$= .999$$

7)

$$\frac{V_{DD} - \text{Resolution}}{V_{DD}} \ll \frac{A_{OLoc}}{1 + A_{OLoc}}$$

$$A_{OLoc} \gg \frac{V_{DD}}{\text{Resolution}}$$

$$f_{in} = A_{CL} \cdot f_{3dB} > \frac{1V}{1\mu s}$$

$$A_{OLoc} > 10^3$$


$$\beta = 1, \quad f_{c3dB} = \underline{\underline{f_{in}}}$$

$\beta = 1$
 S/H \uparrow
 this
 is
 true.

8)

$$s/4 \rightarrow \frac{1}{1 + j\frac{f}{f_{cut}}} \xrightarrow{f \rightarrow \text{RE}} \frac{1}{1 + j\frac{f}{f_{cut}}}$$

$$\rightarrow (1 - e^{-t/RC})$$

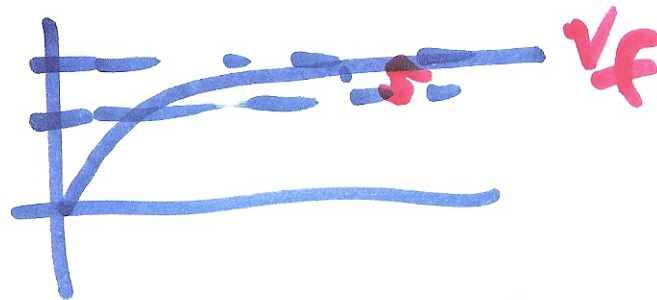

$$f_{3dB} = \frac{1}{2\pi RC}$$

~~$$RC = \frac{1}{2\pi f_{3dB}}$$~~

$$RC = \frac{1}{2\pi f_{cut}}$$

$$.999 V_f = V_f (1 - e^{-t/RC})$$

$$-RC \ln .001 = t_{settle}$$

9)

$$v_{NT} = v_{in} (1 - e^{-t 2\pi f_{in}})$$

$$\text{Resolution} = 1 - \frac{v_{NT}}{v_{in}} = e^{-t 2\pi f_{in}}$$

$$t_{\text{settling}} < \frac{1}{2f_s} = \frac{T_s}{2}$$

$$1 - \frac{1}{.999}$$

$$f_{in} = A_{\text{over}} \cdot f_{3dB} > \frac{-f_s \ln(\text{res})}{\pi}$$

\checkmark

$$\frac{-10^8 \cdot \ln(.0015001)}{\pi}$$

$$f_{in} > 2.205 \text{ MHz}$$

10)

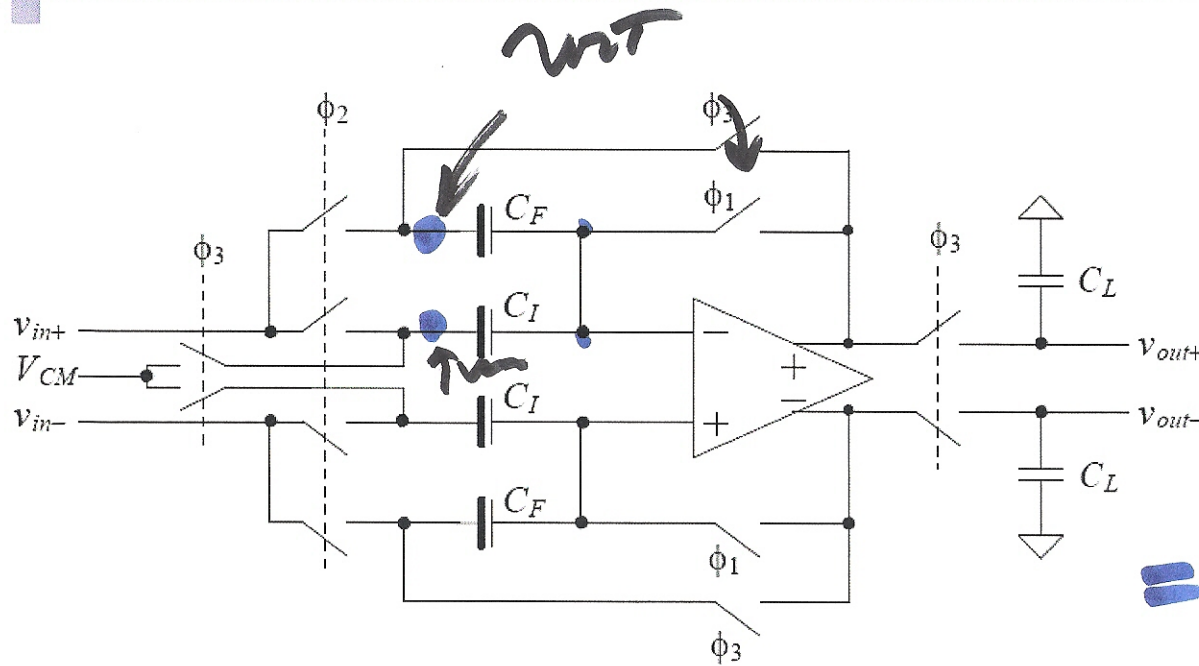


Figure 2.46 A S/H with gain.

$$Q_{I,F} = C_I (v_{in} - v_{cm} \pm v_{os}) = C_F (v_{nt} - v_{cm} \pm v_{os})$$

$$(C_I + C_F) \cdot (v_{in} - v_{cm} \pm v_{os}) = C_F (v_{nt} - v_{cm} \pm v_{os}) + C_I (v_{cm} - v_{cm} \pm v_{os})$$


ϕ_1 closed

$$v_{nt} = \left(1 + \frac{C_I}{C_F}\right) \cdot v_{in} - \frac{C_I}{C_F} \cdot v_{cm}$$

ϕ_3 closed

ii)
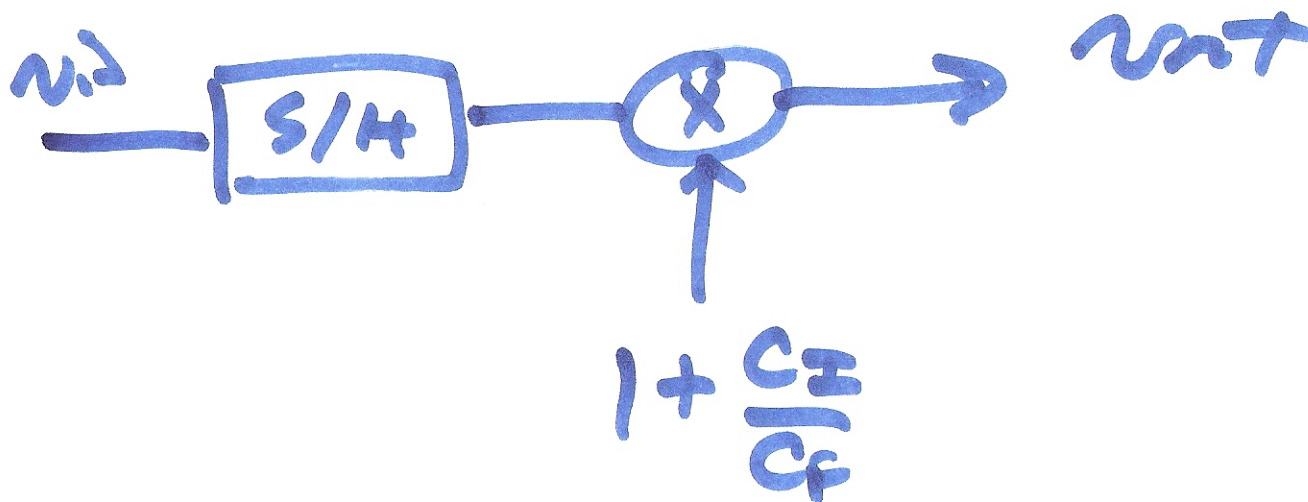
$$v_{out+} - v_{out-} = \left(1 + \frac{C_E}{C_F}\right) (v_{in+} - v_{in-})$$



12)

$V_{DD} = 1$

$V_{eff} = 1$

$V_{eff} = 20$

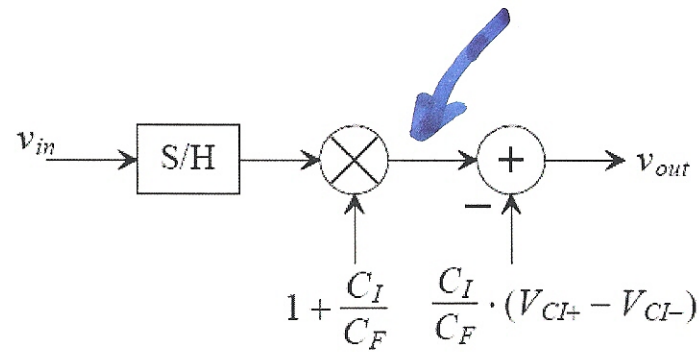
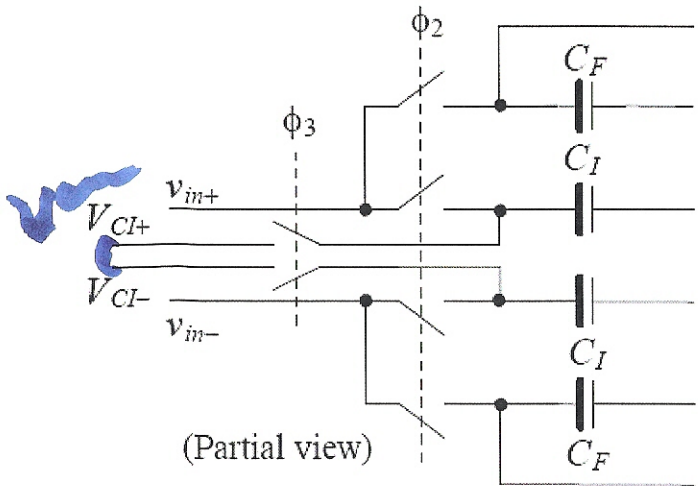


Figure 2.49 Implementing subtraction in the S/H.

137

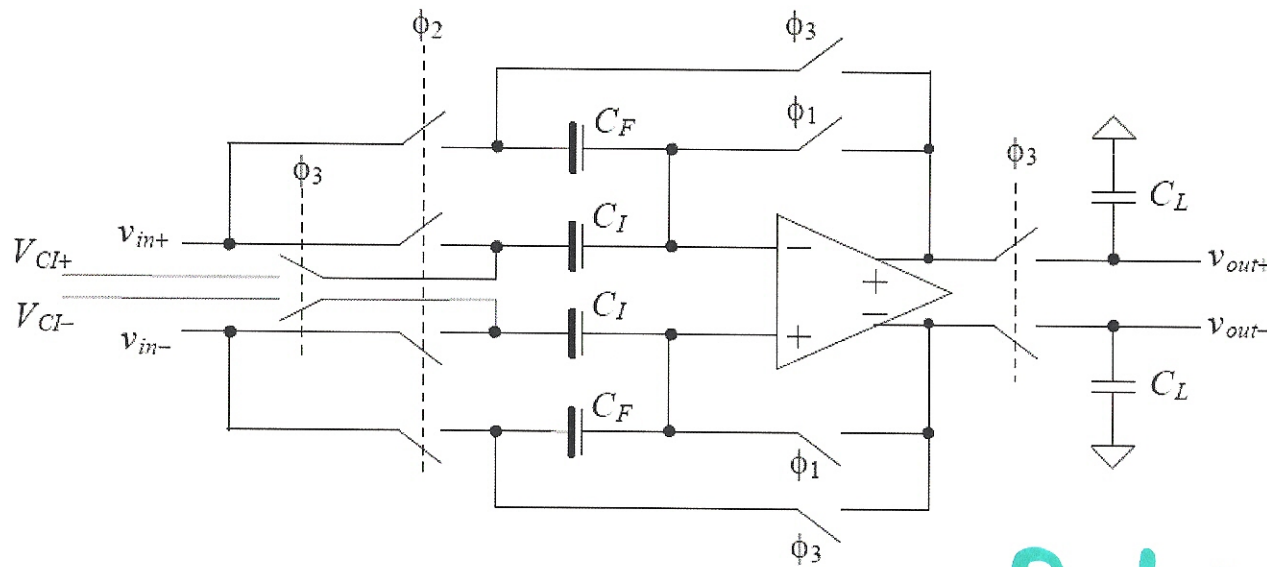


Figure 2.51 S/H used in Ex. 2.5.

fully-differential

Does this S/H use
CDs?

14)

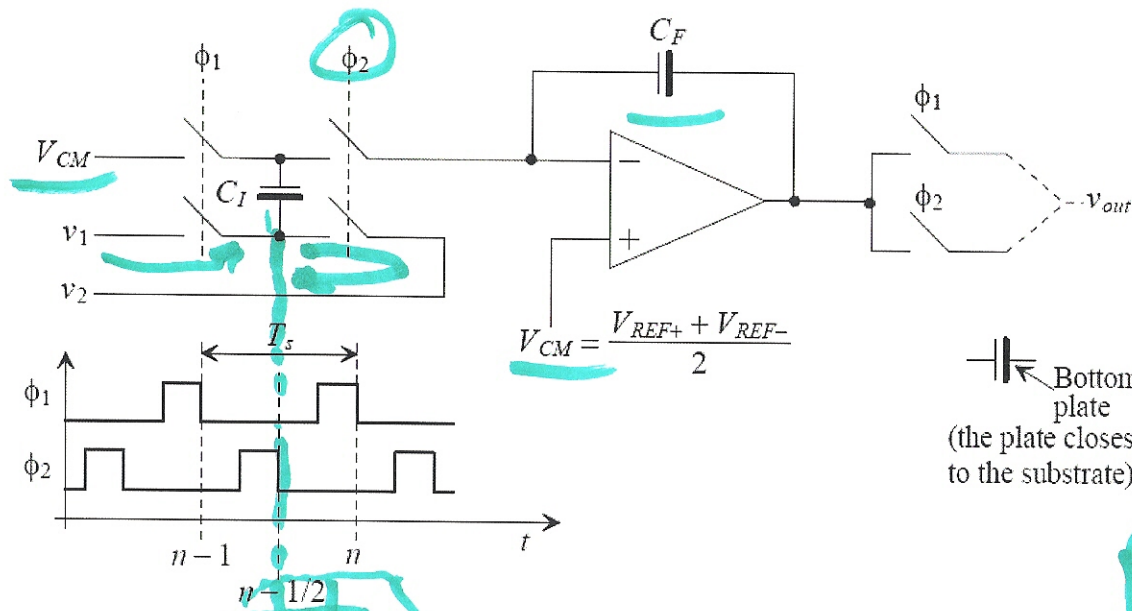


Figure 2.54 Schematic diagram of a discrete analog integrator (DAI).

parasitic insensitive integrator



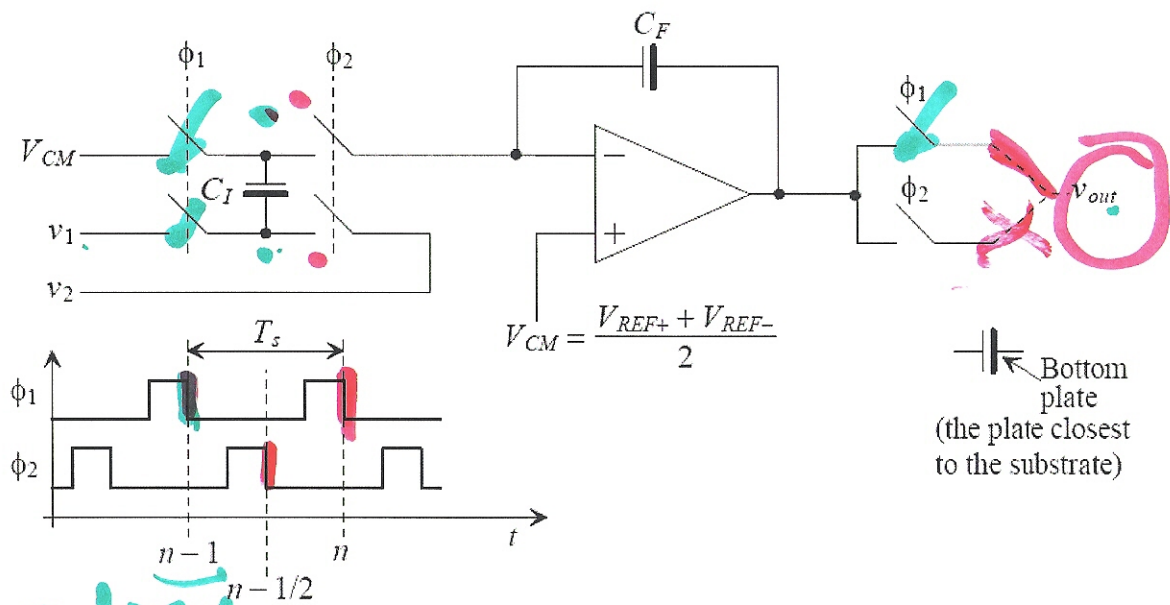


Figure 2.54 Schematic diagram of a discrete analog integrator (DAI).

$\phi_1 - \text{close}$

$$Q_1 = C_I (V_{cm} - v_1((N-1)T_s)) \cdot v_{out}[(N-1) \cdot T_s] \leftarrow$$

$\phi_2 - \text{close}$


$$Q_2 = C_I \cdot (V_{cm} - v_2[(N-1/2)T_s])$$

16)

$$C_F (V_{OUT}[NT_s] - V_{OUT}[(N-1)T_s]) =$$

$$= C_I (V_1[(N-1)T_s] - V_2[(N-1/2)T_s])$$

z -transform




$$C_F (V_{OUT}(z) - V_{OUT}(z) \cdot z^{-1})$$


$$= C_I (V_1(z) \cdot z^{-1} - V_2(z) z^{-1/2})$$

$$V_{OUT} = \frac{C_I}{C_F} \cdot \frac{V_1(z) z^{-1} - V_2(z) z^{-1/2}}{1 - z^{-1}}$$

17)

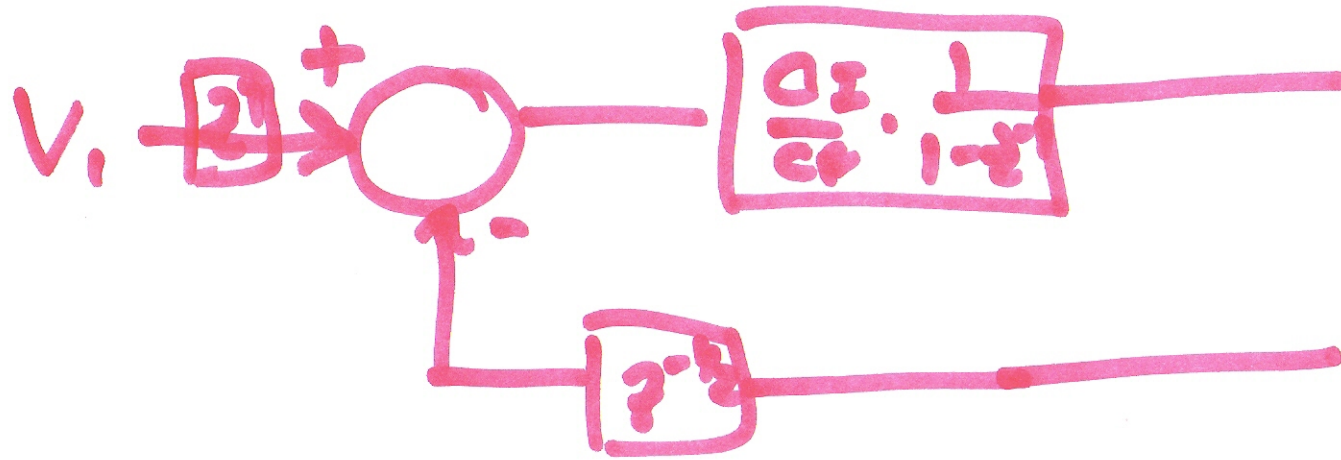

18)

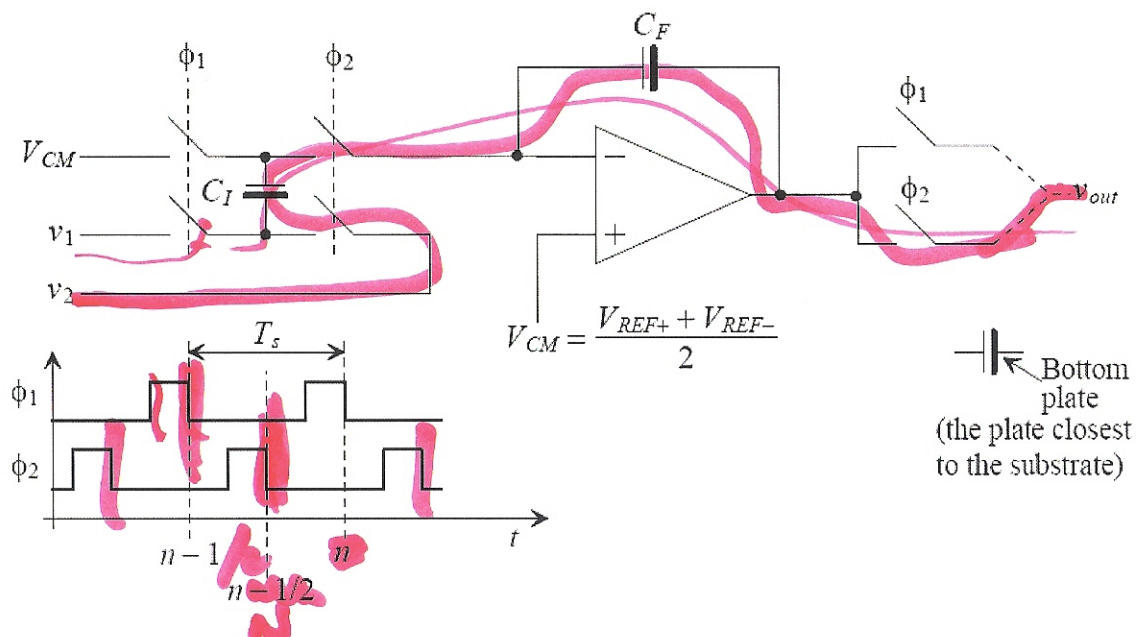

$$\frac{v_1 z^{-1/2} - v_2 z^{-1}}{1 - z^{-1}}$$

Figure 2.54 Schematic diagram of a discrete analog integrator (DAI).

$$C_F [v_{out}(NT_s) - v_{out}((N-1)T_s)] =$$

$$C_I [v_1((N-1/2)T_s) - v_2(NT_s)]$$

17)

$$SNR_{max} = 20 \log \frac{V_{DD}/\sqrt{2} \cdot 2}{\sqrt{\frac{2kT}{C_I}}}$$

$SNR_{max} = ?$

$R_{rms} = \frac{V_{DD}}{2\sqrt{2}}$

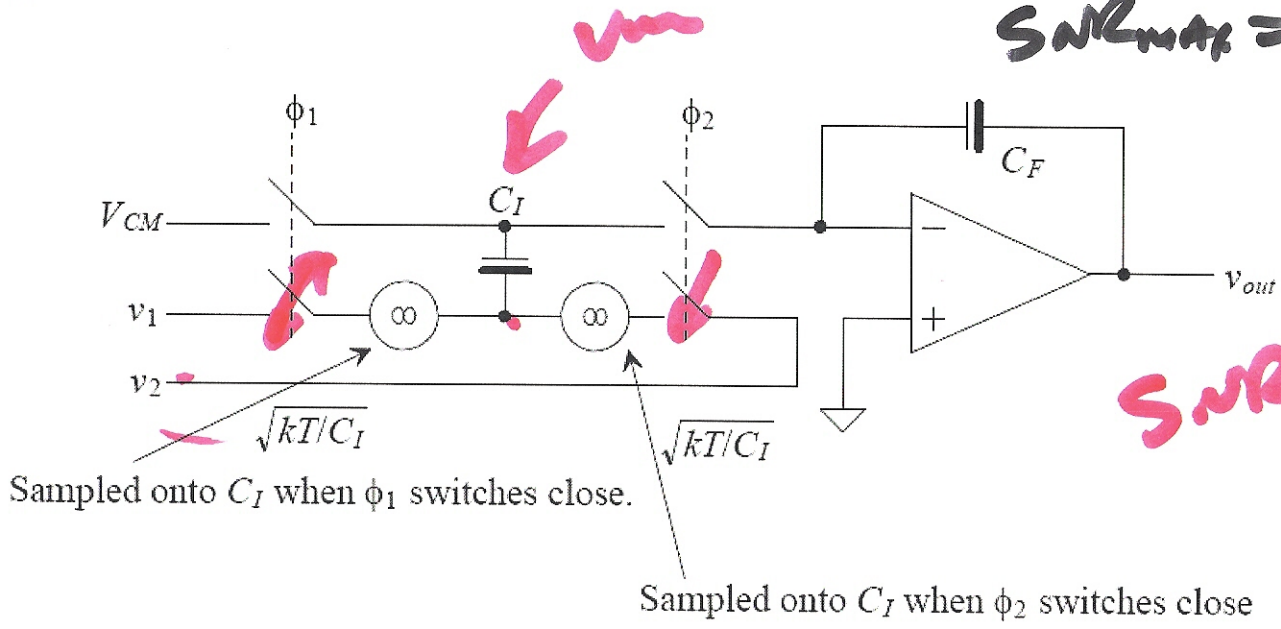


Figure 2.58 Noise performance of the DAI.

$V_{1rms} = \sqrt{\frac{kT}{C_I}}$

$V_{2rms} = \sqrt{\frac{kT}{C_I}}$

$V_{REF} = \sqrt{\frac{2kT}{C_I}}$

20)