
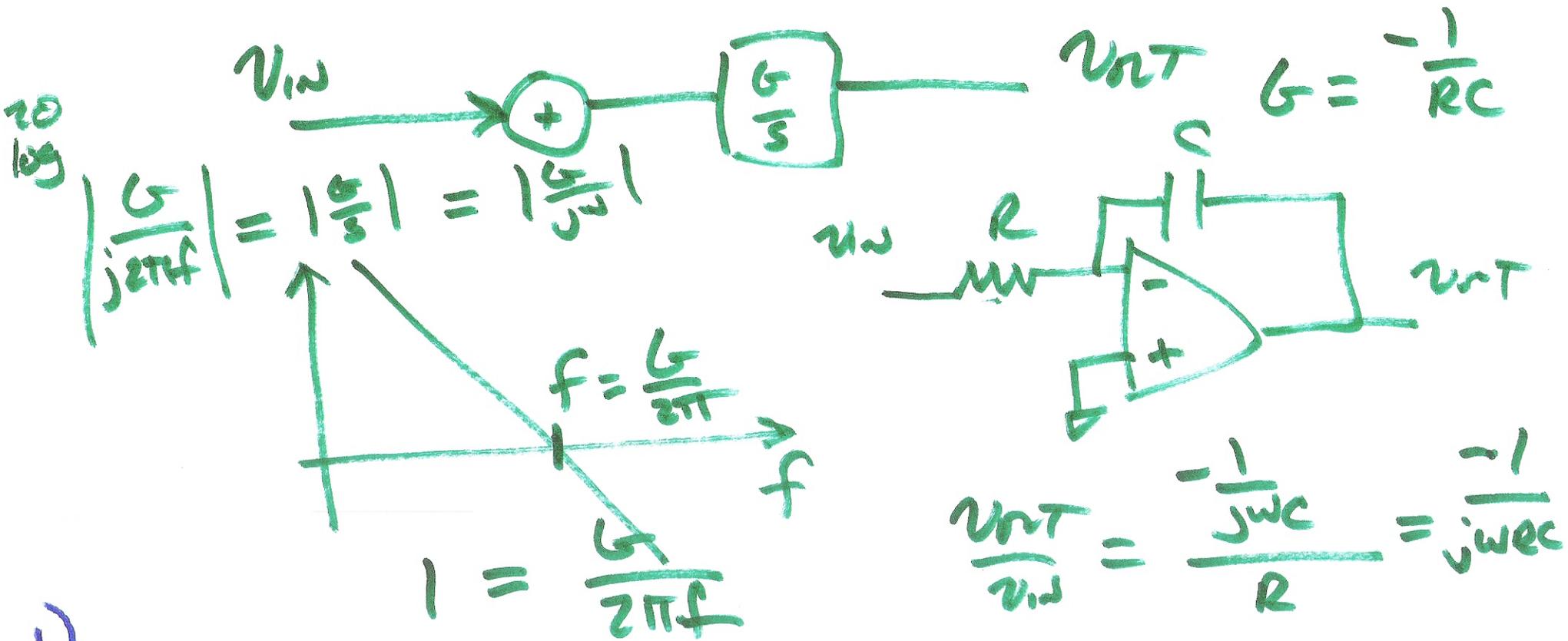


Lecture 9

sept. 22, 2010

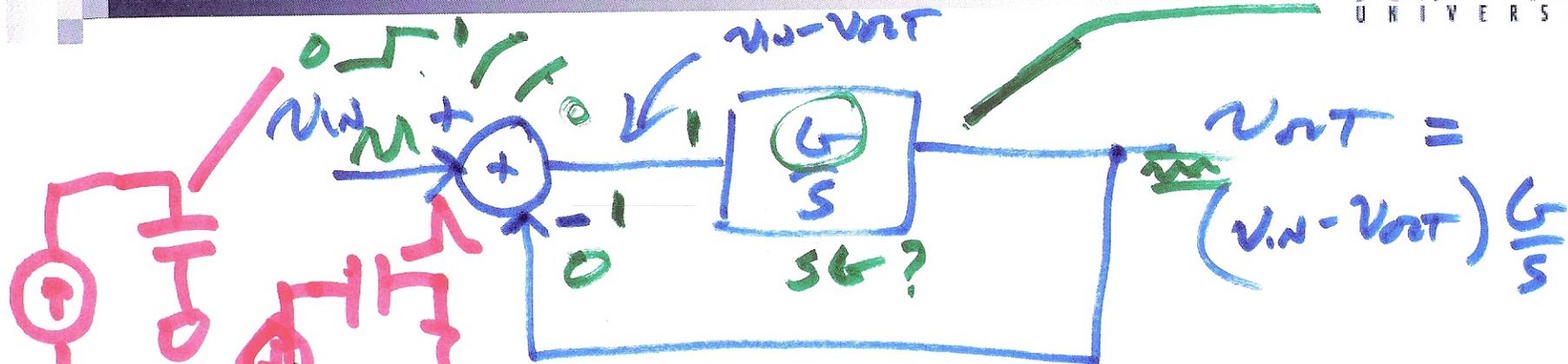


1)



Summed \rightarrow

$$v_{out} \left(1 + \frac{G}{s}\right) = v_{in} \cdot \frac{G}{s}$$

Summed \rightarrow

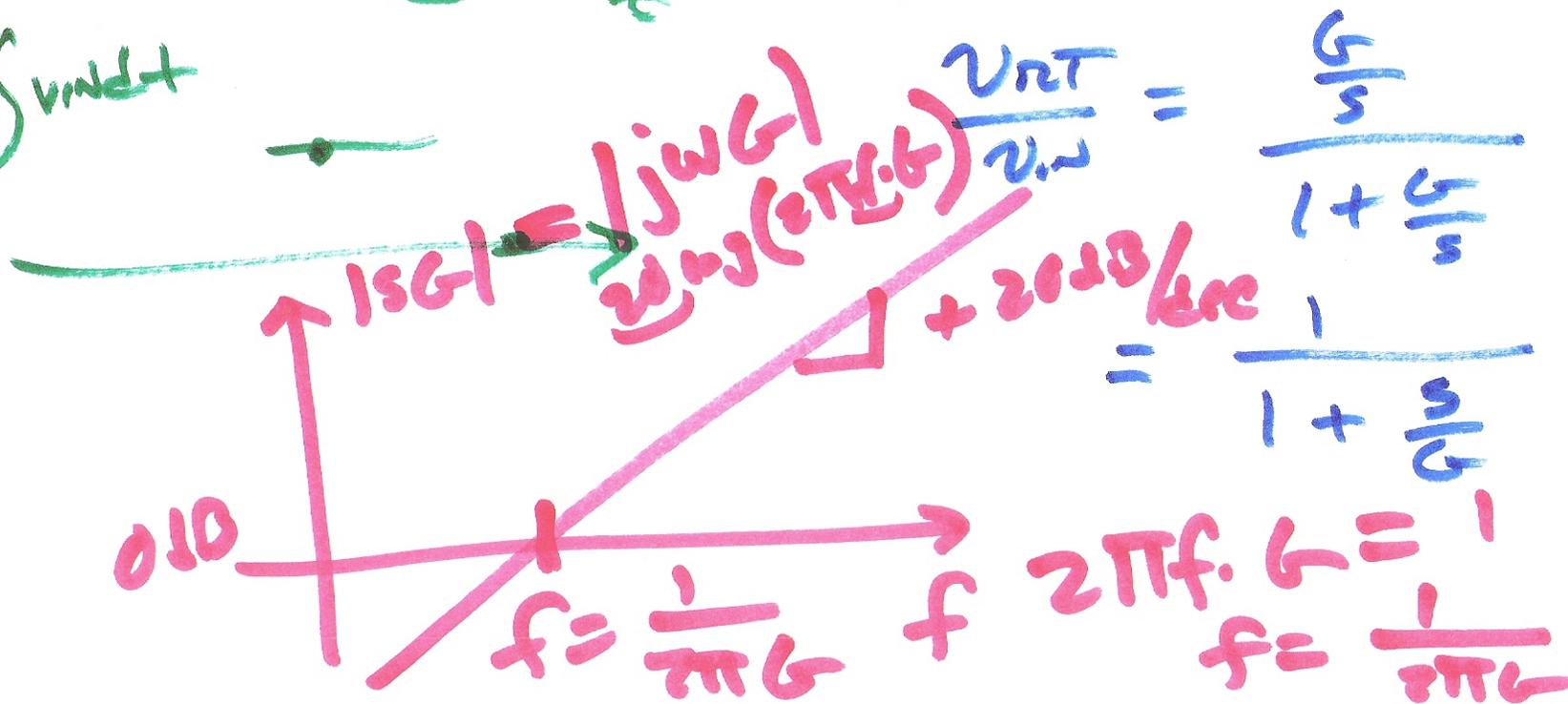

2)

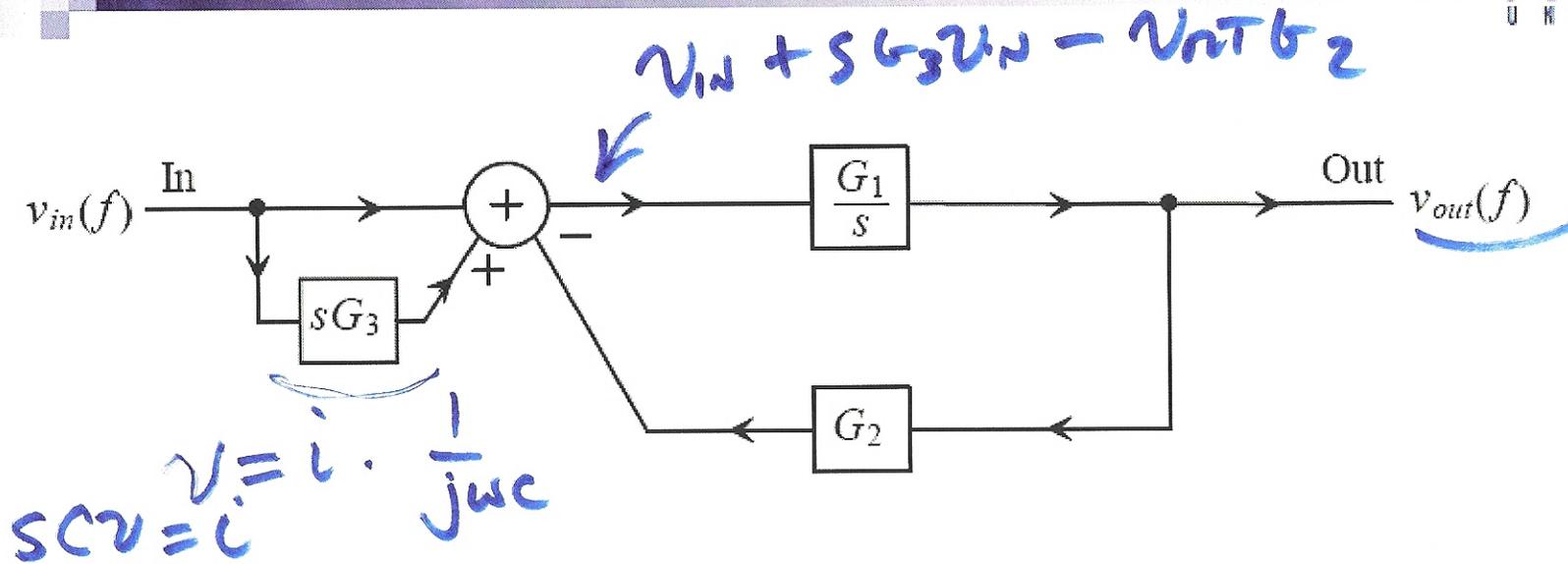


Figure 3.29 Implementation of a bilinear transfer function using an integrator.

$$v_{out} = \frac{G_1}{s} (v_{in} (1 + sG_3) - v_{out} \cdot G_2)$$

$$v_{out} \left(1 + \frac{G_1 G_2}{s} \right) = v_{in} \left(\frac{G_1}{s} + \frac{s G_1 G_3}{s} \right)$$

$$\frac{v_{out}}{v_{in}} = \frac{\frac{G_1}{s} + G_1 G_3}{1 + \frac{G_1 G_2}{s}} = \frac{\frac{G_1}{s} + G_1 G_3}{G_2 \frac{1}{G_2} + \frac{G_1}{s}}$$

3)



$$\frac{v_{out}}{v_{in}} = \frac{1 + s/\omega_3}{1 + s/\omega_1\omega_2} \cdot \frac{1}{\omega_2}$$

$$j2\pi f_{zero} = s_{zero} = -\frac{1}{\omega_3}, \quad f_{zero} = \frac{1}{2\pi\omega_3}$$

$$s_{pole} = -\frac{1}{\omega_1\omega_2}, \quad f_{pole} = \frac{1}{2\pi\omega_1\omega_2}$$

bilinear filter!

4)

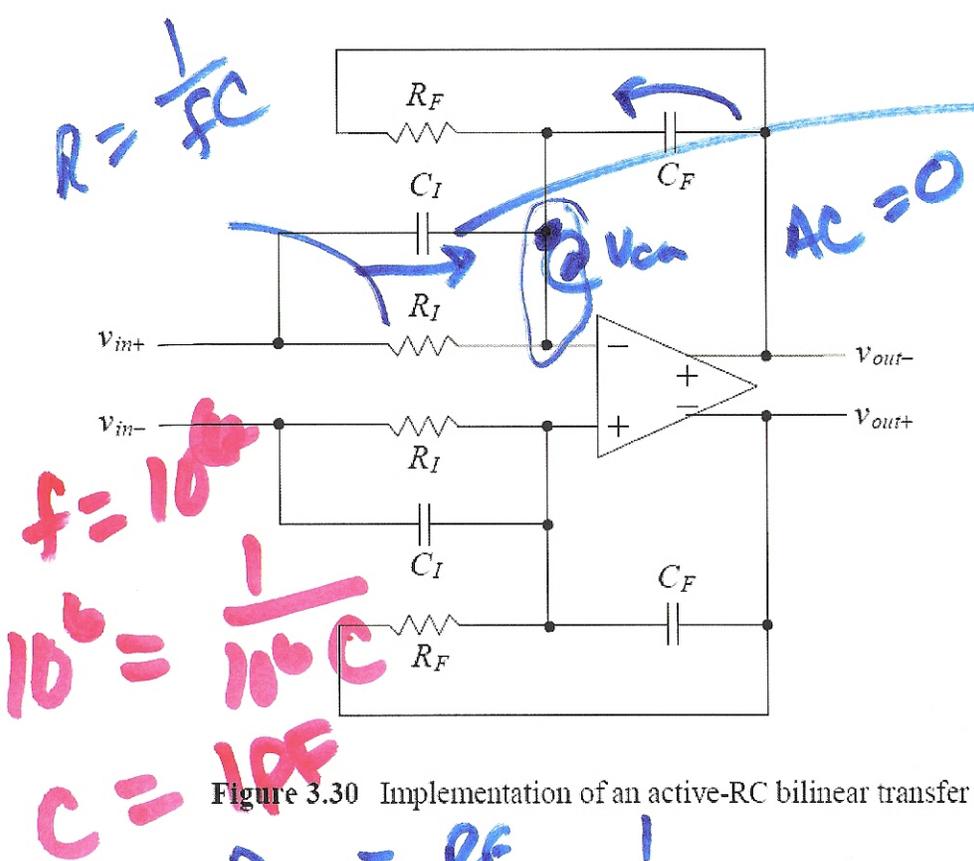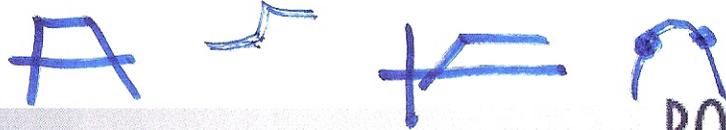

$R = \frac{1}{fC}$
 $f = 10^4$
 $10^6 = \frac{1}{10^6 C}$
 $C = 100F$

Figure 3.30 Implementation of an active-RC bilinear transfer function filter.

$$i = SC_I \cdot V_{in}$$

$$\frac{V_{in}}{R_I} + V_{in} \cdot SC_I + \frac{V_{out}}{R_F} = -V_{out} \cdot SC_F$$

$$G_1 = \frac{1}{R_I C_F}$$

$$G_2 = \frac{R_I}{R_F}$$

$$G_3 = R_I C_I$$

$$V_{out} \left(\frac{1}{R_F} + SC_F \right) = -V_{in} \left(\frac{1}{R_I} + SC_I \right)$$


$$ACL = \frac{R_F}{R_I} = \frac{1}{G_2}$$

$$f_{zero} = \frac{1}{2\pi R_I C_I}$$

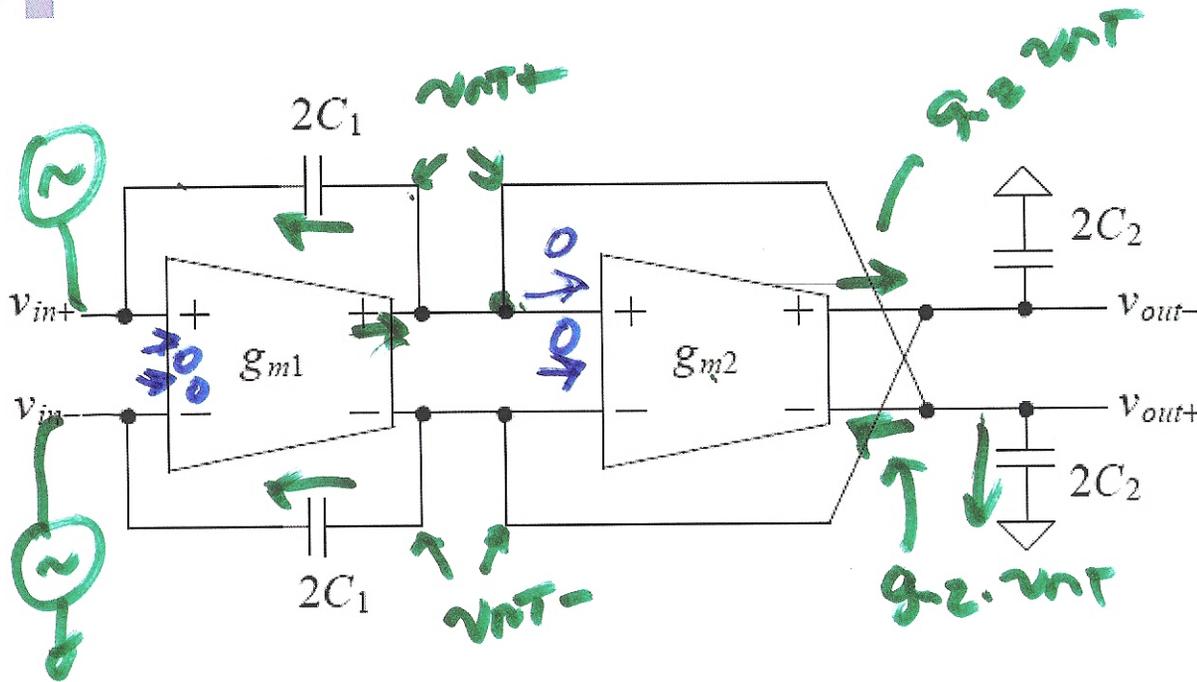5) $f_{pole} = \frac{1}{2\pi R_F C_F}$

$$\frac{V_{out}}{V_{in}} = \frac{-\left(\frac{1}{R_I} + SC_I \right)}{\frac{1}{R_F} + SC_F}$$

$$= -\frac{R_F}{R_I} \cdot \frac{1 + SC_I R_I}{1 + SC_F R_F}$$



$$G_1 = g_{m1} / (C_1 + C_2)$$

$$G_2 = \frac{g_{m2}}{g_{m1}}$$

$$G_3 = \frac{C_1}{g_{m1}}$$

Figure 3.31 Implementation of a bilinear filter using transconductors.

$$(v_{NT} - v_{in}) \cdot 2C_1 \cdot s = g_{m1} \cdot v_{in} \quad \text{Handwritten: } v_{NT} \text{ and } g_{m1} \cdot v_{in}$$

$$+ v_{NT} \cdot 2C_2 \cdot s + g_{m2} \cdot v_{NT}$$

RC = time

$$C \cdot f = \frac{C}{T} = \frac{1}{R}$$

$$sC \rightarrow \frac{1}{R}$$

5)

$$v_{out} (2C_1s + 2C_2s + g_{-2}) = v_{in} (2C_1s + g_{-1})$$

$$\frac{v_{out}}{v_{in}} = \frac{2C_1s + g_{-1}}{(C_1 + C_2)2s + g_{-2}} = \frac{g_{-1}}{g_{-2}} \left(\frac{1 + s \cdot \frac{2C_1}{g_{-1}}}{1 + s \cdot \frac{2(C_1 + C_2)}{g_{-2}}} \right)$$

2 drops out fully-diff. paths: $G_2 = \frac{g_{-2}}{g_{-1}}$
with equal paths: $G_1 G_2 = g_{-2}$


$$f_w = \frac{g_{-1}}{2\pi C_c} = \frac{1}{2\pi \frac{1}{f} C_c} \quad G_3 = \frac{2C_1}{g_{-1}}$$

$$s_{pole} = \frac{-g_{-2}}{2(C_1 + C_2)}$$

$$G_1 = \frac{g_{-1}}{2g_{-2}(C_1 + C_2)}$$

$$= \frac{1}{1/g_{-2}(C_1 + C_2)}$$

2)

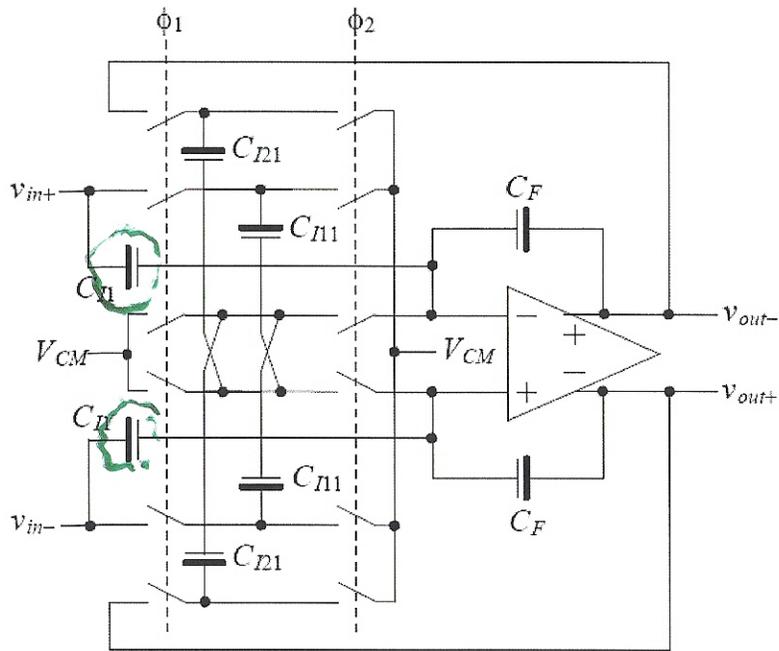

$$G_1 = \frac{C_{N1}}{C_F} \cdot f_s = \frac{1}{C_F \cdot R_{EII}} \quad R_{EII} = \frac{1}{f_s C_{N1}}$$

$$G_2 = \frac{C_{D1}}{C_{N1}}$$

$$G_3 = \frac{C_{N1}}{C_{N1} \cdot f_s}$$

$$\frac{v_{out}(f)}{v_{in}(f)} = \frac{1}{G_2} \cdot \frac{1 + \frac{s}{1/G_3}}{1 + \frac{s}{G_1 G_2}}$$

Figure 3.32 Implementation of a bilinear filter using switched capacitors.

BiQuad




$$\omega_0 = 2\pi f_0$$

$$\frac{V_{out}}{V_{in}} = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + \left(\frac{2\pi f_0}{Q}\right) s + (2\pi f_0)^2}$$

$$Q = \frac{\text{energy stored}}{\text{energy lost}}$$

$$= \frac{f_{center}}{\Delta f_{3dB}}$$

$$= \frac{f_{center}}{BW}$$

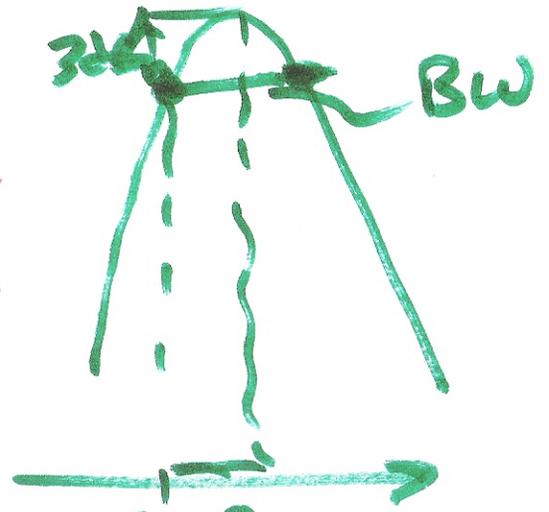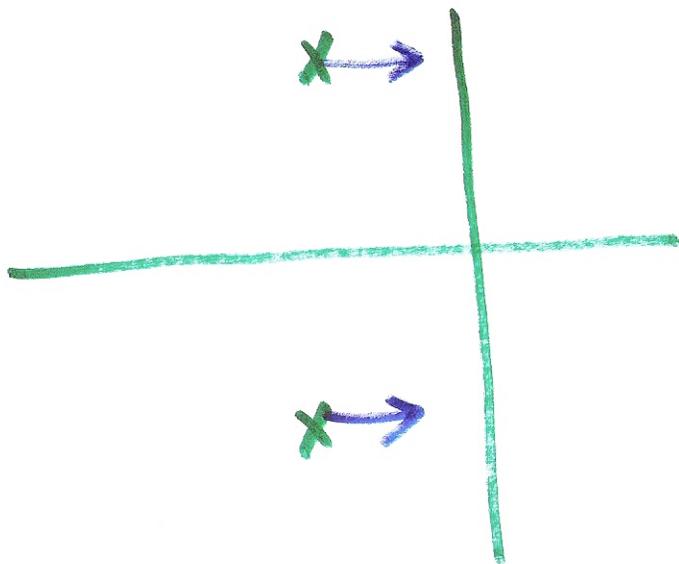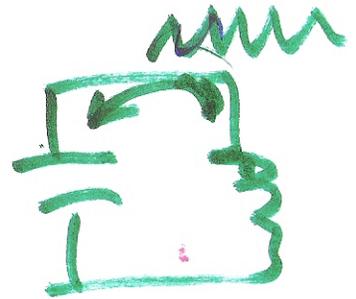

9)

$$p_1, p_2 = -\frac{\pi f_0}{Q} \pm \frac{1}{2} \sqrt{\left(\frac{2\pi f_0}{Q}\right)^2 - 4(\pi f_0)^2}$$

$$= \frac{-\pi f_0}{Q} + j 2\pi f_0 \sqrt{1 - \left(\frac{1}{2Q}\right)^2}$$

$$\begin{aligned} \frac{1}{2Q} &\geq 1 \\ 1 &\geq 2Q \\ Q &\leq \frac{1}{2} \end{aligned}$$

(a)


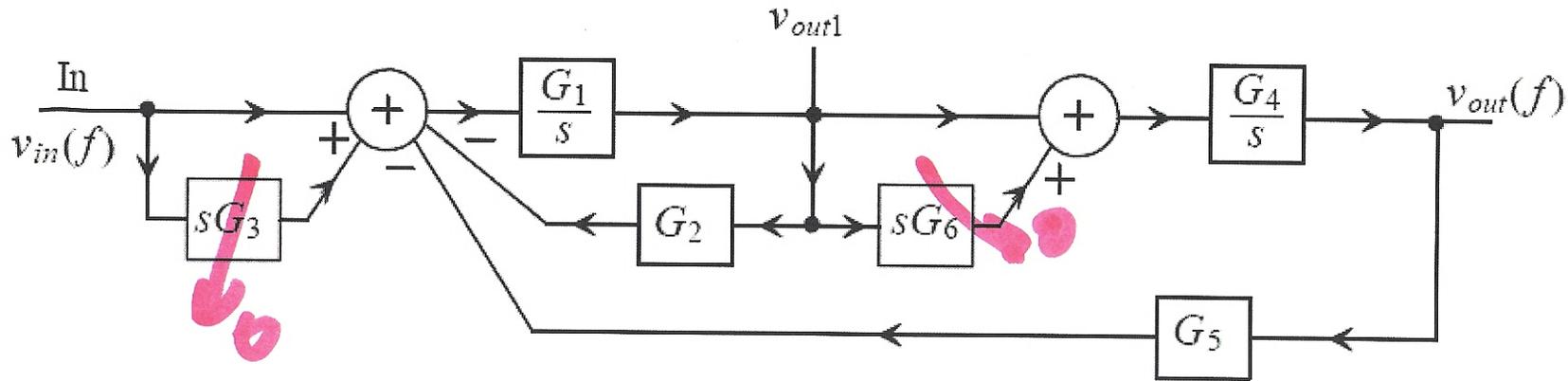


Figure 3.33 Implementation of a biquadratic transfer function using two integrators.

(3.70) $\frac{v_{out}}{v_{in}} = \frac{s^2 \cancel{G_1 G_3 G_4 G_6} + s(\cancel{G_1 G_3 G_4} + \cancel{G_1 G_4 G_6}) + G_1 G_4}{s^2 + s(G_1 G_2 + G_1 G_4 \cancel{G_5 G_6}) + G_1 G_4 G_5}$

$(2\pi f_0)^2 = G_1 G_4 G_5$

iii)

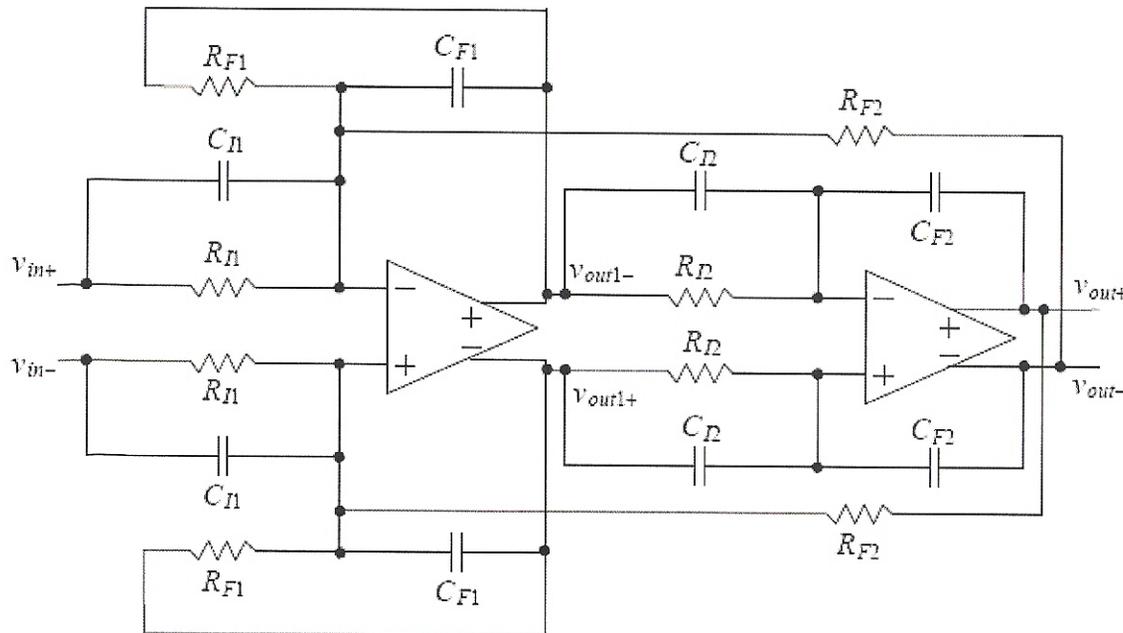


$$G_1 = \frac{1}{R_N C_{F1}} \quad G_2 = \frac{R_N}{R_{F1}} \quad G_3 = R_N C_N \quad G_4 = \frac{1}{R_N C_{F2}} \quad G_5 = \frac{R_N}{R_{F2}} \quad G_6 = R_N C_N$$

$$a_2 = \frac{C_N C_N}{C_{F1} C_{F2}} \quad a_1 = \frac{C_N}{R_N C_{F1} C_{F2}} + \frac{C_N}{R_N C_{F1} C_{F2}} \quad a_0 = \frac{1}{R_N C_{F1} R_N C_{F2}}$$

$$\frac{\omega_0}{Q} = \frac{2\pi f_0}{Q} = \frac{1}{R_{F1} C_{F1}} + \frac{C_N}{C_{F1} R_{F2} C_{F2}} \quad f_0 = \frac{1}{2\pi} \cdot \sqrt{\frac{1}{C_{F1} R_N C_{F2} R_{F2}}}$$

Figure 3.34 Implementation of the active-RC biquadratic transfer function filter.

12)

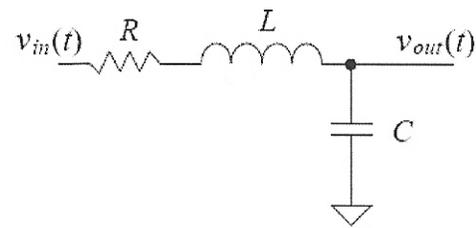

$$\frac{v_{out}}{v_{in}} = \frac{\frac{1}{LC}}{s^2 + s\frac{R}{L} + \frac{1}{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$Q = \frac{1}{R}\sqrt{\frac{L}{C}}$$

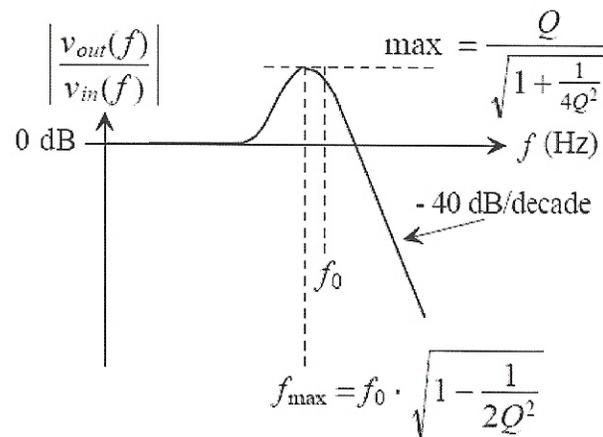
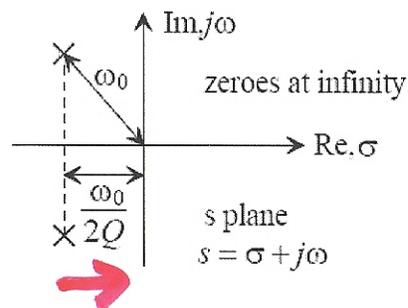


Figure 3.35 Second-order lowpass filter.

13)

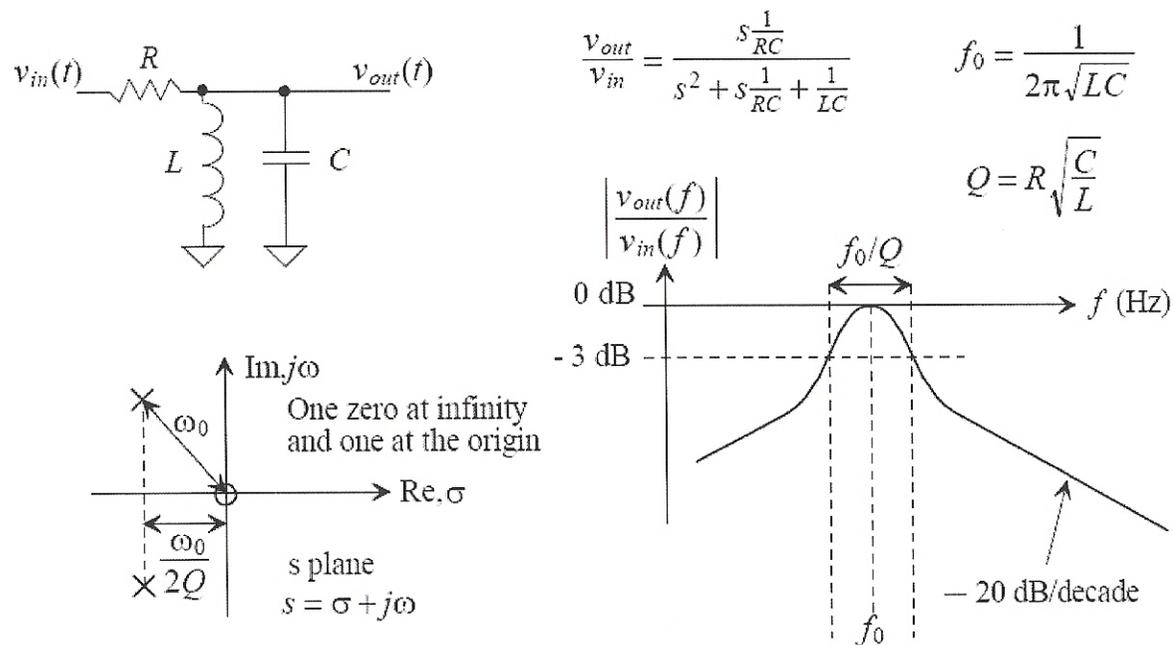


Figure 3.39 Second-order bandpass filter.

14)