
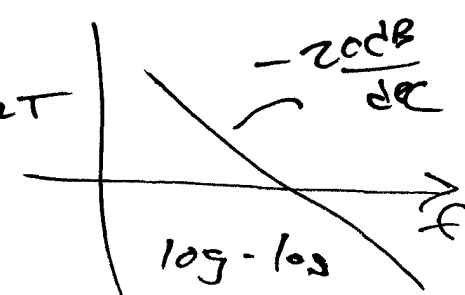
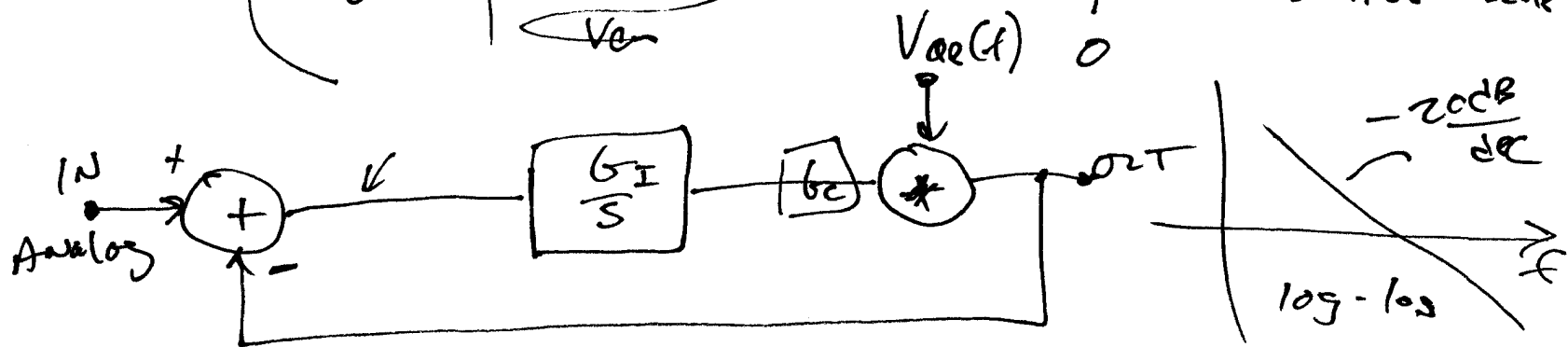
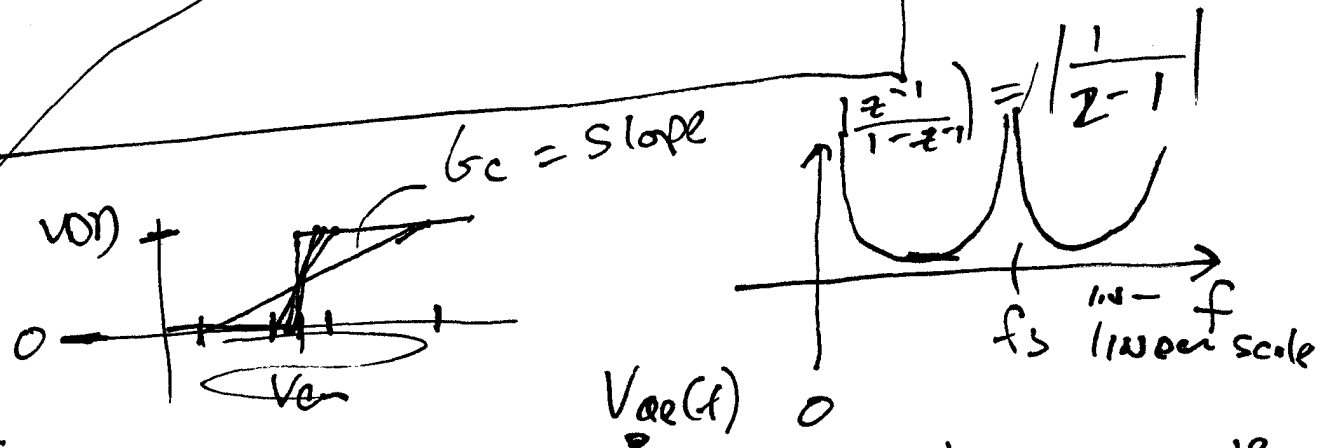


## Lecture 19

4/6/09

Discrete-time


$\Delta \Sigma$  modulator

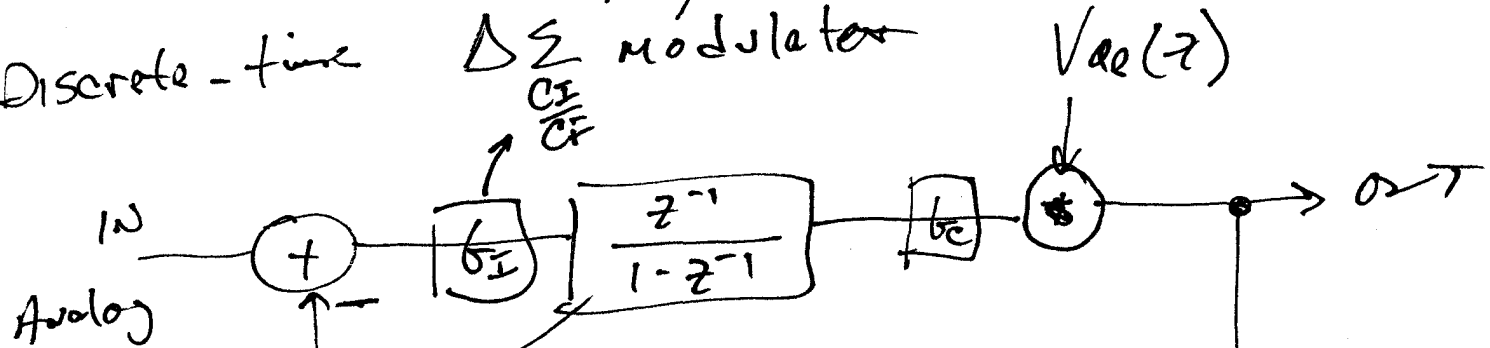

$$(V_{in} - V_{out}) \frac{G_I \cdot G_C}{s} = V_{out}$$

$$V_{in} \cdot \frac{G_I \cdot G_C}{s} = V_{out} \left( 1 + \frac{G_I \cdot G_C}{s} \right)$$
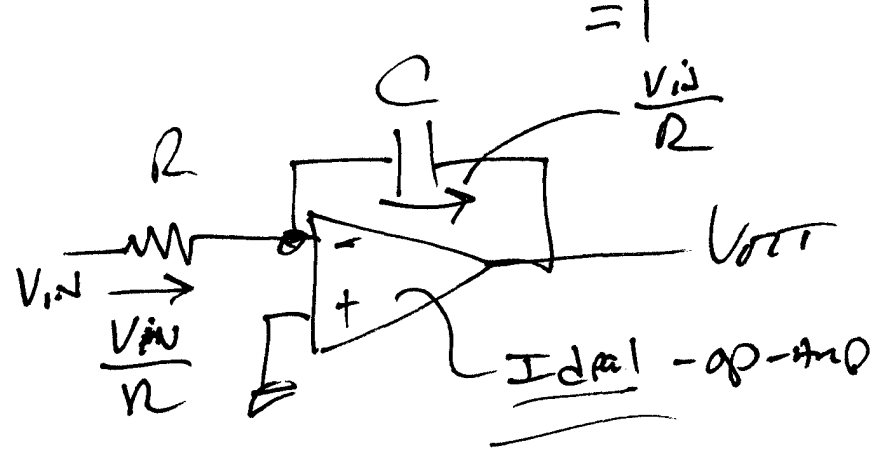
$$\frac{V_{out}}{V_{in}} = \frac{V_{in}}{\frac{s}{G_I \cdot G_C} + 1} = \frac{V_{in}}{s + 1}$$



$$V_{out} = -\frac{V_{in}}{R} \cdot \frac{1}{j\omega C}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{1}{j\omega RC} \right|$$

$$G_I = \frac{1}{RC}$$

$$s = j\omega$$

2)

NON-ideal op-amp (integrator)


$$\frac{v_{out}}{v_+ - v_-} \approx \frac{A_{olDC}}{j \frac{f}{f_{3dB}}}$$

$$A_{ol}(f) \approx \frac{f_{BW}}{j f}$$

finite DC gain (open-loop)


finite BW


$|A_{ol}(f)|$

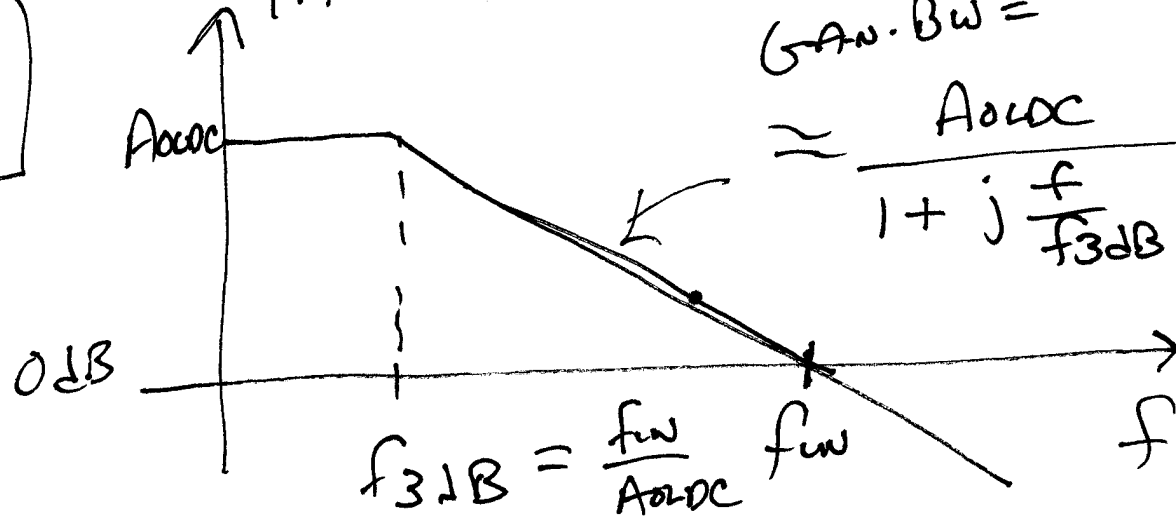

$$G_{AW} \cdot BW = \frac{A_{olDC}}{1 + j \frac{f}{f_{3dB}}} \approx \frac{A_{olDC}}{j \frac{f}{f_{3dB}}} = \frac{v_{out}}{v_+ - v_-}$$

$$f_{3dB} \cdot A_{olDC} = f_{uW}$$

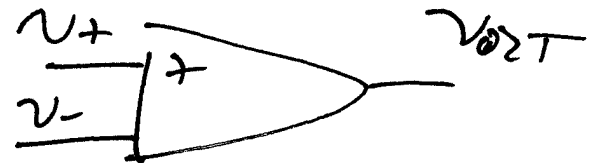

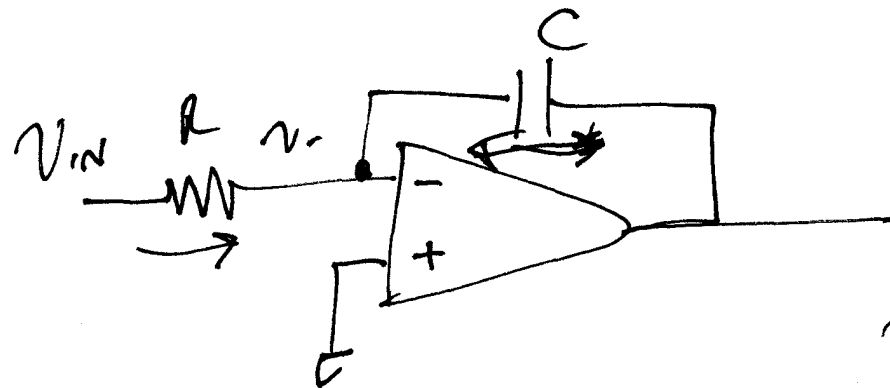

$$v_{out} = \frac{f_{\omega}}{j\omega} = A_{OL}$$

$$v_{out} = (v_{+} - v_{-}) A_{OL}$$

$$v_{-} = -\frac{v_{out}}{A_{OL}}$$

$$\frac{v_{in} + \frac{v_{out}}{A_{OL}}}{R} + \frac{v_{out} + \frac{v_{out}}{A_{OL}}}{\frac{1}{j\omega C}} = 0$$

$$v_{in} + \frac{v_{out}}{A_{OL}} + j\omega RC \left( v_{out} + \frac{v_{out}}{A_{OL}} \right) = 0$$

$$v_{out} \left( \frac{1}{A_{OL}} + j\omega RC \right) = -v_{in} \left( 1 + \frac{1}{A_{OL}} \right)$$

4)

$$\frac{V_{out}}{V_{in}} = \frac{-1}{\frac{1}{A_{OL}} + j\omega RC \left(1 + \frac{1}{A_{OL}}\right)}$$

$$A_{OL} \approx \frac{f_{sw}}{j \cdot f}$$

$$\frac{V_{in}}{1 + j\omega RC} = \frac{-1}{\frac{jf}{f_{sw}} + j\omega RC \left(1 + \frac{jf}{f_{sw}}\right)}$$

$$\frac{V_{in}}{1 + j2\pi f RC}$$

$$f_{in} < \frac{1}{2\pi RC}$$


$$= \frac{-1}{\frac{jf}{f_{sw}} \left(1 + j\omega RC\right) + j\omega RC}$$

$\approx 1$

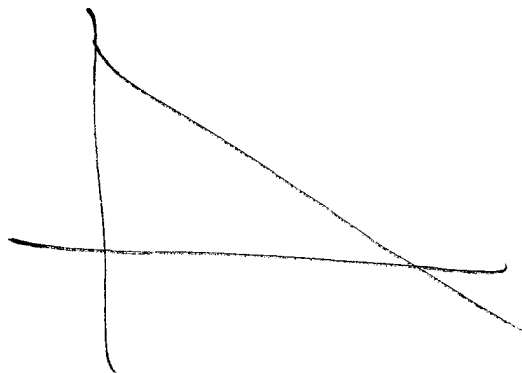5)

$$\frac{v_{out}}{v_{in}} \approx \frac{-1}{j\frac{f \cdot 2\pi}{f_{w \cdot 2\pi}} + j\omega RC}$$

$$= \frac{-1}{j\omega \left( RC + \frac{1}{2\pi f_{w \cdot 2\pi}} \right)}$$



$$\left| \frac{v_{out}}{v_{in}} \right| = 1 = \frac{1}{2\pi f_{w \cdot 2\pi} \left( RC + \frac{1}{2\pi f_{w \cdot 2\pi}} \right)}$$

How finite BW  
affects  $\Delta \Sigma$  modulator's  
performance

$$f_{w \cdot 2\pi} = \frac{1}{2\pi \left( RC + \frac{1}{2\pi f_{w \cdot 2\pi}} \right)}$$


Shifted integrator w/ unity gain freq.

$$f_{w \cdot 2\pi} > \frac{1}{2\pi RC}$$

Op-Amp unity-gain

b)


How does DC gain come in to play?

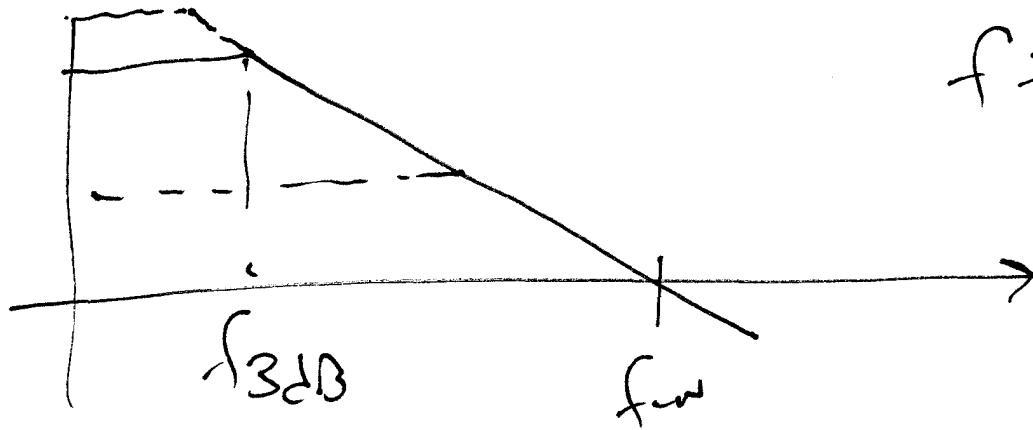



$f \gg f_{3dB}$

Page 247

integrator leakage

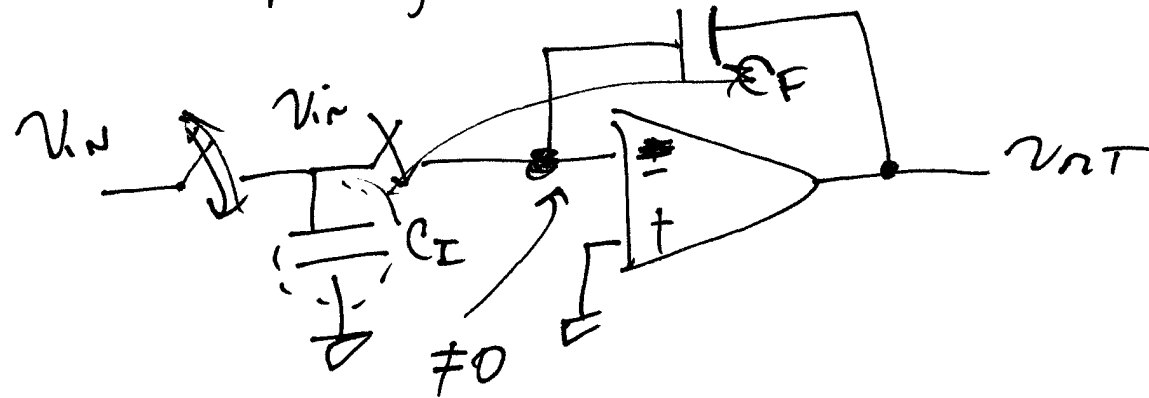

7)

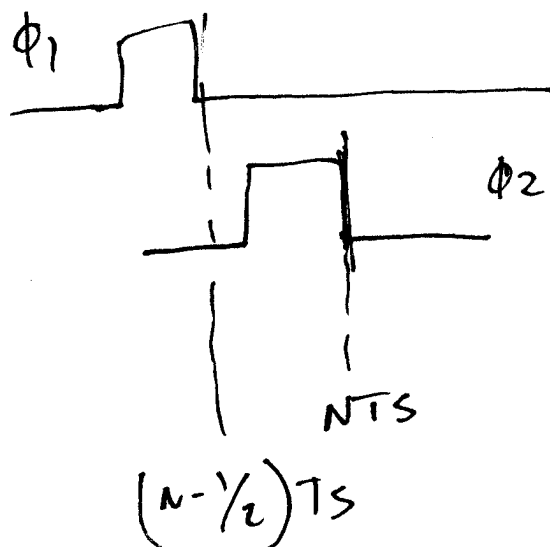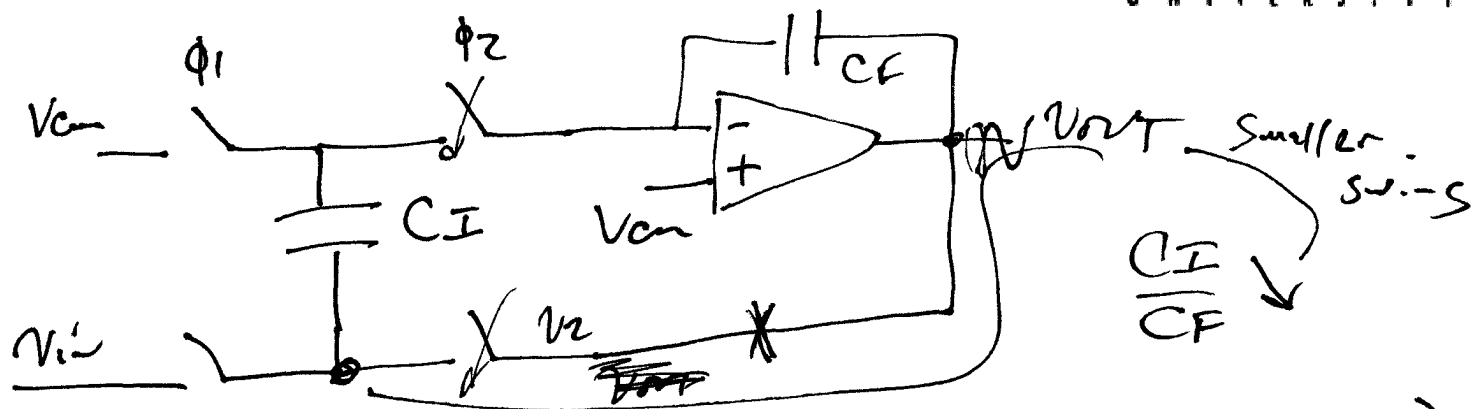


$$Q_1 = \left( \cancel{V_{in}} V_{in} \left( (N - \frac{1}{2}) TS \right) \right)$$

$$Q_2 = \left( V_{in} - \frac{V_{OUT}(NTS)}{A_{OL}(f)} - V_2(NTS) \right) C_I$$

$$V_{OUT}(z) = \frac{C_I}{C_F} \cdot \frac{V_1 z^{-1/2} - V_2}{\left( 1 + \frac{C_I}{C_F} \frac{1}{A_{OL}(f)} \right) z^{-1}}$$

Eq. (7.32)
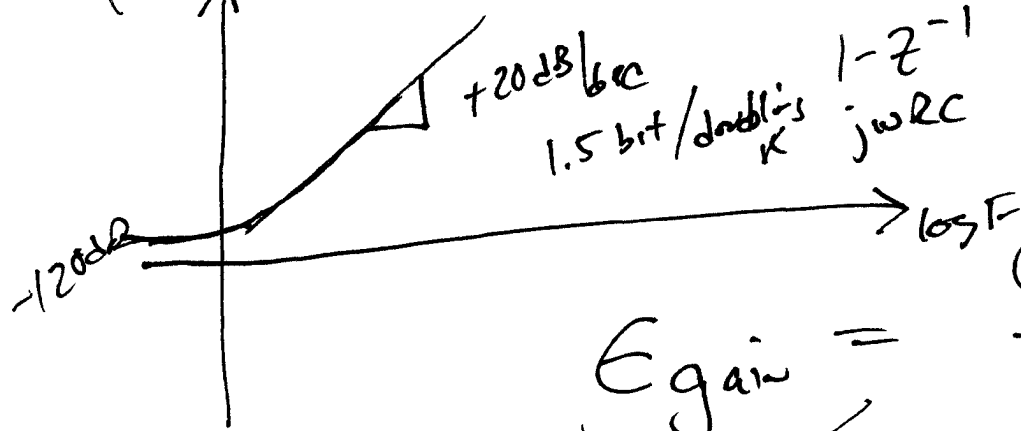
$$\left( \frac{V_{\text{ref}}^2}{CF} \right) \cdot \left( \frac{1}{A_{OL}} \right) \cdot V_{\text{NT}}(z) = \frac{z^{-1}}{1 + \frac{C_I}{CF} \cdot \frac{1}{A_{OL}}} \cdot V_{\text{in}} + \frac{V_{\text{ref}}(z)}{1 + \frac{C_I}{CF} \cdot \frac{1}{A_{OL}} - z^{-1}}$$



$$S_{\text{NR}} = 6.02N + 1.76 - 5.13 + 30 \log K$$


$$\epsilon_{\text{gain}} = \frac{C_I}{CF} \cdot \frac{1}{A_{OL}} \quad K = 100$$

Small

$$V_{\text{AES}}^2 = 2 \cdot \frac{V_{\text{LSB}}^2}{12 f_s} \left[ 4(1 + \epsilon_{\text{gain}}) \frac{\pi^2}{f_s^2} \cdot \frac{1}{3} \left( \frac{f_s}{2K} \right)^2 + \epsilon_{\text{gain}}^2 \cdot \frac{f_s}{2K} \right]$$

$$\boxed{A_{OL} > K}$$


9)

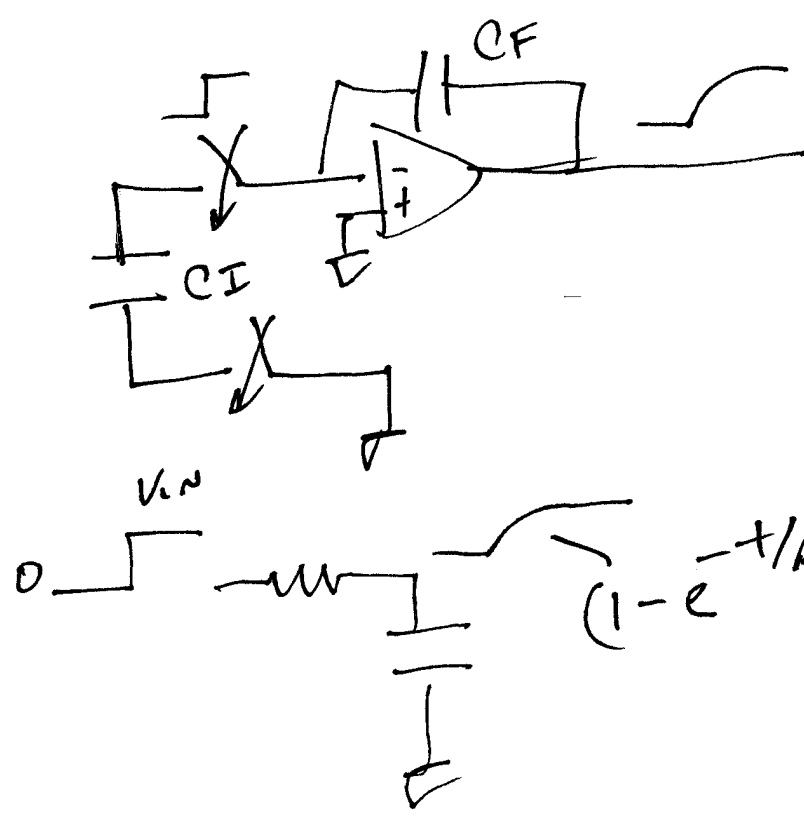


$$V_{out} = V_{out,final} (1 - e^{-t/\tau})$$

$$\tau = \frac{1}{2\pi f_{BW}}$$

$$B = \frac{C_F}{C_F + C_I}$$

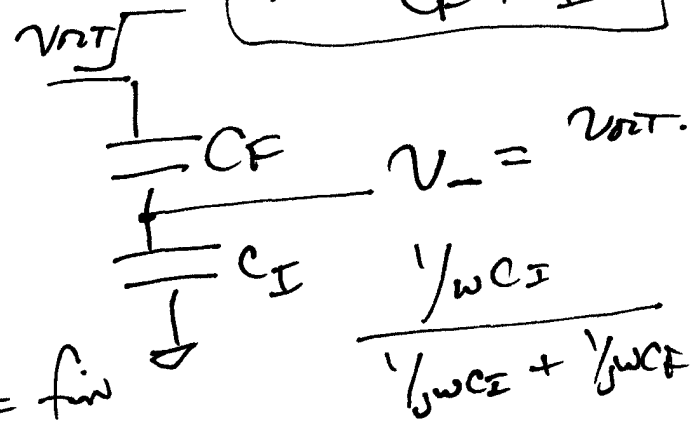



$$f_{3dB} \cdot A_{OLDC} = f_{in}$$

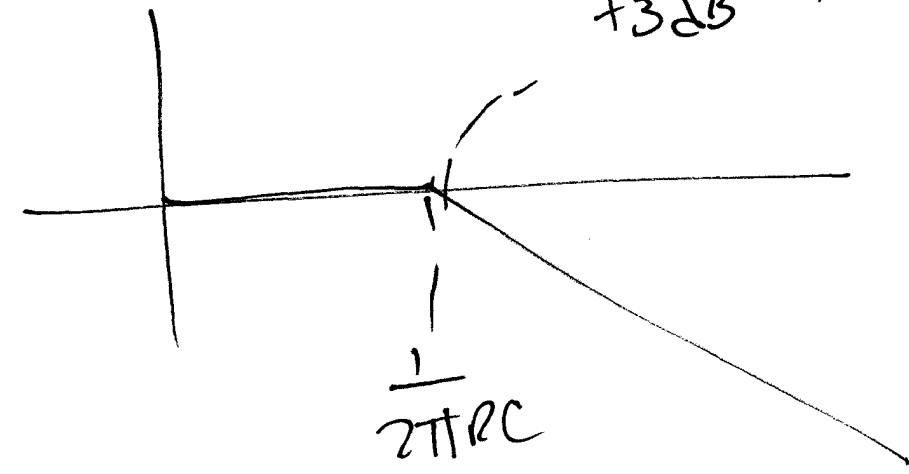

$$\frac{A_{OLDC}}{1 + j \frac{f}{f_{3dB}}} = \frac{1}{\frac{1}{A_{OLDC}} + j \frac{f}{f_{in}}}$$

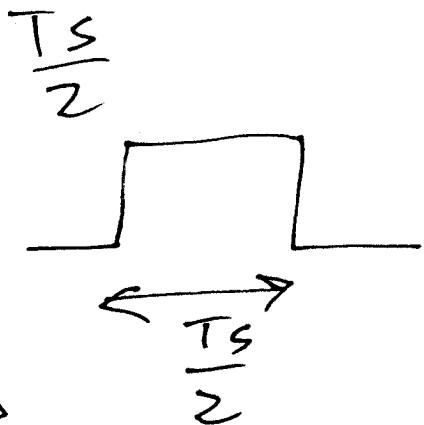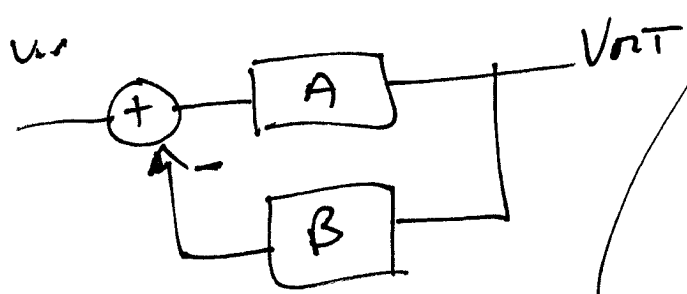10)

$$V_{out}(z) = \frac{C_I}{C_F} \cdot \left(1 - e^{-\pi\beta \cdot f_{in}/f_s}\right) \cdot \frac{V_1(z)z^{-1/2} - V_2(z)}{1 - z^{-1}}$$



NO slewing

$$\frac{V_{out}}{u_w} = \frac{A}{1 + BA}$$

$$= \frac{1}{\frac{1}{A} + \beta}$$



11)