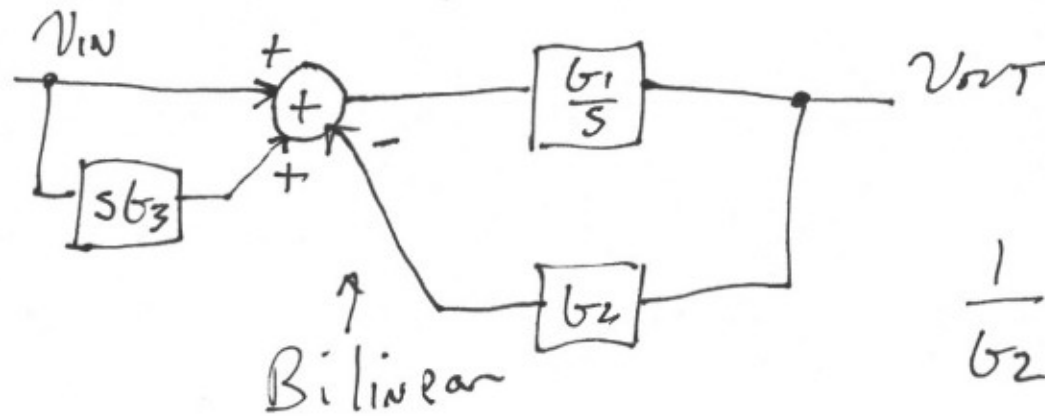



ECE 615 CMOS Mixed-Signal Circuit Design

Sec. 4.3 Digital Filtering



$$\frac{1}{G_2} \cdot \frac{1 + s \cdot G_3}{1 + \frac{s}{G_1 G_2}}$$

Bilinear
 $\frac{1}{1-z^{-1}}$ $\frac{z^{-1}}{1-z^{-1}}$ Biquadratic

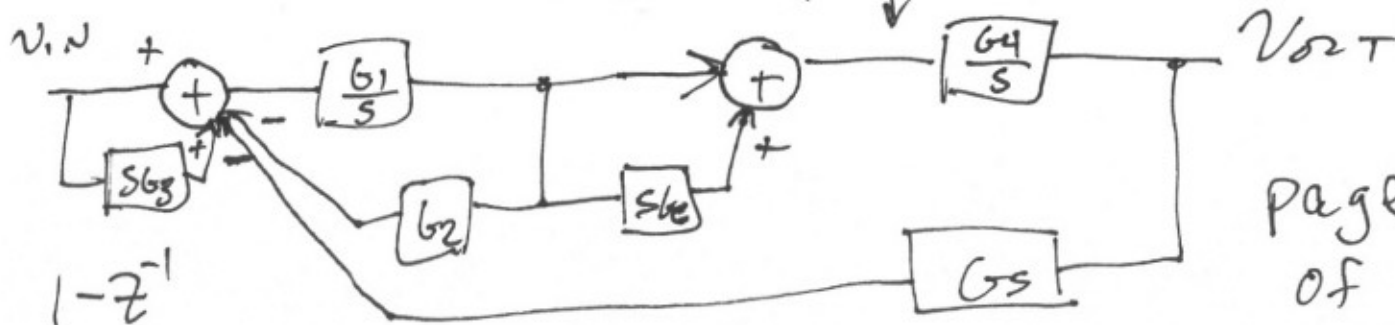

Page 100
 of the
 MSD book




1)

$$H(z) = A_0 + A_1 z^{-1} + A_2 z^{-2} + A_3 z^{-3}$$


$$A_0 = A_1 = A_2 = A_3 = 1$$

FIR
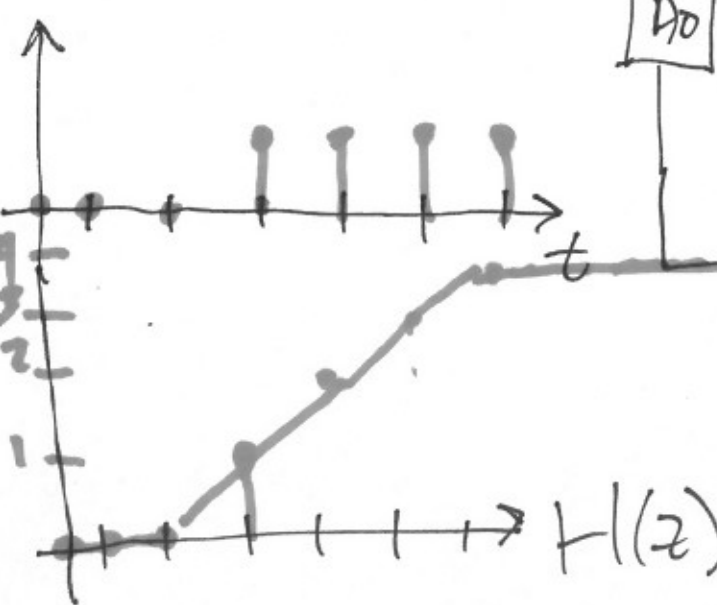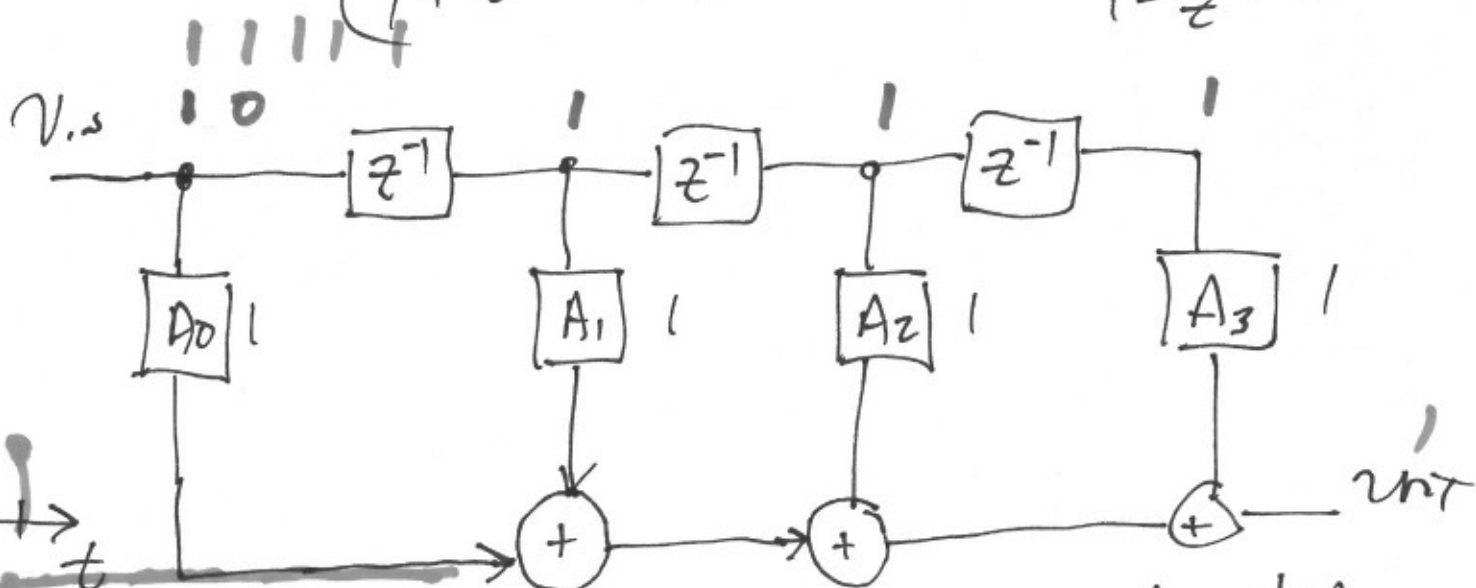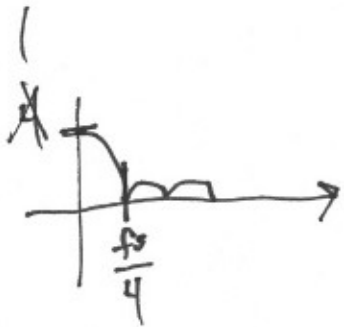
$$(1 + z^{-1} + z^{-2} + z^{-3}) \cdot \frac{1 - z^{-4}}{1 - z^{-1}}$$




$$H(z) = \frac{1 - z^{-4}}{1 - z^{-1}}$$

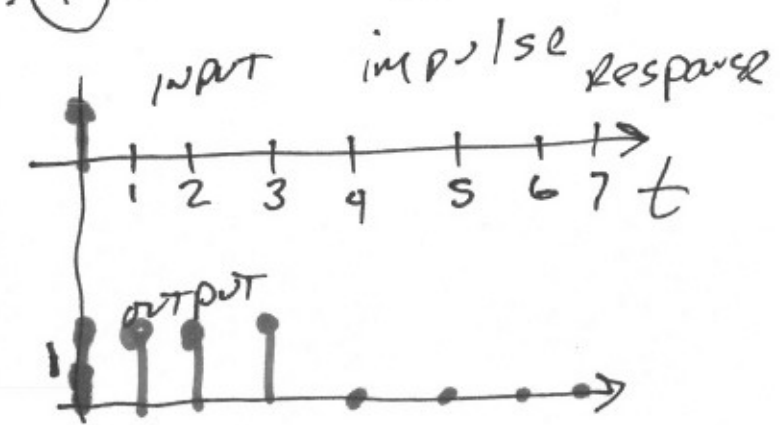

2)

weighted integrating filter

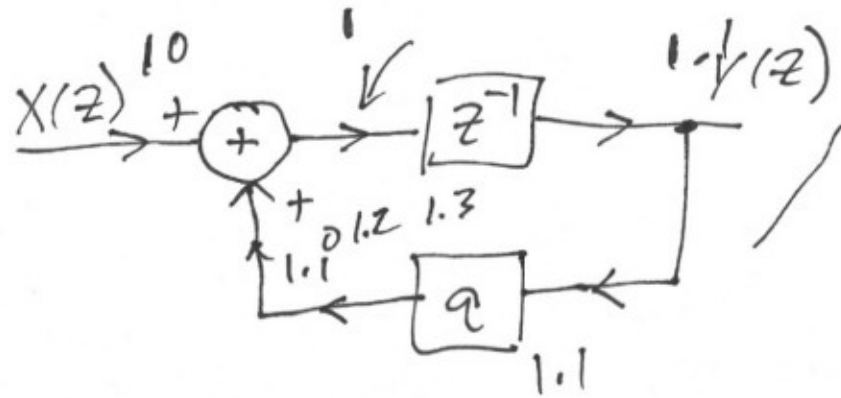


$$a = 1$$

$$\frac{z^{-1}}{1 - z^{-1}}$$

delay integ.

$$(X(z) + Y(z) \cdot a) \cdot z^{-1} = Y(z)$$

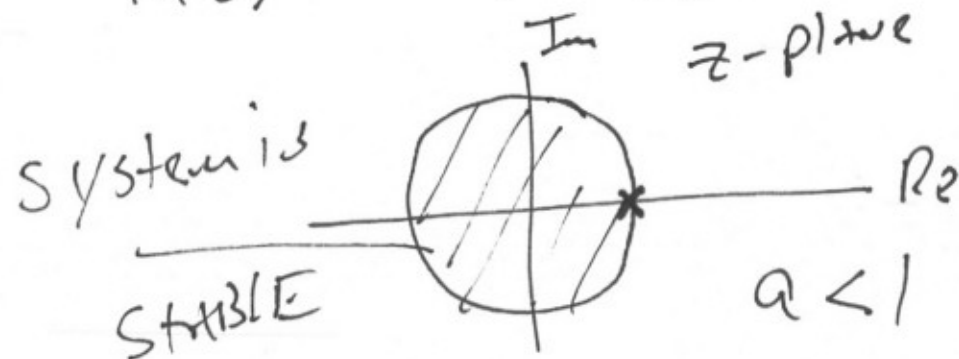
$$\frac{Y(z)}{X(z)} = \frac{z^{-1}}{1 - az^{-1}} = \frac{1}{z - a}$$



$a < 1$ pole is inside unit circle

3)

Bilinear filter

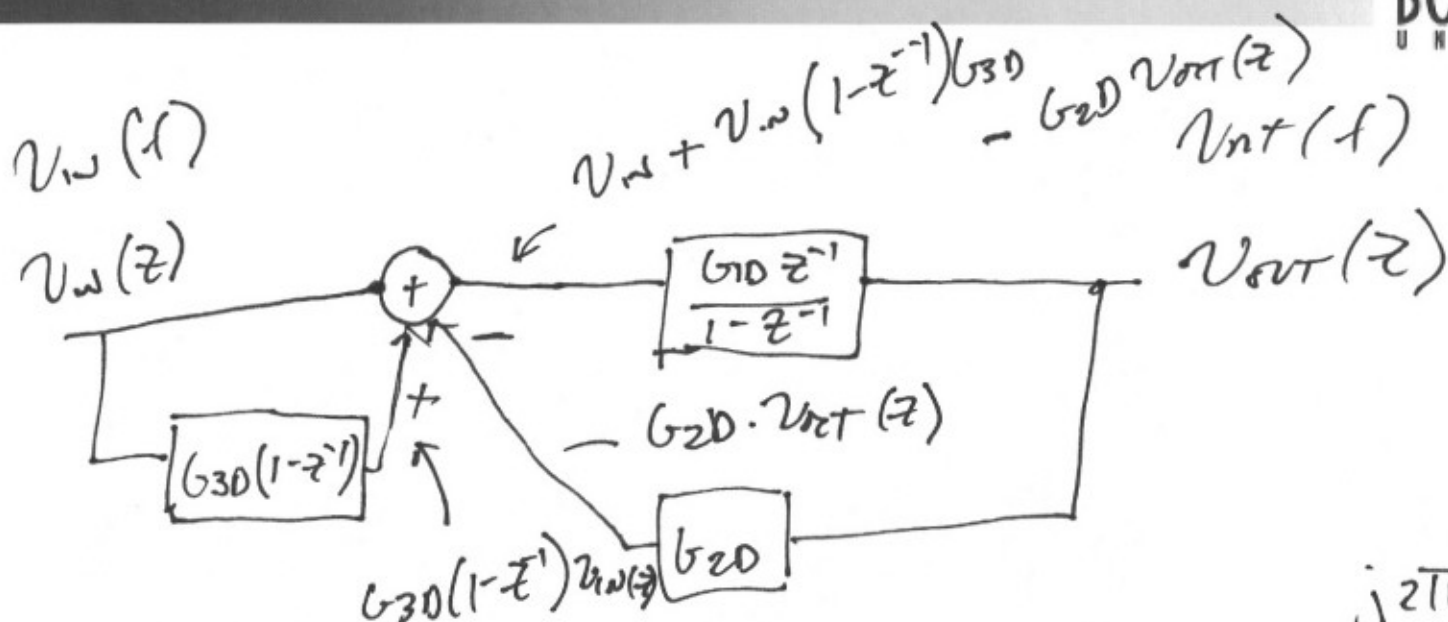

$$\frac{v_{out}}{v_{in}} = \frac{1}{G_{2D}} \cdot \frac{1 + s \cdot G_{3D}}{1 + \frac{s}{G_{1D} G_{2D}}} \quad \text{with } z = e^{j2\pi \frac{f}{f_s}}$$

$$v_{in} \left[\left(1 + G_{3D}(1-z^{-1}) \right) - \left(G_{2D} v_{out} \right) \right] \cdot \frac{G_{1D} z^{-1}}{1-z^{-1}} \approx \underbrace{1 + \frac{s}{f_s}}_{\text{Taylor series expansion}}, \quad f \ll f_s, \quad s = j\omega$$

$$= v_{out}$$

$$(4.44) \quad \frac{V_{out}}{V_{in}} = \frac{G_{10}(1+G_{30})}{z - (1-G_{10})} \cdot \frac{z - G_{30}/(1+G_{30})}{z}$$

$$\left(z \approx 1 + \frac{s}{f_s} \right)$$


$$\frac{V_{out}}{V_{in}} = \frac{1 + j \frac{f}{f_s/2\pi G_{30}}}{1 + j \frac{f}{G_{10} \cdot f_s/2\pi}} \rightarrow \text{same as eq (4.41)}, G_{20} = 1$$

5)

$$\frac{G_{3D}}{f_s} = 10 \mu\text{s} \rightarrow G_{3D} = 10$$


$$\text{if } f_s = 100 \text{ MHz, } \frac{1}{f_s} = 10 \text{ ns}$$
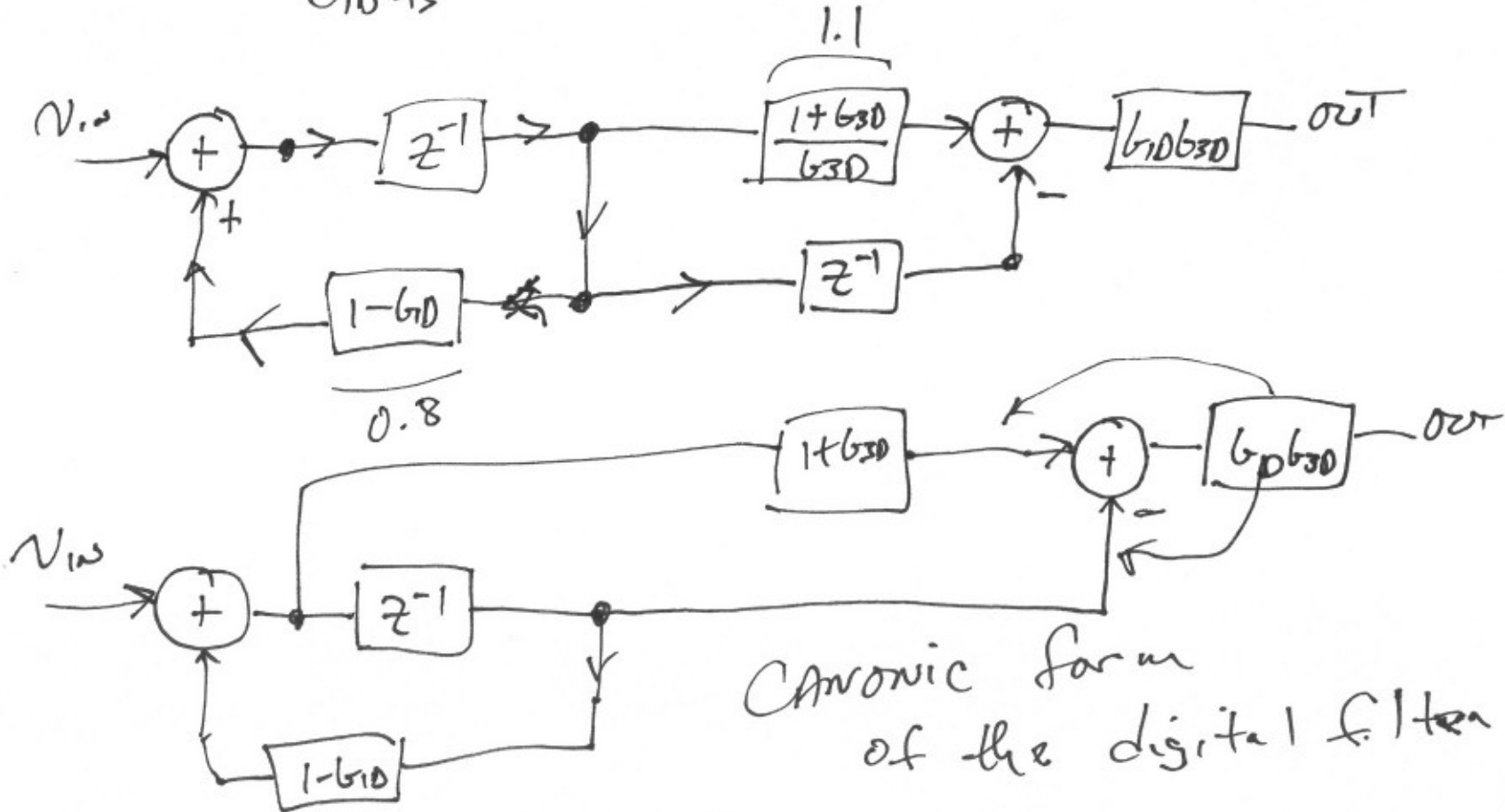
$$\frac{1}{G_{1D} \cdot f_s} = 50 \text{ ns} \quad G_{1D} = 0.2$$



Canonical form of the digital filter

6)

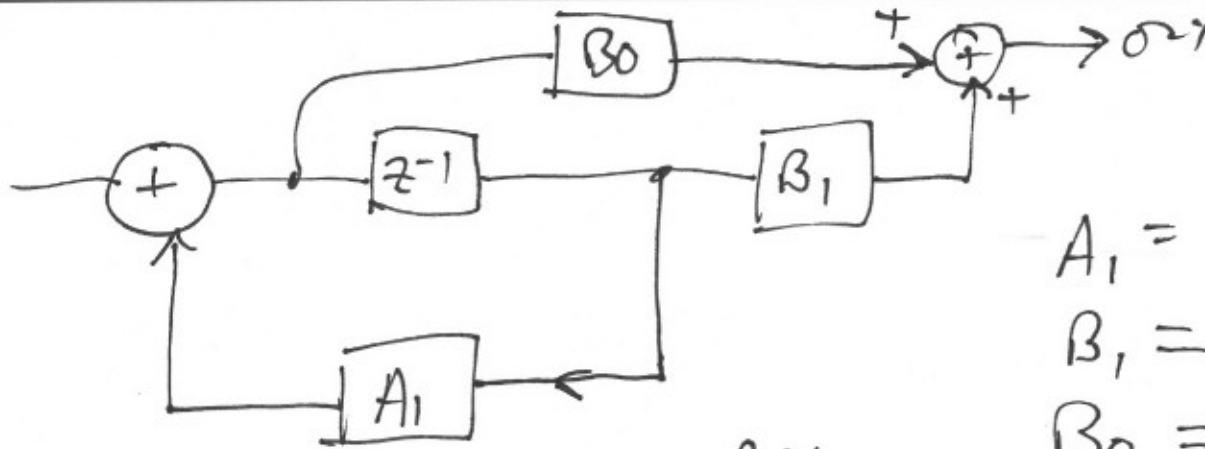

CANONIC first order filter

$$A_1 = 1 - G_{1D}$$


$$B_1 = -G_{1D} G_{3D}$$

$$B_0 = (1 + G_{3D}) G_{1D} G_{3D}$$

$$H(z) = \frac{B_0 + B_1 z^{-1}}{1 - A_1 z^{-1}}$$

$$B_0 \cdot \frac{z + \frac{B_1}{B_0}}{z - A_1}$$

Big quad

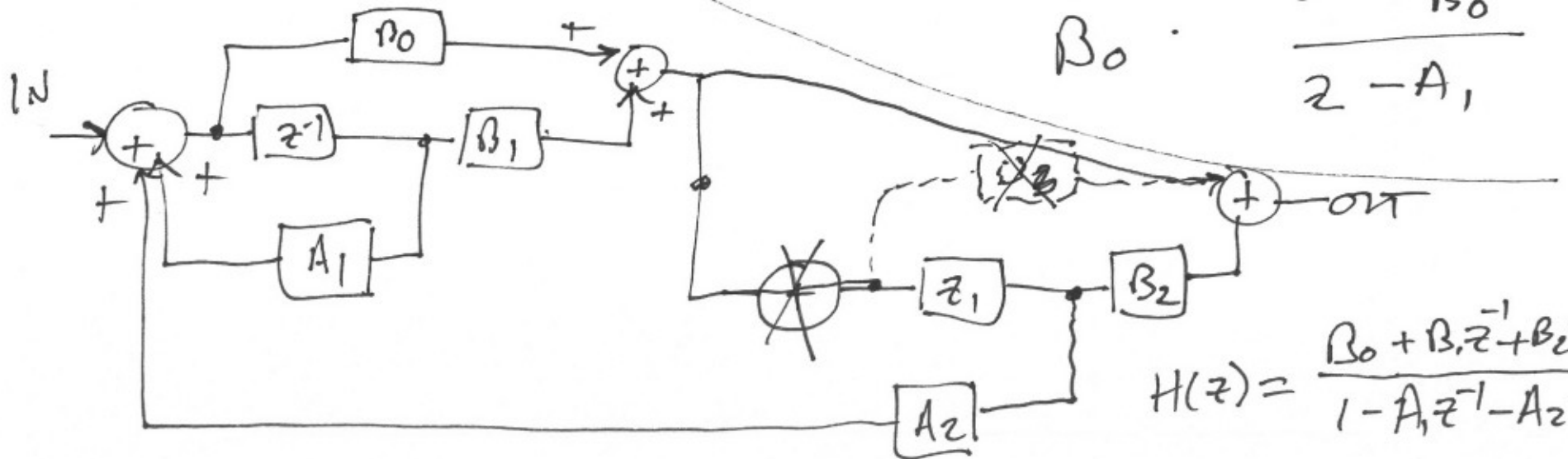

$$H(z) = \frac{B_0 + B_1 z^{-1} + B_2 z^{-2}}{1 - A_1 z^{-1} - A_2 z^{-2}}$$

(3.62)

$$\frac{V_{out}}{V_{in}} = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + \left(\frac{2\pi f_0}{Q}\right)s + (2\pi f_0)^2}$$

$$H(z) = \frac{V_{out}(z)}{V_{in}(z)} = \frac{B_0 z^2 + B_1 z + B_2}{z^2 - A_1 z - A_2}$$

$$z \approx 1 + \frac{s}{f_s}, \quad f \ll f_s$$

$$a_2 = B_0$$

$$a_1 = f_s (2B_0 + B_1)$$

$$a_0 = f_s^2 (B_0 + B_1 + B_2)$$


$$\frac{2\pi f_0}{Q} = f_s (2 - A_1), \quad f_0 = \frac{f_s}{2\pi} \sqrt{(1 - A_1 - A_2)}$$

8)

Ex. 4.12

digital Biquad is $f_s = 100\text{kHz}$

$$f_0 = 1.59\text{ MHz} \quad Q = 0.707$$

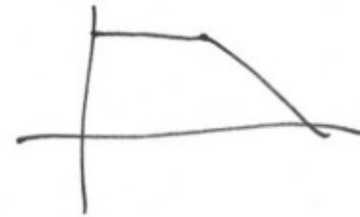

page 156

$$B_0 = B_1 = 0$$

$$A_1 = 1.859$$

$$A_2 = -0.869$$



$$B_2 = 0.01$$

a)

$\frac{1}{2}, \frac{1}{4}, \frac{1}{8}$

010000 $\times \frac{1}{2}$
 001000 $\frac{1}{4}$
 000100

.9375

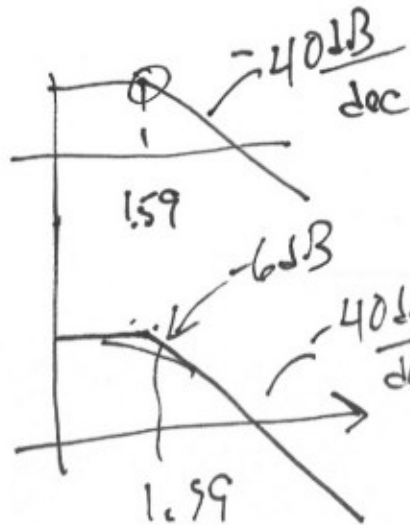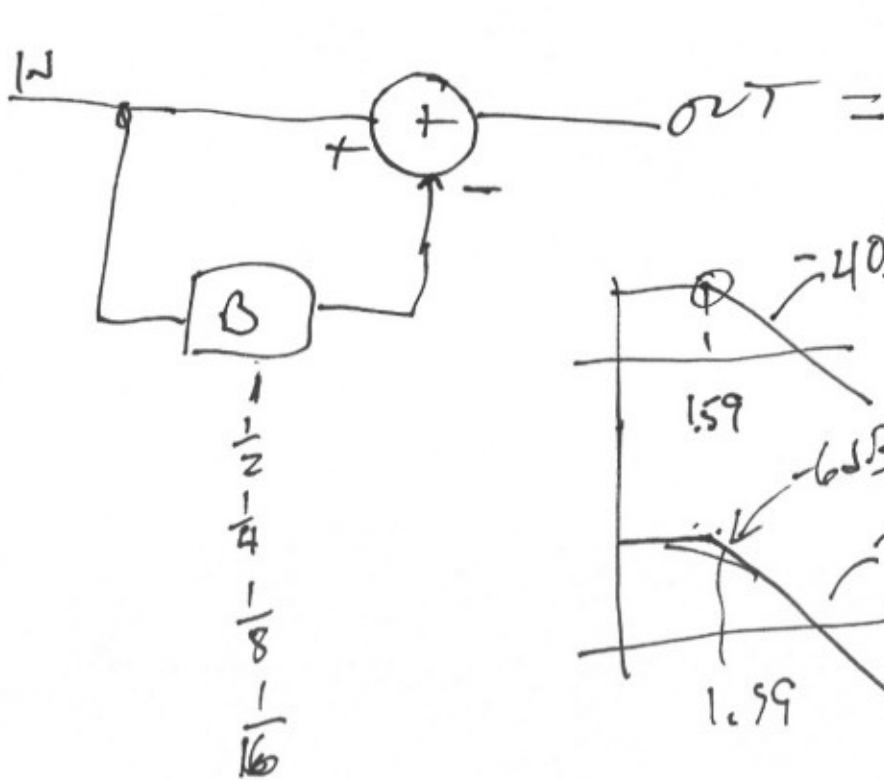

B
 1
 $\frac{1}{2}$
 $\frac{1}{4}$
 $\frac{1}{8}$
 $\frac{1}{16}$ (0.0625)

Multiply by
 0
 $\frac{1}{2}$
 0.75 1.125
 .875
 .9375

10)