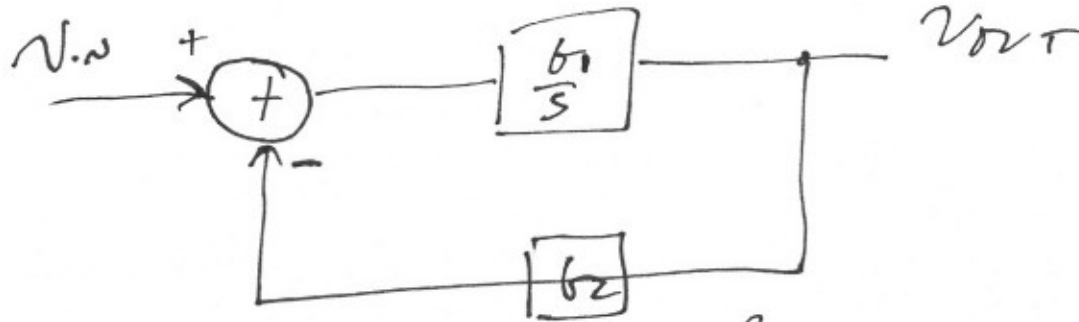



ECE 615 CMOS Mixed-Signal Circuit Design



$$\frac{v_{out}}{v_{in}} = \frac{1}{G_2} \cdot \frac{1}{1 + \frac{s}{G_1 G_2}}$$



$$G_2 = \frac{R_I}{R_F}$$

$$G_1 = \frac{1}{R_I \cdot C}$$

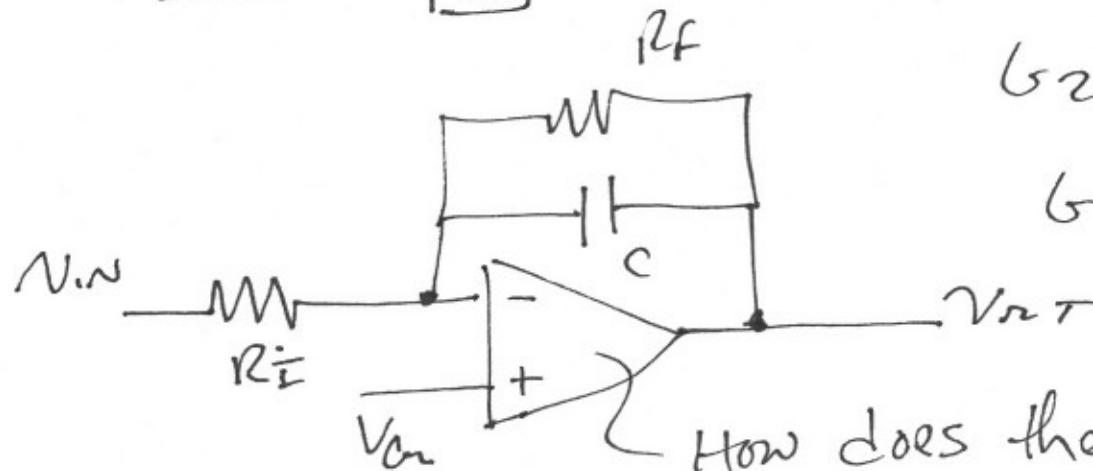

How does the op-amp limit performance?
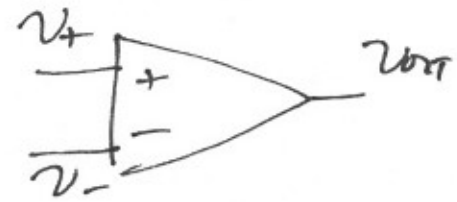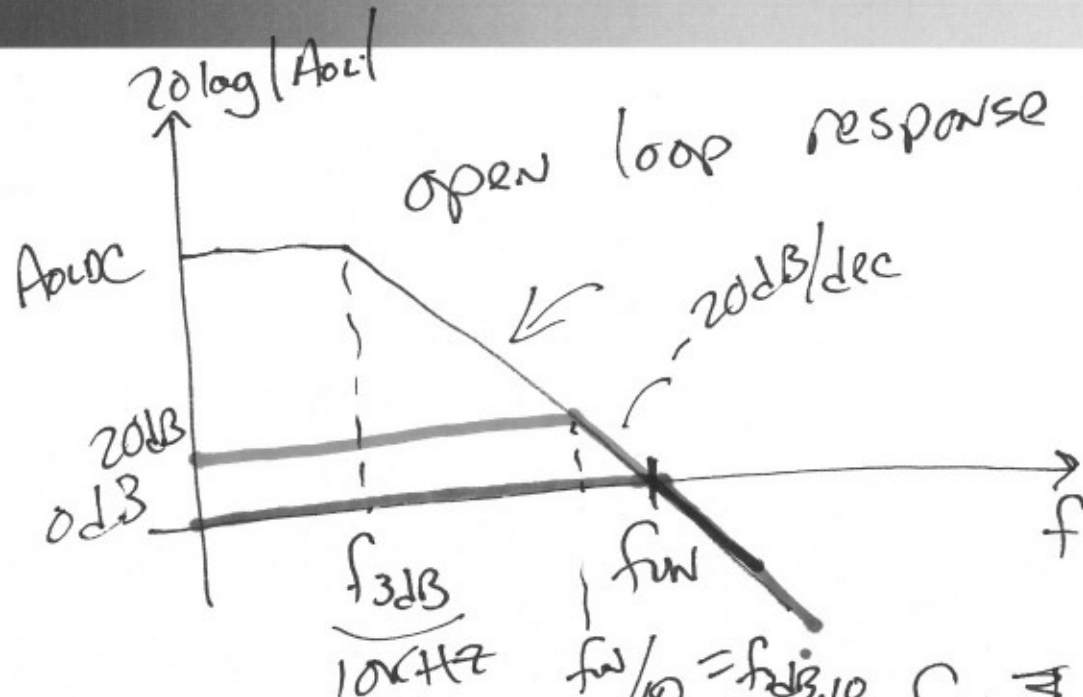
$$A_{OL} \approx \frac{v_{OUT}}{v_{IN} - v_{-}}$$



$10,000 = A_{OLDC}$
 $100MHz$

$$f_{3dB} = \frac{100MHz}{10,000} = \frac{10^8}{10^4} = 10kHz$$

$$f_w = 100MHz$$

$$f_w = GAIN \cdot BW$$

$$f_w / 10 = f_{3dB,10} \quad f_w = A_{OLDC} \cdot f_{3dB}$$

$$A_{CL} = 1$$


$$A_{CL} = \frac{A_{OLDC}}{1 + j \frac{f}{f_{3dB}}}$$

$$\frac{v_{OUT}}{v_{IN}} = 10 \rightarrow 20dB = 10MHz$$

$$A_{CL} = 10$$

$f_w = 100MHz, f_{3dB,10}$


2)

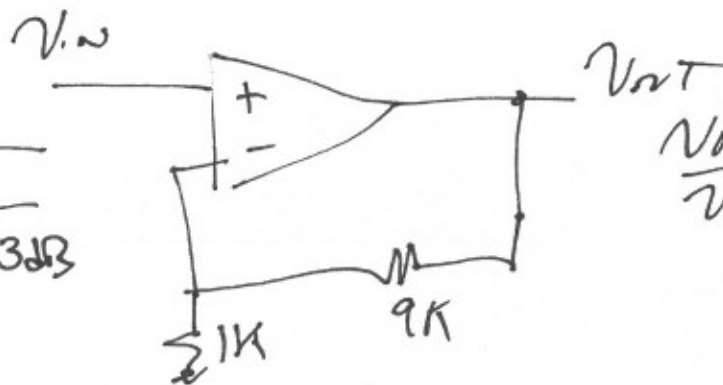

OP-AMP frequency response

$$A_{ol} \approx \frac{A_{olDC}}{j \cdot f / f_{3dB}} = \frac{f_{3dB} \cdot A_{olDC}}{j \cdot f}$$
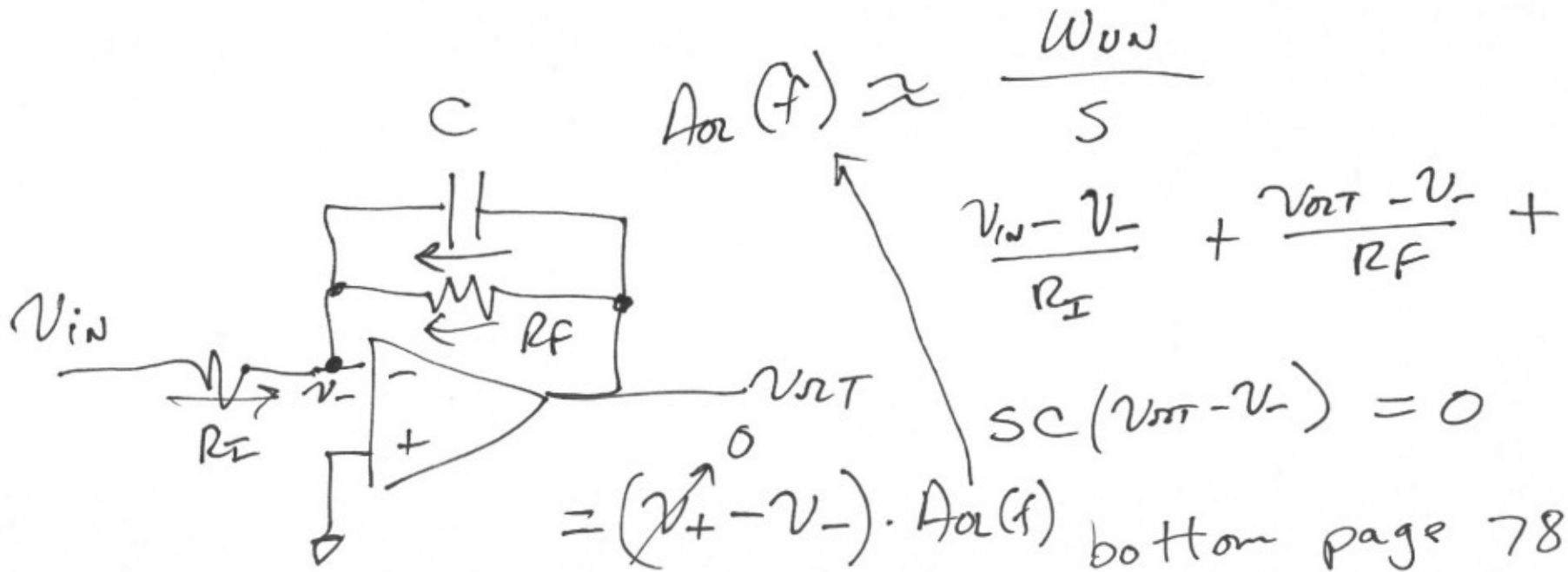
$$A_{ol} \approx \frac{f_{in} \cdot \pi}{j \cdot f \cdot \pi} = \frac{1}{j \cdot f / f_{in}} \approx \frac{v_{inT}}{v_+ - v_-}$$



$$v_{out} = -A_{ol}(f) \cdot v_-$$


3)

$$\frac{V_{out}}{V_{in}} = \frac{-\frac{R_F}{R_I}}{1 + sCR_F + \frac{sCR_F}{A_{oc}(f)} + \frac{1}{A_{oc}(f)} \cdot \left(1 + \frac{R_F}{R_I}\right)}$$

$R_F = R_I \quad G_2 = 1$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + s/G_1} \cdot \frac{1}{1 + j \frac{f}{f_{w}}}$$



Models of Amp frequency response.

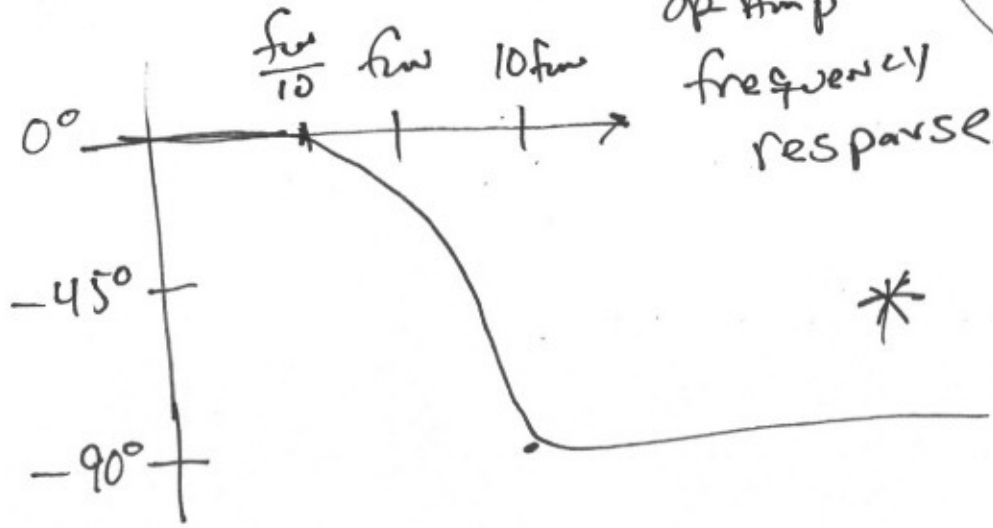

- if $A_{oc}(f)$ is Big
- * A_{oc} to be big
- * $\frac{R_F}{R_I} \rightarrow 1$ as possible

* $f_{w} \geq 10 \cdot f_{3dB} = 10 \cdot \frac{G_1}{2\pi}$

4)

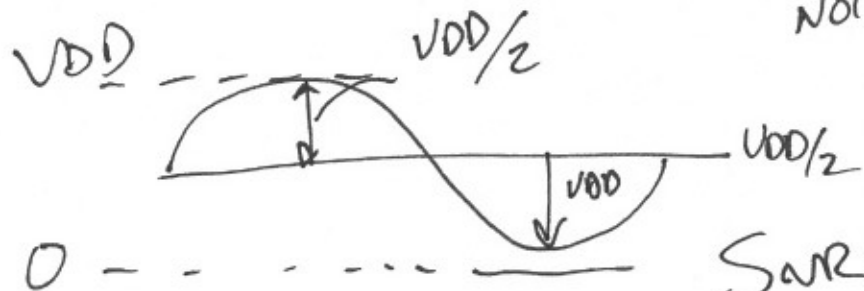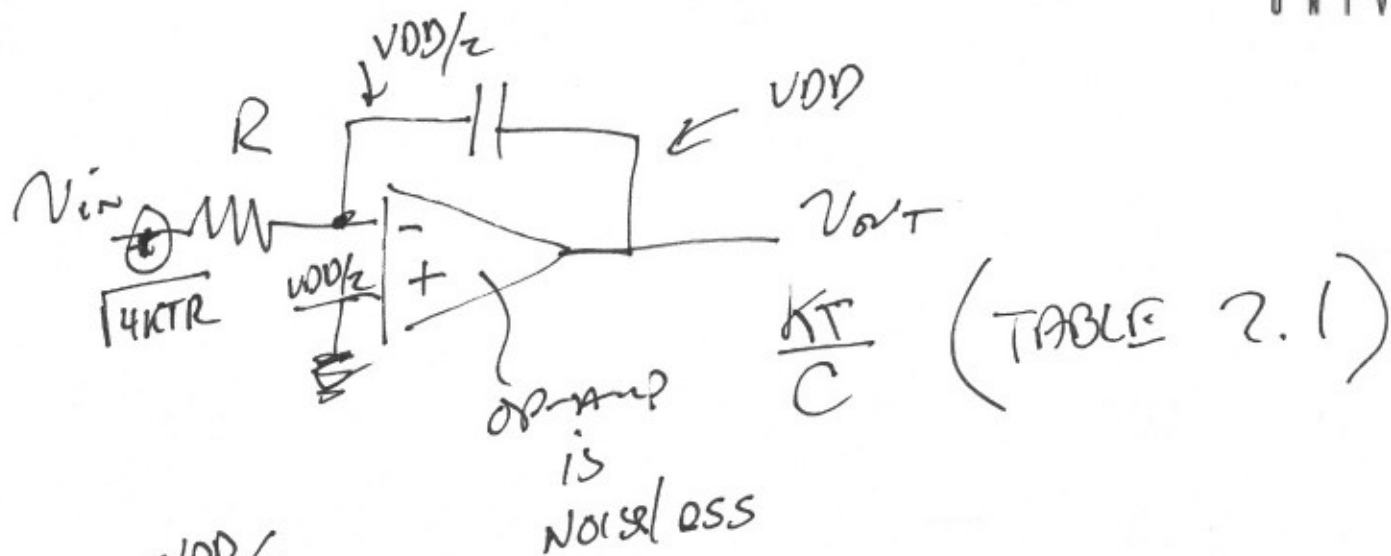

$$SNR = 20 \log \left[\frac{V_{DD}/2 \cdot \sqrt{2}}{\sqrt{kT/C}} \right] = \frac{\frac{1}{2} C \left(\frac{V_{DD}}{2} \right)^2}{kT}$$



Electrical Energy / Thermal Energy

RC - filter


$SNR \rightarrow \underline{\underline{90 \text{ dB}}}$

s)




MOSFET-C Integration

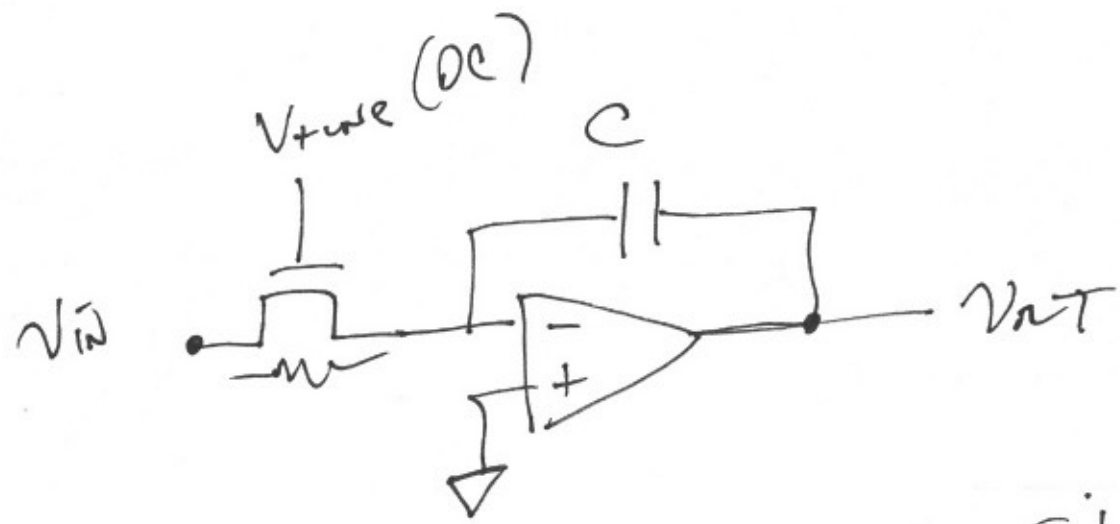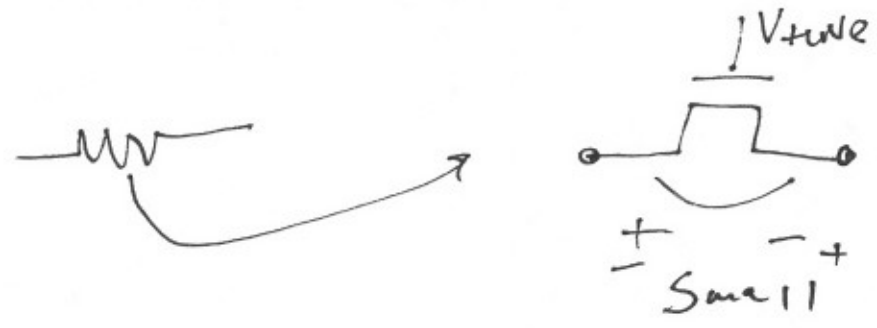

Simple MOSFET-C Filter

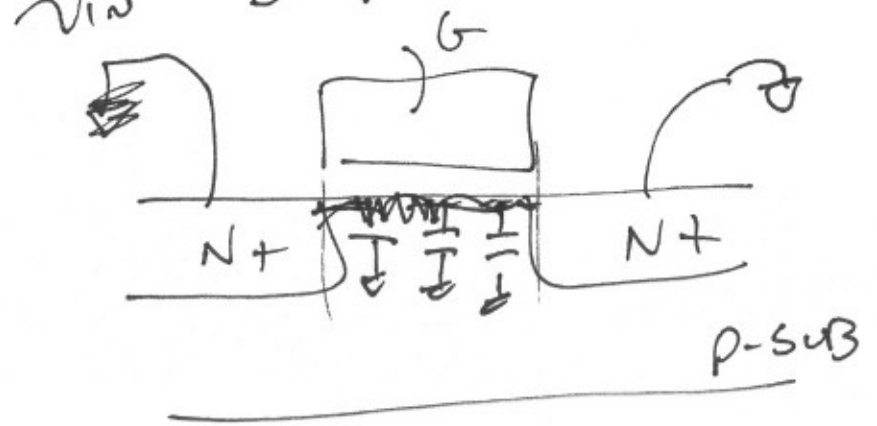

6)

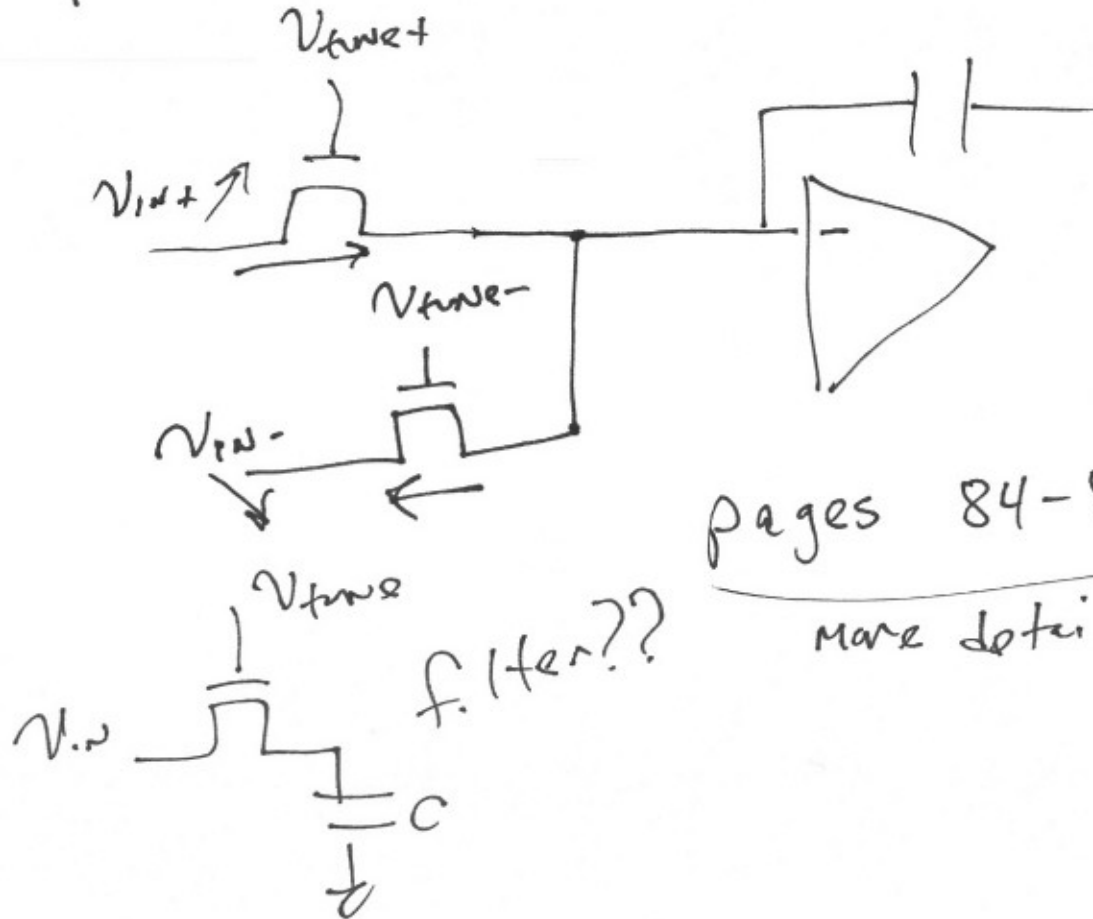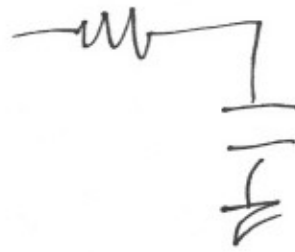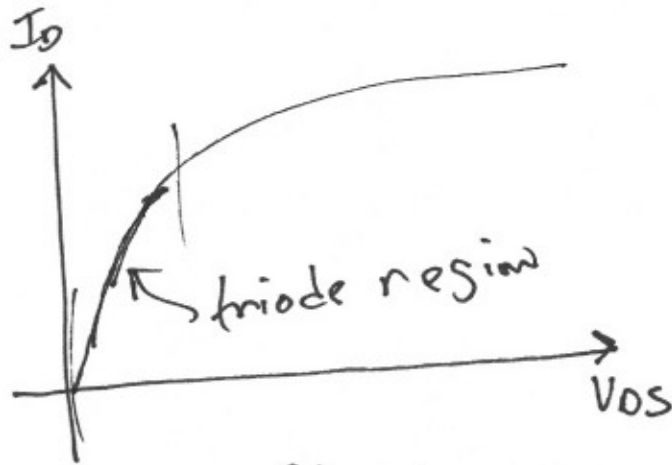


pages 84-85
more details

→




OP-AMP provides isolation

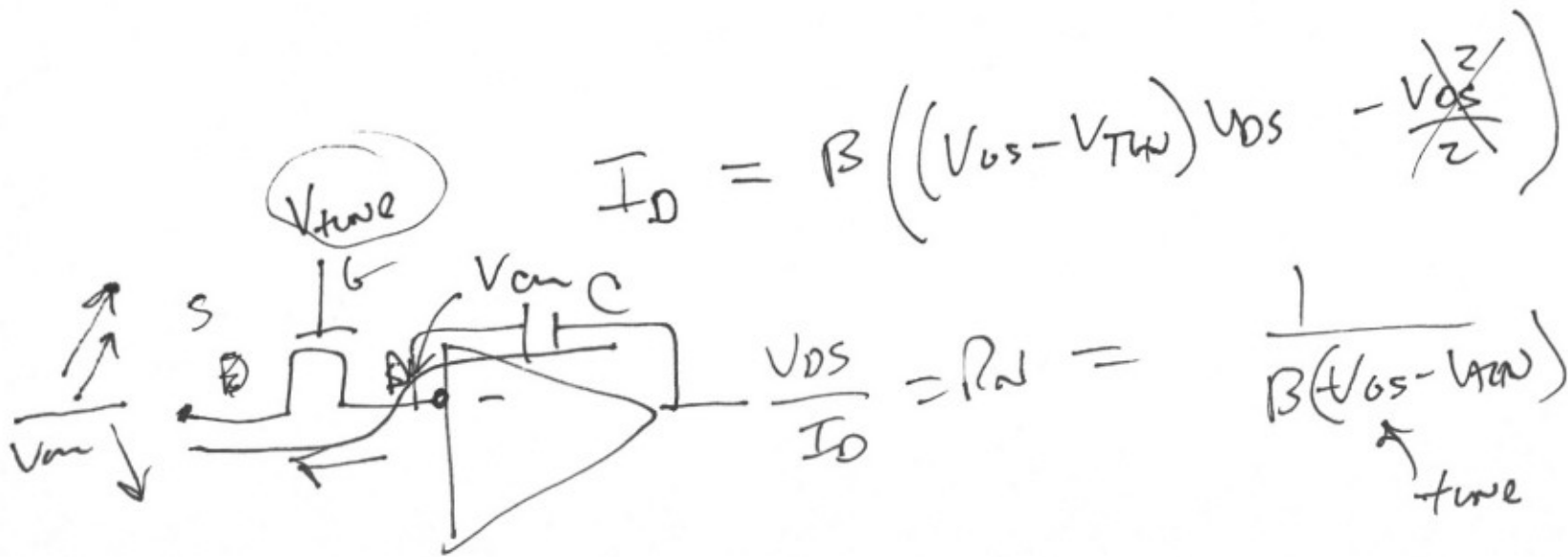

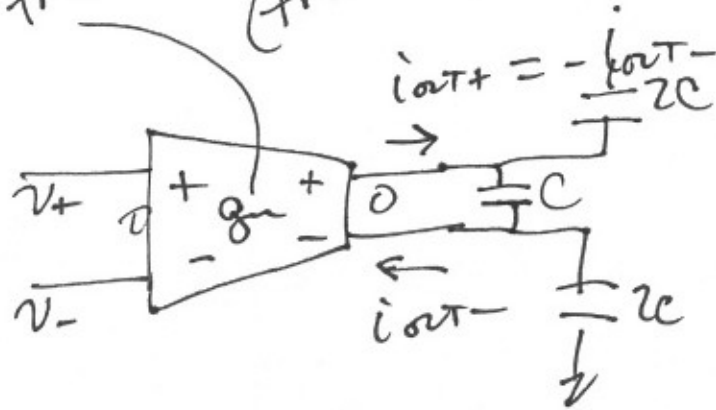
8)

$g_m - C$ (transconductance filters)
 transconductance (transconductance Amp)





$$i_{out+} = -\frac{i_{out-}}{2C}$$
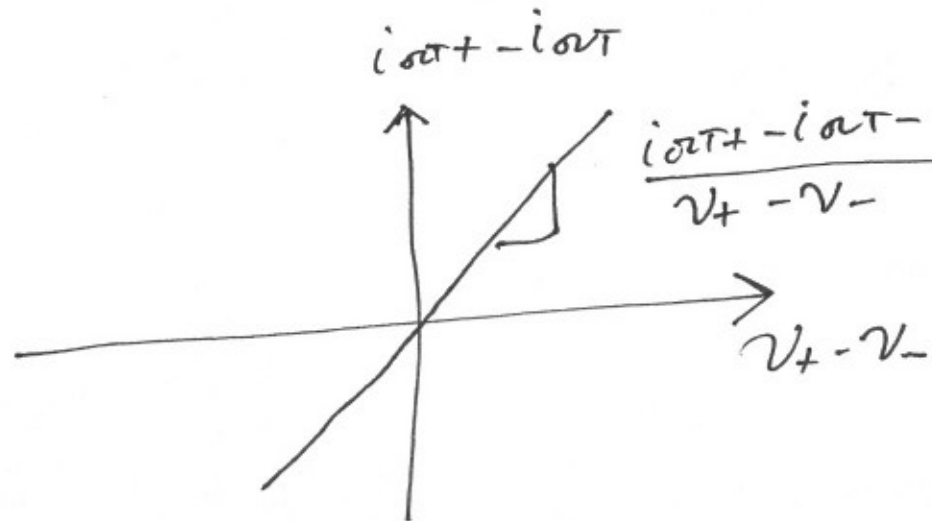
$$g_m (v_+ - v_-) = i_{out+} - i_{out-}$$



$$\frac{i_{out+} - i_{out-}}{v_+ - v_-} = \frac{g_m}{2C}$$

a)

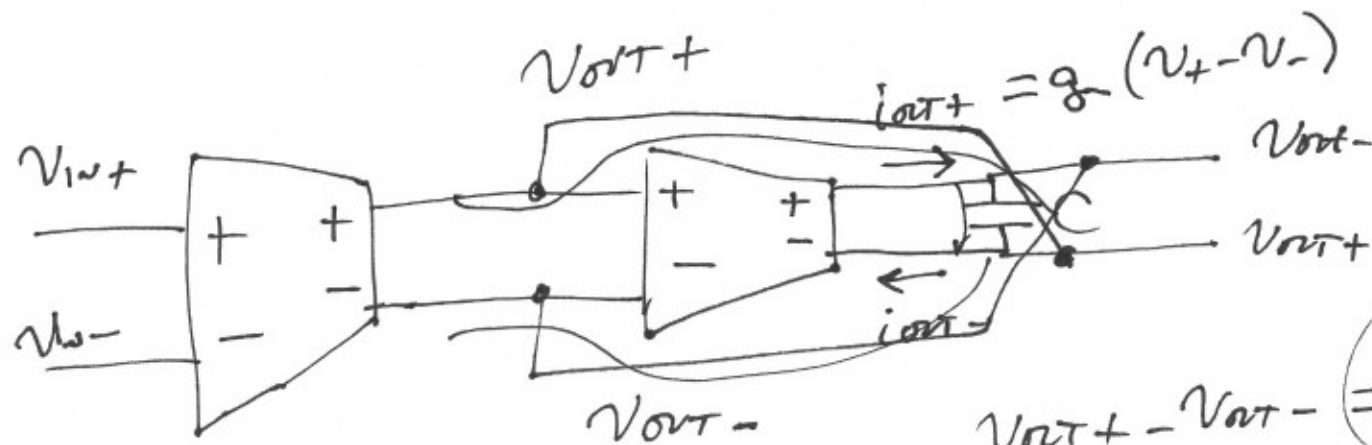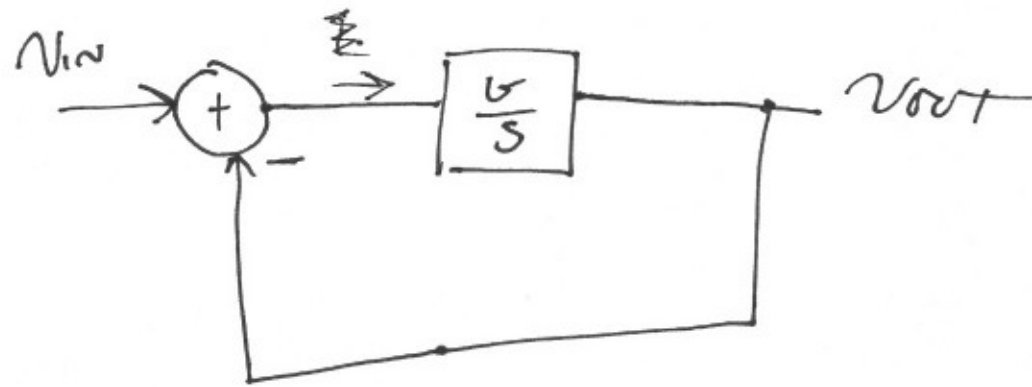

$$V_{out+} - V_{out-} = \frac{i_{out+}}{j\omega C}$$

$$G = \frac{g_m}{C} = \frac{1}{C \cdot \frac{1}{g_m}}$$

$\frac{V_{out+} - V_{out-}}{V_{in+} - V_{in-}} = \frac{1}{j \cdot \omega \cdot \frac{C}{g_m}}$

$\frac{C}{g_m} \rightarrow$ easily adjustable

10)

