

ECE 615 CMOS Mixed Signal Circuit Design

Discrete Analog Integrators (DAIs)

see Ch.

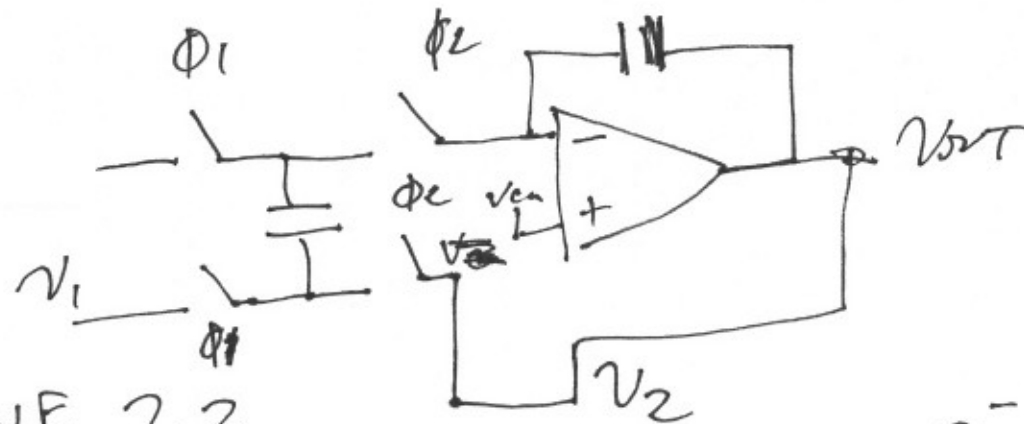


TABLE 2.2



pages 66-67

$$\frac{V_{OUT}}{V_I - V_{OUT}} = \frac{C_I}{C_F} \cdot \frac{z^{-1}}{1 - z^{-1}}$$

$$z \approx e^{j2\pi \frac{f}{f_s}} \approx 1 + j2\pi \frac{f}{f_s} \frac{1}{2|s| \frac{f}{f_s}} \quad \text{Eqs. (1.62) (1.66)}$$




$$\frac{V_{out}}{V_{in} - V_{out}} \approx \frac{C_I}{C_F} \cdot \frac{1}{2\pi f / f_s} = G \cdot \frac{1}{s}$$
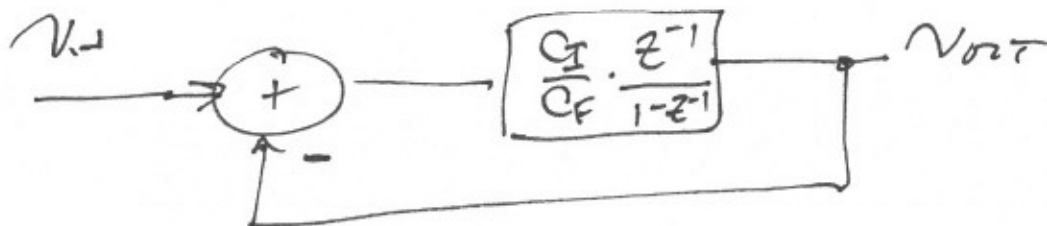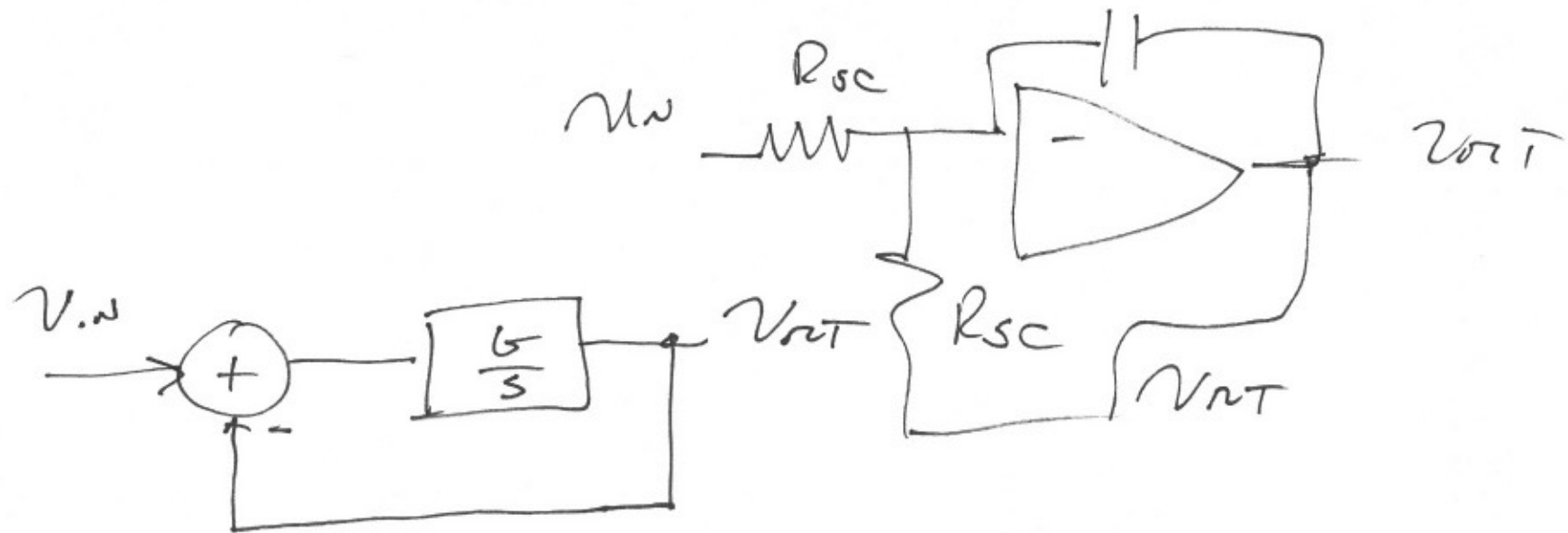
$$R_{sc} = \frac{1}{C_I \cdot f_s} = \frac{T_s}{C_I}$$




2)

Example 3.6

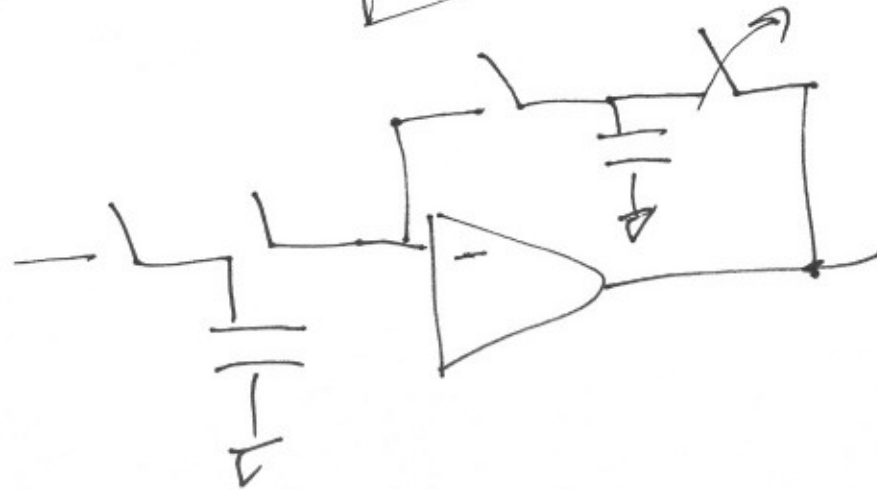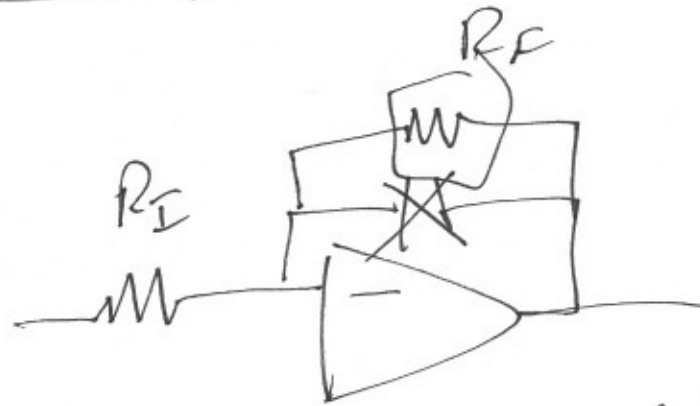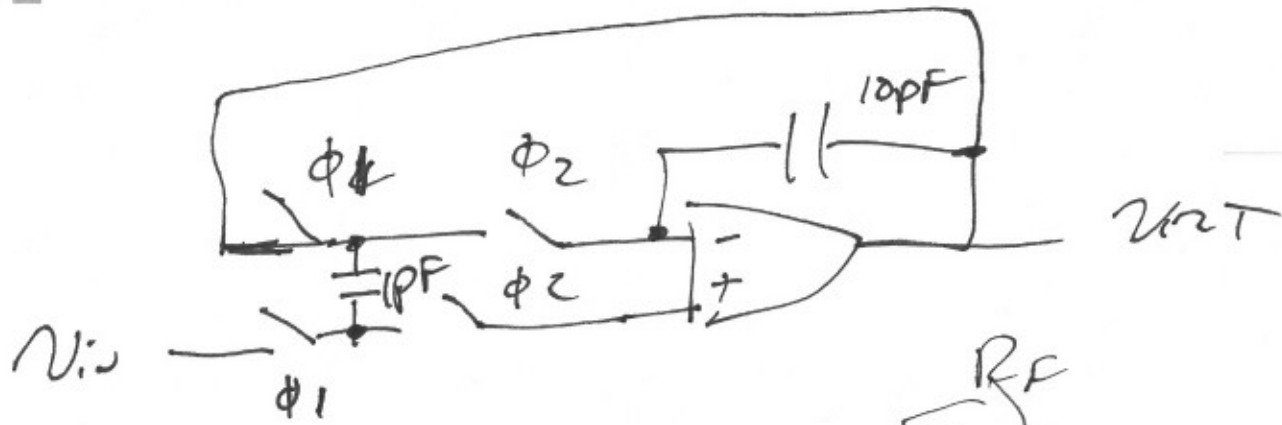

good??

3)

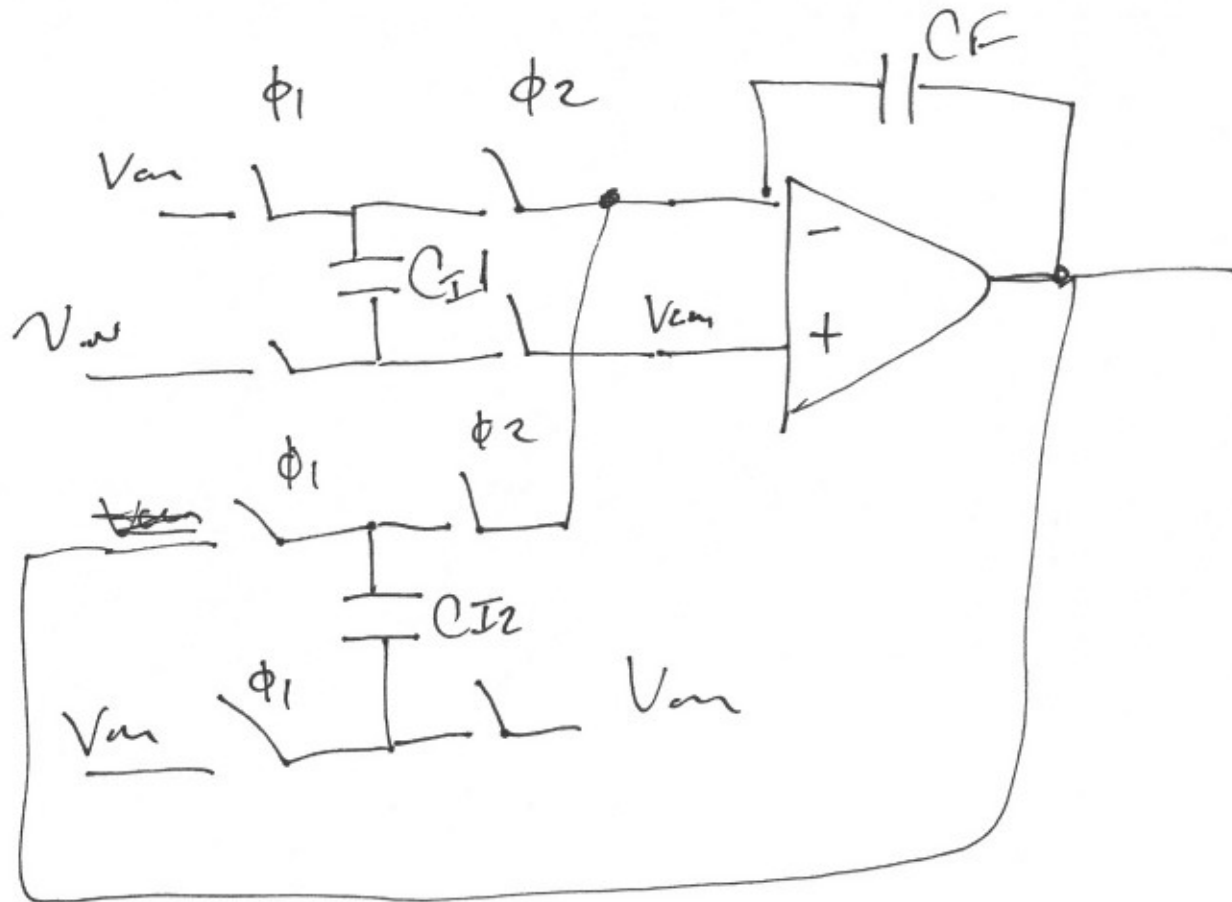

$$G_1 = \frac{C_{I1}}{C_F} \cdot f_s, \quad G_2 = \frac{C_{I2}}{C_F} \cdot f_s \cdot \frac{1}{G_1}$$

GAIN SCALING

$$= \frac{C_{I2}}{C_{I1}}$$

4)