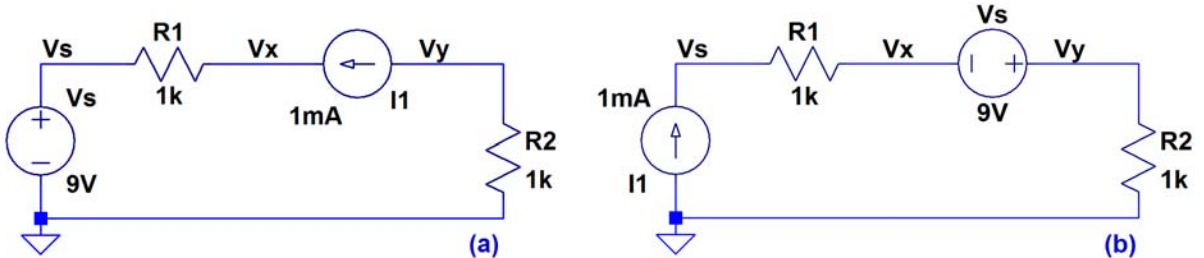



H.W. #5 EE 220 Fall 2016

Show your work for credit!

- Find the voltages V_x and V_y in each of the following circuits. Verify your hand calculations using LTspice. (4 points)



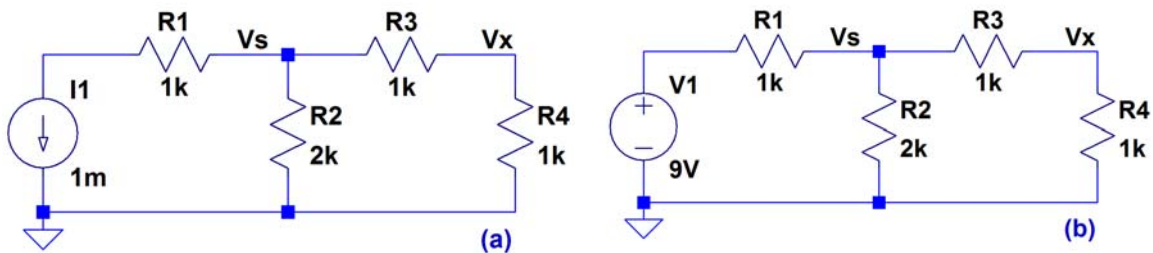- Find the voltages V_s and V_x and the current through R_2 in each of the following circuits. Verify your hand calculations using LTspice. (6 points)



- Using **superposition** show how to find V_x in the following circuits. Verify your hand calculations using LTspice. (6 points)

