

Quiz #1 EE 220 Fall 2016 Name: _____

Closed book and notes.

Show your work for credit!

1. Find the voltages V_s and V_x as well as the current flowing in the direction shown. (5 points)

