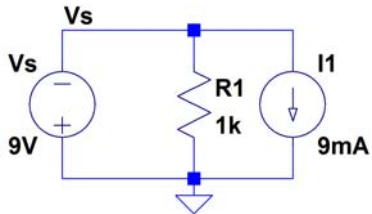


Quiz #4 EE 220 Fall 2016 Name: \_\_\_\_\_

Closed book and notes.

Show your work for credit!

1. Determine the current through  $V_s$ . Again, show your work for credit. (2 points)



2. Find  $V_x$  in the following circuit. (5 points)

