

Quiz #6 EE 220 Fall 2016 Name: \_\_\_\_\_

Closed book and notes.

Show your work for credit!

1. Find the Thevenin and Norton equivalent circuits, with  $R_2$  removed, at the terminals marked by red dots seen below. (5 points)

