

Quiz #8 EE 220 Fall 2016 Name: _____

Closed book and notes.

Show your work for credit!

1. Find the voltage across R1. As always, show your work for credit. (3 points)

