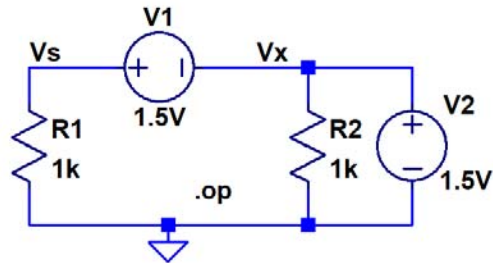


H.W. #2 EE 220 Fall 2017

Show your work for credit and place a box around each of your answers!

1. Write a text file containing the LTSpice netlist for the following circuit. Verify that the simulation results match your hand calculations. (3 points)



2. Find the voltages and currents in each of the following circuits. Verify your answers with LTSpice. (9 points)

